

題目: 無線充電IC設計

報告人: 郭永超 (Yeong-Chau Kuo)

現職: 高雄科技大學電子系教授

專長: 綠能 IC與系統設計, 電源管理 IC與系統設計,  
電子設計自動化

經歷: 國家晶片中心晶片製作審查委員,  
太陽光電發電系統設置審查委員,  
IC設計公司研發顧問, 電機技師,  
永續能源與資源管理師, 永續發展碳管理師

# Latest Publications

---

- Peng-Chang Huang, Yeong-Chau Kuo\*, Yi-Chen Liu, and Tai-Haur Kuo, "An Analog Optimum Torque Control IC for a 200W Wind Energy Harvesting System," accepted by and to be published in IEEE Trans. Circuits Syst. II, Exp. Briefs.
- Y. C. Kuo\*, Y. M. Huang, and L. J. Liu, "Integrated Circuit and System Design for Renewable Energy Inverters," International Journal of Electrical Power & Energy Systems, Vol. 64, pp. 50-57, Jan. 2015. (SCI/SSCI, impact factor: 3.289, SCI/SSCI rank factor: 51/262, ENGINEERING, ELECTRICAL & ELECTRONIC, times cited: 6)
- Y. C. Kuo\*, Y. J. Luo, and L. J. Liu, "Synthesizable Integrated Circuit and System Design for Solar Chargers," IEEE Transactions on Power Electronics, Vol. 28, Iss. 9, pp. 4260-4266, Sep. 2013. (SCI, impact factor: 7.151, SCI/SSCI rank factor: 13/262, ENGINEERING, ELECTRICAL & ELECTRONIC, times cited: 4)
- Y. C. Kuo\*, W. H. Tung, and L. J. Liu, "Smart Integrated Circuit and System Design for Renewable Energy Harvesters," IEEE Journal of Photovoltaics, Vol. 3, Iss. 1, pp. 401-406, Jan. 2013. (SCI, impact factor: 3.712, SCI/SSCI rank factor: 25/92, ENERGY & FUELS, times cited: 5)
- Y. C. Kuo\*, Y. J. Luo, and L. J. Liu, "Synthesis Design of Digital Solar Energy Harvesting Integrated Circuits and Systems," IET Optoelectronics, Vol. 6, Iss. 6, pp. 282-289, Dec. 2012. (SCI, impact factor: 1.165, SCI/SSCI rank factor: 176/262, ENGINEERING, ELECTRICAL & ELECTRONIC)
- Y. C. Kuo\*, C. H. Liu, and L. J. Liu, "Synthesisable Solar-Harvesting Integrated Circuit and System," IET Renewable Power Generation, Vol. 6, Iss. 6, pp. 408-413, Nov. 2012. (SCI, impact factor: 2.635, SCI/SSCI rank factor: 76/262, ENGINEERING, ELECTRICAL & ELECTRONIC)

# Latest Patents and Honor

## Patent

- JM Liu, YC Kuo, and TH Kuo, Analog Variable-Frequency Controller and Switching Converter Therewith, Invention patent, USA, Patent. No.: US 7923975 B2, 2011.
- Y. C. Kuo\*, W. C. Liu, and T. H. Kuo, “Analog Controller for Inverter,” Invention patent, USA, US 8,842,456 B2, Sep. 23, 2014.
- 劉家銘、郭永超、郭泰豪,類比式可變頻率控制器,發明專利,臺灣,發明第I396373號.
- 郭永超、李貞慶、郭泰豪、黃鵬彰,類比式最大功率追蹤控制方法,發明專利,臺灣,發明第I381263號.
- 郭永超\*、郭泰豪,換流器之類比控制器,發明專利,臺灣,發明第I444807號, 2014/7/11.

## Honor

- 2018 無人機及智慧製造自造者競賽優等(無人機之動態充電積體電路與系統合成設計)
- 2018年金融科技創新競賽佳作(內建人工智慧金融模型之無線能源傳輸積體電路系統設計)
- 2015年龍騰微笑創業競賽晉級總決賽(智慧型無線充電器)
- 2014年全國大學校院智慧電子系統(IE)設計競賽優等獎(太陽能無線充電積體電路與系統設計)
- 2011年旺宏金矽獎設計組優勝獎(能量採集積體電路系統之自動合成設計)
- 2010年旺宏金矽獎設計組評審團銅獎與指導教授獎(以類比積體電路實現太陽能最大發電功率追蹤器)
- 2010年立錡盃電源IC設計暨系統應用競賽佳作獎(智慧型電網與太陽能充電IC之自動合成設計)
- 2009年Discovery Channel採訪報導太陽能充電器之研究成果
- 2009年立錡盃電源IC設計暨系統應用競賽佳作獎(太陽能與風能最大效率之充電器設計)
- 2009年奇景盃IC佈局設計競賽佳作獎

# Latest Project and Result

## Project

- 107年無人機之動態充電積體電路系統合成設計(MOST 107-2221-E-992-099)
- 106年微換流器之無線充電積體電路系統合成設計(MOST106-2221-E-327-026)
- 104-105年微換流器之積體電路系統合成設計(MOST 104-2221-E-327 -037 -MY2)
- 103年技術移轉授權-智慧型無線充電器(錠暉自動化科技有限公司)
- 103年技術移轉授權-智慧型植物栽培箱(綠光能科技有限公司)
- 103年綠能積體電路系統之合成設計 (主持人, NSC 103-2623-E-327 -001 –ET)
- 102年高低溫度測試模組(主持人, 金屬中心)
- 101年太陽能和風力最佳化轉換效率模擬與理論驗證(主持人, 金屬中心)
- 100年高效能儲電模組性能測試(主持人, 金屬中心)
- 100年整合型計畫-可攜式機電裝置之節能關鍵技術研發 (3/3) (共同主持人, NSC 1002218E006001)
- 99年整合型計畫-具最大功率追蹤與控制之併聯型混合太陽能與風力發電電源轉換器晶片設計與系統研製(3/3) (共同主持人, NSC992220E006 006)
- 99年整合型計畫-可攜式機電裝置之節能關鍵技術研發 (2/3) (共同主持人, NSC 992218E006003)
- 98年整合型計畫-具最大功率追蹤與控制之併聯型混合太陽能與風力發電電源轉換器晶片設計 與系統研製(2/3) (共同主持人, NSC 982220E006014)
- 98年整合型計畫-可攜式機電裝置之節能關鍵技術研發 (1/3)(共同主持人, NSC982218E006242)

## Research result (可供技轉或合作)

1. 太陽能與風能充電IC與系統設計
2. 電池充電IC與系統設計
3. 綠能IC與系統自動化設計軟體 GEIC Lab., EE, NKUST
4. 綠能IC與系統監控軟體

# BIPV智慧型無線充電器

- 建材一體型太陽能板(Building integrated photovoltaic, BIPV)：可替代建築物的外表包覆材料、代替屋頂、牆面、窗戶、可遮陽，降低建築物外表溫度，兼具建材及發電之功能，降低整體建築成本。
- 全天候的電源供應、結合綠建築的無線充電：由於室內光源發電量低，需透過兼具低功耗和最佳化設計的積體化高效能光能獵能器才能大幅降低功率損耗以增加輸出電能。另外，發展兼具高系統效率和大傳輸距離之無線充電系統則可與建材一體型太陽能板結合，增加電能取得便利性。也能透過能量互補概念連結並解決光源輸出不穩問題，達到不論白天夜晚皆能有效供給電源甚至達到充電效果的目標。
- 結合物聯網的產業應用：在BIPV無線充電模組內，發展一個新型量測系統，此系統主要包含偵測器與無線通訊介面，偵測器能偵測BIPV、無線充電系統與電池的運作資訊，並藉由無線通訊介面形成物聯網，該平台內有本計畫發展的自我診斷軟體，可診斷系統操作情況並作出適當決策，該模組的使用者也能隨時得到模組的運作情形與關鍵參數。

# System Synthesis Software

PV\_fitting

MPPT

Solar Cells Specification

Environment temperature (T)=	25	°C
Maximum output power (Pmax)=	11	W
Open circuit voltage (Voc)=	6	V
Short circuit current (Isc)=	2.5	A
Maximum output voltage (Vpmax)=	4.9	V
Maximum output current (Ipmax)=	2.3	A

Environment Variables

Temperature (T)=	32	°C
Illumination (S)=	500	KW/m <sup>2</sup>

Curve  I-V curve  P-V curve

Matlab Code

```
clc;
clear all;
isc=2.5;
k1=0.0017;
s=50;
n=1.92;
k=117.5;
a=0.0000862;
ior=0.000035;
ego=1.11;
```

Result

Pmax=5.16W  
Vmax=4.6V  
Imax=1.12A  
Voc=5.89V  
Isc=1.26A

Circuit Choose

Buck  Boost

Compensator specification

fc=  Hz  
(0.1\*fsw~0.2\*fsw)

PM=  degree  
(45~70 is better)

Result

fc= 50000  
fo= 4170.55  
fesz= 17683.9  
GDC= 5  
Aco= 10.17  
P= -99.94  
Boost= 59.94  
Q= 2.73  
Type = 2

Compensator device value

R1=  Ohm C1=  F

R2=  Ohm C2=  F

R3=  Ohm C3=  F


System param

VM=  V

H=

K controller  PID controller

# IC Synthesis Software

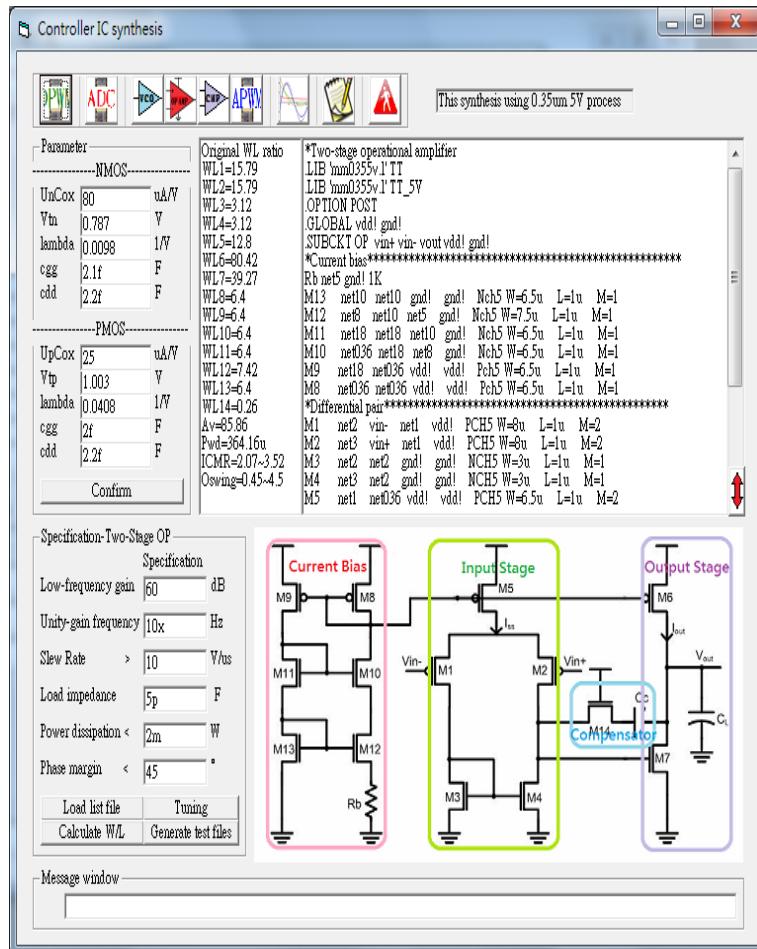

## Two-Stage OP

Term	Target	Simulation
Av	>60dB	75.17dB
Phase Margin	>45°	54.75 °
ICMR	0V-5V	0.06V-4.45V
CMRR	>60 dB	73.52dB
PSRR	>60 dB	76.88dB
Slew Rate	10 V/us	28.75 V/us
Unit-gain frequency	10 MHz	36.92 MHz
Output swing	>3V	0.075V-5V
Offset	>1V	53.31mV
Pwr dissipation	<2mW	0.9mW

## Hysteresis Comparator

Vtrp	110mV
------	-------


## Ramp Generator

Frequency	1kHz~60MHz
-----------	------------


## Programmable APWM

Power Dissipation	24.24 mW
Oscillator Frequency	16 MHz
Chip size	0.7 mm x 0.7mm <sup>7</sup>

# Controller Architecture (1/2)

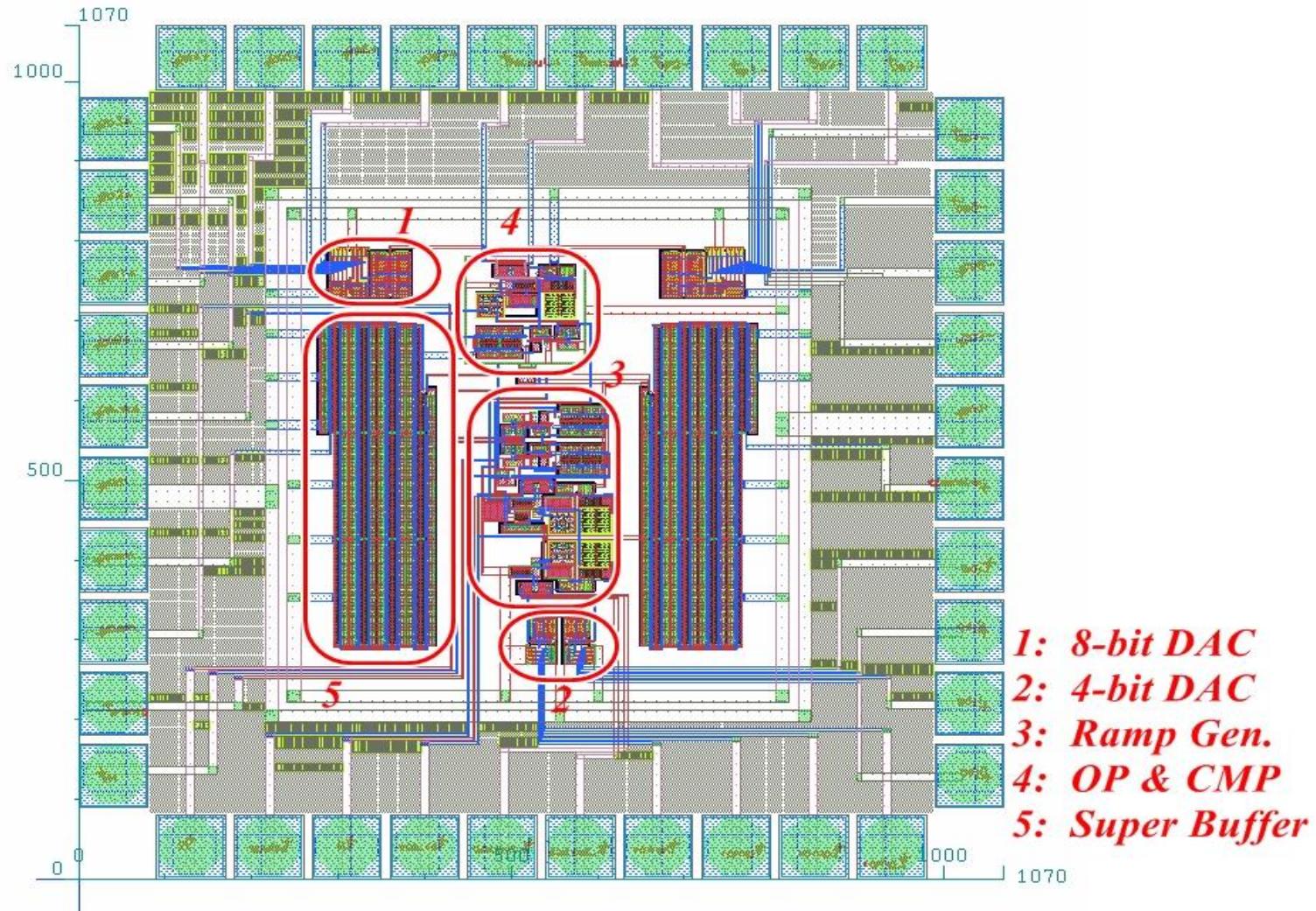


# Controller Architecture (2/2)

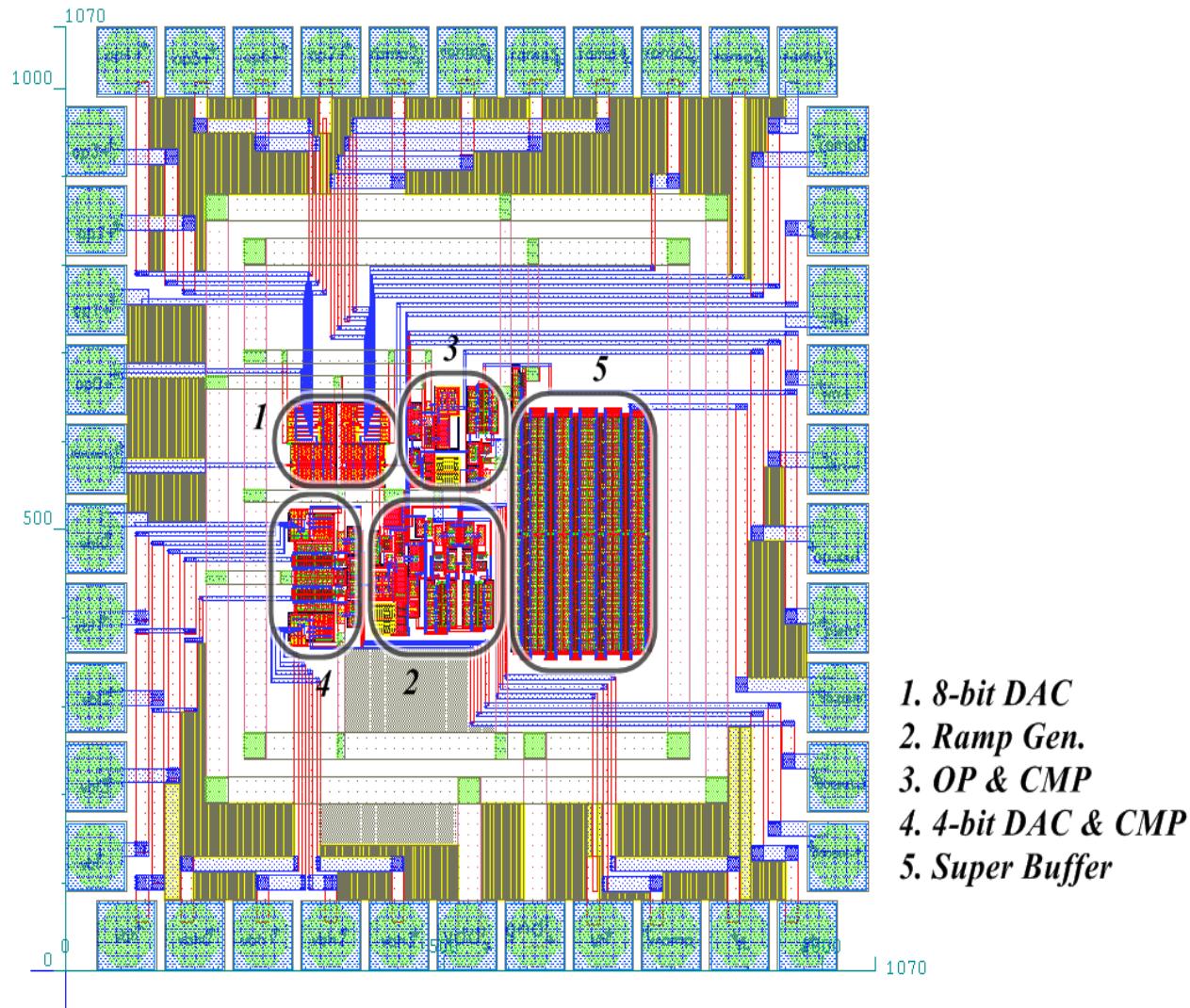


# Measurement

CIGS Solar Panel

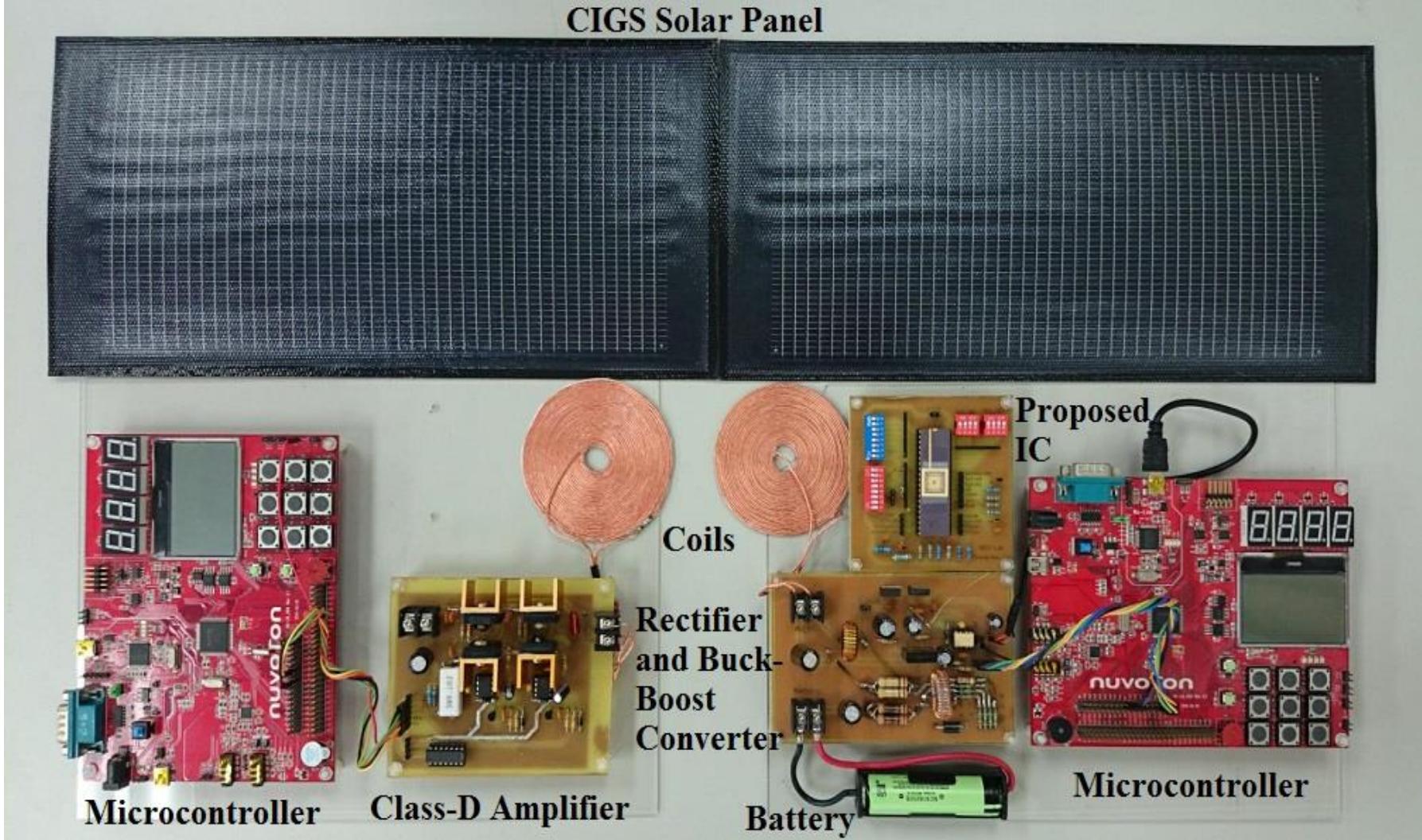

# Synthesis and Diagnosis Tool

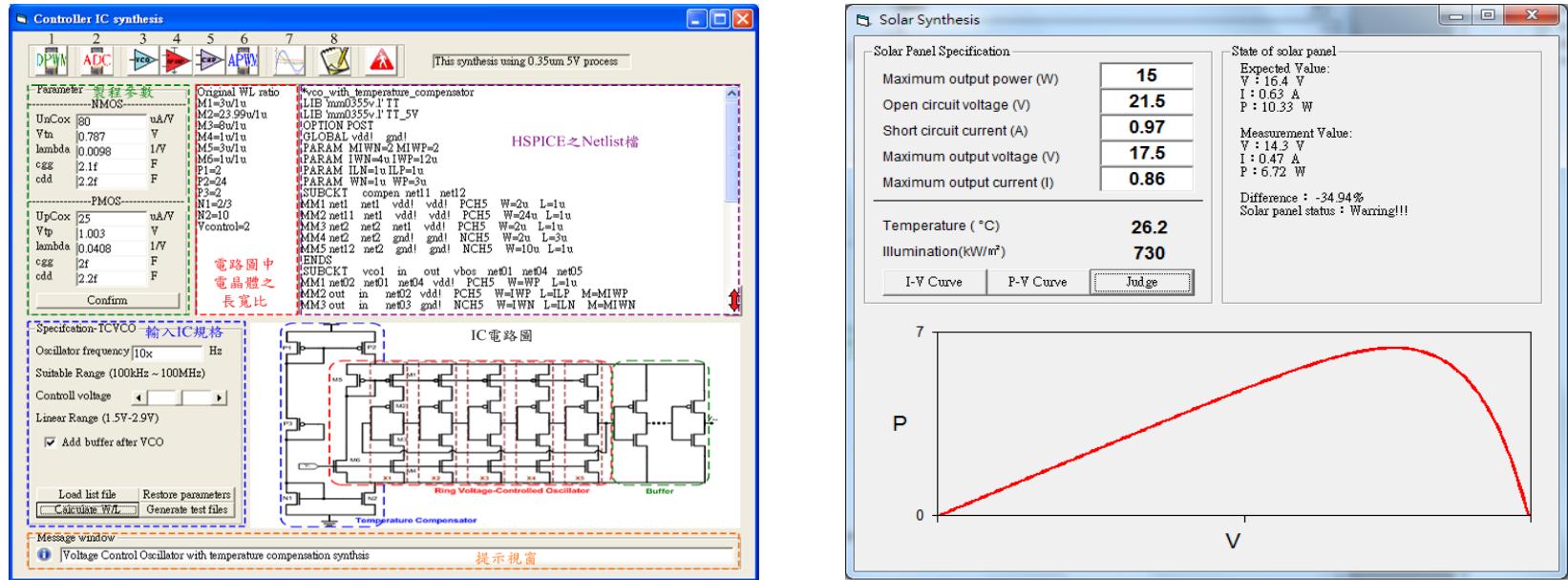

系統特點：

- 自行研發軟體合成無線充電積體電路系統，減少上市時間
- 本無線充電積體電路系統之電源為再生能源，不用市電
- 研發之軟體，可診斷積體電路系統操作現況，方便維護
- 可適用手機、家電、電動車、BIPV等產品


適用領域：能源與環境—其他—能源採集(Energy harvesting)

潛在客戶：手機業者/積體電路業者/軟體業者


# Outline

- 1-1. Steady-state analysis
  - 1) Buck converter
  - 2) Boost converter
  - 3) Buck-Boost converter
- 1-2. Transient-state analysis
  - 1) Buck converter
  - 2) Boost converter
  - 3) Buck-Boost converter


# Buck Model (1/7)

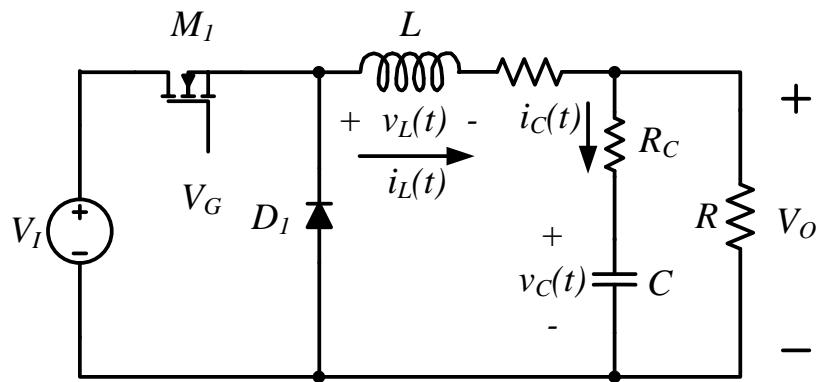

Position 1

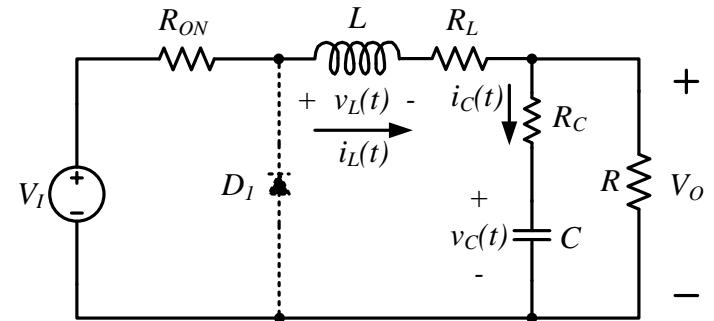

Position 2

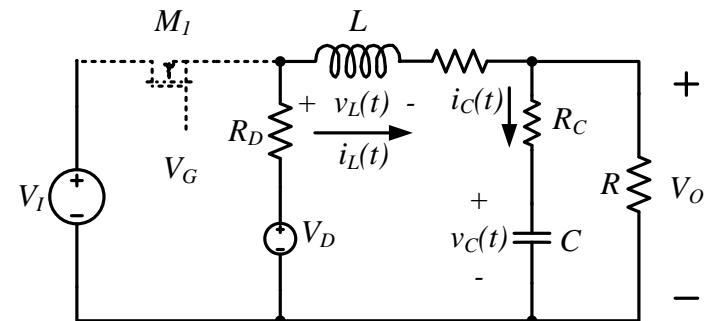


# Buck Model (2/7)

- Position 1

$$v_L(t) = V_I - i_L(t)(R_L + R_{ON} + R \parallel R_C) - v_C(t) \left( \frac{R}{R + R_C} \right)$$
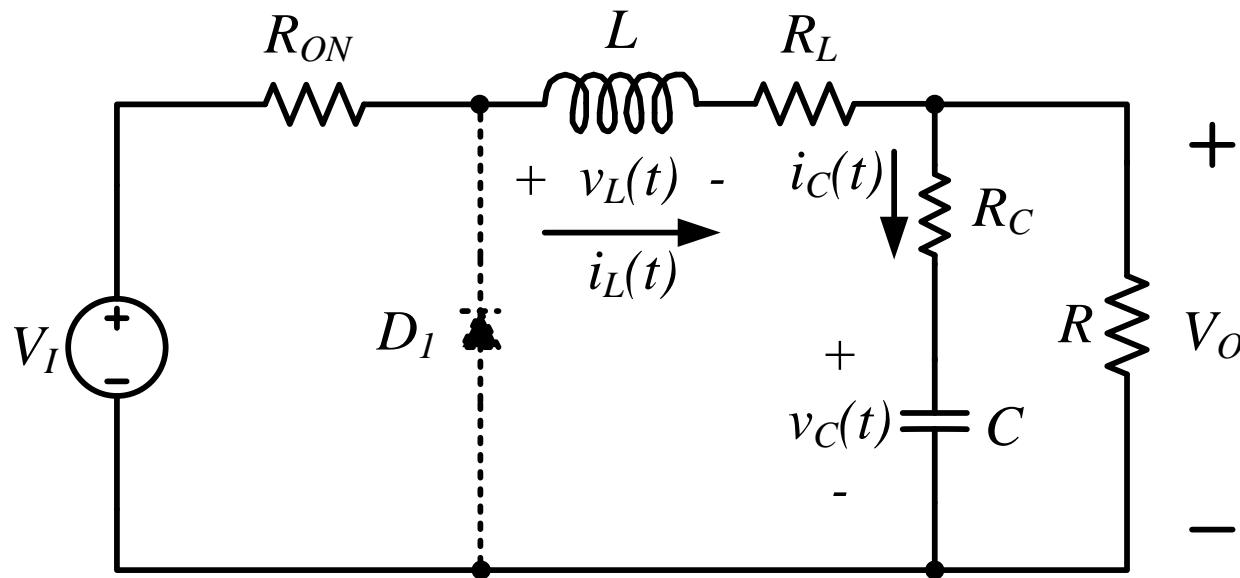
$$i_C(t) = i_L(t) \left( \frac{R}{R + R_C} \right) - v_C(t) \left( \frac{1}{R + R_C} \right)$$




# Buck Model (3/7)

- Small-ripple approximation
- Neglect  $R_C$ ,  $V_C = V_O$

$$v_L(t) = V_I - I_L(R_L + R_{ON}) - V_C$$

$$i_C(t) = I_L - \frac{V_C}{R}$$

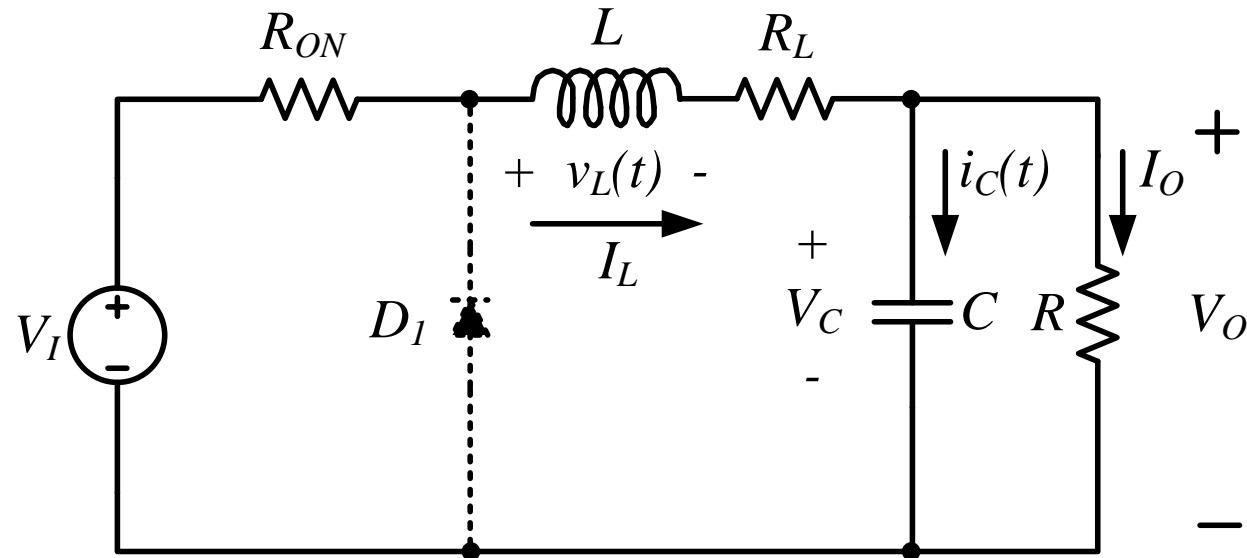


# Buck Model (4/7)

- Position 2

$$v_L(t) = -V_D - i_L(t)(R_L + R_D + R \parallel R_C) + v_C(t) \left( \frac{R}{R + R_C} \right)$$
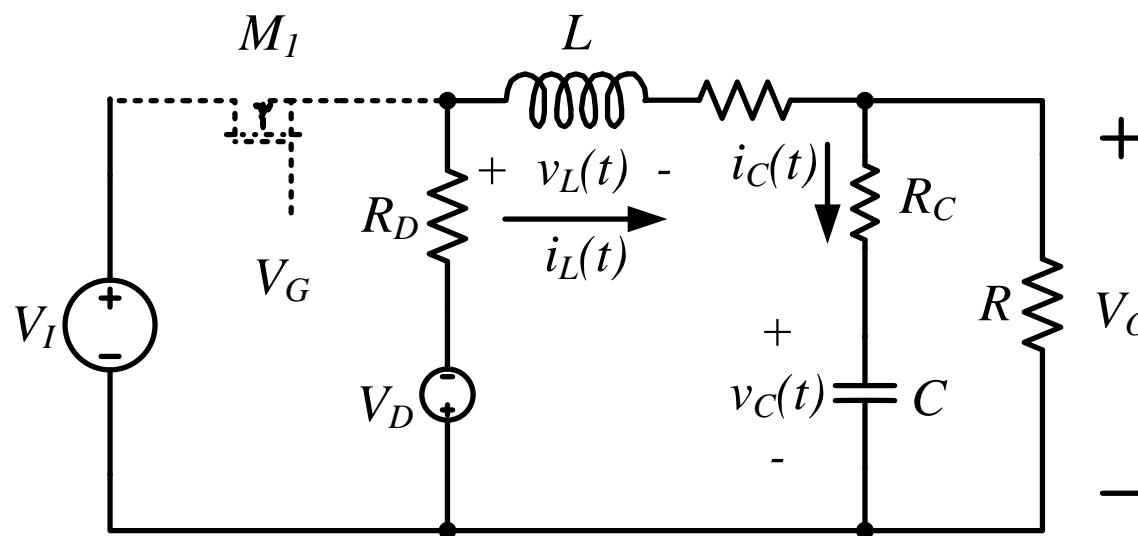
$$i_C(t) = i_L(t) \left( \frac{R}{R + R_C} \right) - v_C(t) \left( \frac{1}{R + R_C} \right)$$




# Buck Model (5/7)

- Small-ripple approximation
- Neglect  $R_C$ ,  $V_C = V_O$

$$v_L(t) = -V_D - I_L(R_L + R_D) + V_C$$

$$i_C(t) = I_L - \frac{V_C}{R}$$

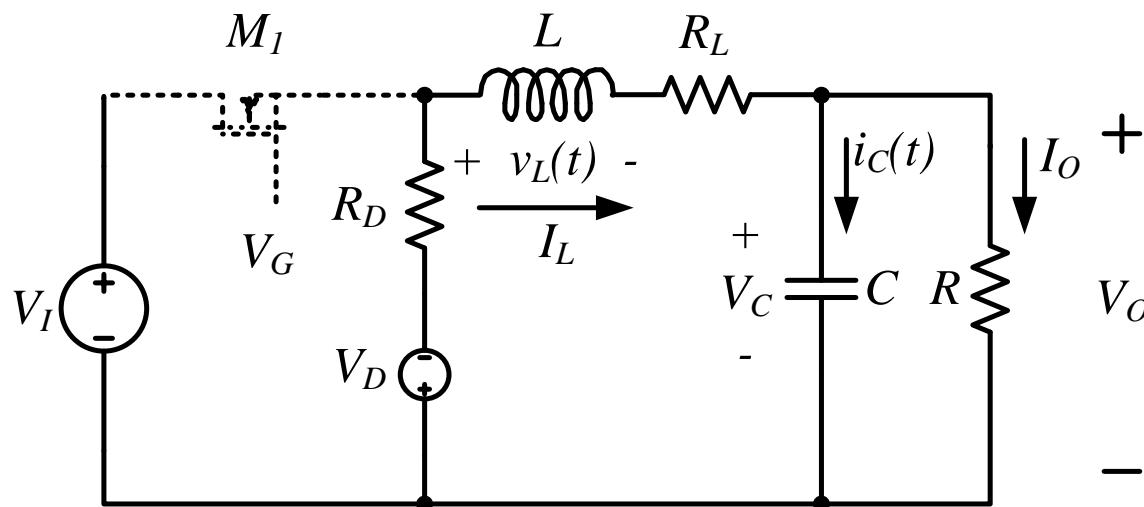


# Buck Model (6/7)

- Inductor volt-second balance
- Capacitor Charge Balance

$$\langle v_L(t) \rangle = DV_s - I_L (R_L + DR_{ON} + D'R_D) - V_o - D'V_D = 0$$

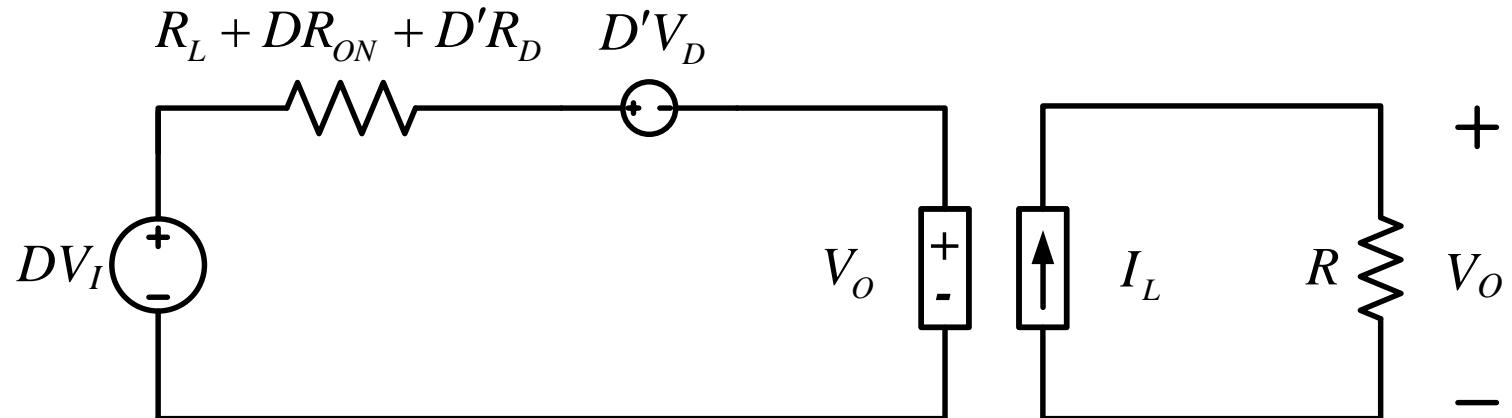
$$\langle i_c(t) \rangle = I_L - \frac{V_o}{R} = 0$$



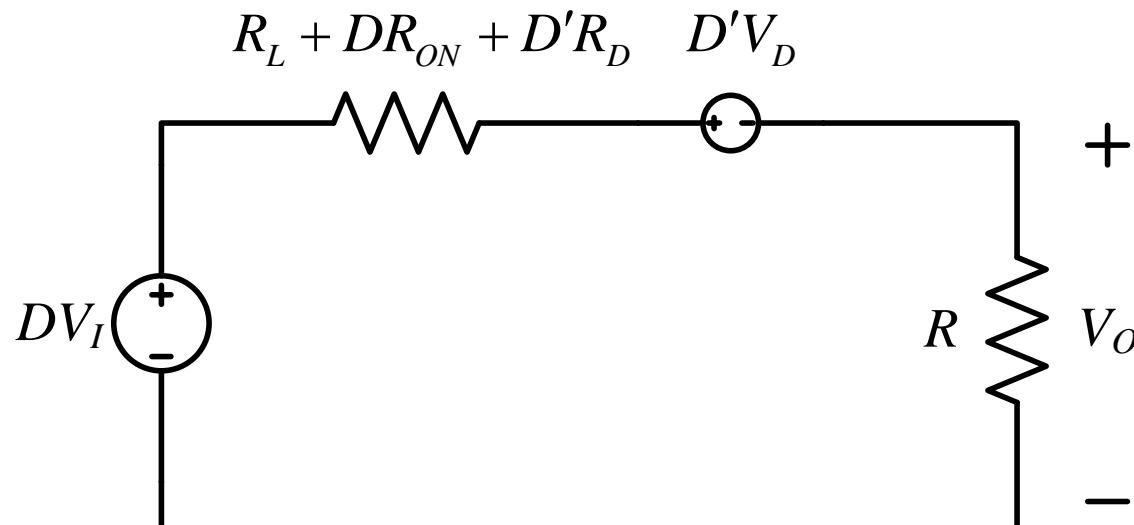
# Buck Model (7/7)

- Efficiency

$$\eta = \frac{V_o I_o}{DV_I I_I} = \frac{V_o}{DV_I} = \frac{\left(1 - \frac{D'V_D}{DV_S}\right)R}{R_L + DR_{ON} + D'R_D + R}$$



# Boost Model (1/7)

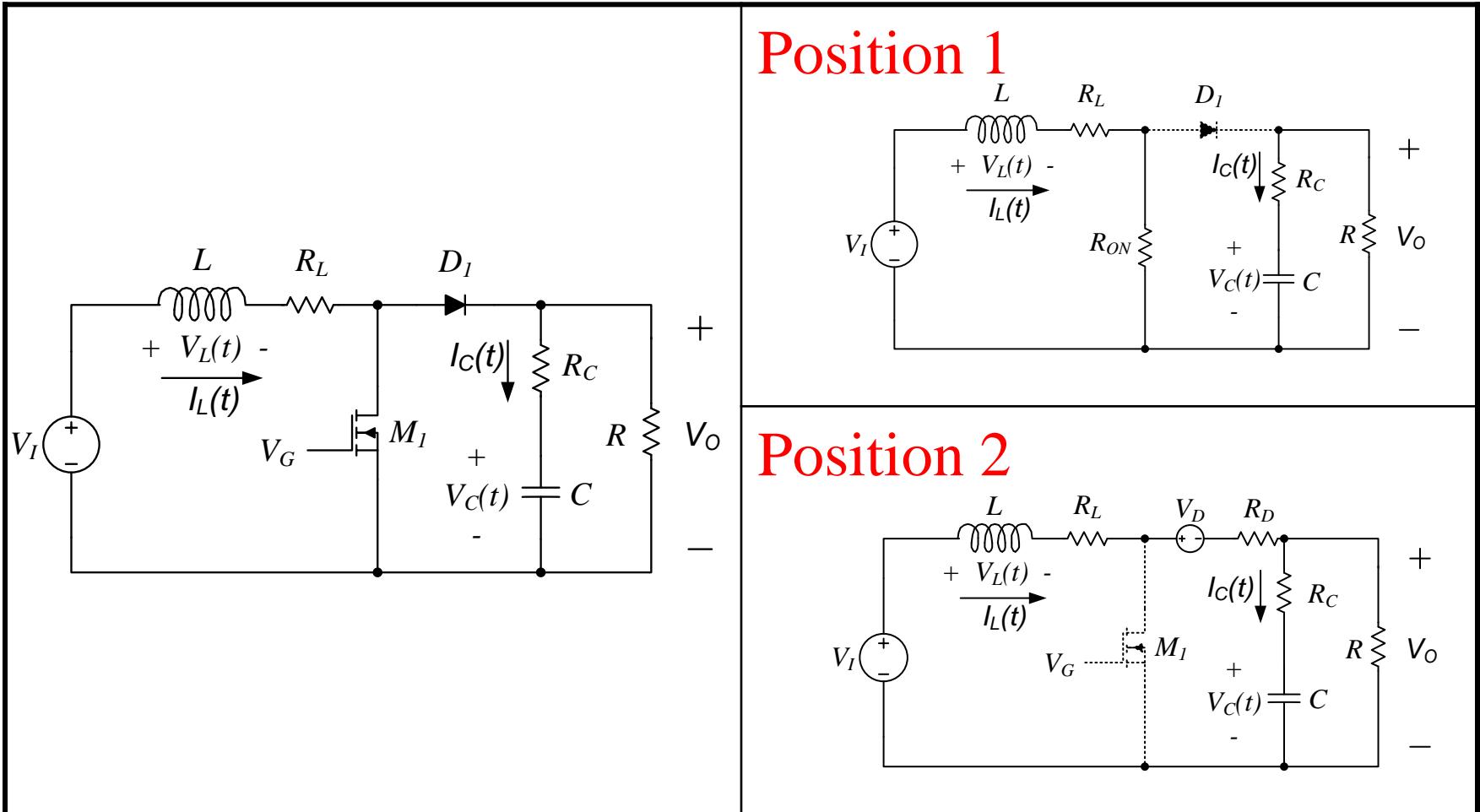


# Boost Model (2/7)

- Position 1

$$v_L(t) = V_I - i_L(t)(R_L + R_{ON})$$
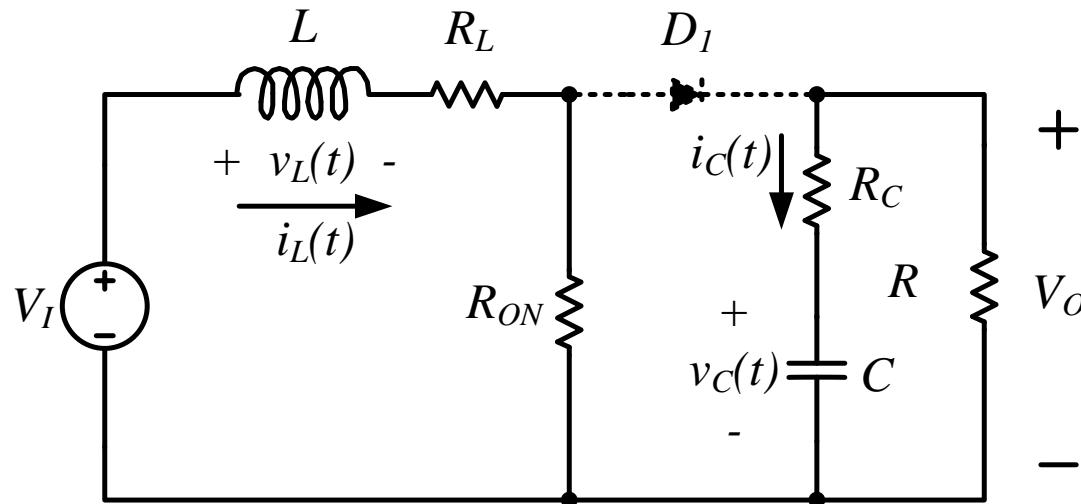
$$i_C(t) = -v_C(t) \left( \frac{1}{R + R_C} \right)$$




# Boost Model (3/7)

- Small-ripple approximation
- Neglect  $R_C$ ,  $V_C = V_O$

$$v_L(t) = V_I - I_L(R_L + R_{ON})$$

$$i_C(t) = -\frac{V_C}{R}$$

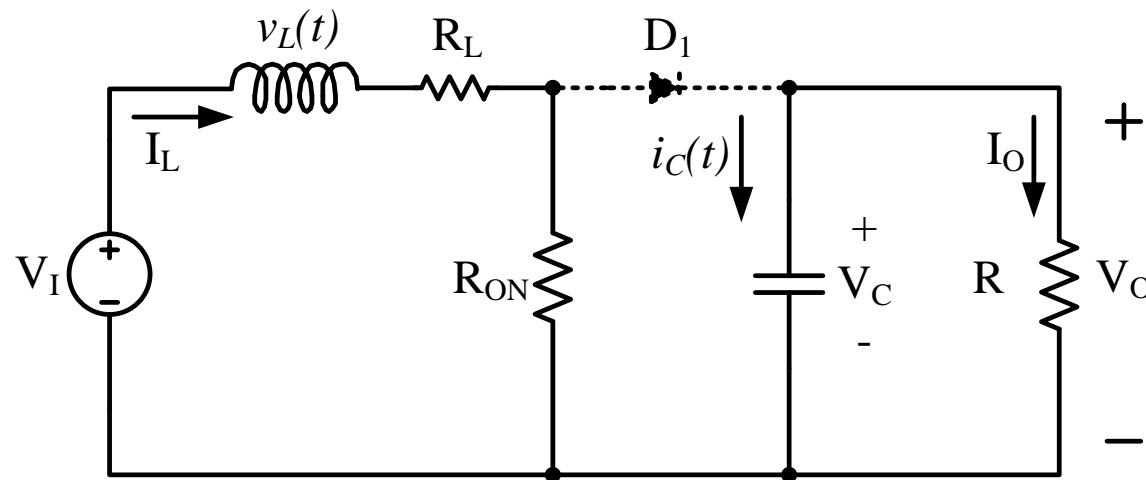


# Boost Model (4/7)

- Position 2

$$v_L(t) = V_I - V_D - i_L(t)(R_L + R_D + R \parallel R_C) - v_C(t) \left( \frac{R}{R + R_C} \right)$$
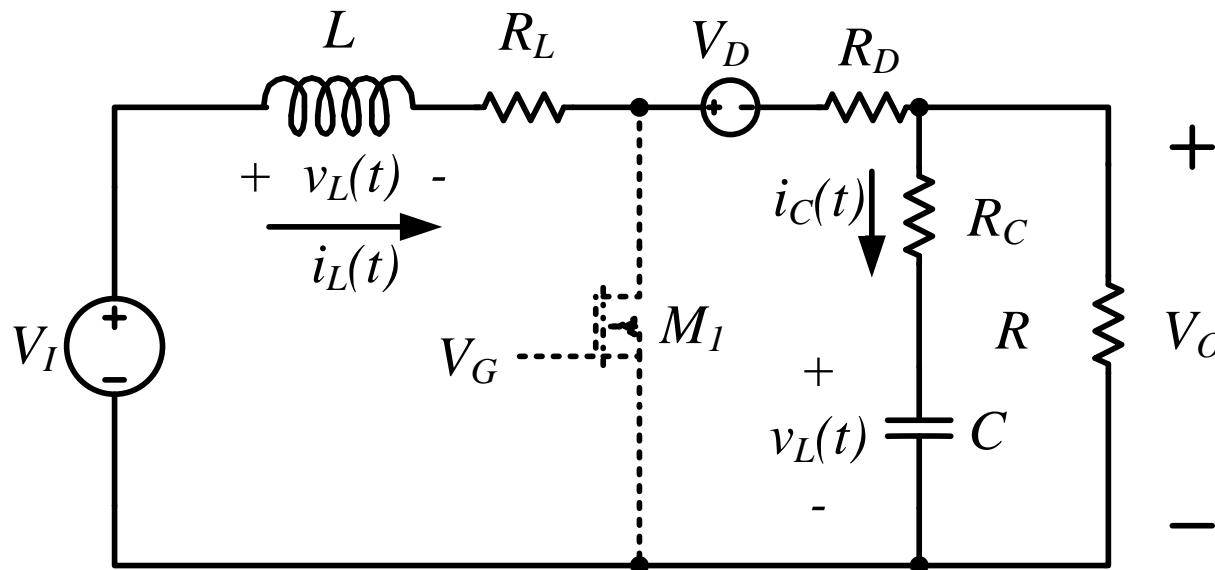
$$i_C(t) = i_L(t) \left( \frac{R}{R + R_C} \right) - v_C(t) \left( \frac{1}{R + R_C} \right)$$




# Boost Model (5/7)

- Small-ripple approximation
- Neglect  $R_C$ ,  $V_C = V_O$

$$v_L(t) = V_I - I_L(R_L + R_D) - V_D - V_C$$

$$i_C(t) = I_L - \frac{V_C}{R}$$

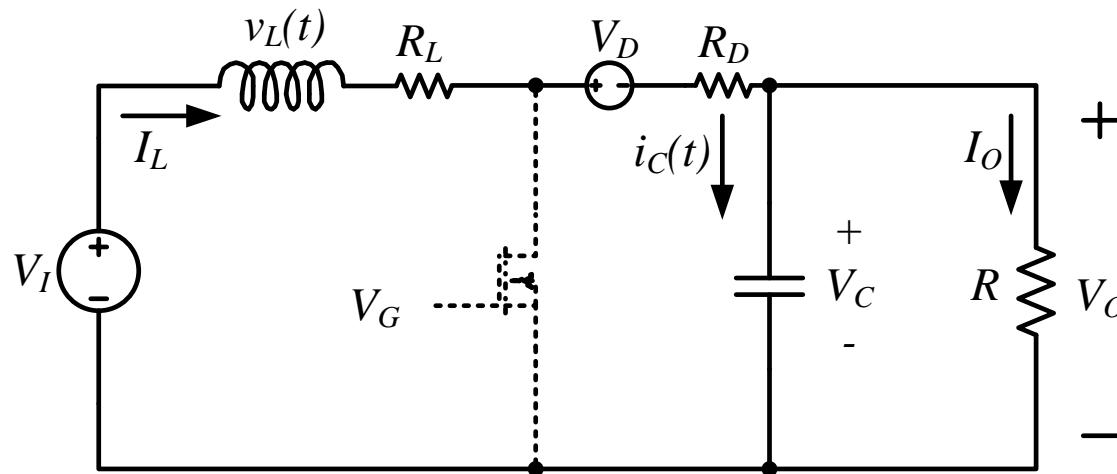


# Boost Model (6/7)

- Inductor volt-second balance
- Capacitor charge balance

$$\langle v_L(t) \rangle = V_I - I_L (R_L + DR_{ON} + D'R_D) - D'(V_o + V_D) = 0$$

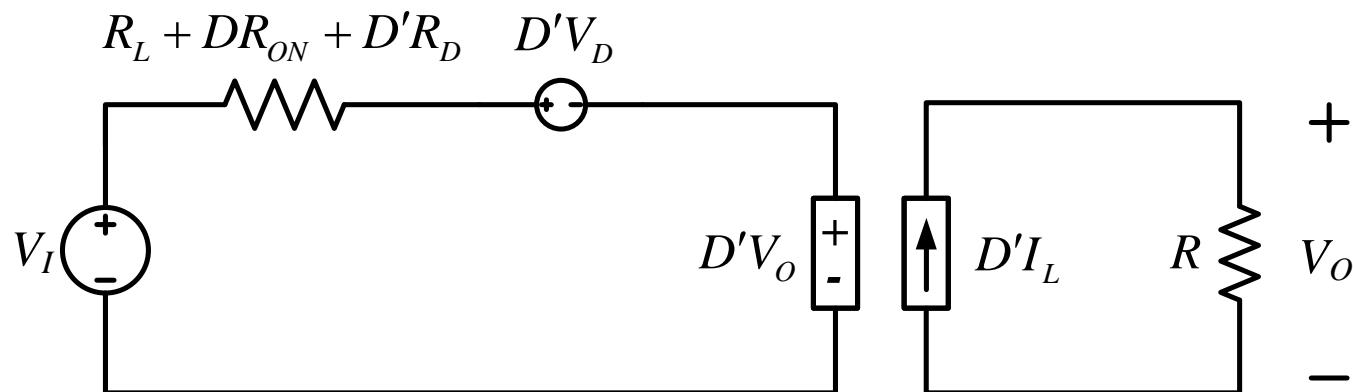
$$\langle i_C(t) \rangle = D'I_L - \frac{V_o}{R} = 0$$



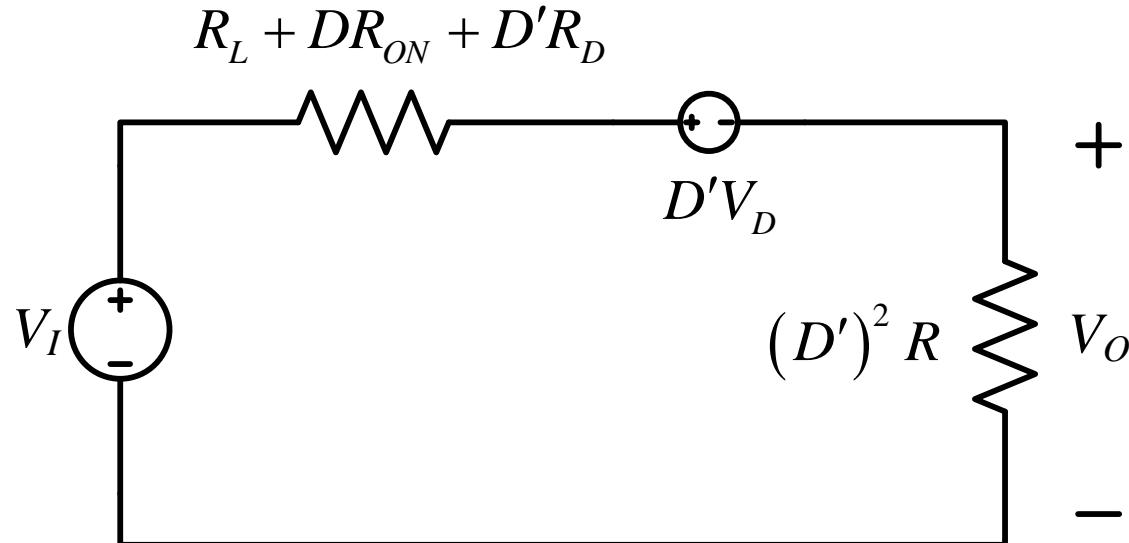
# Boost Model (7/7)

- Efficiency


$$\eta = \frac{V_o I_o}{V_I I_I} = \frac{V_o}{V_I} = \frac{\left(1 - D' \frac{V_D}{V_I}\right) (D')^2 R}{R_L + DR_{ON} + D'R_D + (D')^2 R} = \frac{1 - D' \frac{V_D}{V_I}}{1 + \frac{(R_L + DR_{ON} + D'R_D)}{(D')^2 R}}$$




# Buck-Boost Model (1/7)

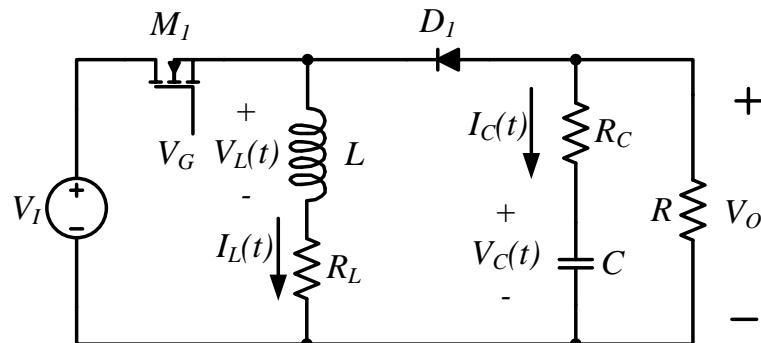

Position 1

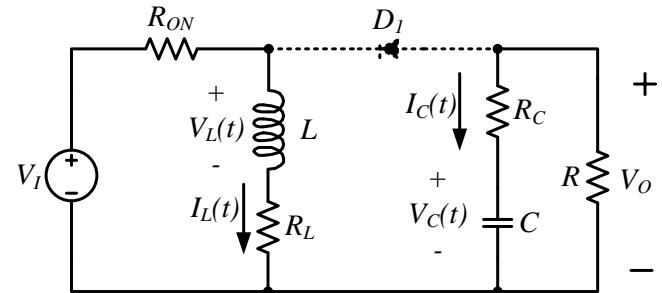

Position 2

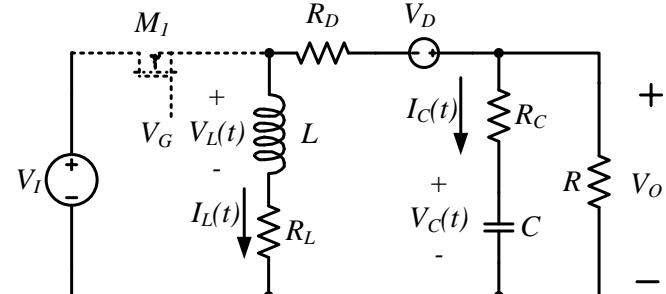


# Buck-Boost Model (2/7)

- Position 1

$$v_L(t) = V_I - i_L(t)(R_L + R_{ON})$$
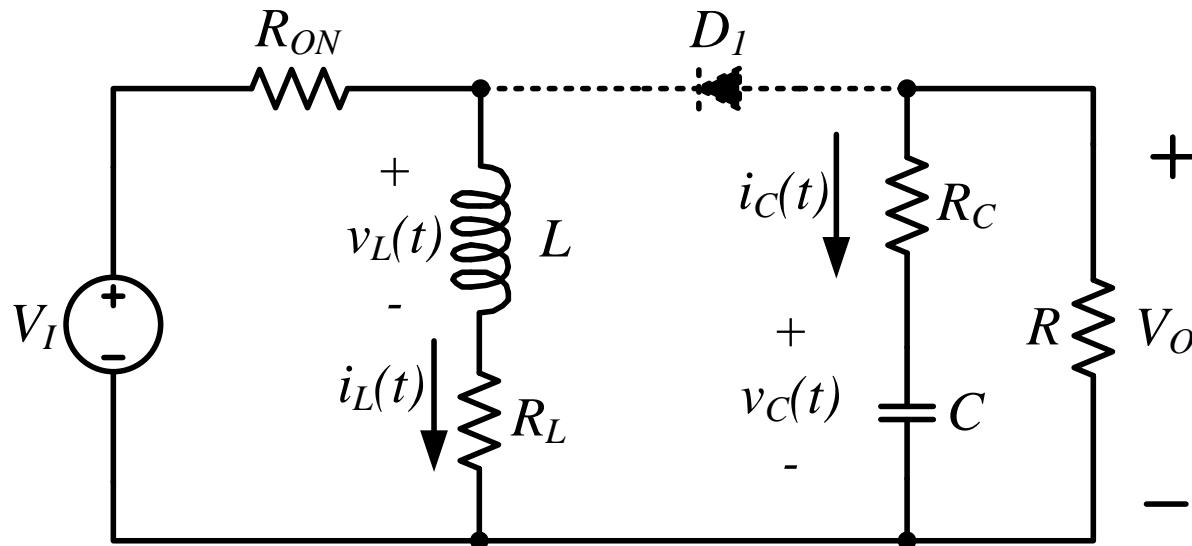
$$i_C(t) = -v_C(t) \left( \frac{1}{R + R_C} \right)$$




# Buck-Boost Model (3/7)

- Small-ripple approximation
- Neglect  $R_C$ ,  $V_C = V_O$

$$v_L(t) = V_I - I_L(R_L + R_{ON})$$

$$i_C(t) = -\frac{V_C}{R}$$

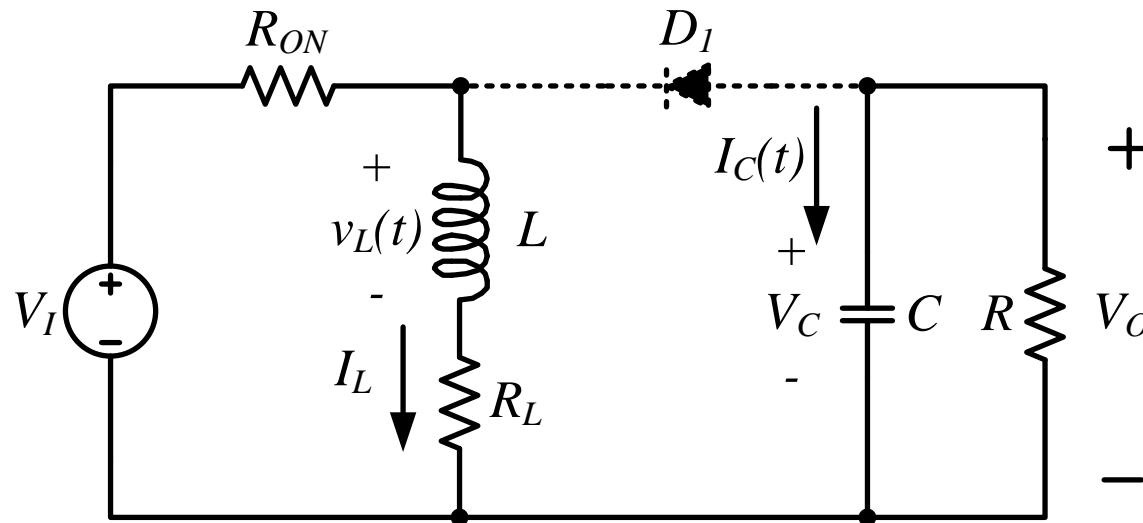


# Buck-Boost Model (4/7)

- Position 2

$$v_L(t) = v_C(t) \left( \frac{R}{R+R_C} \right) - i_L(t) (R_L + R_D + R \parallel R_C) - V_D$$
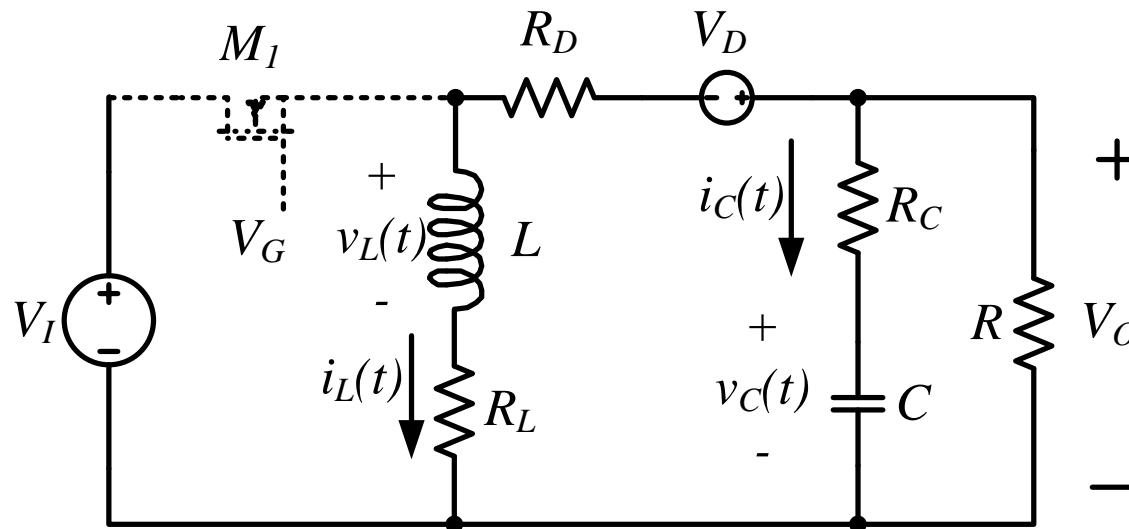
$$i_C(t) = -i_L(t) \left( \frac{R}{R+R_C} \right) - v_C(t) \left( \frac{1}{R+R_C} \right)$$




# Buck-Boost Model (5/7)

- Small-ripple approximation
- Neglect  $R_C$ ,  $V_C = V_O$

$$v_L(t) = V_C - I_L(R_L + R_D) - V_D$$

$$i_C(t) = -I_L - \frac{V_C}{R}$$

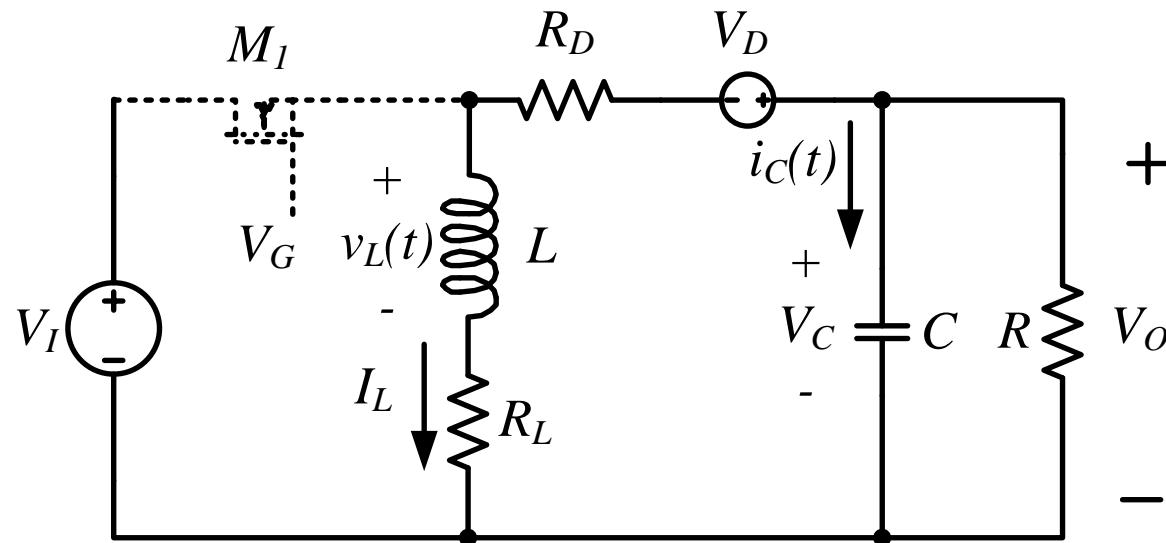


# Buck-Boost Model (6/7)

- Inductor volt-second balance
- Capacitor charge balance

$$\langle v_L(t) \rangle = DV_I - I_L (R_L + DR_{ON} + D'R_D) - D'V_D + D'V_o = 0$$

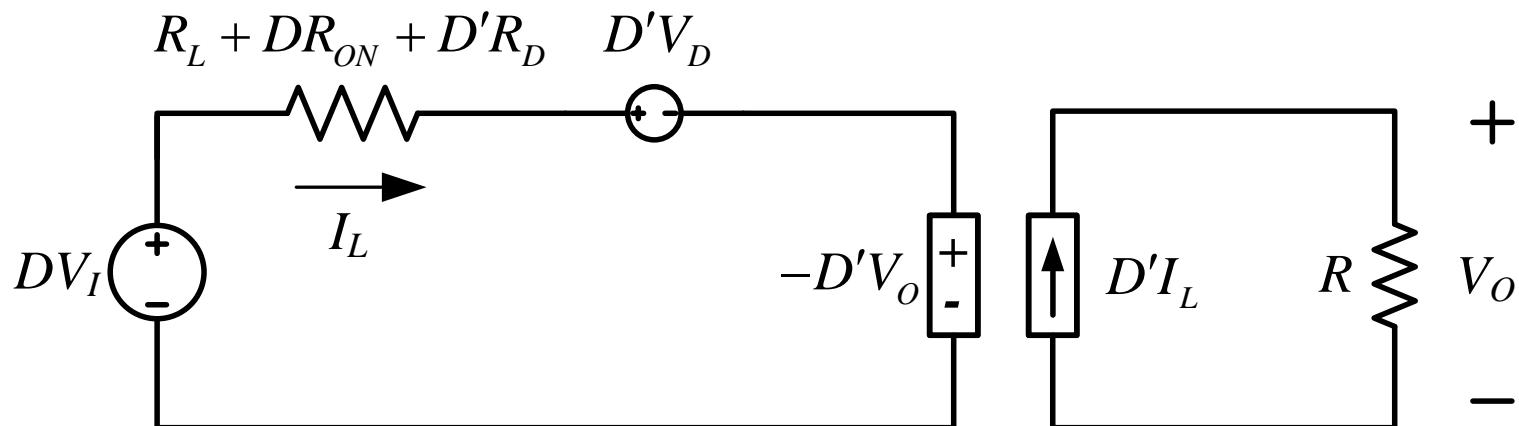
$$\langle i_C(t) \rangle = D'I_L - \frac{V_o}{R} = 0$$


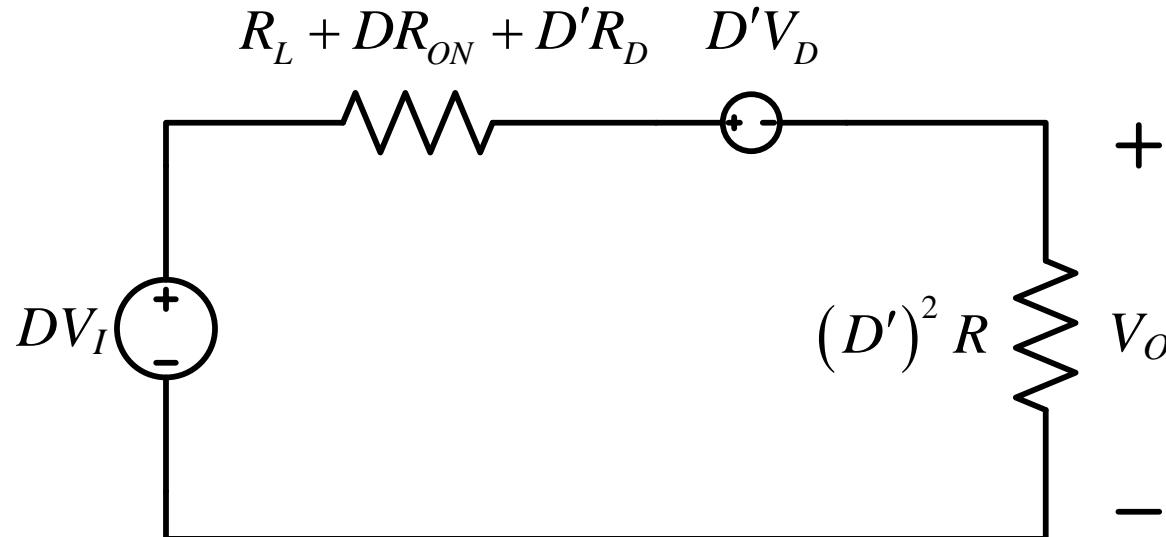
# Buck-Boost Model (7/7)

- Efficiency


$$\eta = \frac{V_o I_o}{D V_I I_I} = \frac{V_o}{D V_I} = \left( 1 - \frac{D' V_D}{D V_I} \right) \left( \frac{(D')^2 R}{R_L + D R_{ON} + D' R_D + (D')^2 R} \right)$$




# Outline

- **1-1. Steady-state analysis**
  - 1) Buck converter
  - 2) Boost converter
  - 3) Buck-Boost converter
- **1-2. Transient-state analysis**
  - 1) Buck converter
  - 2) Boost converter
  - 3) Buck-Boost converter


# Converter's Transient-state Block

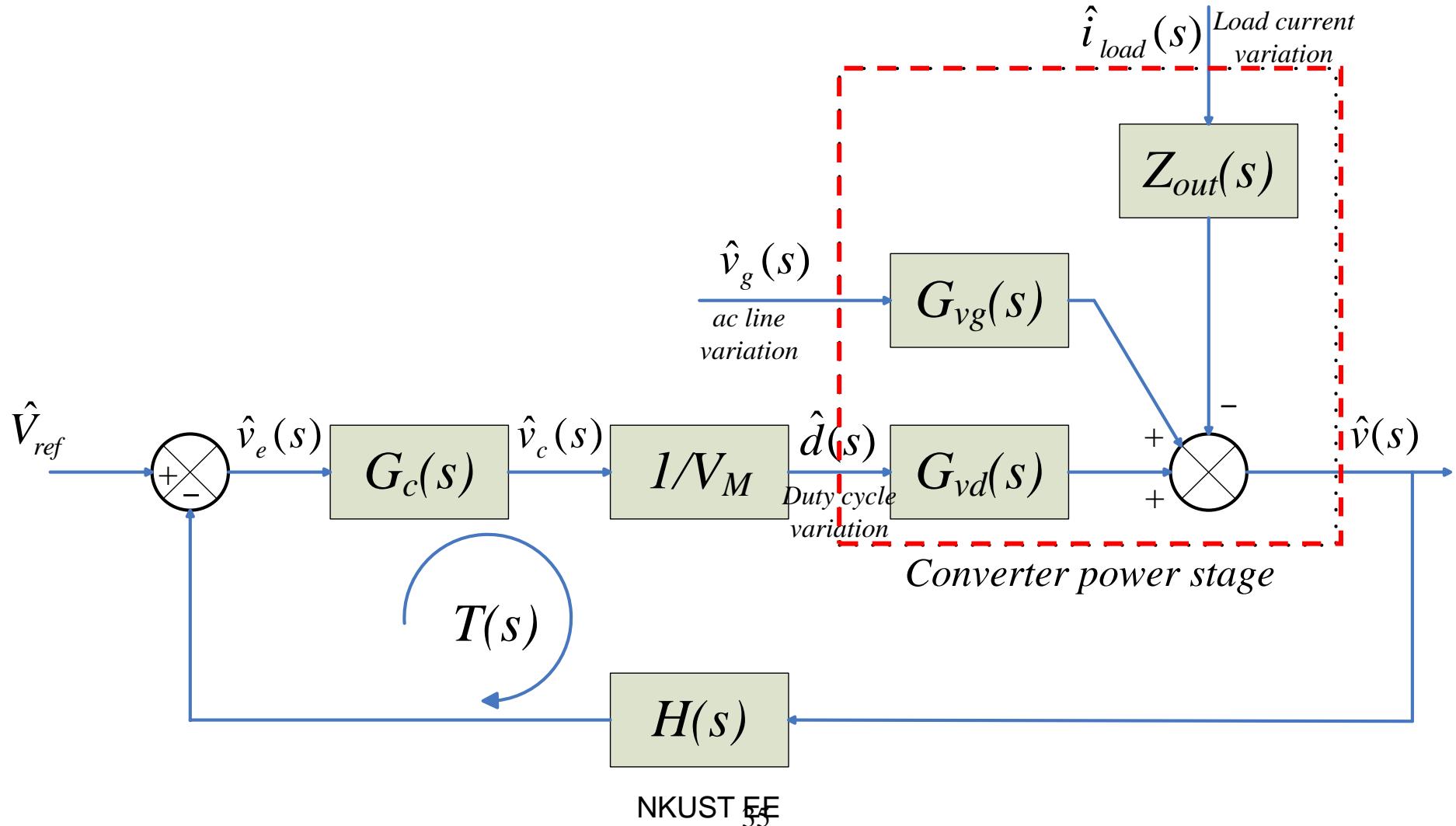

# Buck (1/10)

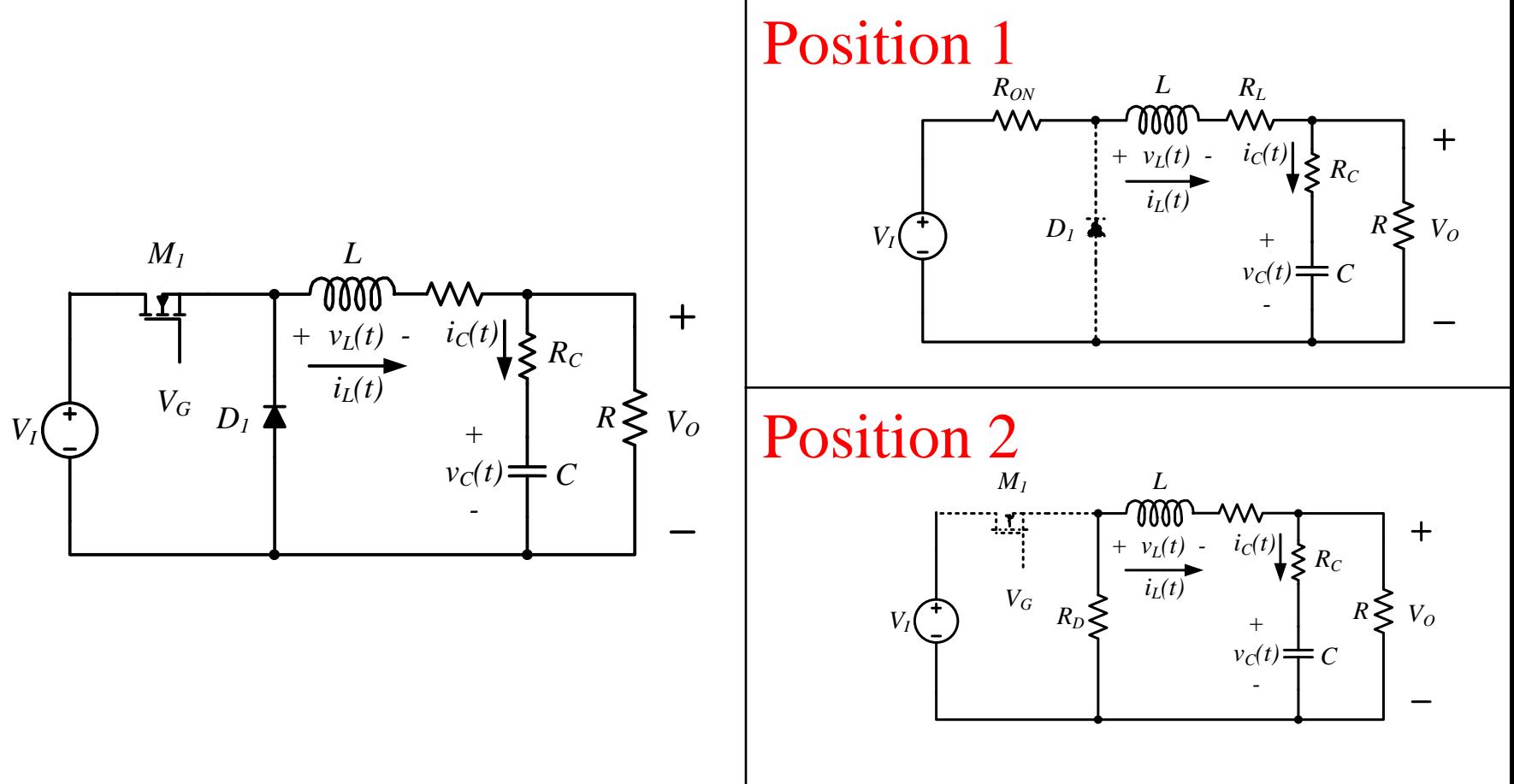

# Buck (2/10)

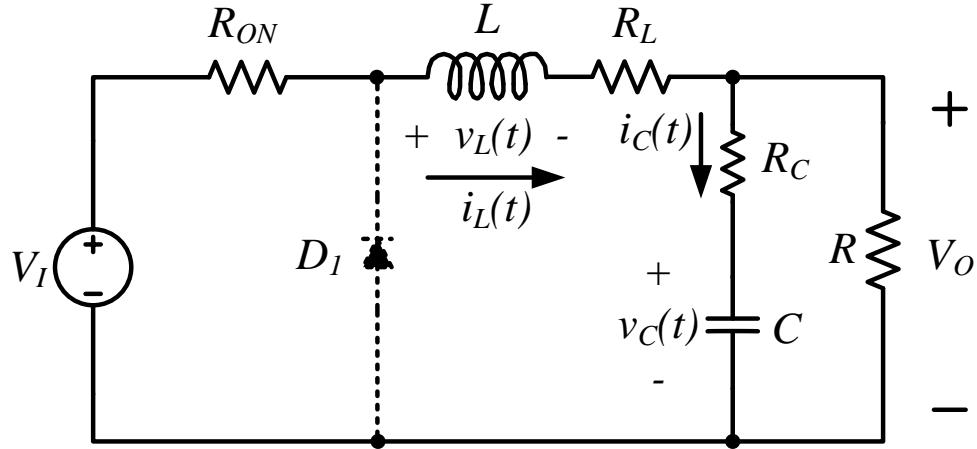

Position 1

$$\begin{bmatrix} \frac{di_L}{dt} \\ \frac{dv_C}{dt} \end{bmatrix} = \begin{bmatrix} -\frac{R_{ON} + R_L + R \parallel R_C}{L} & -\frac{R}{(R+R_C)L} \\ \frac{R}{(R+R_C)C} & -\frac{1}{(R+R_C)C} \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix} + \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} V_I$$

$$[v_o] = \begin{bmatrix} R \parallel R_C & \frac{R}{R+R_C} \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix}$$

$$[i_i] = [1 \ 0] \begin{bmatrix} i_L \\ v_C \end{bmatrix}$$


$$A_1 = \begin{bmatrix} -\frac{R_{ON} + R_L + R \parallel R_C}{L} & -\frac{R}{(R+R_C)L} \\ \frac{R}{(R+R_C)C} & -\frac{1}{(R+R_C)C} \end{bmatrix}$$

$$B_1 = \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix}$$

$$C_1 = \begin{bmatrix} R \parallel R_C & \frac{R}{R+R_C} \end{bmatrix}$$

$$C'_1 = [1 \ 0]$$

# Buck (3/10)

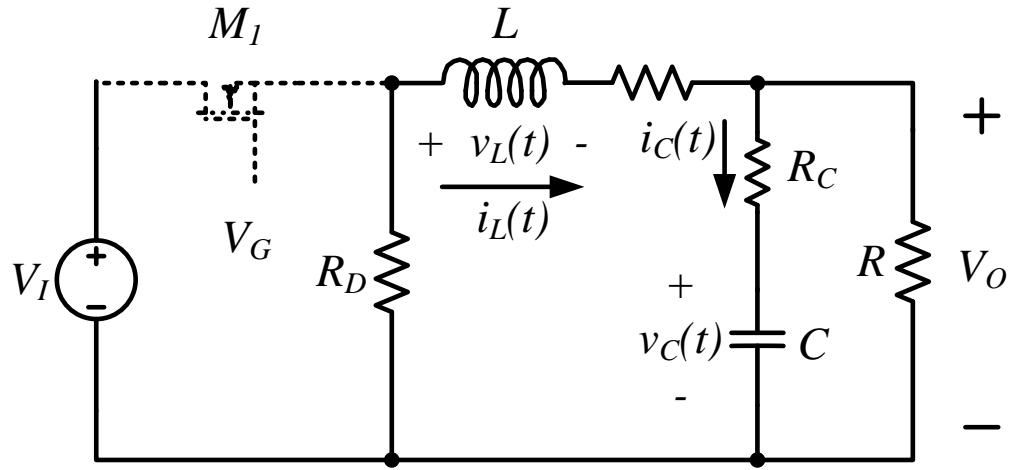

Position 2

$$\begin{bmatrix} \frac{di_L}{dt} \\ \frac{dv_C}{dt} \end{bmatrix} = \begin{bmatrix} -\frac{R_D + R_L + R \parallel R_C}{L} & -\frac{R}{(R+R_C)L} \\ \frac{R}{(R+R_C)C} & -\frac{1}{C(R+R_C)} \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \end{bmatrix} V_I$$

$$[v_o] = \begin{bmatrix} R \parallel R_C & \frac{R}{R+R_C} \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix}$$

$$[i_i] = \begin{bmatrix} 0 & 0 \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix}$$

$$A_2 = \begin{bmatrix} -\frac{R_D + R_L + R \parallel R_C}{L} & -\frac{R}{(R+R_C)L} \\ \frac{R}{(R+R_C)C} & -\frac{1}{C(R+R_C)} \end{bmatrix}$$

$$B_2 = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

$$C_2 = \begin{bmatrix} R \parallel R_C & \frac{R}{R+R_C} \end{bmatrix}$$

$$C'_1 = [0 \quad 0]$$

# Buck (4/10)

$$A = DA_1 + D'A_2 = \begin{bmatrix} -\frac{(DR_{ON} + D'R_D + R_L + R \| R_C)}{L} & -\frac{R}{(R + R_C)L} \\ \frac{R}{(R + R_C)C} & -\frac{1}{(R + R_C)C} \end{bmatrix}$$

$$B = DB_1 + D'B_2 = \begin{bmatrix} \frac{D}{L} \\ 0 \end{bmatrix}$$

$$C = DC_1 + D'C_2 = \begin{bmatrix} R \| R_C & \frac{R}{R + R_C} \end{bmatrix}$$

$$C' = DC'_1 + D'C'_2 = [D \quad 0]$$

$$A_1 - A_2 = \begin{bmatrix} \frac{-R_{ON} + R_D}{L} & 0 \\ 0 & 0 \end{bmatrix}$$

$$B_1 - B_2 = \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix}$$

$$C_1 - C_2 = 0$$

$$F = \begin{bmatrix} \frac{-R_{ON} + R_D}{L} & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} I_L \\ V_C \end{bmatrix} + \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} \begin{bmatrix} V_I \end{bmatrix}$$

# Buck (5/10)

$$(SI - A)^{-1} = \frac{adj(SI - A)}{|SI - A|}$$

$$(SI - A)^{-1} = \begin{bmatrix} S + \frac{DR_{ON} + D'R_D + R_L + R \| R_C}{L} & \frac{R}{(R + R_C)L} \\ -\frac{R}{(R + R_C)C} & S + \frac{1}{(R + R_C)C} \end{bmatrix}^{-1}$$

$$adj(SI - A) = \begin{bmatrix} S + \frac{1}{(R + R_C)C} & -\frac{R}{(R + R_C)L} \\ \frac{R}{(R + R_C)C} & S + \frac{DR_{ON} + D'R_D + R_L + R \| R_C}{L} \end{bmatrix}$$

$$|SI - A| = S^2 + S \left( \frac{1}{L} \right) \left( DR_{ON} + D'R_D + R_L + R \| R_C + \frac{L}{(R + R_C)C} \right) + \left( \frac{DR_{ON} + D'R_D + R_L + R}{LC(R + R_C)} \right)$$

# Buck (6/10)

$$\left. \frac{\hat{v}_o(S)}{\hat{v}_i(S)} \right|_{\hat{d}(s)=0} = C(SI - A)^{-1} B$$

$$\left. \frac{\hat{v}_o(S)}{\hat{v}_i(S)} \right|_{\hat{d}(s)=0} = \begin{bmatrix} R \parallel R_C & \frac{R}{R+R_C} \end{bmatrix} \begin{bmatrix} S + \frac{DR_{ON} + D'R_D + R_L + R \parallel R_C}{L} & \frac{R}{(R+R_C)L} \\ -\frac{R}{(R+R_C)C} & S + \frac{1}{(R+R_C)C} \end{bmatrix}^{-1} \begin{bmatrix} \frac{D}{L} \\ 0 \end{bmatrix}$$

$$\left. \frac{\hat{v}_o(S)}{\hat{v}_i(S)} \right|_{\hat{d}(s)=0} = \frac{DR}{\Delta} \left( \frac{SR_C C + 1}{(R+R_C)LC} \right)$$

# Buck (7/10)

$$\left. \frac{\hat{v}_o(S)}{\hat{d}(S)} \right|_{\hat{u}(s)=0} = C(SI - A)^{-1} F$$

$$\left. \frac{\hat{v}_o(S)}{\hat{d}(S)} \right|_{\hat{u}(s)=0} = \begin{bmatrix} R \| R_C & R \\ R & R + R_C \end{bmatrix} \begin{bmatrix} S + \frac{DR_{ON} + D'R_D + R_L + R \| R_C}{L} & \frac{R}{(R + R_C)L} \\ -\frac{R}{(R + R_C)C} & S + \frac{1}{(R + R_C)C} \end{bmatrix}^{-1} \begin{pmatrix} \begin{bmatrix} -R_{ON} + R_D \\ L \end{bmatrix} & 0 \\ \begin{bmatrix} I_L \\ V_C \end{bmatrix} & \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} \end{pmatrix} + \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} [V_I]$$

$$\left. \frac{\hat{v}_o(S)}{\hat{d}(S)} \right|_{\hat{u}(s)=0} = C(SI - A)^{-1} \begin{bmatrix} \frac{(-R_{ON} + R_D)I_L + V_I}{L} \\ 0 \end{bmatrix}$$

$$\left. \frac{\hat{v}_o(S)}{\hat{d}(S)} \right|_{\hat{u}(s)=0} = \frac{1}{\Delta} \left( \frac{R((-R_{ON} + R_D)I_L + V_I)(SR_C C + 1)}{(R + R_C)LC} \right)$$

# Buck (8/10)

$$\left. \frac{\hat{i}_i(S)}{\hat{v}_i(S)} \right|_{\hat{d}(s)=0} = C'(SI - A)^{-1}B$$

$$\left. \frac{\hat{i}_i(S)}{\hat{v}_i(S)} \right|_{\hat{d}(s)=0} = [D \quad 0] \begin{bmatrix} S + \frac{DR_{ON} + D'R_D + R_L + R \| R_C}{L} & \frac{R}{(R+R_C)L} \\ -\frac{R}{(R+R_C)C} & S + \frac{1}{(R+R_C)C} \end{bmatrix}^{-1} \begin{bmatrix} \frac{D}{L} \\ 0 \end{bmatrix}$$

$$\left. \frac{\hat{i}_i(S)}{\hat{v}_i(S)} \right|_{\hat{d}(s)=0} = \frac{D}{\Delta} \left( \frac{S(R+R_C)C + 1}{(R+R_C)LC} \right)$$

$$\Delta = S^2 + S \left( \frac{1}{L} \right) \left( DR_{ON} + D'R_D + R_L + R \| R_C + \frac{L}{(R+R_C)C} \right) + \left( \frac{DR_{ON} + D'R_D + R_L + R}{LC(R+R_C)} \right)$$

$$Z'_{in} = D^2 Z_{in}$$

$$Z_{out}(S) = \frac{Z_1 Z_2}{Z'_{in}} = \left( 1 - \frac{R(SR_C C + 1)}{\Delta(R+R_C)LC} \right) \left( \frac{R(SR_C C + 1)}{S(R+R_C)C + 1} \right)$$

# Buck (9/10)

$$\left. \frac{\hat{v}_o(S)}{\hat{v}_i(S)} \right|_{\hat{d}(s)=0} = \frac{DR}{\Delta} \left( \frac{SR_c C + 1}{(R + R_c)LC} \right)$$

$$\Delta = S^2 + S \left( \frac{1}{L} \right) \left( DR_{ON} + D'R_D + R_L + R \parallel R_C + \frac{L}{(R + R_c)C} \right) + \left( \frac{DR_{ON} + D'R_D + R_L + R}{(R + R_c)LC} \right)$$

$$\left. \frac{\hat{v}_o(S)}{\hat{v}_i(S)} \right|_{\hat{d}(s)=0} = \frac{C_3 S^{-1} + C_4 S^{-2}}{1 - (-C_1 S^{-1} - C_2 S^{-2})}$$


$$C_1 = \left( \frac{1}{L} \right) \left( DR_{ON} + D'R_D + R_L + R \parallel R_C + \frac{L}{(R + R_c)C} \right)$$

$$C_2 = \frac{DR_{ON} + D'R_D + R_L + R}{(R + R_c)LC}$$

$$C_3 = R_c C$$

$$C_4 = 1$$

$$K = \frac{DR}{(R + R_c)LC}$$

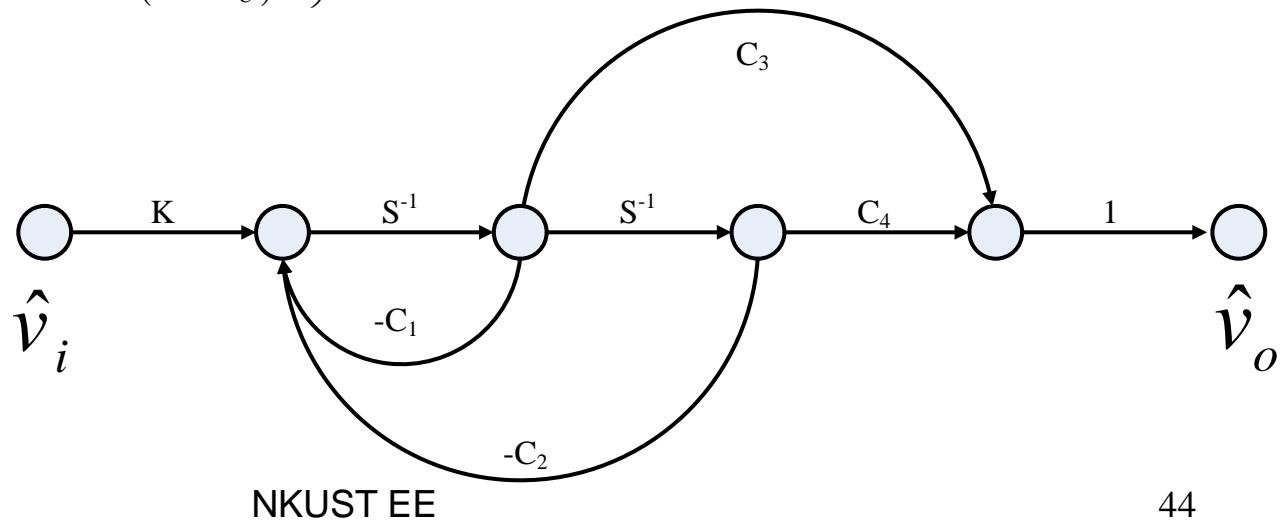

# Buck (10/10)

$$\left. \frac{\hat{v}_o(S)}{\hat{d}(S)} \right|_{\hat{u}(s)=0} = \frac{1}{\Delta} \left( \frac{R((-R_{ON} + R_D)I_L + V_I)(SR_C C + 1)}{(R + R_C)LC} \right)$$

$$\Delta = S^2 + S \left( \frac{1}{L} \right) \left( DR_{ON} + D'R_D + R_L + R \parallel R_C + \frac{L}{(R + R_C)C} \right) + \left( \frac{DR_{ON} + D'R_D + R_L + R}{(R + R_C)LC} \right)$$

$$\left. \frac{\hat{v}_o(S)}{\hat{d}(S)} \right|_{V_I(s)=0} = \frac{K(C_3 S^{-1} + C_4 S^{-2})}{1 - (-C_1 S^{-1} - C_2 S^{-2})}$$


$$C_1 = \left( \frac{1}{L} \right) \left( DR_{ON} + D'R_D + R_L + R \parallel R_C + \frac{L}{(R + R_C)C} \right)$$

$$C_2 = \frac{DR_{ON} + D'R_D + R_L + R}{(R + R_C)LC}$$

$$C_3 = R_C C$$

$$C_4 = 1$$

$$K = R((-R_{ON} + R_D)I_L + V_I)$$

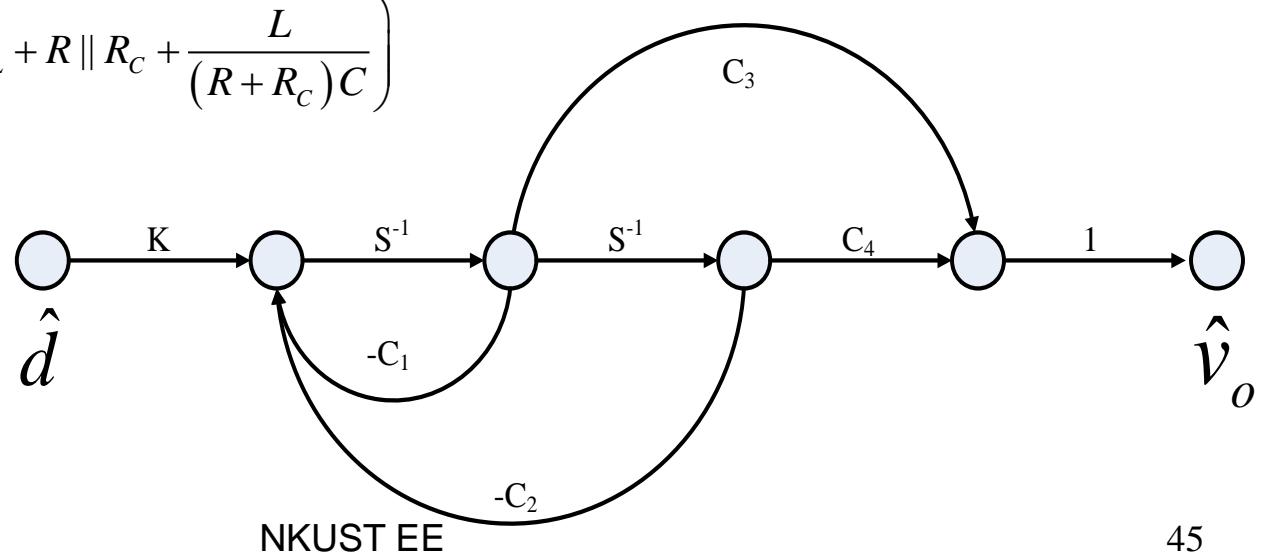


Type	Buck
$G_{vg}(S)$	$\frac{DR}{\Delta} \left( \frac{SR_c C + 1}{(R + R_c)LC} \right)$
$G_{vd}(S)$	$\frac{1}{\Delta} \left( \frac{R((-R_{ON} + R_D)I_L + V_I)(SR_c C + 1)}{(R + R_c)LC} \right)$
$Z_{out}(s)$	$\left( 1 - \frac{R(SR_c C + 1)}{\Delta(R + R_c)LC} \right) \left( \frac{R(SR_c C + 1)}{S(R + R_c)C + 1} \right)$
$\omega_z$	$-\frac{1}{R_c C}$
$\Delta = S^2 + S \left( \frac{1}{L} \right) \left( DR_{ON} + D'R_D + R_L + R \parallel R_c + \frac{L}{(R + R_c)C} \right) + \left( \frac{DR_{ON} + D'R_D + R_L + R}{LC(R + R_c)} \right)$	


# Outline

- 1-1. Steady-state analysis
  - 1) Buck converter
  - 2) Boost converter
  - 3) Buck-Boost converter
- 1-2. Transient-state analysis
  - 1) Buck converter
  - 2) Boost converter
  - 3) Buck-Boost converter

# Boost (1/10)

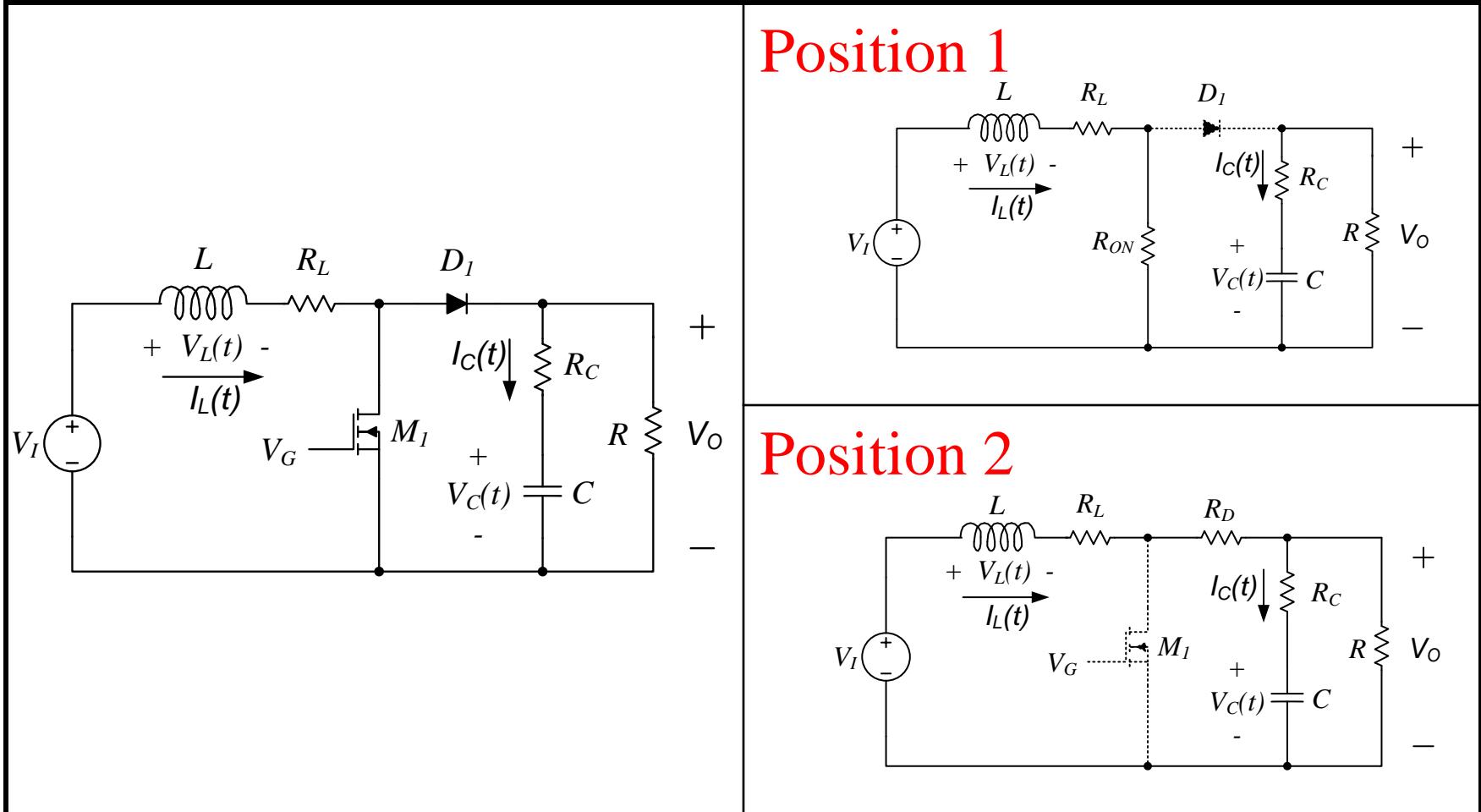

# Boost (2/10)

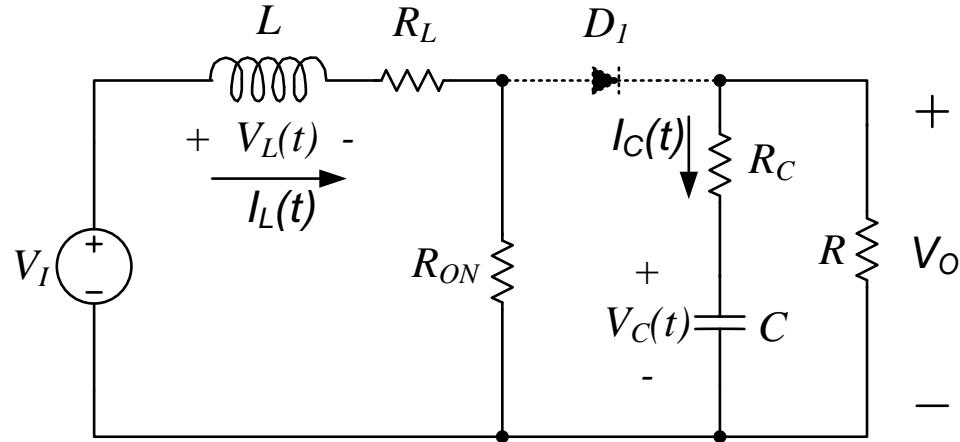

Position 1

$$\begin{bmatrix} \frac{di_L}{dt} \\ \frac{dv_C}{dt} \end{bmatrix} = \begin{bmatrix} -\frac{R_{ON} + R_L}{L} & 0 \\ 0 & -\frac{1}{(R + R_C)C} \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix} + \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} V_I$$

$$[v_o] = \begin{bmatrix} 0 & \frac{R}{R + R_C} \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix}$$

$$[i_i] = [1 \quad 0] \begin{bmatrix} i_L \\ v_C \end{bmatrix}$$

NKUST EE


$$A_1 = \begin{bmatrix} -\frac{R_{ON} + R_L}{L} & 0 \\ 0 & -\frac{1}{(R + R_C)C} \end{bmatrix}$$

$$B_1 = \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix}$$

$$C_1 = \begin{bmatrix} 0 & \frac{R}{R + R_C} \end{bmatrix}$$

$$C'_1 = [1 \quad 0]$$

# Boost (3/10)

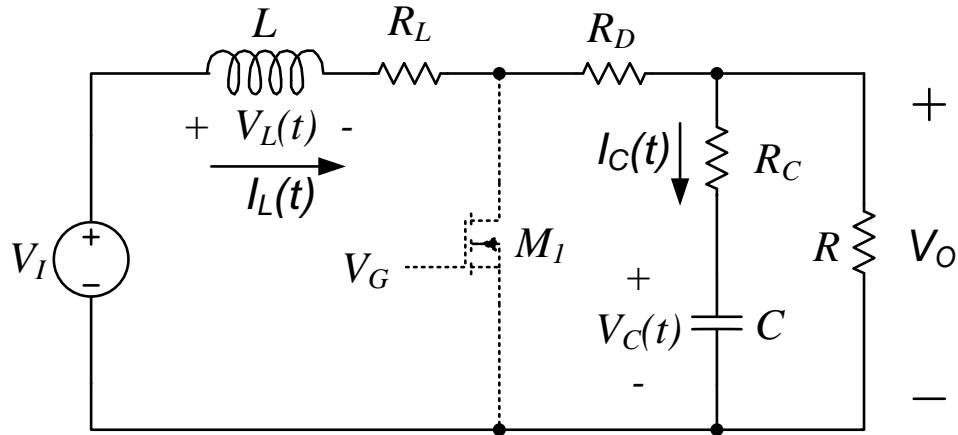

Position 2

$$\begin{bmatrix} \frac{di_L}{dt} \\ \frac{dv_C}{dt} \end{bmatrix} = \begin{bmatrix} -\frac{R_D + R_L + R \parallel R_C}{L} & -\frac{R}{(R + R_C)L} \\ \frac{R}{(R + R_C)C} & -\frac{1}{C(R + R_C)} \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix} + \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} V_I$$

$$[v_o] = [R \parallel R_C \quad \frac{R}{R + R_C}] \begin{bmatrix} i_L \\ v_C \end{bmatrix}$$

$$[i_i] = [1 \quad 0] \begin{bmatrix} i_L \\ v_C \end{bmatrix}$$

$$A_2 = \begin{bmatrix} -\frac{R_D + R_L + R \parallel R_C}{L} & -\frac{R}{(R + R_C)L} \\ \frac{R}{(R + R_C)C} & -\frac{1}{C(R + R_C)} \end{bmatrix}$$

$$B_2 = \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix}$$

$$C_2 = \begin{bmatrix} R \parallel R_C & \frac{R}{R + R_C} \end{bmatrix}$$

$$C_2' = [1 \quad 0]$$

# Boost (4/10)

$$A = DA_1 + D'A_2 = \begin{bmatrix} -\frac{(R_L + DR_{ON} + D'(R_D + R \| R_C))}{L} & -\frac{D'R}{(R+R_C)L} \\ \frac{D'R}{(R+R_C)C} & -\frac{1}{(R+R_C)C} \end{bmatrix}$$

$$B = DB_1 + D'B_2 = \begin{bmatrix} 1 \\ L \\ 0 \end{bmatrix}$$

$$C = DC_1 + D'C_2 = \begin{bmatrix} D'(R \| R_C) & \frac{R}{R+R_C} \end{bmatrix}$$

$$C' = DC'_1 + D'C'_2 = \begin{bmatrix} D' & \frac{1}{R_C} \end{bmatrix}$$

$$A_1 - A_2 = \begin{bmatrix} \frac{-R_{ON} + R_D + R \| R_C}{L} & \frac{R}{(R+R_C)L} \\ -\frac{R}{(R+R_C)C} & 0 \end{bmatrix}$$

$$B_1 - B_2 = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

$$C_1 - C_2 = 0$$

$$F = \begin{bmatrix} \frac{-R_{ON} + R_D + R \| R_C}{L} & \frac{R}{(R+R_C)L} \\ -\frac{R}{(R+R_C)C} & 0 \end{bmatrix} \begin{bmatrix} I_L \\ V_C \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \end{bmatrix} [V']$$

# Boost (5/10)

$$(SI - A)^{-1} = \frac{adj(SI - A)}{|SI - A|}$$

$$(SI - A)^{-1} = \begin{bmatrix} S + \frac{R_L + DR_{ON} + D'(R_D + R \| R_C)}{L} & \frac{D'R}{L(R + R_C)} \\ \frac{-D'R}{C(R + R_C)} & S + \frac{1}{C(R + R_C)} \end{bmatrix}^{-1}$$

$$adj(SI - A) = \begin{bmatrix} S + \frac{1}{C(R + R_C)} & \frac{-D'R}{L(R + R_C)} \\ \frac{D'R}{C(R + R_C)} & S + \frac{R_L + DR_{ON} + D'(R_D + R \| R_C)}{L} \end{bmatrix}$$

$$|SI - A| = S^2 + S \left( \frac{L + C(R + R_C)(R_L + DR_{ON} + D'(R_D + R \| R_C))}{(R + R_C)LC} \right) + \left( \frac{R_L + DR_{ON} + D'(R_D + R \| R_C) + \frac{(D'R)^2}{R + R_C}}{(R + R_C)LC} \right)$$

$$\Delta = |SI - A|$$

# Boost (6/10)

$$\left. \frac{\hat{v}_o(S)}{\hat{v}_i(S)} \right|_{\hat{d}(s)=0} = C(SI - A)^{-1} B$$

$$\Delta = |SI - A| = S^2 + S \left( \frac{L + C(R + R_c)(R_L + DR_{ON} + D'(R_D + R \| R_c))}{LC(R + R_c)} \right) + \left( \frac{R_L + DR_{ON} + D'(R_D + R \| R_c) + \frac{(D'R)^2}{R + R_c}}{LC(R + R_c)} \right)$$

$$\left. \frac{\hat{v}_o(S)}{\hat{v}_i(S)} \right|_{\hat{d}(s)=0} = \frac{1}{\Delta} \begin{bmatrix} D'(R \| R_c) & \frac{R}{R + R_c} \end{bmatrix} \begin{bmatrix} \frac{SC(R + R_c) + 1}{C(R + R_c)} & -\frac{D'R}{L(R + R_c)} \\ \frac{D'R}{C(R + R_c)} & \frac{SL + R_L + DR_{ON} + D'(R_D + R \| R_c)}{L} \end{bmatrix} \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix}$$

$$\left. \frac{\hat{v}_o(S)}{\hat{v}_i(S)} \right|_{\hat{d}(s)=0} = \frac{1}{\Delta} \left( \frac{D'R(SR_c C + 1)}{LC(R + R_c)} \right)$$

# Boost (7/10)

$$\frac{\hat{v}_o(S)}{\hat{d}(S)} \Big|_{\hat{V}_I(s)=0} = C(SI - A)^{-1} F$$

$$\Delta = |SI - A|$$

$$\frac{\hat{v}_o(S)}{\hat{d}(S)} \Big|_{\hat{V}_I(s)=0} = \frac{1}{\Delta} \begin{bmatrix} D'(R \| R_C) & \frac{R}{R+R_C} \end{bmatrix} \begin{bmatrix} \frac{SC(R+R_C)+1}{C(R+R_C)} & -\frac{D'R}{L(R+R_C)} \\ \frac{D'R}{C(R+R_C)} & \frac{SL+R_L+DR_{ON}+D'(R_D+R \| R_C)}{L} \end{bmatrix} \begin{bmatrix} \frac{-R_{ON}+R_D+R \| R_C}{L} & \frac{R}{(R+R_C)L} \\ -\frac{R}{(R+R_C)C} & 0 \end{bmatrix} \begin{bmatrix} I_L \\ V_C \end{bmatrix}$$

$$\frac{\hat{v}_o(S)}{\hat{d}(S)} \Big|_{\hat{V}_I(s)=0} = \frac{1}{\Delta} \begin{bmatrix} D'R(SR_C C + 1) & \frac{R(SL+R_L+DR_{ON}+D'R_D+DD'(R \| R_C))}{L(R+R_C)} \end{bmatrix} \begin{bmatrix} \frac{-R_{ON}+R_D+R \| R_C}{L} & \frac{R}{(R+R_C)L} \\ -\frac{R}{(R+R_C)C} & 0 \end{bmatrix} \begin{bmatrix} I_L \\ V_C \end{bmatrix}$$

$$\alpha_1 = (-R_{ON} + R_D + R \| R_C) I_L + \frac{V_C}{R+R_C}$$

$$\alpha_2 = (R_L + DR_{ON} + D'R_D + DD'(R \| R_C)) I_L$$

$$\frac{\hat{v}_o(S)}{\hat{d}(S)} \Big|_{\hat{V}_I(s)=0} = \frac{\alpha_1 \left( S \left( R_C C - \frac{R_L I_L L}{D' \alpha_1} \right) + \frac{\alpha_1 - \alpha_2}{\alpha_1} \right)}{\Delta (R + R_C) LC}$$

# Boost (8/10)

$$\left. \frac{\hat{i}_i(S)}{\hat{v}_i(S)} \right|_{\hat{d}(s)=0} = C'(SI - A)^{-1}B$$

$$\left. \frac{\hat{i}_i(S)}{\hat{v}_i(S)} \right|_{\hat{d}(s)=0} = \frac{1}{\Delta} \begin{bmatrix} 1 & 0 \end{bmatrix} \begin{bmatrix} \frac{SC(R+R_C)+1}{C(R+R_C)} & \frac{-D'R}{L(R+R_C)} \\ \frac{D'R}{C(R+R_C)} & \frac{SL+R_L+DR_{ON}+D'(R_D+R \parallel R_C)}{L} \end{bmatrix} \begin{bmatrix} 1 \\ L \\ 0 \end{bmatrix}$$

$$\left. \frac{\hat{i}_i(S)}{\hat{v}_i(S)} \right|_{\hat{d}(s)=0} = \frac{1}{\Delta} \left( \frac{S(R+R_C)C+1}{(R+R_C)LC} \right)$$

$$Z'_{out}(S) = \left( \frac{1}{D'} \right)^2 Z_{out}(S) = \left( \frac{1}{D'} \right)^2 \left( \frac{\Delta(R+R_C)LC}{S(R+R_C)C+1} \right)$$

$$Z_{out}(S) = \left( 1 - \frac{(D')^2 R(SR_C C + 1)}{\Delta LC(R+R_C)} \right) \left( \frac{R(SR_C C + 1)}{S(R+R_C)C+1} \right)$$

# Boost (9/10)

$$\left. \frac{\hat{v}_o(S)}{\hat{v}_i(S)} \right|_{\hat{d}(s)=0} = \frac{1}{\Delta} \left( \frac{D'R(SR_C C + 1)}{LC(R + R_C)} \right)$$

$$\Delta = S^2 + S \left( \frac{L + C(R + R_C)(R_L + DR_{ON} + D'(R_D + R \| R_C))}{(R + R_C)LC} \right) + \left( \frac{R_L + DR_{ON} + D'(R_D + R \| R_C) + \frac{(D'R)^2}{R + R_C}}{(R + R_C)LC} \right)$$

$$\left. \frac{\hat{v}_o(S)}{\hat{v}_i(S)} \right|_{\hat{d}(s)=0} = \frac{K(C_3 S^{-1} + C_4 S^{-2})}{1 - (-C_1 S^{-1} - C_2 S^{-2})}$$


$$C_1 = \frac{L + C(R + R_C)(R_L + DR_{ON} + D'(R_D + R \| R_C))}{(R + R_C)LC}$$

$$C_2 = \frac{R_L + DR_{ON} + D'(R_D + R \| R_C) + \frac{(D'R)^2}{R + R_C}}{(R + R_C)LC}$$

$$C_3 = R_C C$$

$$C_4 = 1$$

$$K = \frac{D'R}{LC(R + R_C)}$$

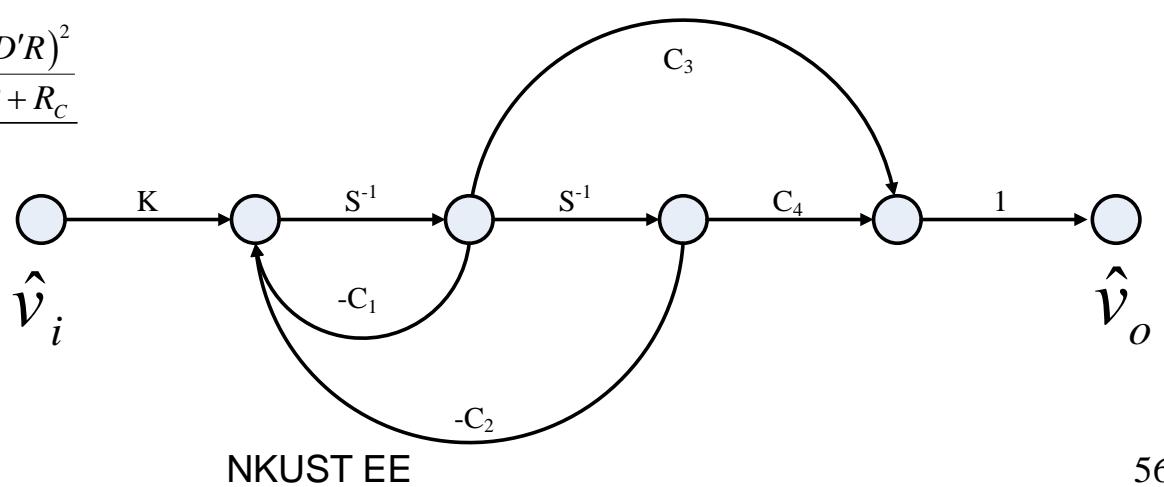

# Boost (10/10)

$$\left. \frac{\hat{v}_o(S)}{\hat{d}(S)} \right|_{\hat{v}_i(s)=0} = \frac{\alpha_1 \left( S \left( R_c C - \frac{R_L I_L L}{D' \alpha_1} \right) + \frac{\alpha_1 - \alpha_2}{\alpha_1} \right)}{\Delta (R + R_c) LC}$$

$$\alpha_1 = (-R_{ON} + R_D + R \parallel R_C) I_L + \frac{V_C}{R + R_C}$$

$$\alpha_2 = (R_L + D R_{ON} + D' R_D + D D' (R \parallel R_C)) I_L$$

$$\Delta = S^2 + S \left( \frac{L + C (R + R_C) (R_L + D R_{ON} + D' (R_D + R \parallel R_C))}{(R + R_C) LC} \right) + \left( \frac{R_L + D R_{ON} + D' (R_D + R \parallel R_C) + \frac{(D' R)^2}{R + R_C}}{(R + R_C) LC} \right)$$

$$\left. \frac{\hat{v}_o(S)}{\hat{d}(S)} \right|_{\hat{v}_i(s)=0} = \frac{K (C_3 S^{-1} + C_4 S^{-2})}{1 - (-C_1 S^{-1} - C_2 S^{-2})}$$


$$C_1 = \frac{L + C (R + R_C) (R_L + D R_{ON} + D' (R_D + R \parallel R_C))}{(R + R_C) LC}$$

$$C_2 = \frac{R_L + D R_{ON} + D' (R_D + R \parallel R_C) + \frac{(D' R)^2}{R + R_C}}{(R + R_C) LC}$$

$$C_3 = R_C C - \frac{R_L I_L L}{D' \alpha_1}$$

$$C_4 = \frac{\alpha_1 - \alpha_2}{\alpha_1}$$

$$K = \frac{\alpha_1}{(R + R_C) LC}$$

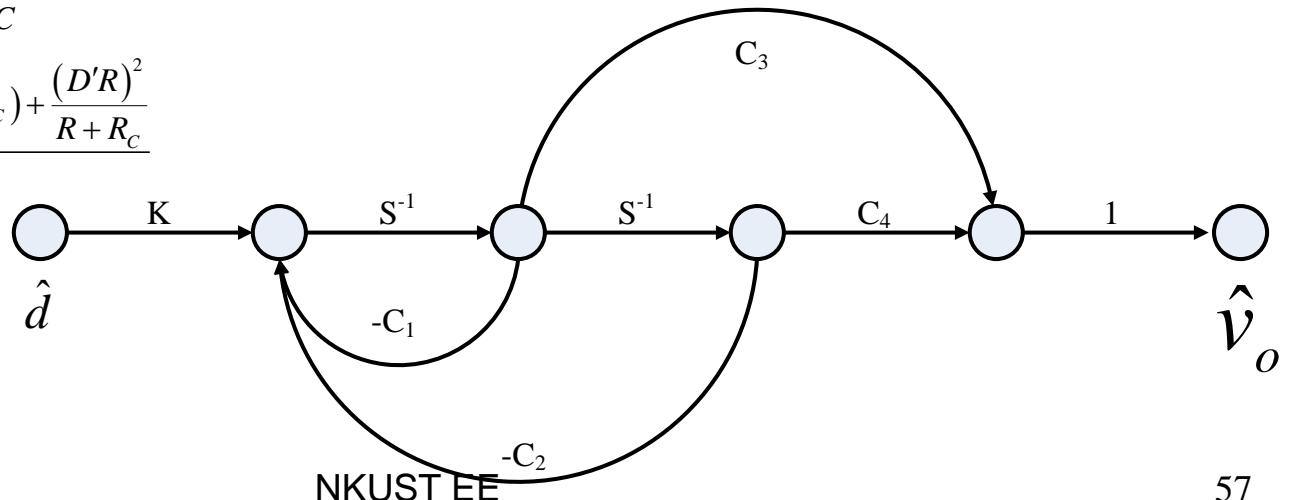


Type	Boost
$G_{vg}(S)$	$\frac{1}{\Delta} \left( \frac{D'R(SR_cC+1)}{LC(R+R_c)} \right)$
$G_{vd}(S)$	$\left( \frac{\alpha_1}{\Delta(R+R_c)LC} \right) \left( S \left( R_cC - \frac{R_L I_L L}{D' \alpha_1} \right) + \frac{\alpha_1 - \alpha_2}{\alpha_1} \right)$
$Z_{out}(s)$	$\left( 1 - \frac{(D')^2 R(SR_cC+1)}{\Delta LC(R+R_c)} \right) \left( \frac{R(SR_cC+1)}{S(R+R_c)C+1} \right)$
$\omega_z$	$\frac{D'(\alpha_1 - \alpha_2)}{R_L I_L L - D' \alpha_1 R_c C}$
$\alpha_1 = (-R_{ON} + R_D + R \  R_C)I_L + \frac{V_C}{R+R_C}$ $\alpha_2 = (R_L + DR_{ON} + D'R_D + DD'(R \  R_C))I_L$ $\Delta = S^2 + S \left( \frac{L + C(R+R_c)(R_L + DR_{ON} + D'(R_D + R \  R_C))}{(R+R_c)LC} \right) + \left( \frac{R_L + DR_{ON} + D'(R_D + R \  R_C) + \frac{(D'R)^2}{R+R_C}}{(R+R_c)LC} \right)$	
NKUST EE	
58	


# Outline

- 1-1. Steady-state analysis
  - 1) Buck converter
  - 2) Boost converter
  - 3) Buck-Boost converter
- 1-2. Transient-state analysis
  - 1) Buck converter
  - 2) Boost converter
  - 3) Buck-Boost converter


# Buck-Boost (1/10)

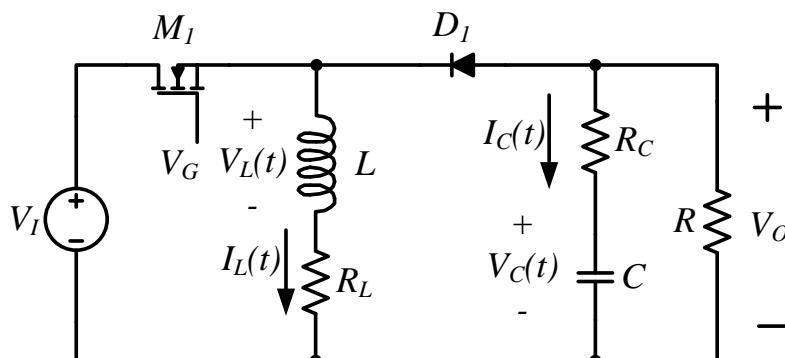


Position 1

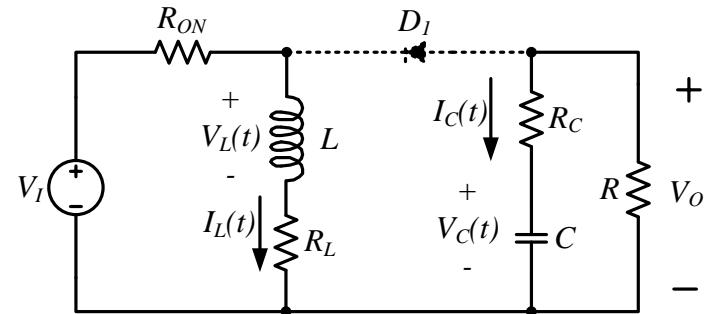

Position 2

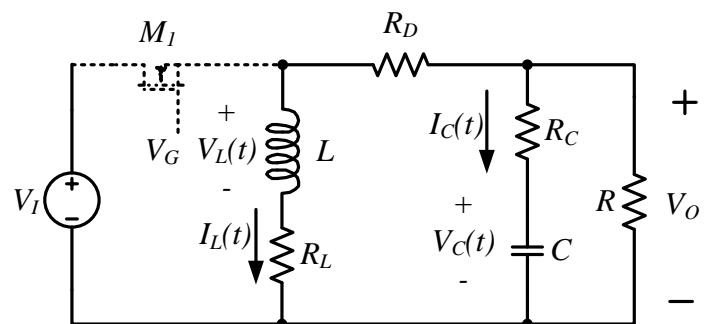

# Buck-Boost (2/10)

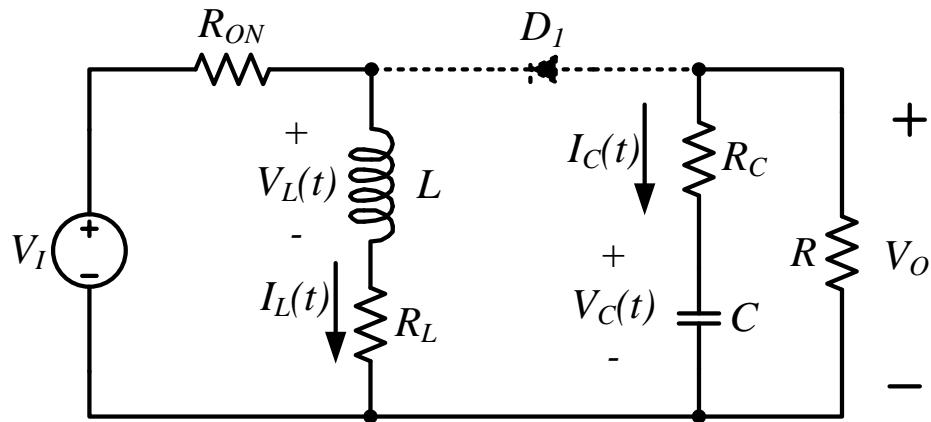

Position 1

$$\begin{bmatrix} \frac{di_L}{dt} \\ \frac{dv_C}{dt} \end{bmatrix} = \begin{bmatrix} -\frac{R_{ON} + R_L}{L} & 0 \\ \frac{R}{(R + R_C)C} & -\frac{1}{(R + R_C)C} \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix} + \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} V_I$$

$$[v_o] = \begin{bmatrix} 0 & \frac{R}{R + R_C} \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix}$$

$$[i_i] = [1 \quad 0] \begin{bmatrix} i_L \\ v_C \end{bmatrix}$$


$$A_1 = \begin{bmatrix} -\frac{R_{ON} + R_L}{L} & 0 \\ 0 & -\frac{1}{(R + R_C)C} \end{bmatrix} +$$

$$B_1 = \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix}$$

$$C_1 = \begin{bmatrix} 0 & \frac{R}{R + R_C} \end{bmatrix}$$

$$C'_1 = \begin{bmatrix} 0 & \frac{1}{R_C} \end{bmatrix}$$

# Buck-Boost (3/10)

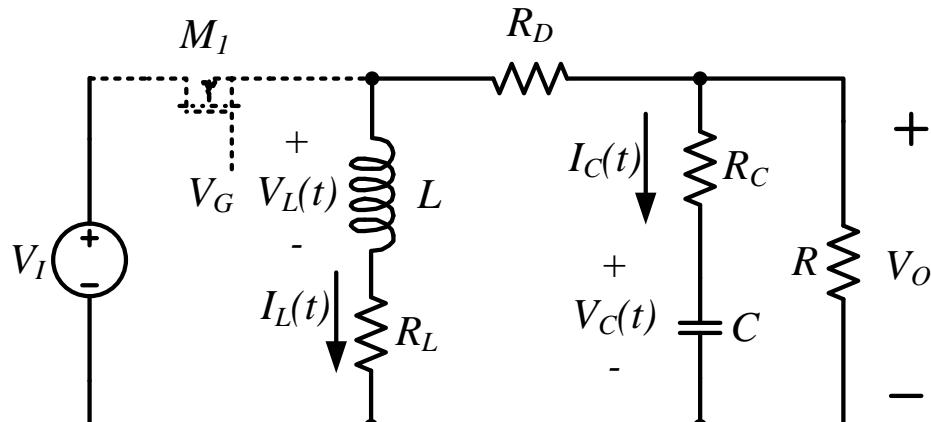

Position 2

$$\begin{bmatrix} \frac{di_L}{dt} \\ \frac{dv_C}{dt} \end{bmatrix} = \begin{bmatrix} R_D + R_L + \frac{R_C}{R+R_C} & \frac{R}{(R+R_C)L} \\ -\frac{L}{R} & -\frac{1}{(R+R_C)C} \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \end{bmatrix} V_I$$

$$[v_o] = \begin{bmatrix} -\frac{R_C}{R+R_C} & \frac{R}{R+R_C} \end{bmatrix} [i_L]$$

$$[i_i] = [0 \quad 0] \begin{bmatrix} i_L \\ v_C \end{bmatrix}$$

$$A_2 = \begin{bmatrix} R_D + R_L + \frac{R_C}{R+R_C} & \frac{R}{(R+R_C)L} \\ -\frac{L}{R} & -\frac{1}{(R+R_C)C} \end{bmatrix}$$

$$B_2 = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

$$C_2 = \begin{bmatrix} -R \parallel R_C & \frac{R}{R+R_C} \end{bmatrix}$$

$$C'_2 = \begin{bmatrix} -1 & \frac{1}{R_C} \end{bmatrix}$$

# Buck-Boost (4/10)

$$A = DA_1 + D'A_2 = \begin{bmatrix} -\frac{R_L + DR_{ON} + D' \left( R_D + \frac{R_C}{R+R_C} \right)}{L} & \frac{D'R}{(R+R_C)L} \\ -\frac{D'R}{(R+R_C)C} & -\frac{1}{(R+R_C)C} \end{bmatrix}$$

$$B = DB_1 + D'B_2 = \begin{bmatrix} D \\ L \\ 0 \end{bmatrix}$$

$$C = DC_1 + D'C_2 = \begin{bmatrix} -\frac{D'R_C}{R+R_C} & \frac{R}{R+R_C} \end{bmatrix}$$

$$C' = DC'_1 + D'C'_2 = [D \quad 0]$$

$$A_1 - A_2 = \begin{bmatrix} -R_{ON} + R_D + \frac{R_C}{R+R_C} & -\frac{R}{(R+R_C)L} \\ \frac{R}{(R+R_C)C} & 0 \end{bmatrix}$$

$$B_1 - B_2 = \begin{bmatrix} 1 \\ \frac{1}{L} \\ 0 \end{bmatrix}$$

$$C_1 - C_2 = \begin{bmatrix} \frac{R_C}{R+R_C} & 0 \end{bmatrix}$$

$$F = \begin{bmatrix} -R_{ON} + R_D + \frac{R_C}{R+R_C} & -\frac{R}{(R+R_C)L} \\ \frac{R}{(R+R_C)C} & 0 \end{bmatrix} \begin{bmatrix} I_L \\ V_C \end{bmatrix} + \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} [V_I]$$

$$G = \begin{bmatrix} \frac{R_C}{R+R_C} & 0 \end{bmatrix} \begin{bmatrix} I_L \\ V_C \end{bmatrix}$$

# Buck-Boost (5/10)

$$(SI - A)^{-1} = \frac{adj(SI - A)}{|SI - A|}$$

$$(SI - A)^{-1} = \begin{bmatrix} R_L + DR_{ON} + D' \left( R_D + \frac{R_C}{R + R_C} \right) & -\frac{D'R}{(R + R_C)L} \\ S + \frac{D'R}{(R + R_C)C} & S + \frac{1}{(R + R_C)C} \end{bmatrix}^{-1}$$

$$adj(SI - A) = \begin{bmatrix} S + \frac{1}{(R + R_C)C} & \frac{D'R}{(R + R_C)L} \\ -\frac{D'R}{(R + R_C)C} & S + \frac{R_L + DR_{ON} + D' \left( R_D + \frac{R_C}{R + R_C} \right)}{L} \end{bmatrix}$$

$$\Delta = |SI - A| = S^2 + S \left( \frac{L + C(R + R_C) \left( R_L + DR_{ON} + D' \left( R_D + \frac{R_C}{R + R_C} \right) \right)}{LC(R + R_C)} \right) + \left( \frac{R_L + DR_{ON} + D' \left( R_D + \frac{R_C}{R + R_C} \right) + \frac{(D'R)^2}{R + R_C}}{LC(R + R_C)} \right)$$

# Buck-Boost (6/10)

$$\left. \frac{\hat{v}_o(S)}{\hat{v}_i(S)} \right|_{\hat{d}(s)=0} = C(SI - A)^{-1}B$$

$$\left. \frac{\hat{v}_o(S)}{\hat{v}_i(S)} \right|_{\hat{d}(s)=0} = \begin{bmatrix} -\frac{D'R_c}{R+R_c} & \frac{R}{R+R_c} \end{bmatrix} \begin{bmatrix} S + \frac{R_L + DR_{ON} + D' \left( R_D + \frac{R_c}{R+R_c} \right)}{L} \\ \frac{D'R}{(R+R_c)C} \end{bmatrix}^{-1} \begin{bmatrix} \frac{D}{L} \\ 0 \end{bmatrix}$$

$$\left. \frac{\hat{v}_o(S)}{\hat{v}_i(S)} \right|_{\hat{d}(s)=0} = \frac{1}{\Delta} \left( -\frac{DD'R(SR_cC+1)}{(R+R_c)LC} \right)$$

# Buck-Boost (7/10)

$$\left. \frac{\hat{v}_o(S)}{\hat{d}(S)} \right|_{\hat{u}(s)=0} = C(SI - A)^{-1} F + G$$

$$\left. \frac{\hat{v}_o(S)}{\hat{d}(S)} \right|_{\hat{u}(s)=0} = \begin{bmatrix} -\frac{D'R_c}{R+R_c} & \frac{R}{R+R_c} \end{bmatrix} \begin{bmatrix} S + \frac{R_L + DR_{ON} + D' \left( R_D + \frac{R_c}{R+R_c} \right)}{L} & -\frac{D'R}{(R+R_c)L} \\ \frac{D'R}{(R+R_c)C} & S + \frac{1}{(R+R_c)C} \end{bmatrix}^{-1} F + G$$

$$\left. \frac{\hat{v}_o(S)}{\hat{d}(S)} \right|_{\hat{u}(s)=0} = \frac{1}{\Delta} \begin{bmatrix} SR_c + \frac{R^2 + R_c}{(R+R_c)C} & S + \frac{R_L + DR_{ON} + D'R_D + D'D \left( \frac{R_c}{R+R_c} \right)}{L} \end{bmatrix} \begin{bmatrix} -\frac{D'}{R+R_c} & 0 \\ 0 & \frac{R}{R+R_c} \end{bmatrix} F + G$$

$$\alpha_1 = \left( -R_{ON} + R_D + \frac{R_c}{R+R_c} \right) I_L - \left( \frac{R_c}{R+R_c} \right) V_C$$

$$\alpha_2 = \left( \frac{R^2}{R+R_c} \right) \left( R_L + DR_{ON} + D'R_D + DD' \left( \frac{R_c}{R+R_c} \right) \right) I_L$$

$$\left. \frac{\hat{v}_o(S)}{\hat{d}(S)} \right|_{\hat{u}(s)=0} = \frac{(D'V_I + \alpha_1)}{\Delta} \left( S \left( \frac{R^2 I_L L}{(R+R_c)(D'V_I + \alpha_1)} - R_c C \right) + \left( \frac{\alpha_2}{(D'V_I + \alpha_1)} - \frac{R^2 + R_c}{R+R_c} \right) \right)$$

# Buck-Boost (8/10)

$$\left. \frac{\hat{i}_i(S)}{\hat{v}_i(S)} \right|_{\hat{d}(s)=0} = C'(SI - A)^{-1} F$$

$$\left. \frac{\hat{i}_i(S)}{\hat{v}_i(S)} \right|_{\hat{d}(s)=0} = [D \quad 0] \begin{bmatrix} S + \frac{R_L + DR_{ON} + D' \left( R_D + \frac{R_C}{R + R_C} \right)}{L} & -\frac{D'R}{(R + R_C)L} \\ \frac{D'R}{(R + R_C)C} & S + \frac{1}{(R + R_C)C} \end{bmatrix}^{-1} \begin{bmatrix} D \\ L \\ 0 \end{bmatrix}$$

$$\left. \frac{\hat{i}_i(S)}{\hat{v}_i(S)} \right|_{\hat{d}(s)=0} = \frac{1}{\Delta} \left( \frac{D^2}{L} \right) \left( \frac{S(R + R_C)C + 1}{(R + R_C)C} \right)$$

$$Z'_{out}(S) = \left( -\frac{D}{D'} \right)^2 Z'_{out}(S) = \left( \frac{1}{D'} \right)^2 \left( \frac{\Delta(R + R_C)LC}{S(R + R_C)C + 1} \right)$$

$$Z'_{out}(S) = \left( 1 - \frac{(D')^2 R(SR_C C + 1)}{\Delta(R + R_C)LC} \right) \left( \frac{R(SR_C C + 1)}{S(R + R_C)C + 1} \right)$$

# Buck-Boost (9/10)

$$\left. \frac{\hat{v}_o(S)}{\hat{v}_i(S)} \right|_{\hat{d}(s)=0} = \frac{1}{\Delta} \left( \left( - \frac{DD'R(SR_C C + 1)}{(R + R_C)LC} \right) \right)$$

$$\Delta = S^2 + S \left( \frac{L + C(R + R_C) \left( R_L + DR_{ON} + D' \left( R_D + \frac{R_C}{R + R_C} \right) \right)}{LC(R + R_C)} \right) + \left( \frac{R_L + DR_{ON} + D' \left( R_D + \frac{R_C}{R + R_C} \right) + \frac{(D'R)^2}{R + R_C}}{LC(R + R_C)} \right)$$

$$\left. \frac{\hat{v}_o(S)}{\hat{v}_i(S)} \right|_{\hat{d}(s)=0} = \frac{K(C_3 S^{-1} + C_4 S^{-2})}{1 - (-C_1 S^{-1} - C_2 S^{-2})}$$


$$C_1 = \frac{L + C(R + R_C) \left( R_L + DR_{ON} + D' \left( R_D + \frac{R_C}{R + R_C} \right) \right)}{LC(R + R_C)}$$

$$C_2 = \frac{R_L + DR_{ON} + D' \left( R_D + \frac{R_C}{R + R_C} \right) + \frac{(D'R)^2}{R + R_C}}{LC(R + R_C)}$$

$$C_3 = R_C C$$

$$C_4 = 1$$

$$K = - \frac{DD'R}{(R + R_C)LC}$$

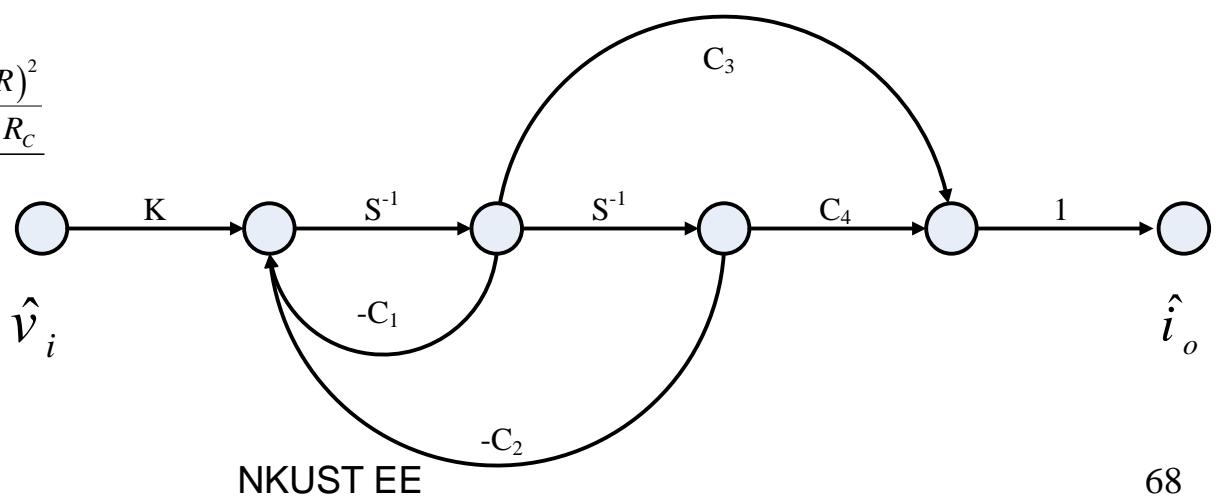

# Buck-Boost (10/10)

$$\left. \frac{\hat{v}_o(S)}{\hat{d}(S)} \right|_{\hat{u}(s)=0} = \frac{(D'V_I + \alpha_1)}{\Delta} \left( S \left( \frac{R^2 I_L L}{(R+R_C)(D'V_I + \alpha_1)} - R_C C \right) + \left( \frac{\alpha_2}{(D'V_I + \alpha_1)} - \frac{R^2 + R_C}{R+R_C} \right) \right)$$

$$\Delta = S^2 + S \left( \frac{L + C(R+R_C) \left( R_L + DR_{ON} + D' \left( R_D + \frac{R_C}{R+R_C} \right) \right)}{LC(R+R_C)} \right) + \left( \frac{R_L + DR_{ON} + D' \left( R_D + \frac{R_C}{R+R_C} \right) + \frac{(D'R)^2}{R+R_C}}{LC(R+R_C)} \right)$$

$$\left. \frac{\hat{v}_o(S)}{\hat{d}(S)} \right|_{\hat{v}_I(s)=0} = \frac{K(C_3 S^{-1} + C_4 S^{-2})}{1 - (-C_1 S^{-1} - C_2 S^{-2})}$$

$$C_1 = \frac{L + C(R+R_C) \left( R_L + DR_{ON} + D' \left( R_D + \frac{R_C}{R+R_C} \right) \right)}{LC(R+R_C)}$$

$$C_2 = \frac{R_L + DR_{ON} + D' \left( R_D + \frac{R_C}{R+R_C} \right) + \frac{(D'R)^2}{R+R_C}}{LC(R+R_C)}$$


$$C_3 = \frac{R^2 I_L L}{(R+R_C)(D'V_I + \alpha_1)} - R_C C$$

$$C_4 = \frac{\alpha_2}{(D'V_I + \alpha_1)} - \frac{R^2 + R_C}{R+R_C}$$

$$K = (D'V_I + \alpha_1)$$

$$\alpha_1 = \left( -R_{ON} + R_D + \frac{R_C}{R+R_C} \right) I_L - \left( \frac{R_C}{R+R_C} \right) V_C$$
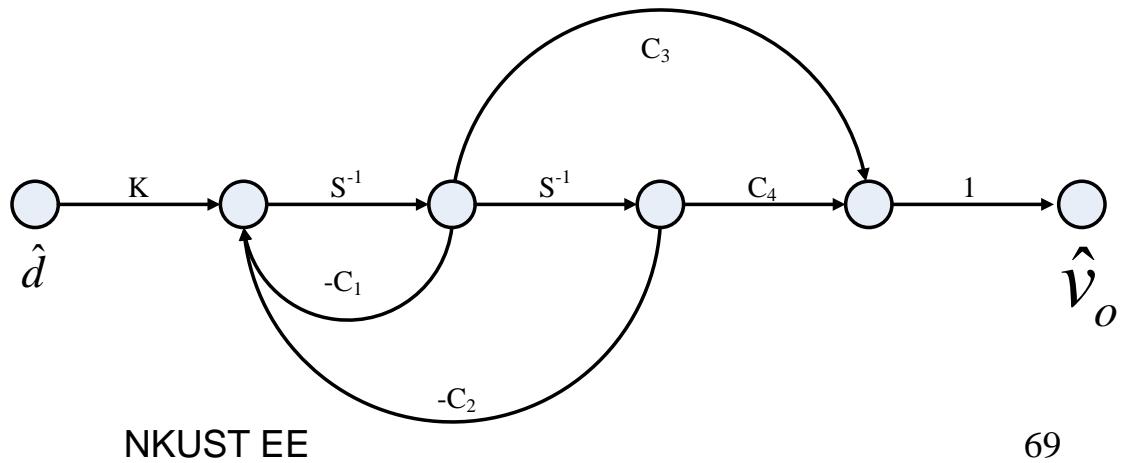
$$\alpha_2 = \left( \frac{R^2}{R+R_C} \right) \left( R_L + DR_{ON} + D'R_D + DD' \left( \frac{R_C}{R+R_C} \right) \right) I_L$$



Type	Buck-Boost
$G_{vg}(S)$	$\frac{1}{\Delta} \left( \left( -\frac{DD'R(SR_cC+1)}{(R+R_c)LC} \right) \right)$
$G_{vd}(S)$	$\frac{(D'V_I + \alpha_1)}{\Delta} \left( S \left( \frac{R^2 I_L L}{(R+R_c)(D'V_I + \alpha_1)} - R_c C \right) + \left( \frac{\alpha_2}{(D'V_I + \alpha_1)} - \frac{R^2 + R_c}{R+R_c} \right) \right)$
$Z_{out}(s)$	$\left( 1 - \frac{(D')^2 R (SR_c C + 1)}{\Delta (R + R_c) LC} \right) \left( \frac{R (SR_c C + 1)}{S (R + R_c) C + 1} \right)$
$\omega_Z$	$-\left( \frac{\alpha_2}{(D'V_I + \alpha_1)} - \frac{R^2 + R_c}{R + R_c} \right) \Bigg/ \left( \frac{R^2 I_L L}{(R + R_c)(D'V_I + \alpha_1)} - R_c C \right)$
$\Delta = S^2 + S \left( \frac{L + C(R + R_c) \left( R_L + DR_{ON} + D' \left( R_D + \frac{R_c}{R + R_c} \right) \right)}{LC(R + R_c)} \right) + \left( \frac{R_L + DR_{ON} + D' \left( R_D + \frac{R_c}{R + R_c} \right) + \frac{(D'R)^2}{R + R_c}}{LC(R + R_c)} \right)$	
$\alpha_1 = \left( -R_{ON} + R_D + \frac{R_c}{R + R_c} \right) I_L - \left( \frac{R_c}{R + R_c} \right) V_c$	NKUST EE
$\alpha_2 = \left( \frac{R^2}{R + R_c} \right) \left( R_L + DR_{ON} + D'R_D + DD' \left( \frac{R_c}{R + R_c} \right) \right) I_L$	70


# Chapter 2. Operational Amplifier Design

# Outline

- 2-1. Introduction
- 2-2. Schematic of OP
- 2-3. Design flow
- 2-4. Layout of OP
- 2-5. Simulation of OP
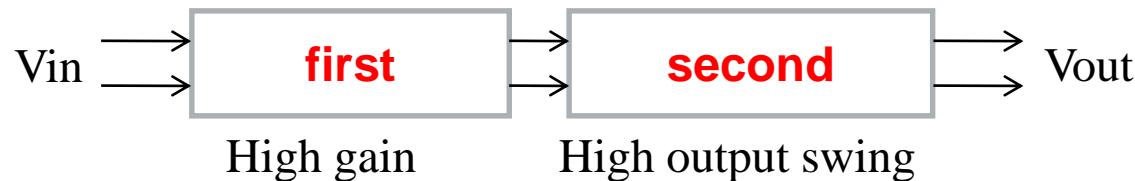
# OP

- Chose the two-stage OP with high gain and high output swing.




	Gain	Output swing	Speed	Power dissipation	Noise
<b>Telescopic</b>	Medium	Medium	High	Low	Low
<b>Folded cascode</b>	Medium	Medium	High	Medium	Medium
<b>Two stage</b>	High	High	Low	Medium	Low
<b>Gain boosting</b>	High	Medium	Medium	High	Medium

# OP (Spec.)

	Specification	Pre-sim	Post-sim
<b>A<sub>v</sub></b>	$A_o \geq 70 \text{ db}$	71 db	71 db
<b>Phase margin</b>	$\Phi M \geq 45^\circ \text{ near } 70^\circ$	67 °	68 °
<b>Unit-gain frequency</b>	$F_o \leq 200 \text{ MHz}$	64 MHz	57 MHz
<b>C<sub>c</sub></b>	< 4 pf	0.4 pf	0.4 pf
<b>Slew rate</b>	$\leq 250 \text{ v}/\mu\text{s}$	75 v/ $\mu\text{s}$	62 v/ $\mu\text{s}$
<b>Setting time</b>	$\leq 100 \text{ ns}$	81 ns	70 ns
<b>Offset</b>	0v	0.2v	0.18v
<b>ICMR</b>	0v – 5v	0.2v – 4.45v	0.18v – 4.48v
<b>PSRR</b>	>60 db	75 db	77db
<b>CMRR</b>	>60 db	64 db	68 db
<b>Power Dissipation</b>	< 10mv	3.009 mv	2.92 mv

# Schematic of OP

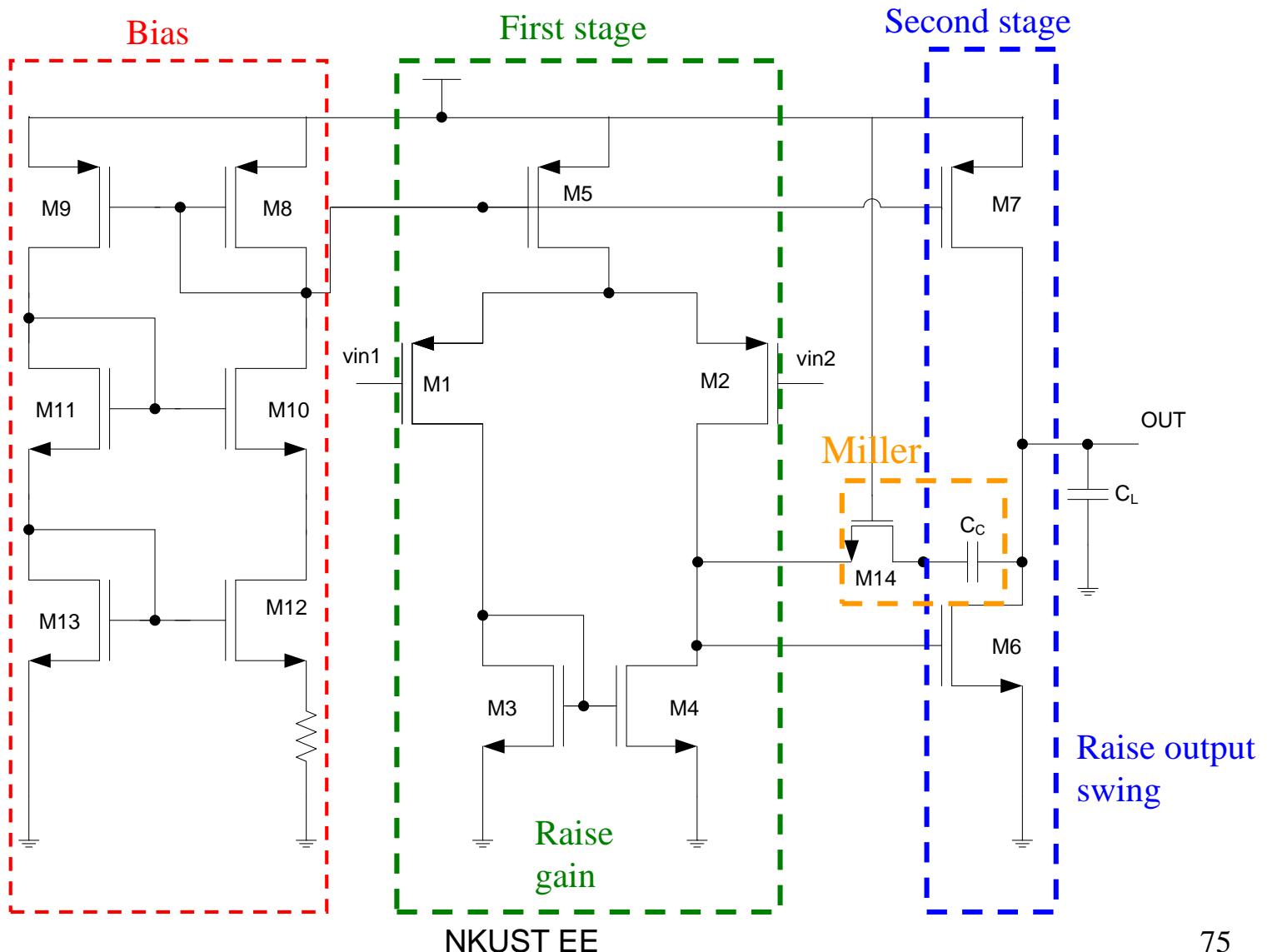

# Design Flow (1/4)

From equation (1) use SR and  $C_c$  find  $I_{D5}$  :

$$\text{Let } SR = 250 \text{v} / \mu\text{s} \quad C_c = 0.4 \text{ pF}$$

$$\Rightarrow I_{D5} = SR \times C_c = 100 \mu\text{A} \quad (1)$$

$$I_8 = I_9 = I_{10} = I_{11} = \frac{I_{D5}}{2} = 50 \mu\text{A}$$

From equation (2) for M6 :

$$\because g_{mi} = g_{m1} = g_{m2} = \omega_o C_c = 2\pi f_0 C_c \quad (2)$$


$$= 2 \times 3.14 \times 200 \times 10^6 \times 0.4 \times 10^{-12} = 500 \mu\text{A/v}$$

$$\therefore g_{m6} = 3g_{m1} = 3 \times 500 = 1500 \mu\text{A/v}$$

From equation (3) For M3 and M4 :

$$\because g_m = \frac{2I_D}{(V_{gs} - V_{th})} \quad (3)$$
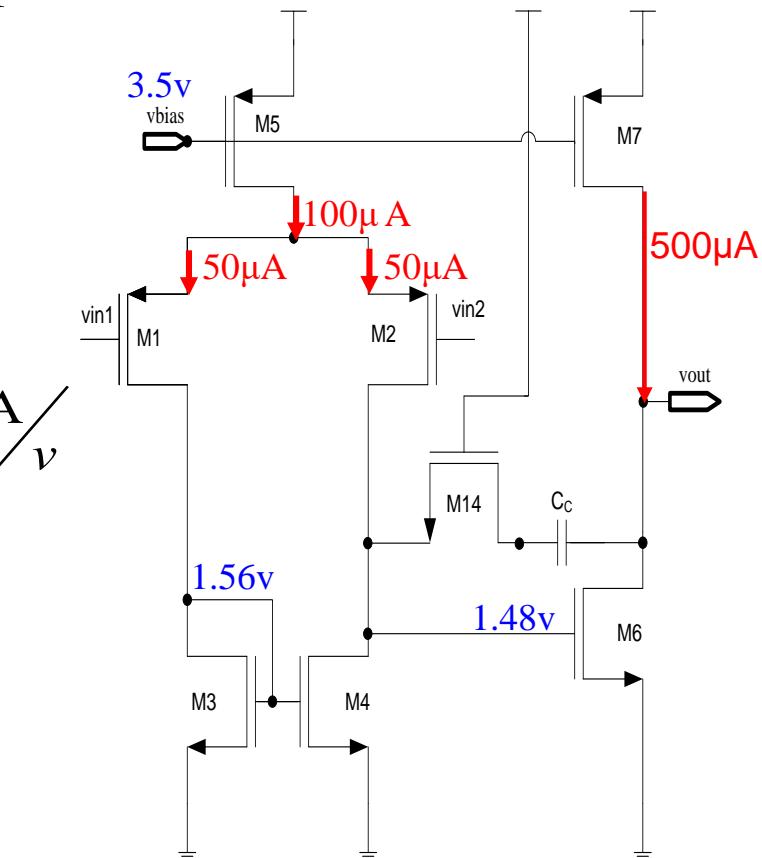
$$\therefore g_{m3} = g_{m4} = \frac{I_o/2}{I_{bias}} \quad g_{m6} = \frac{50 \mu\text{A}}{500 \mu\text{A}} \quad g_{m6} = 150 \mu\text{A/v}$$



# Design Flow (2/4)

- Assume  $|V_{GS5} - V_{tp}| = |V_{GS7} - V_{tp}| = 0.5v$  :


$$\left(\frac{W}{L}\right)_5 = \frac{I_{D5}}{\frac{1}{2}\mu_p C_{OX} (V_{SG5} - |V_{tp}|)} = \frac{100 \times 10^{-6}}{\frac{1}{2} \times 26.271 \times (0.5)^2} = 30$$

$$\left(\frac{W}{L}\right)_7 = \frac{I_{D7}}{\frac{1}{2}\mu_p C_{OX} (V_{SG7} - |V_{tp}|)} = \frac{500 \times 10^{-6}}{\frac{1}{2} \times 26.271 \times (0.5)^2} = 150$$

$$\left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_4 = \frac{(gm_3)^2}{2\mu_n C_{OX} I_{D3}} = \frac{(150 \times 10^{-6})^2}{2 \times 42.801 \times 10^{-6} \times 50 \times 10^{-6}} = 5$$

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = \frac{(gm_1)^2}{2\mu_n C_{OX} I_{D1}} = \frac{(500 \times 10^{-6})^2}{2 \times 26.271 \times 10^{-6} \times 50 \times 10^{-6}} = 95$$
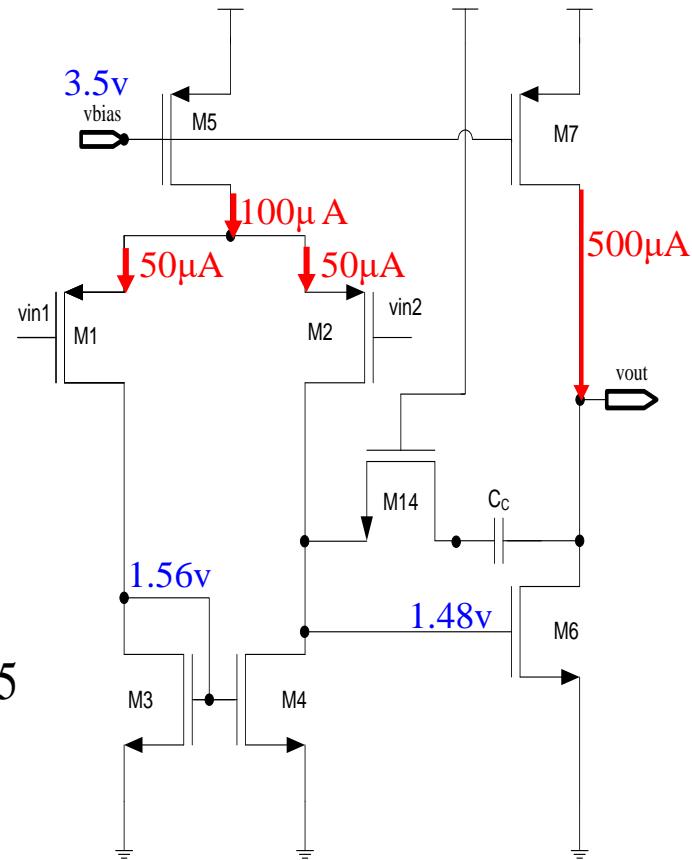
$$\left(\frac{W}{L}\right)_6 = \frac{I_{D6}}{I_{D3}} \left(\frac{W}{L}\right)_3 = \frac{500 \mu A}{50 \mu A} \times 5 = 50$$



# Design Flow (3/4)

- Find  $V_{G5}$  from equation (4) :


$$I_{D5} = \frac{1}{2} \mu_p C_{OX} \left( \frac{W}{L} \right)_5 \left( V_{GS5} - |V_{tp}| \right)^2 \quad (4)$$

$$\begin{aligned} V_{G5} &= V_{S5} - \left[ \frac{2I_{D5}}{\mu_p C_{OX}} \left( \frac{L}{W} \right)_5 \right]^{\frac{1}{2}} + V_{tp} \\ &= 5 - \left[ \frac{2 \times 100 \times 10^{-6}}{26.271 \times 10^{-6}} \times \frac{1}{30} \right]^{\frac{1}{2}} - 1.009 = 3.491 \approx 3.5 \end{aligned}$$

- M8 and M9 can be :

$$\begin{aligned} \left( \frac{W}{L} \right)_8 &= \frac{2 \times I_{D5}}{\mu_p C_{OX} \left( V_{SG8} - |V_{tp}| \right)^2} \\ &= \frac{2 \times 50 \times 10^{-6}}{26.271 \times 10^{-6} \times (5 - 3.5 - 1.009)^2} = 15.8 \end{aligned}$$
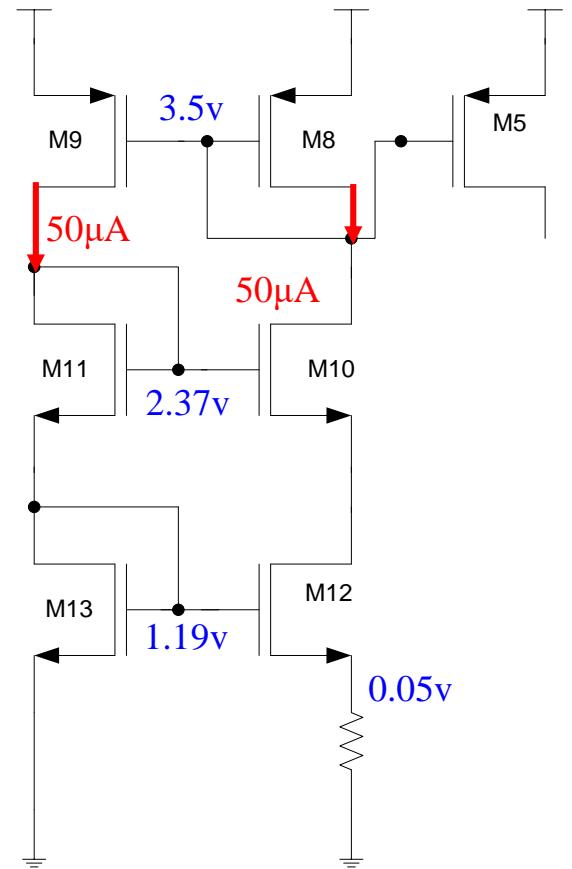
$$\left( \frac{W}{L} \right)_8 = \left( \frac{W}{L} \right)_9 = \left( \frac{W}{L} \right)_{10} = \left( \frac{W}{L} \right)_{11} = \left( \frac{W}{L} \right)_{13} = 15.8$$



# Design Flow (4/4)

- $V_{G13}$  can be find from equation :

$$V_{G13} = \left( \frac{2I_{D5}}{\mu_n C_{ox} \left( \frac{W}{L} \right)_{13}} \right)^{\frac{1}{2}} + V_{tn} \quad (5)$$

$$= \left( \frac{2 \times 50}{42.801 \times 15.8} \right)^{\frac{1}{2}} + 0.799 = 1.19$$


- $(W/L)_{13}$  can be find :

$$I_{D5} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_{12} (V_{GS12} - V_{tn})^2$$


$$\Rightarrow \left( \frac{W}{L} \right)_{12} = \frac{2I_{D5}}{\mu_n C_{ox} (V_{GS12} - V_{tn})^2}, \text{ where } V_{S12} = I_{D5} R_b$$

$$\Rightarrow \left( \frac{W}{L} \right)_{12} = \frac{2I_{D5}}{\mu_n C_{ox} (V_{G12} - I_{D5} R_b - V_{tn})^2} = \frac{2 \times 50 \times 10^{-6}}{42.801 \times 10^{-6} \times (1.19 - 50 \times 10^{-6} \times R_b - 0.799)^2}$$

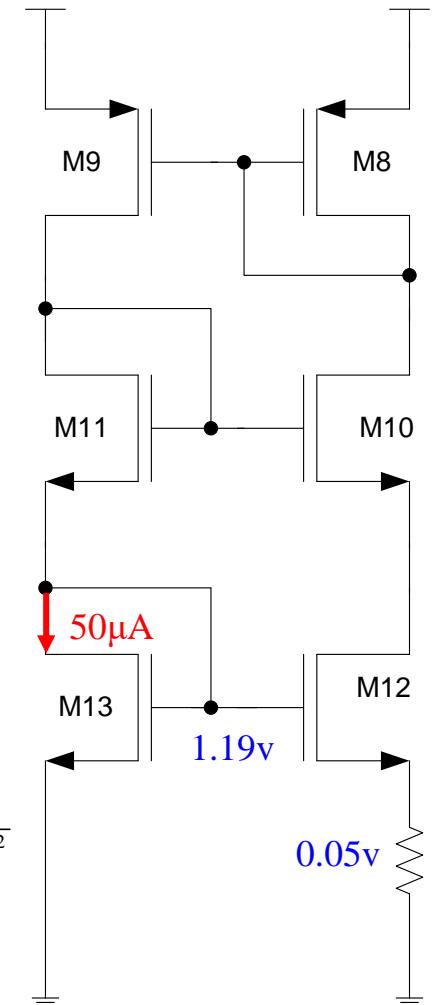
let  $R_b = 1k\Omega \Rightarrow \left( \frac{W}{L} \right)_{12} = \frac{2 \times 50 \times 10^{-6}}{42.801 \times 10^{-6} \times (1.19 - 50 \times 10^{-6} \times 10^3 - 0.799)^2} = 20$





# Size of OP

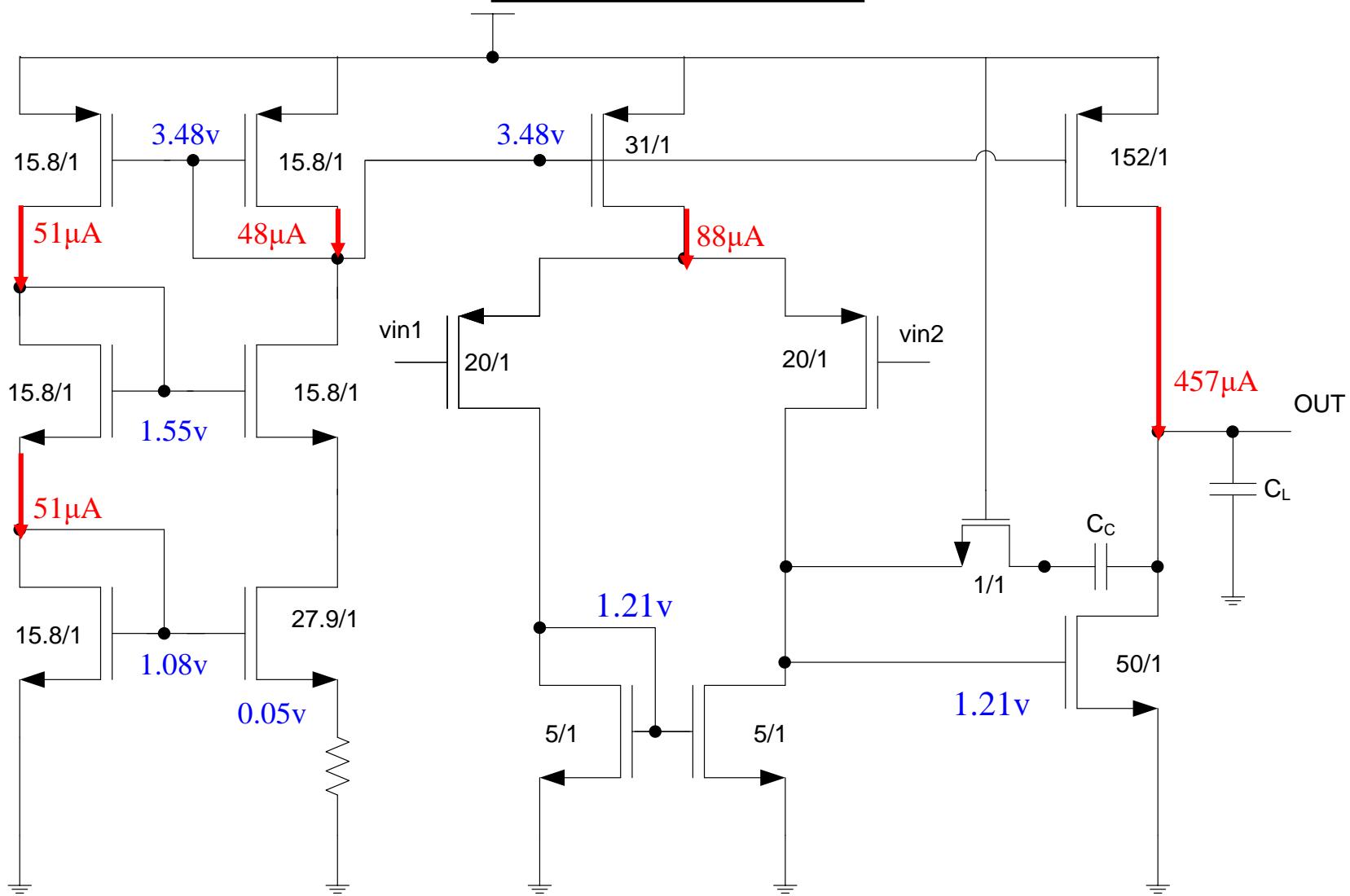


# Layout of OP

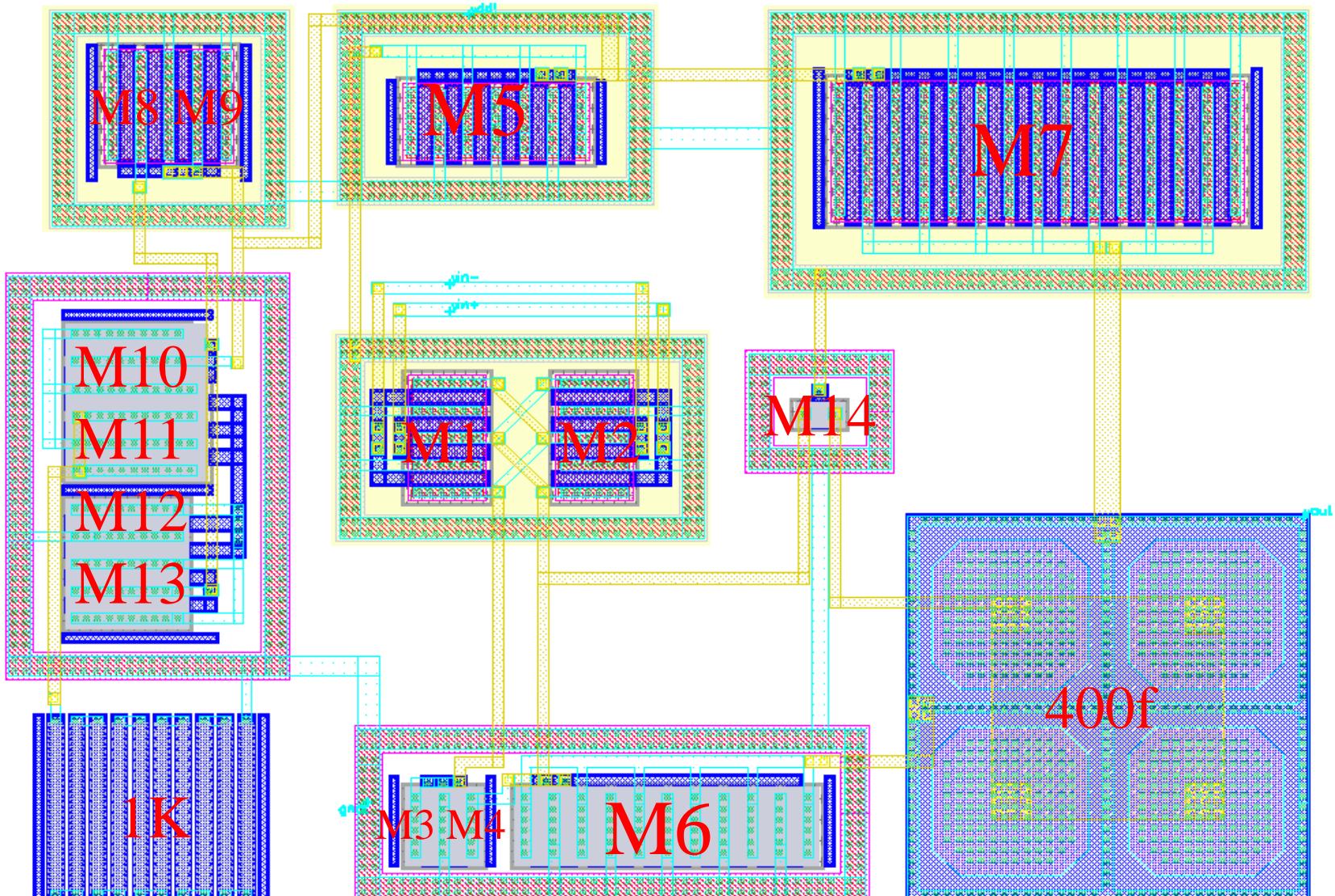


# Simulation of Output

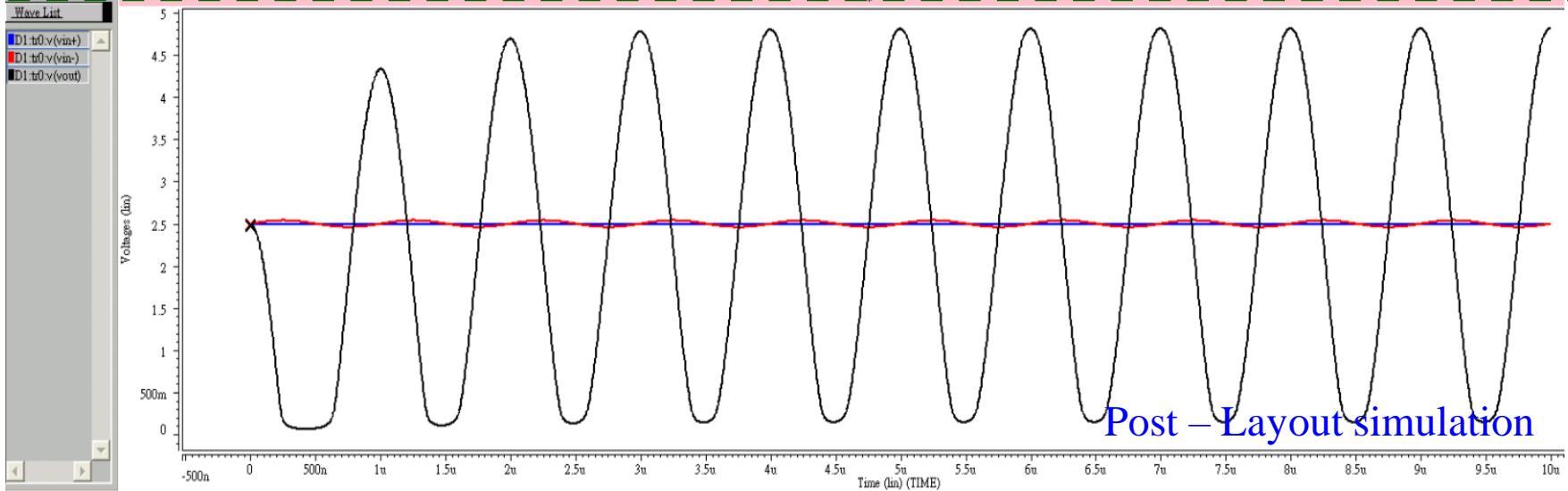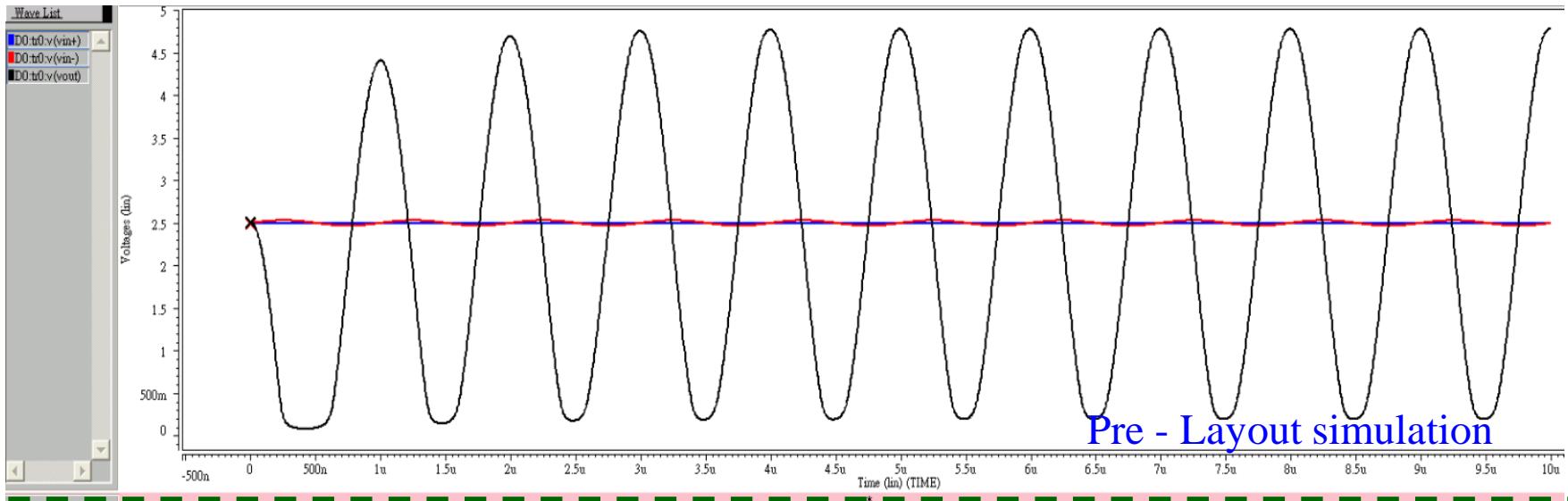


# Simulation of Phase Margin

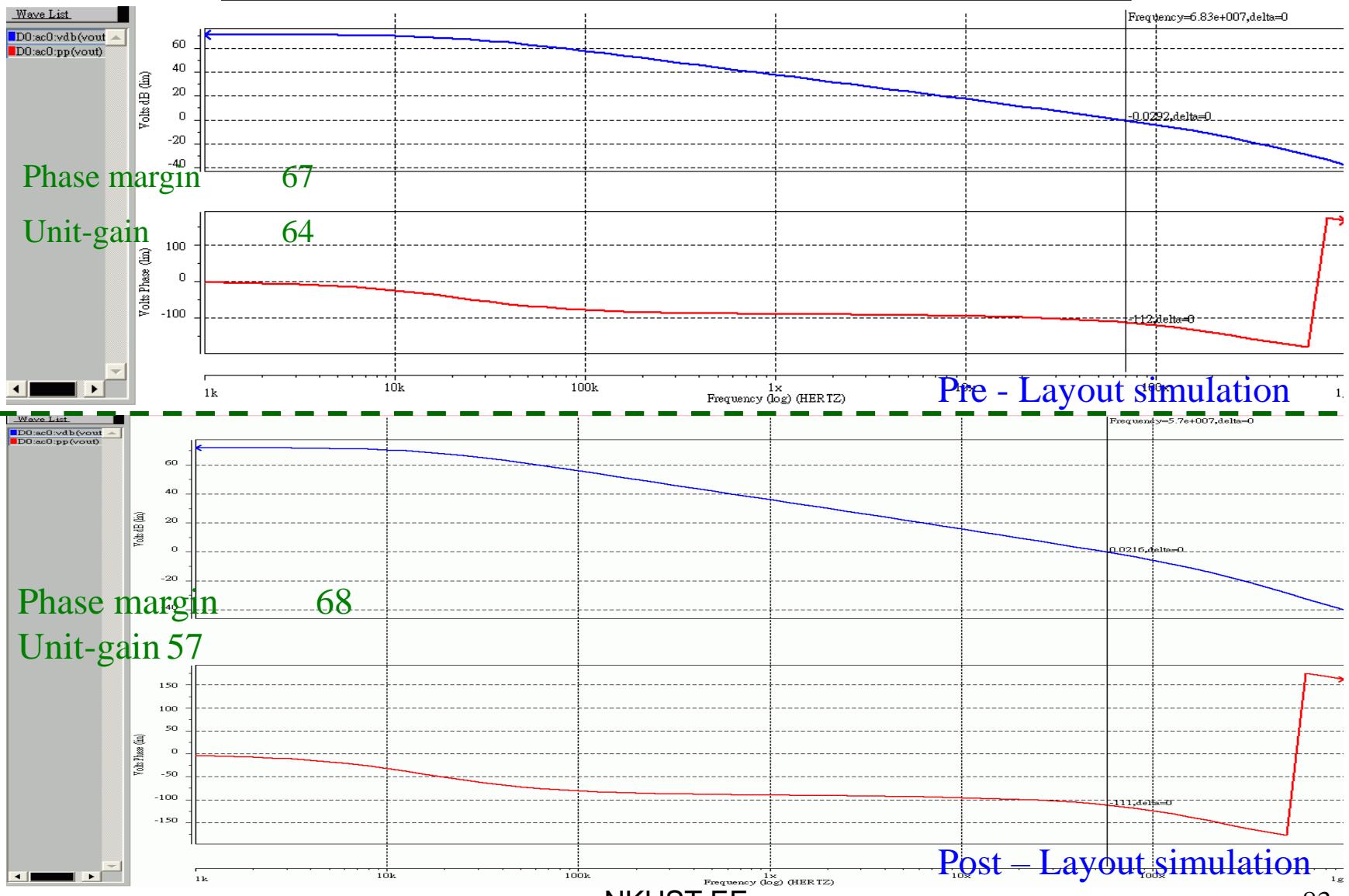


# Simulation of Slew Rate

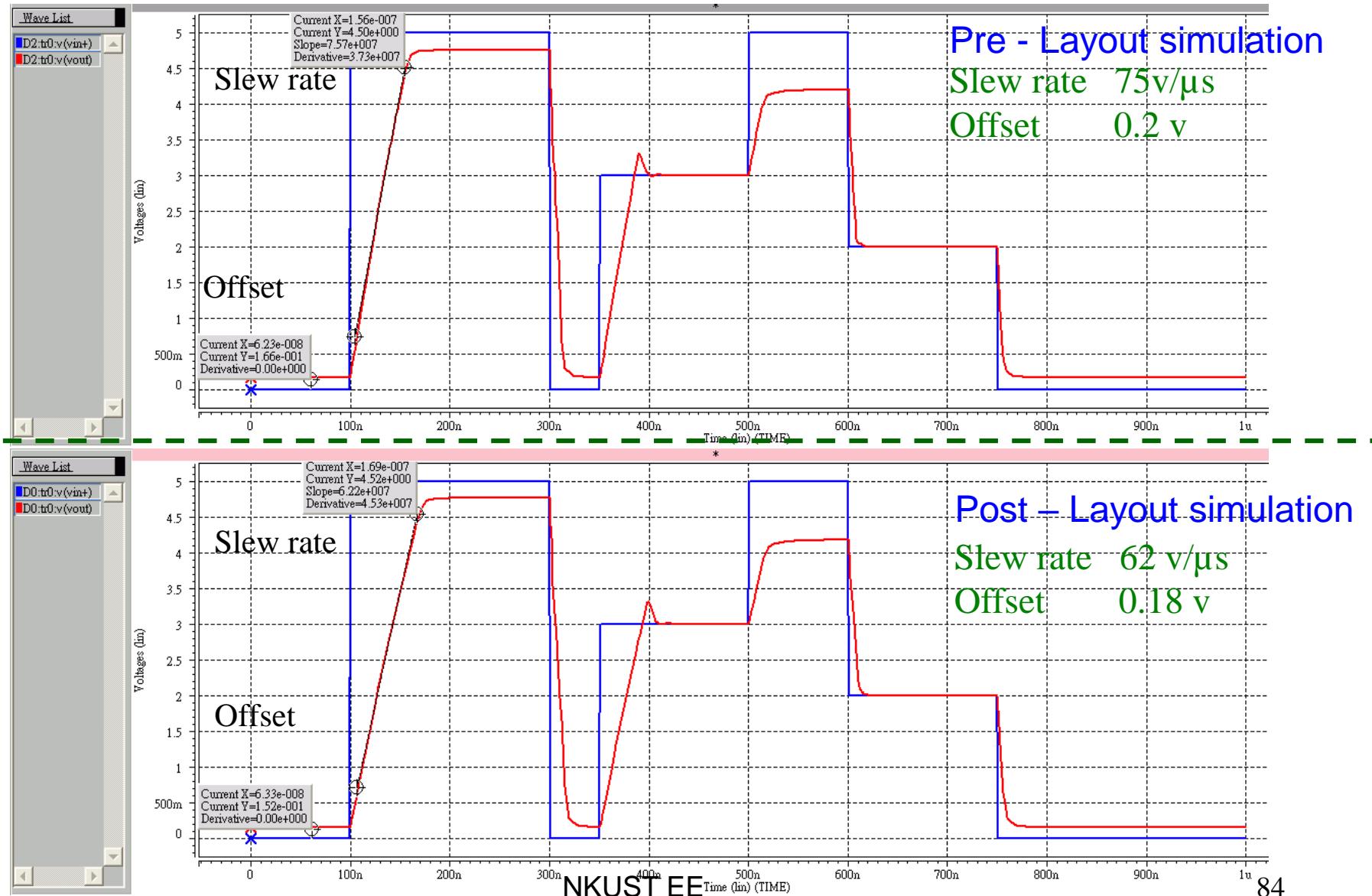


# Simulation of Settling Time

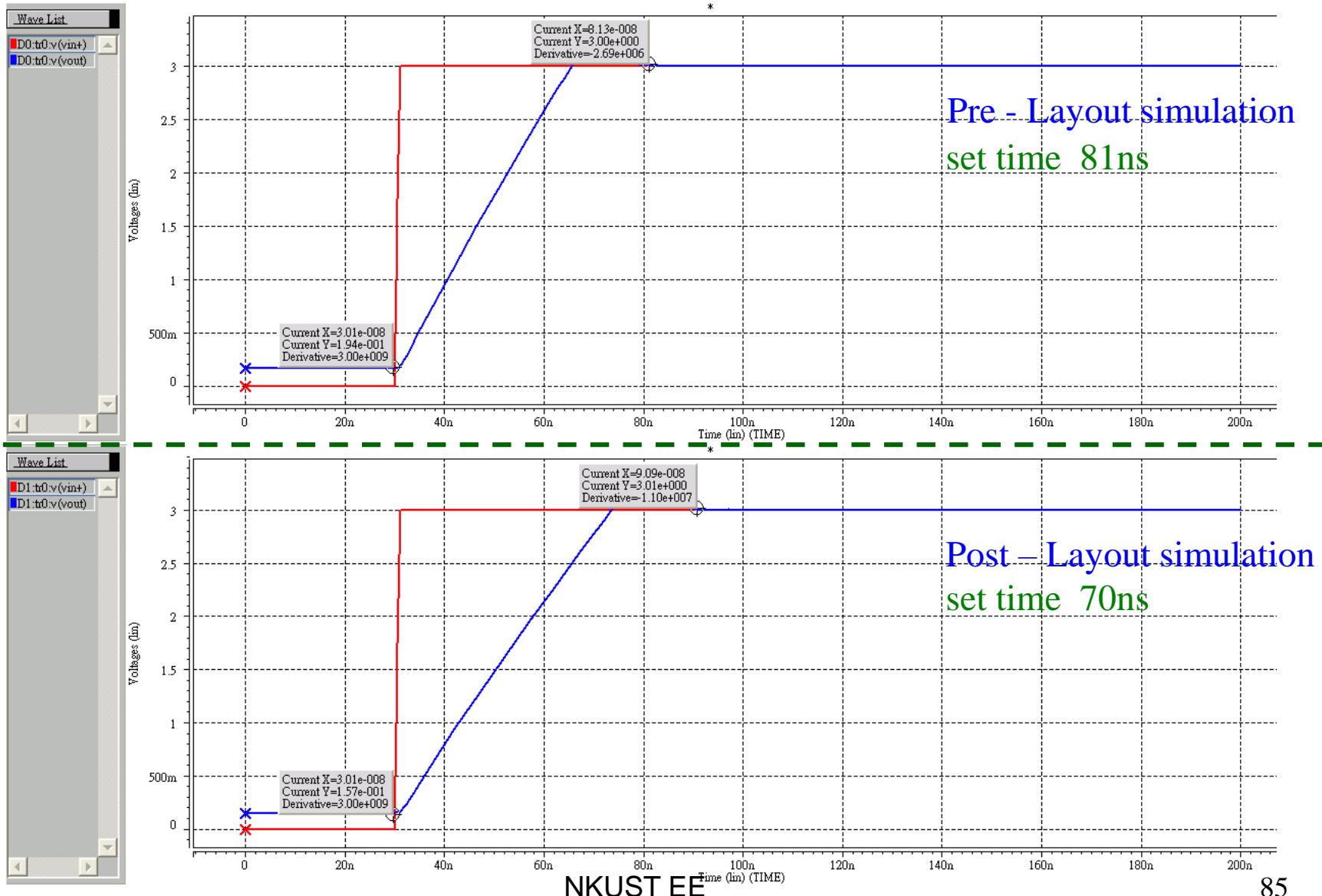

# Simulation of ICMR

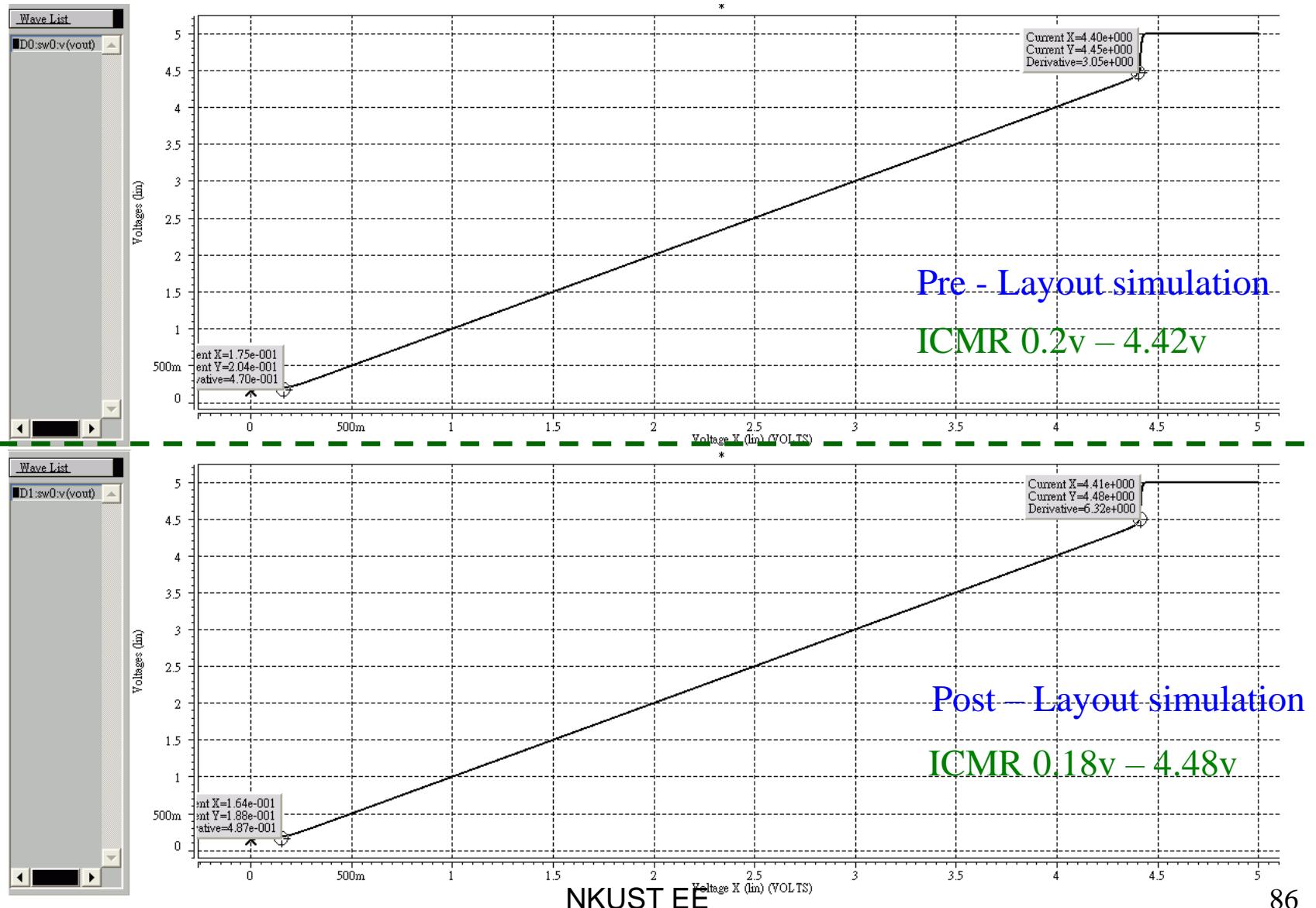

# Simulation of PSRR

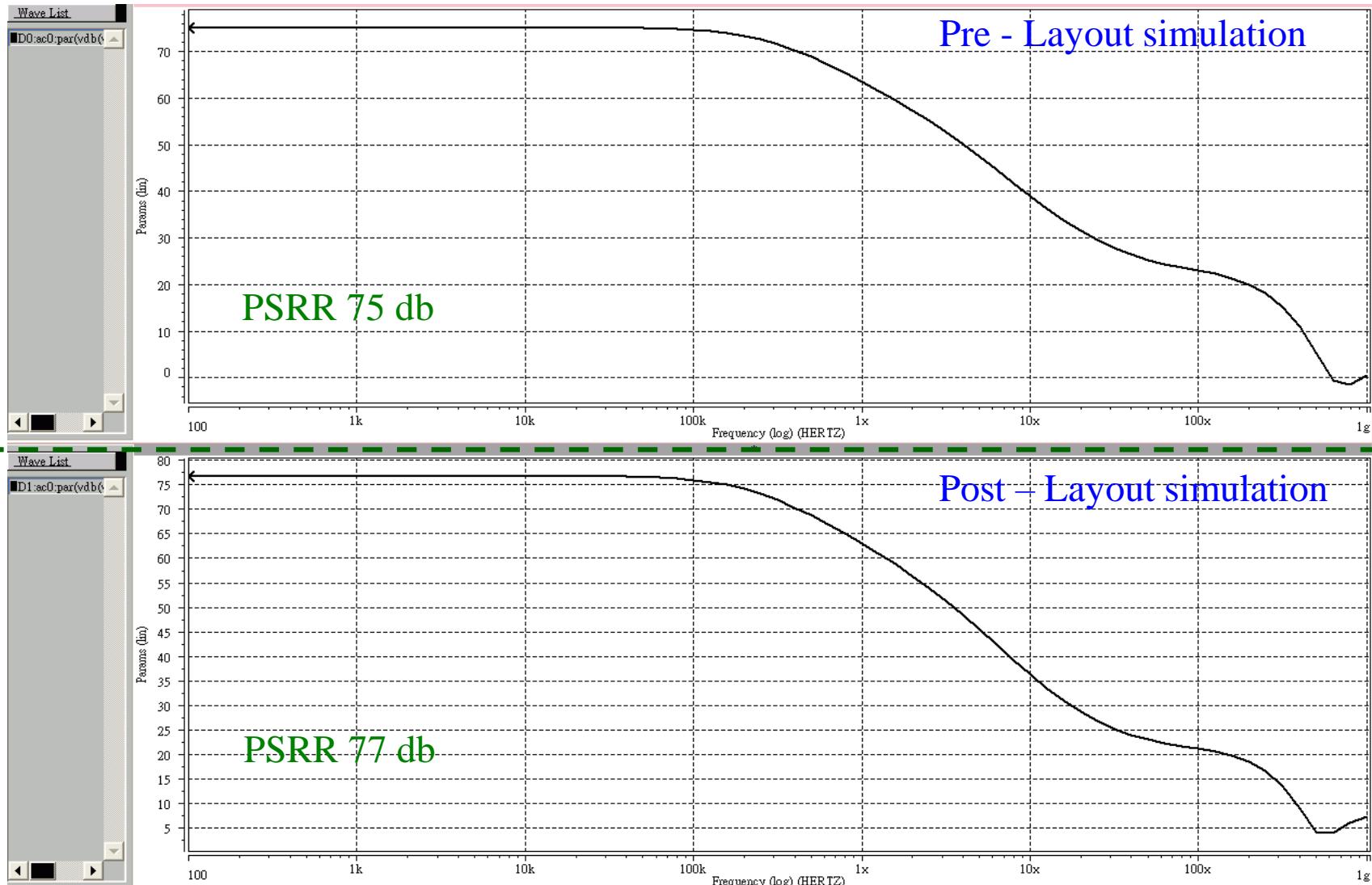


# Chapter 3. PWM IC Implementation

## (Full-Custom Design Tool Operation : Hspice, Laker, and Calibre)


# Outline

- 3-1. Operational Amplifier
- 3-2. Comparator
- 3-3. Oscillator
- 3-4. PWM (Pulse-Width Modulation)


# PWM Schematic

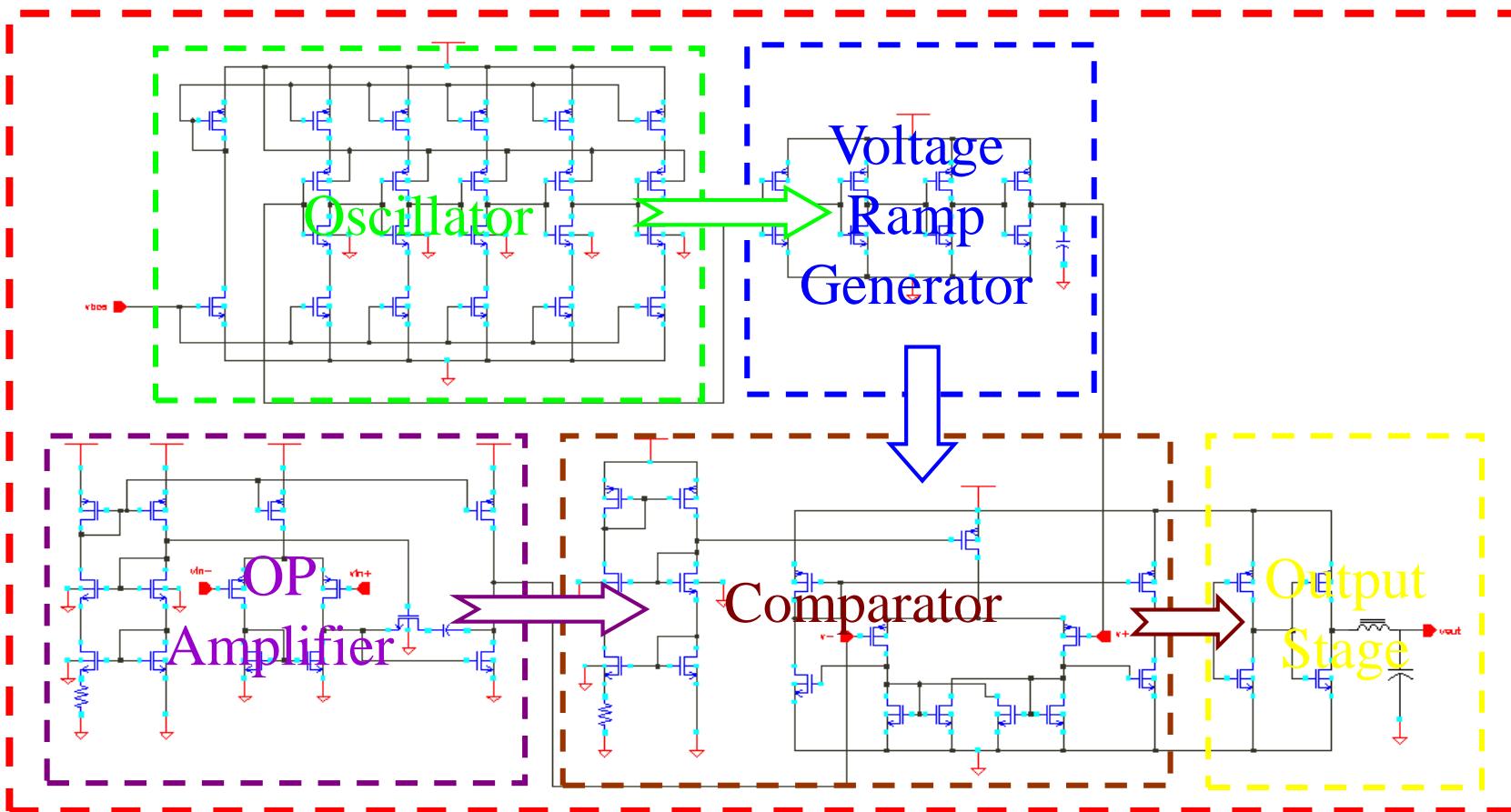


# OP-Bias-Schematic

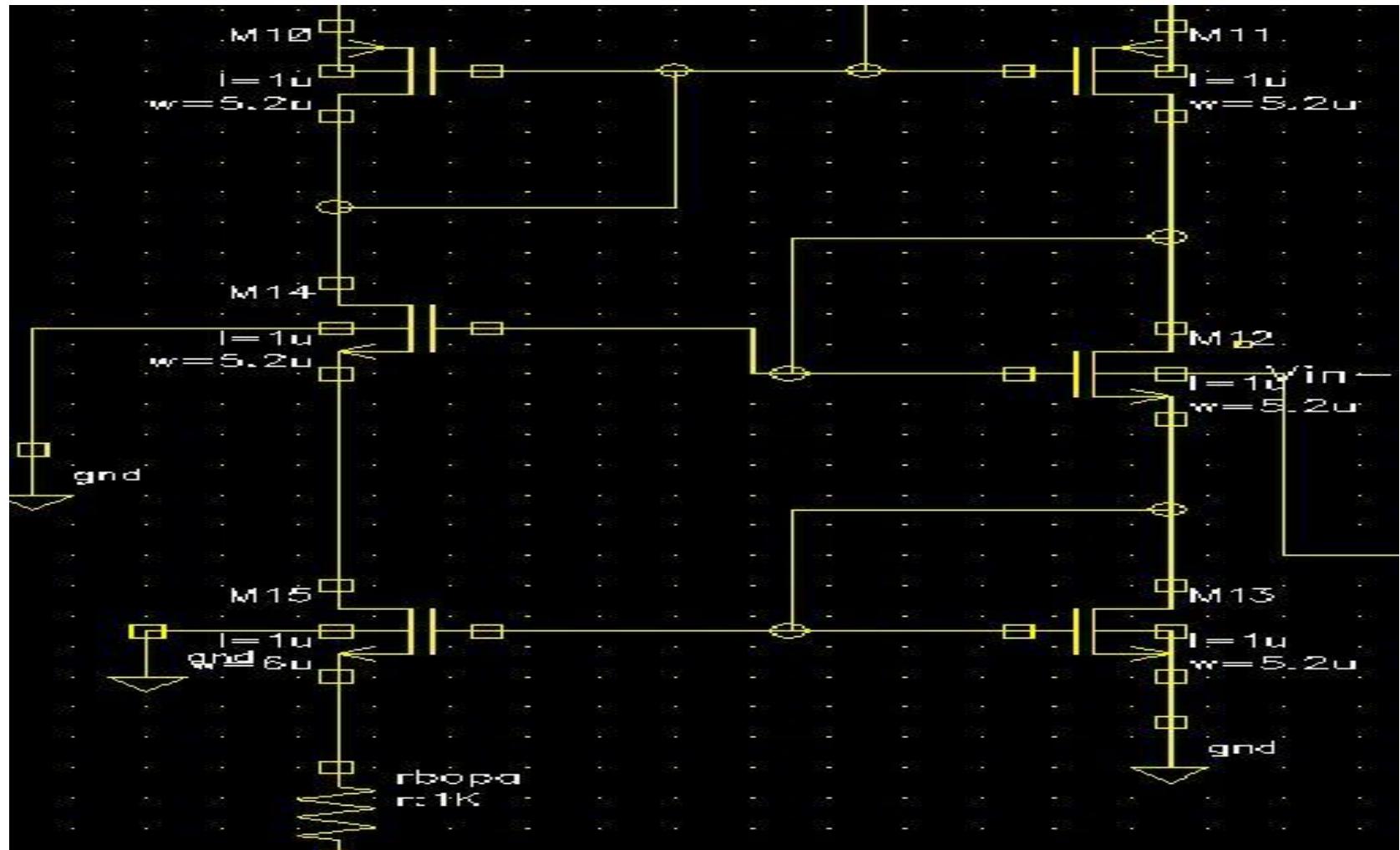


# OP-Bias-Layout

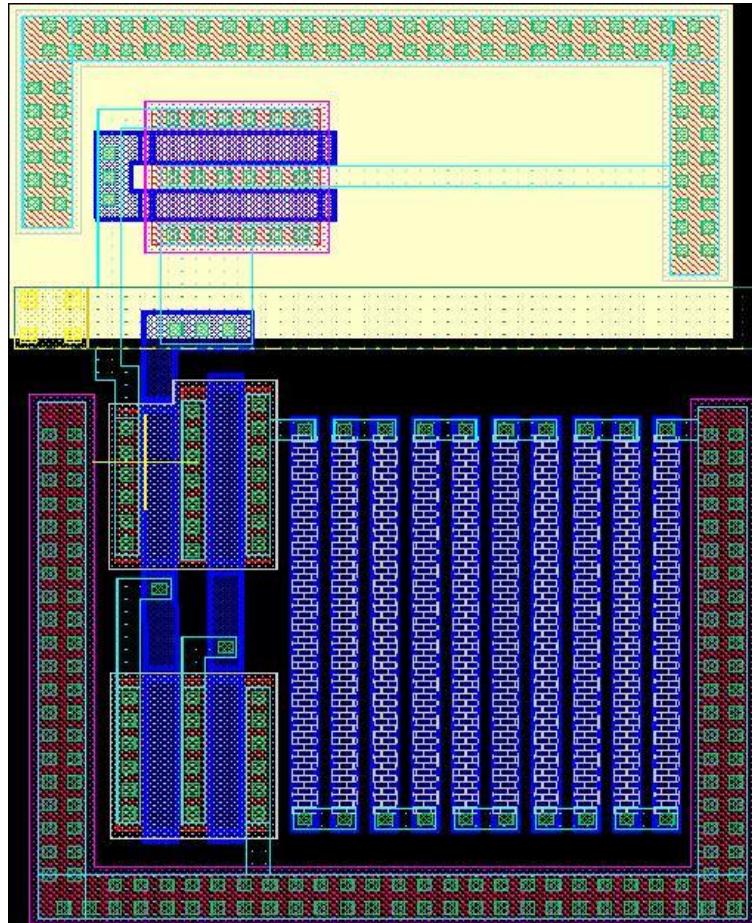


# OP-M1~2-Schematic

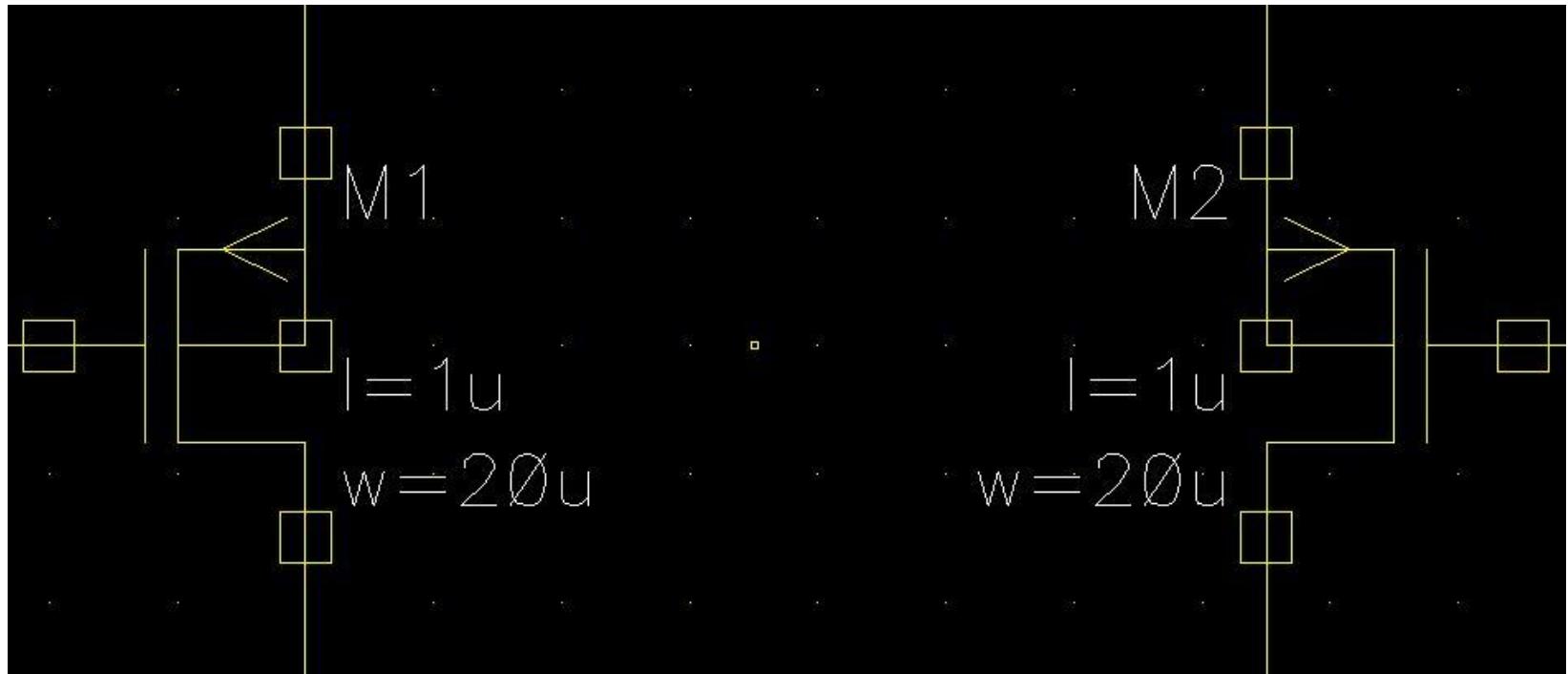


# OP-M1~2 Layout

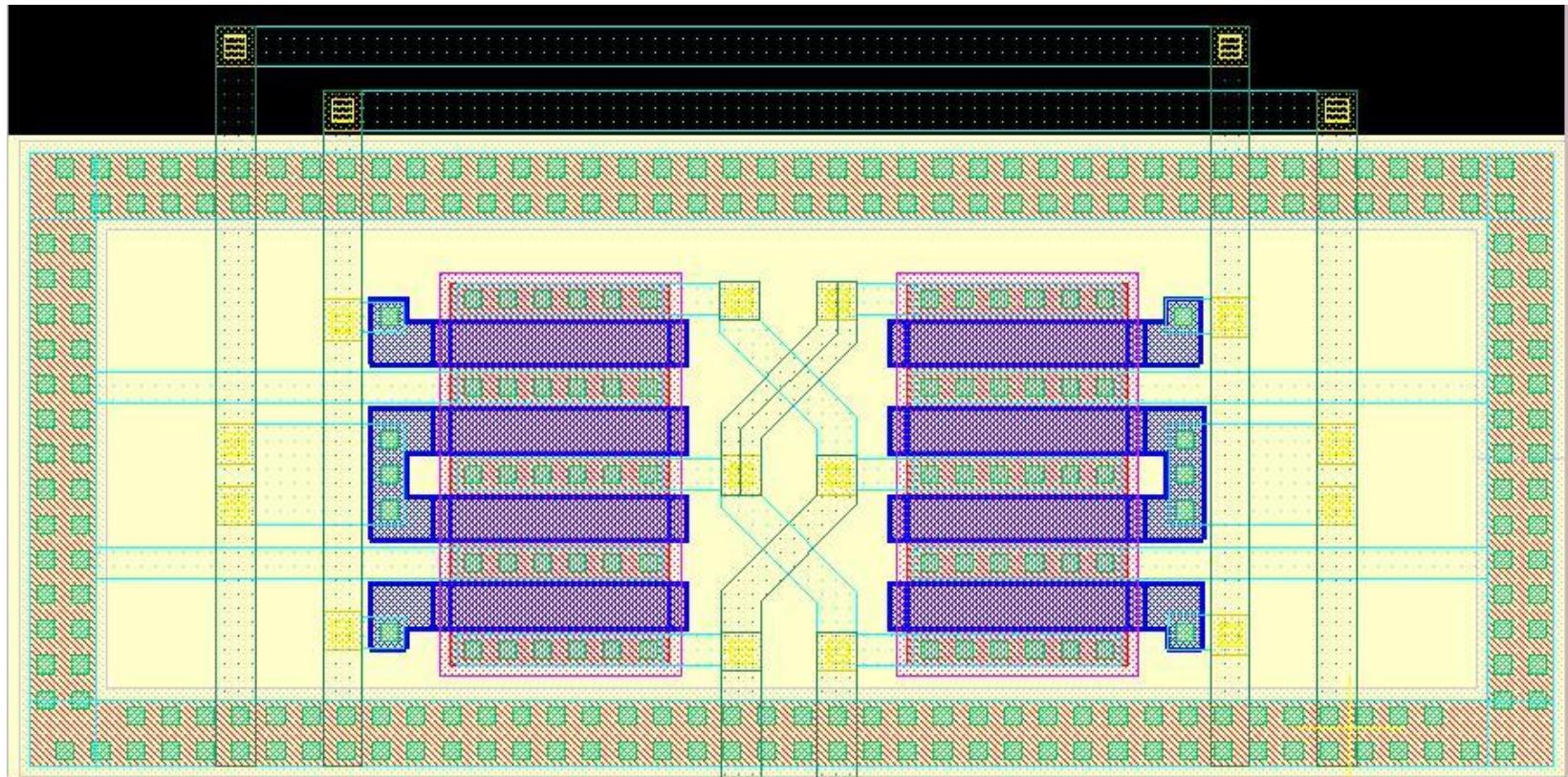


# OP-M3,4,7-Schematic

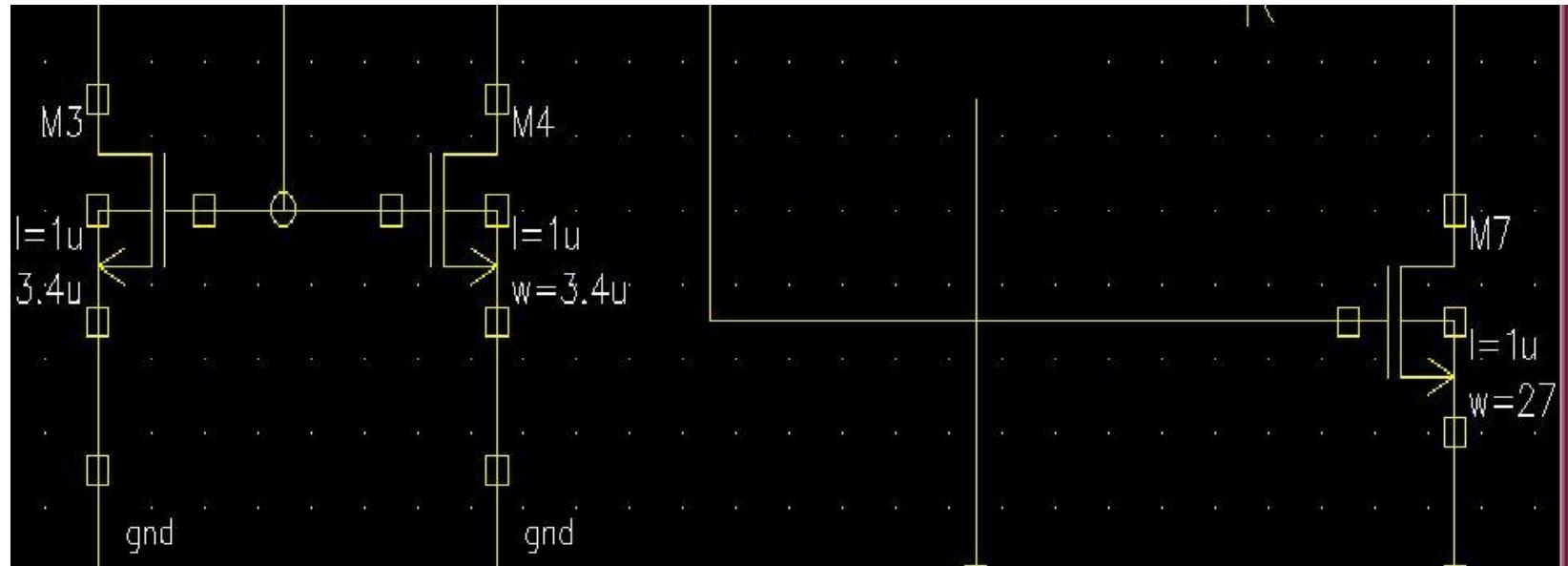


# OP-M3,4,7-Layout

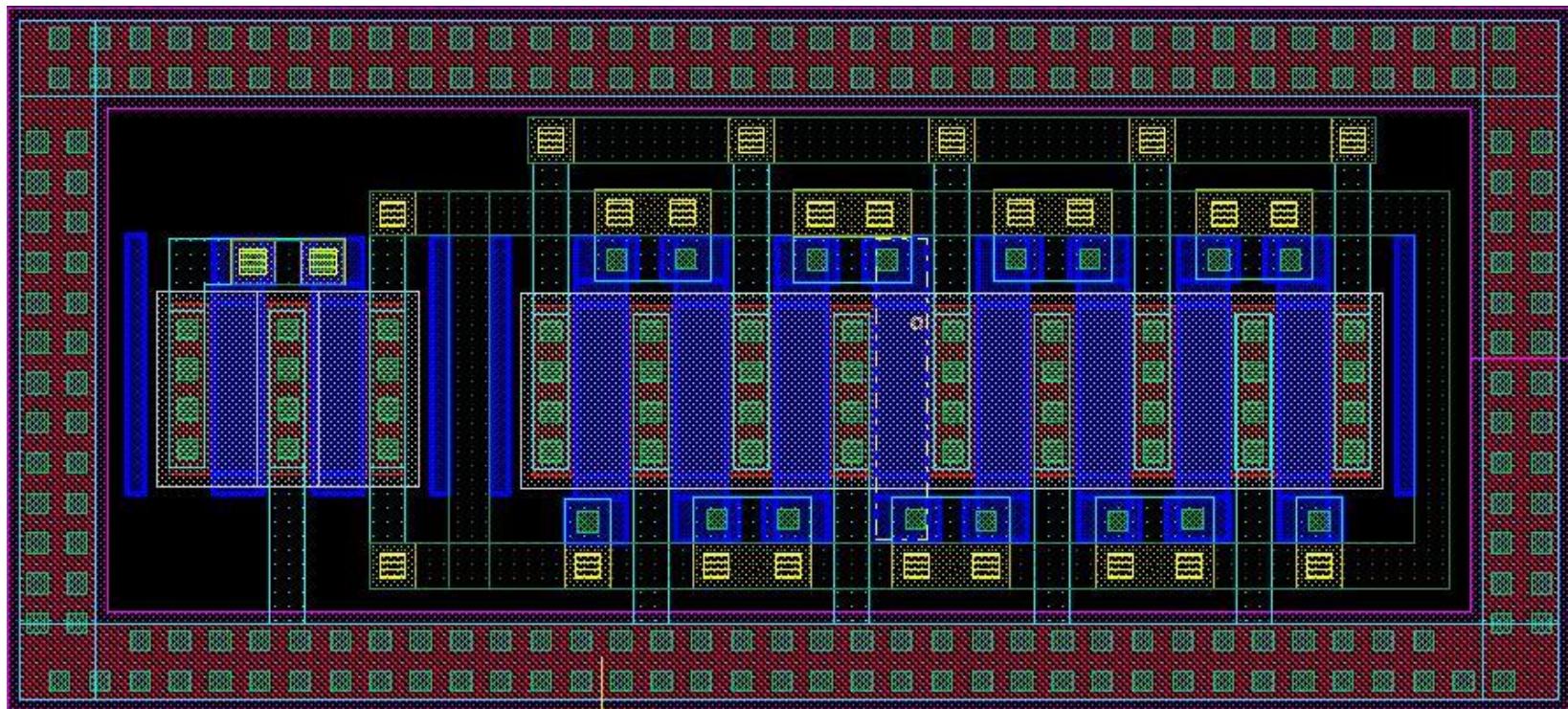


# OP-M5-Schematic

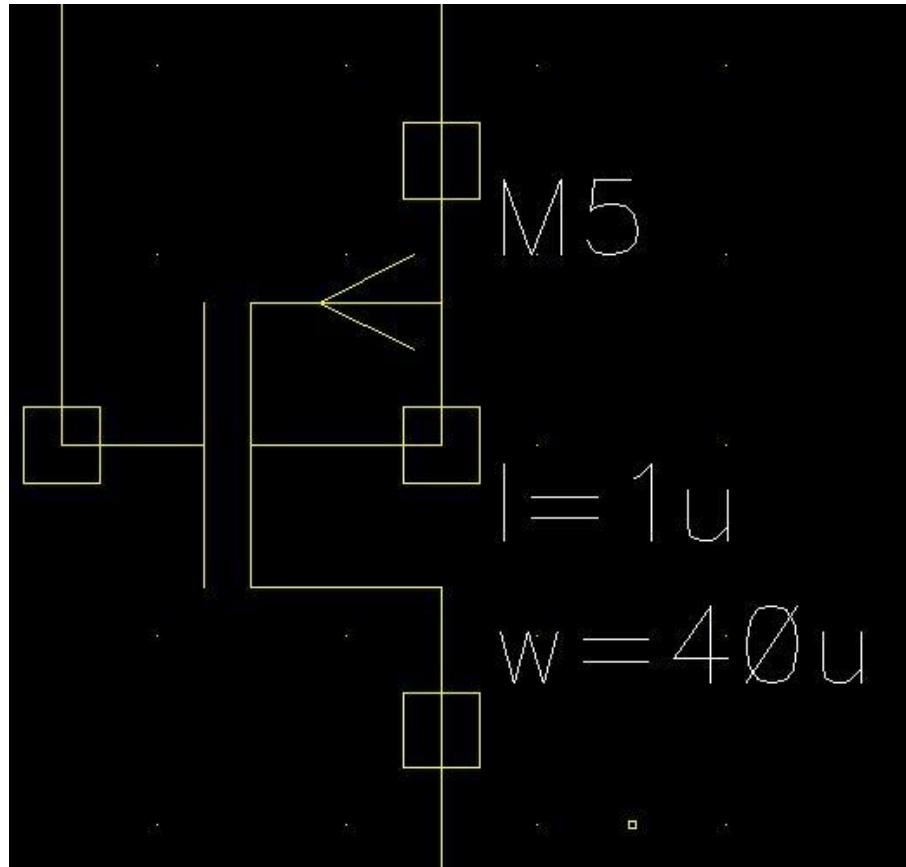


# OP-M5-Layout

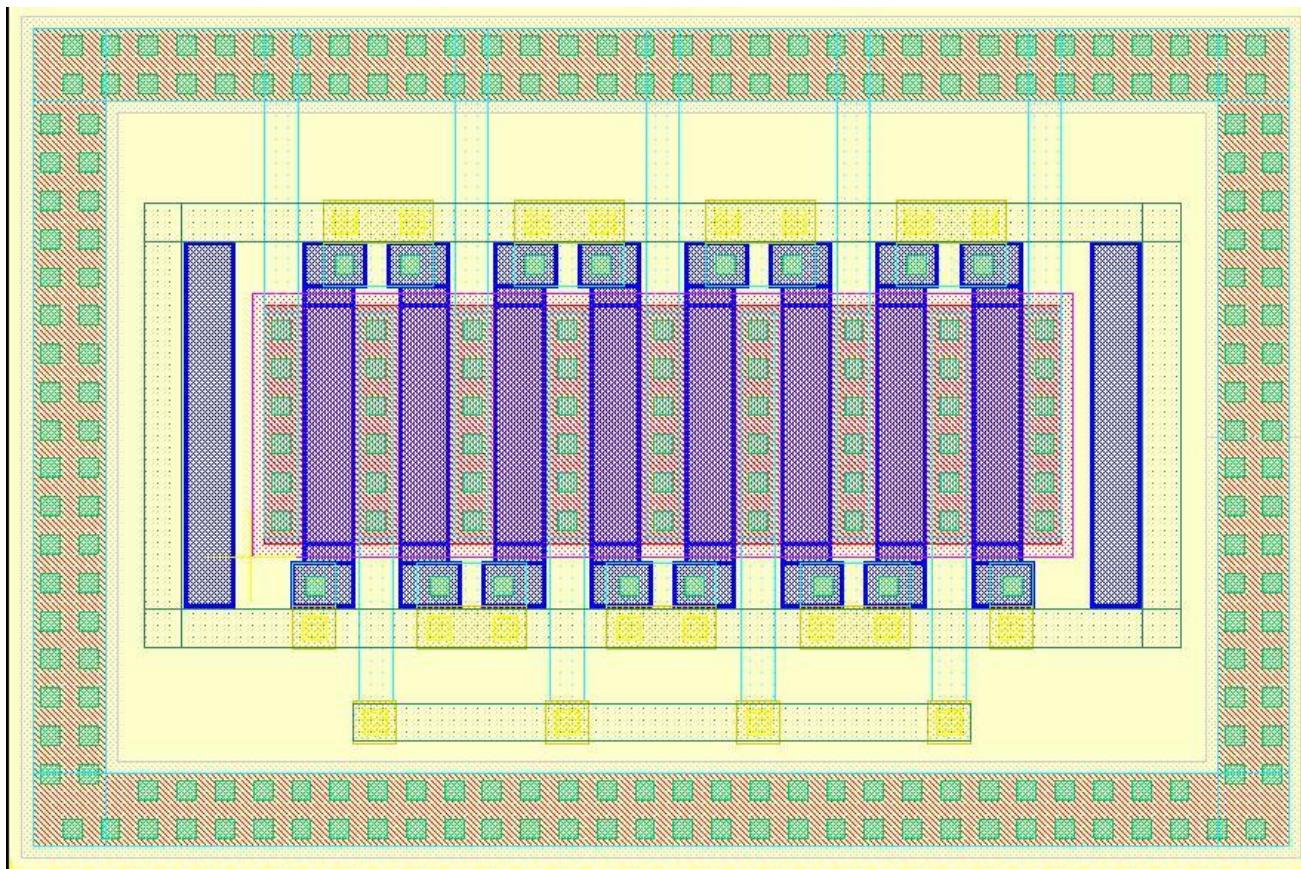


# OP-M6-Schematic

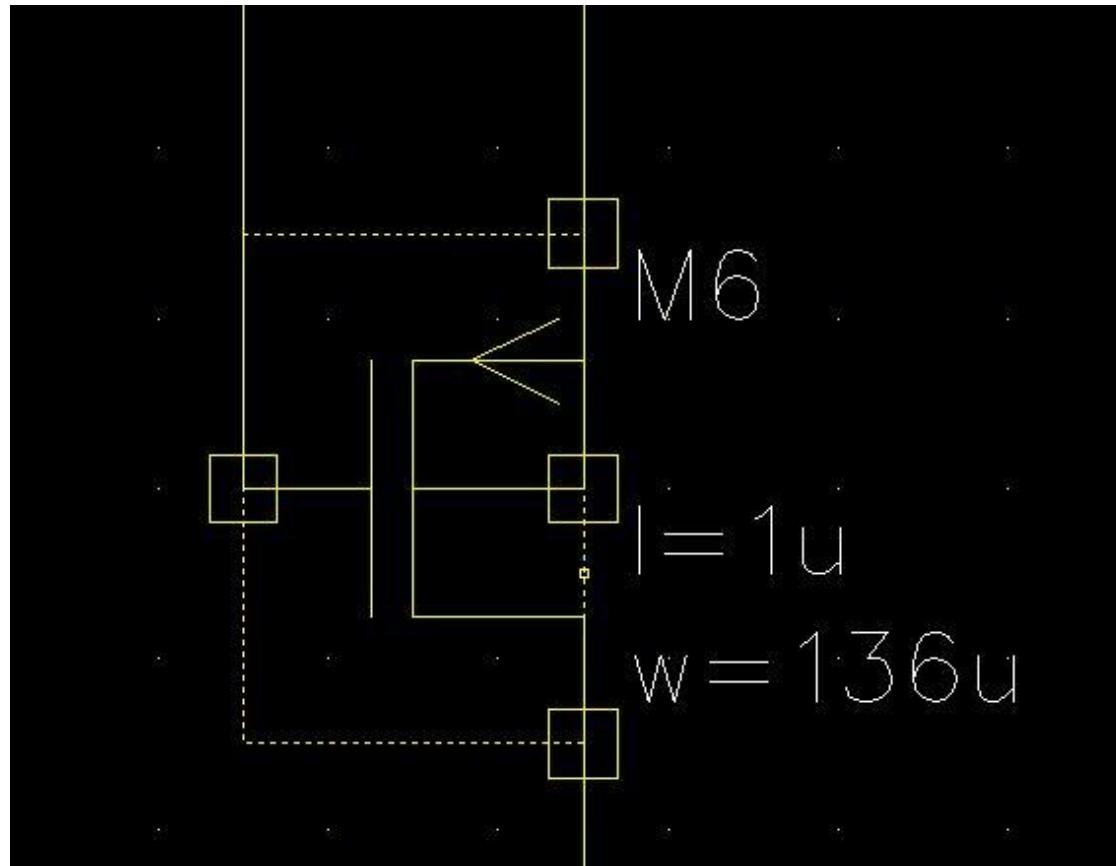


# OP-M6-Layout

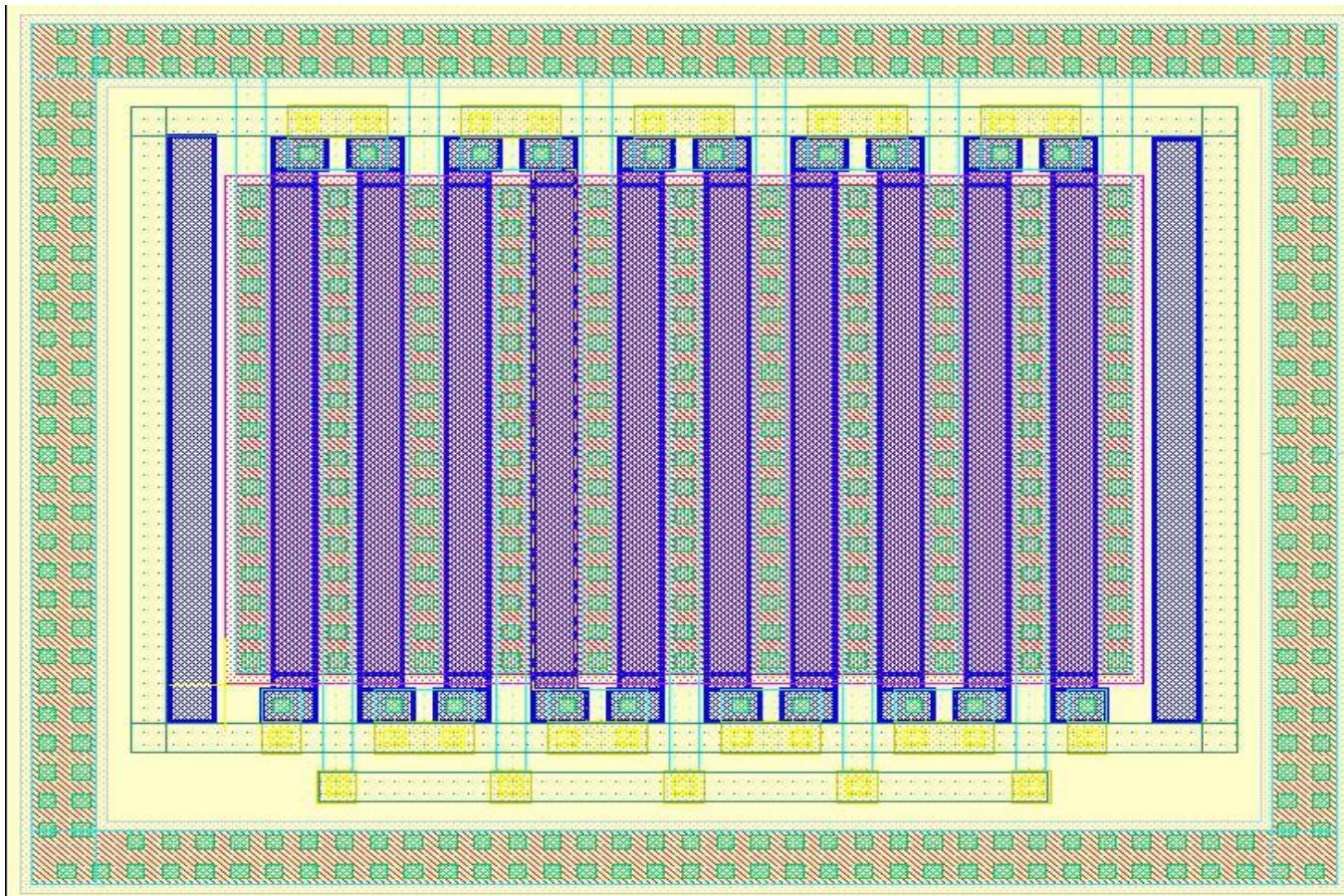


# OP-M16-Schematic

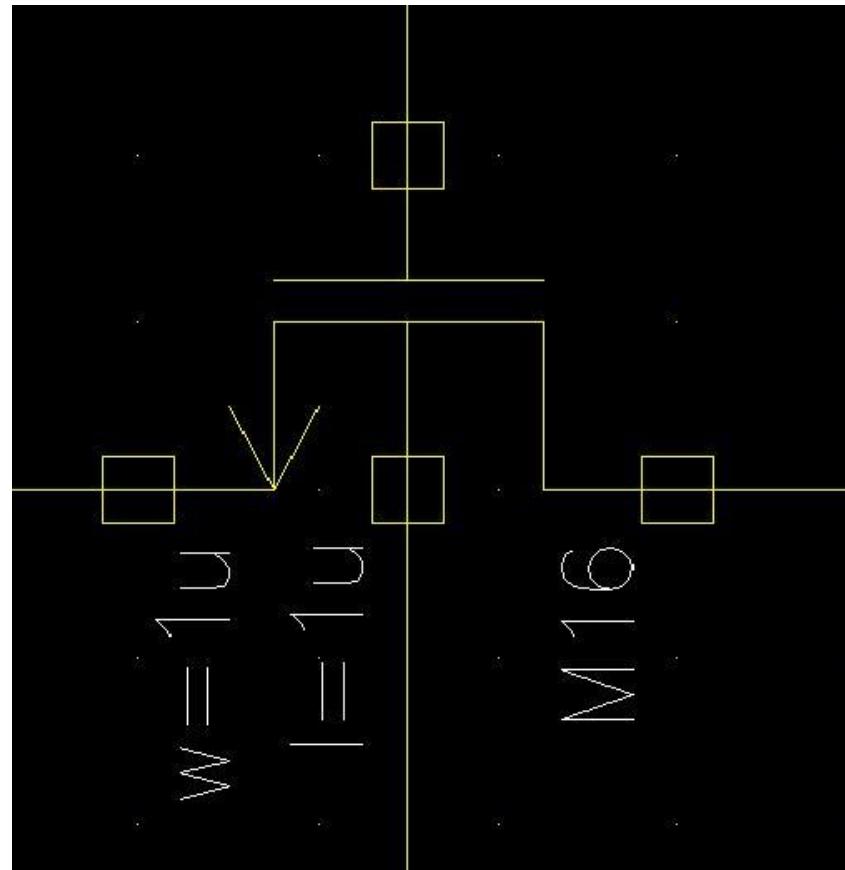


# OP-M16-Layout

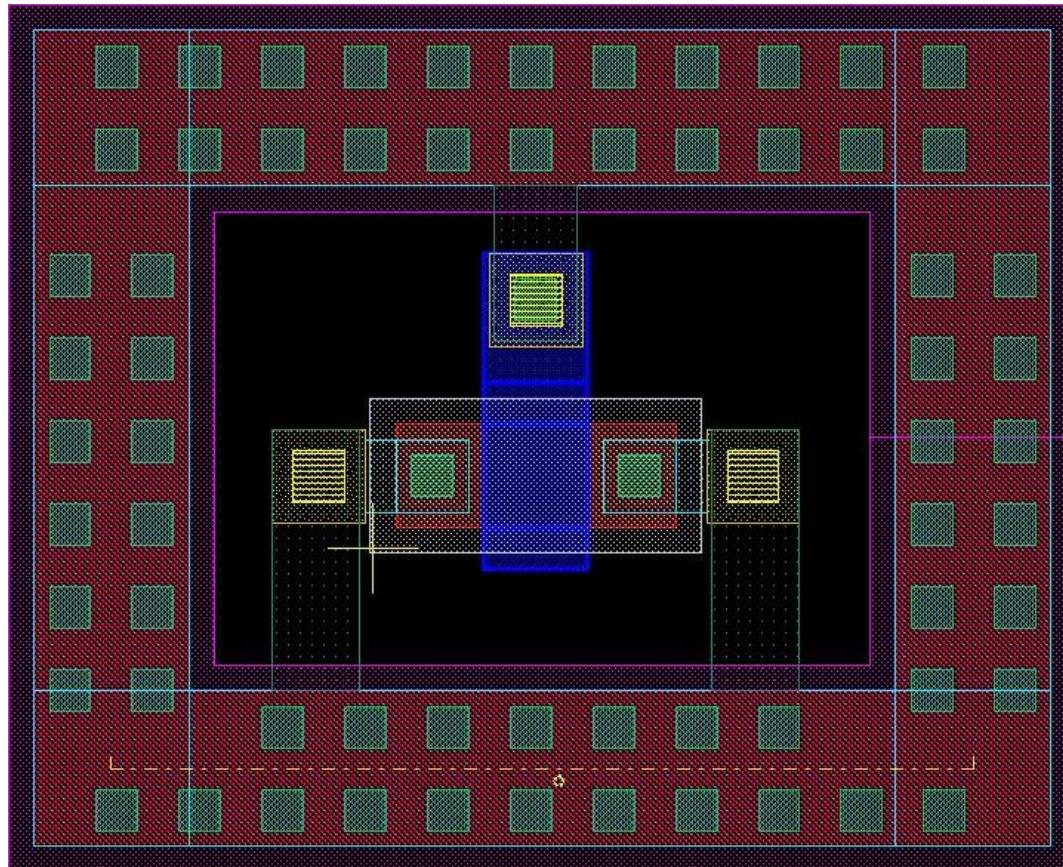


# OP-Cc-Schematic

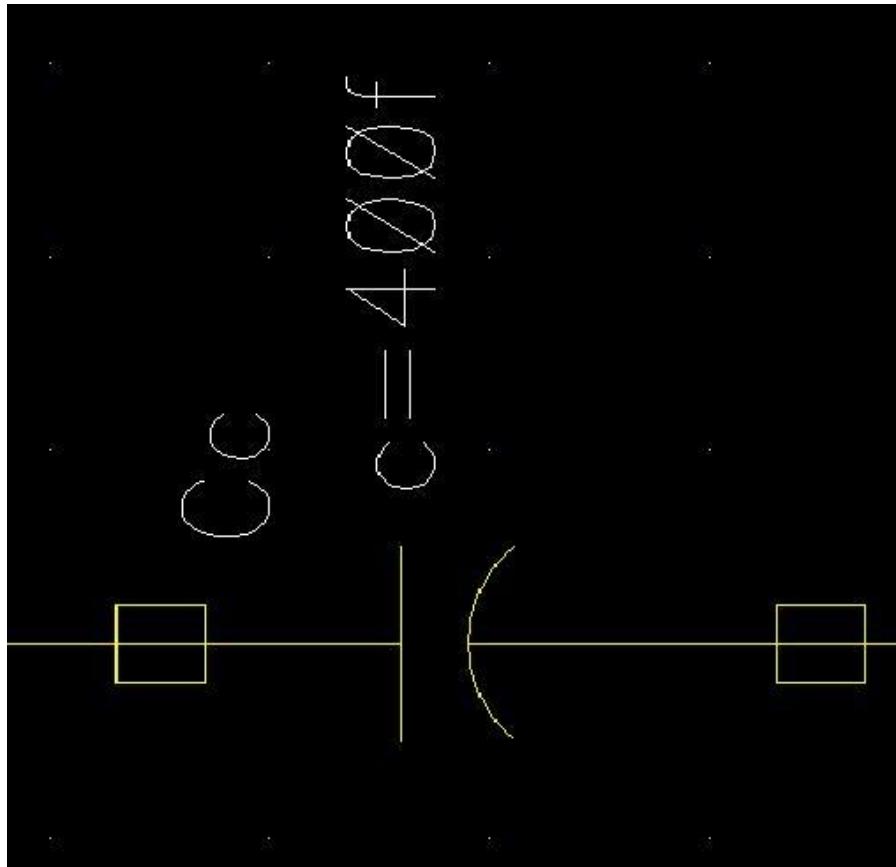


# OP-Cc-Layout

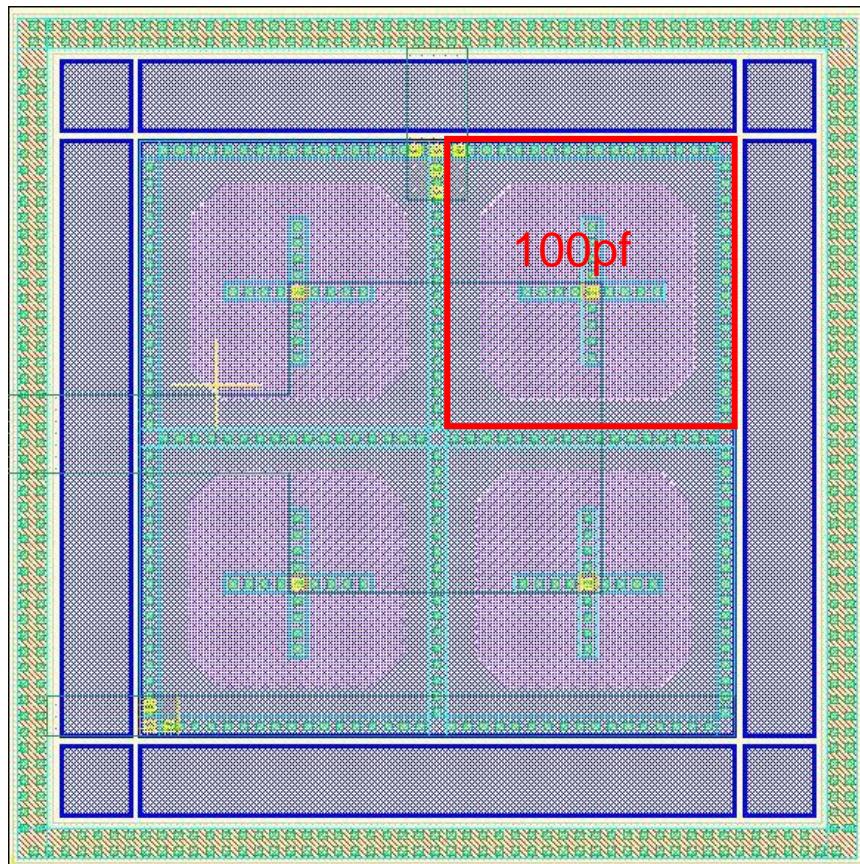


# OP-Layout

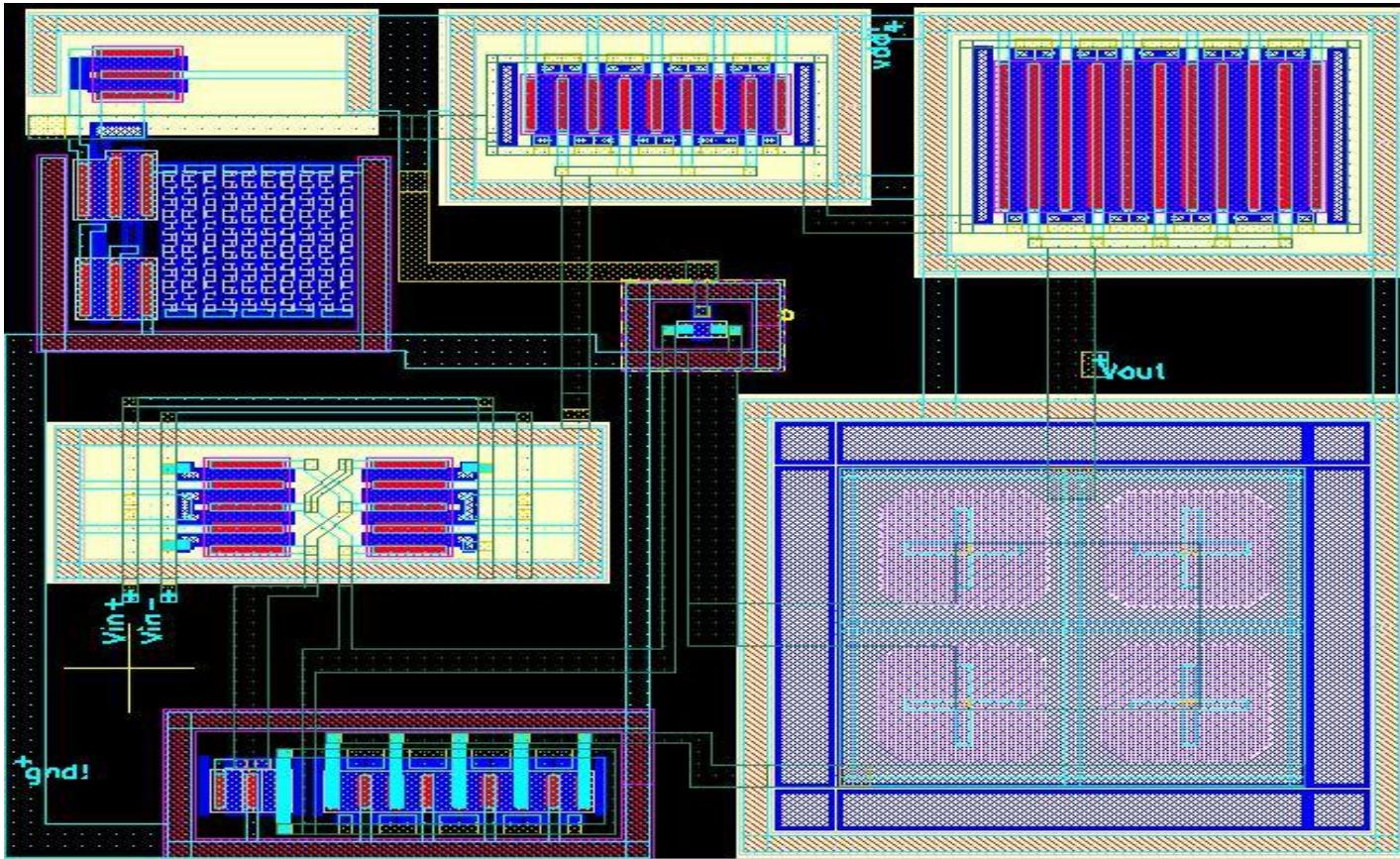


# OP-Drc

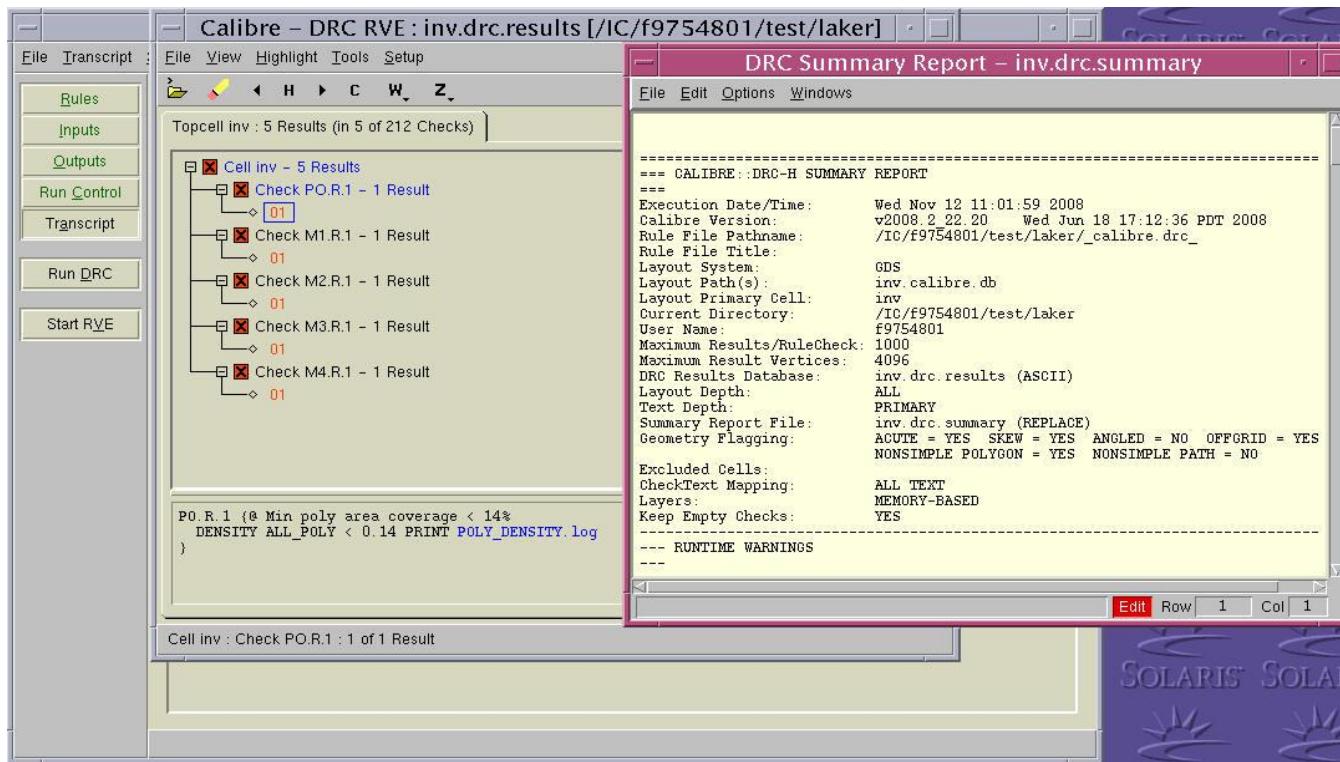


# OP-Lvs

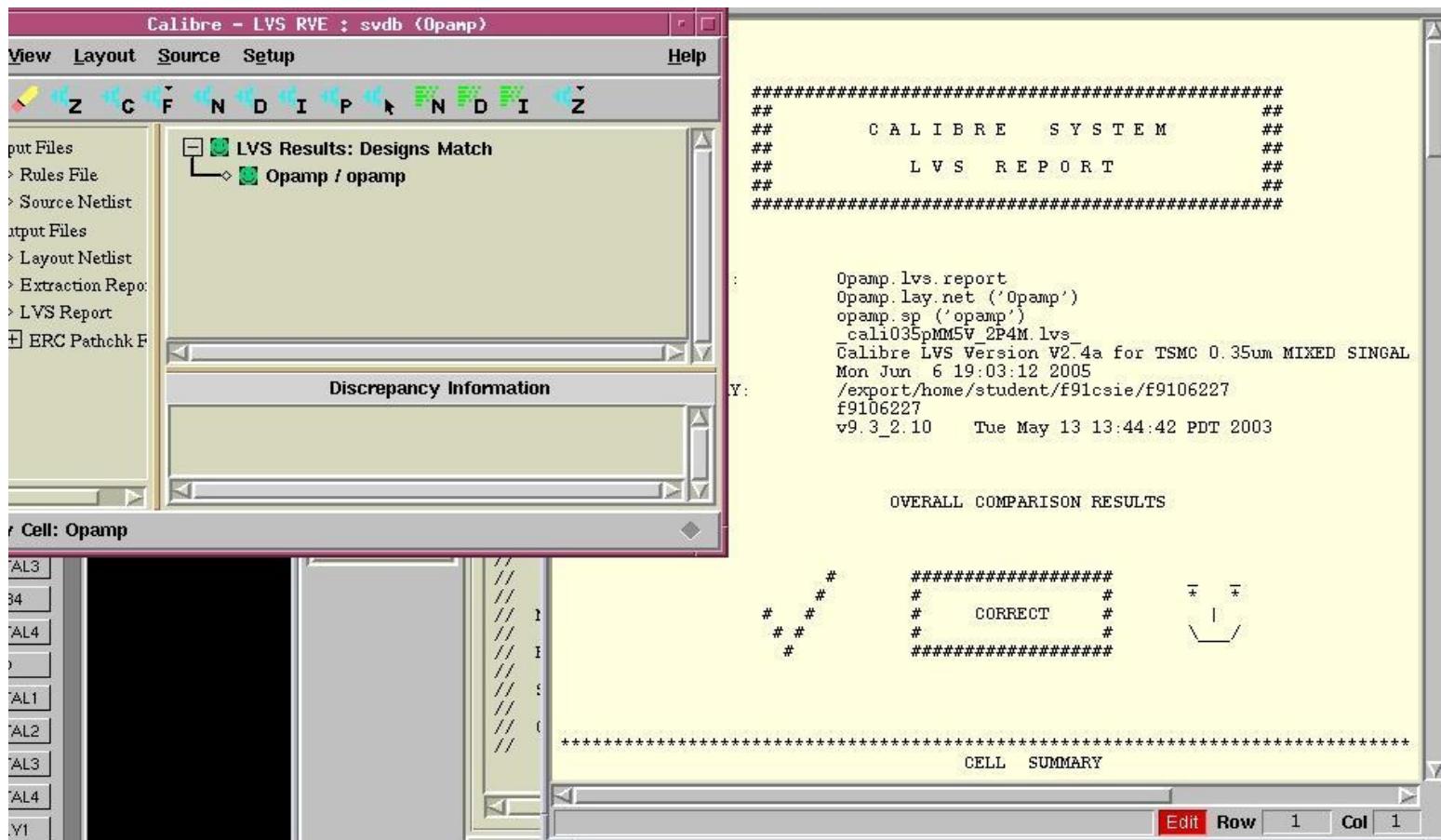


# OP-R/C Run PEX

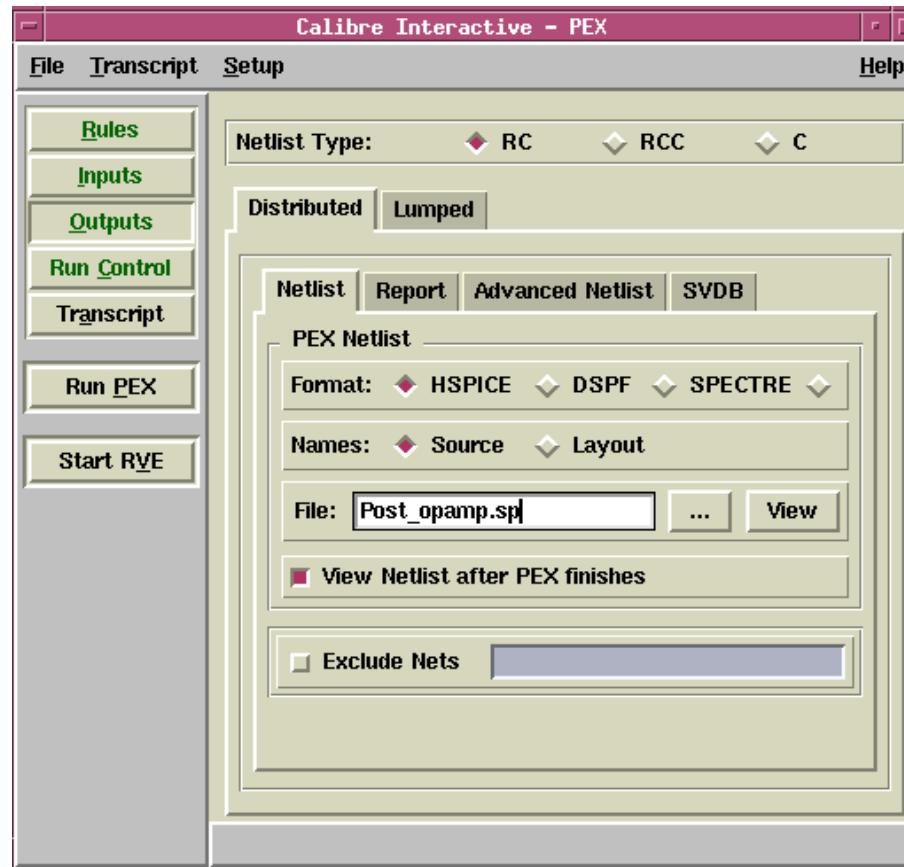


# OP-R/C Run PEX Success

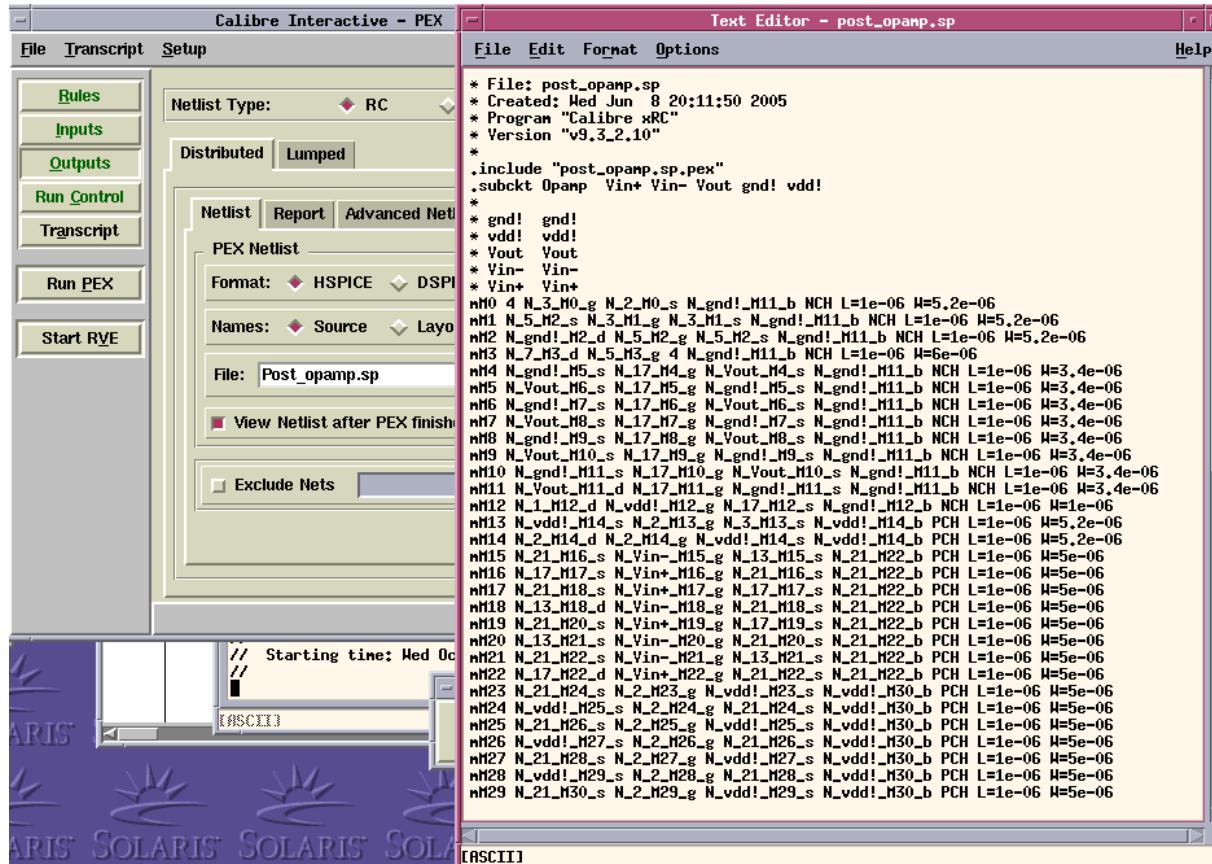


# Comparator-Bias-Schematic

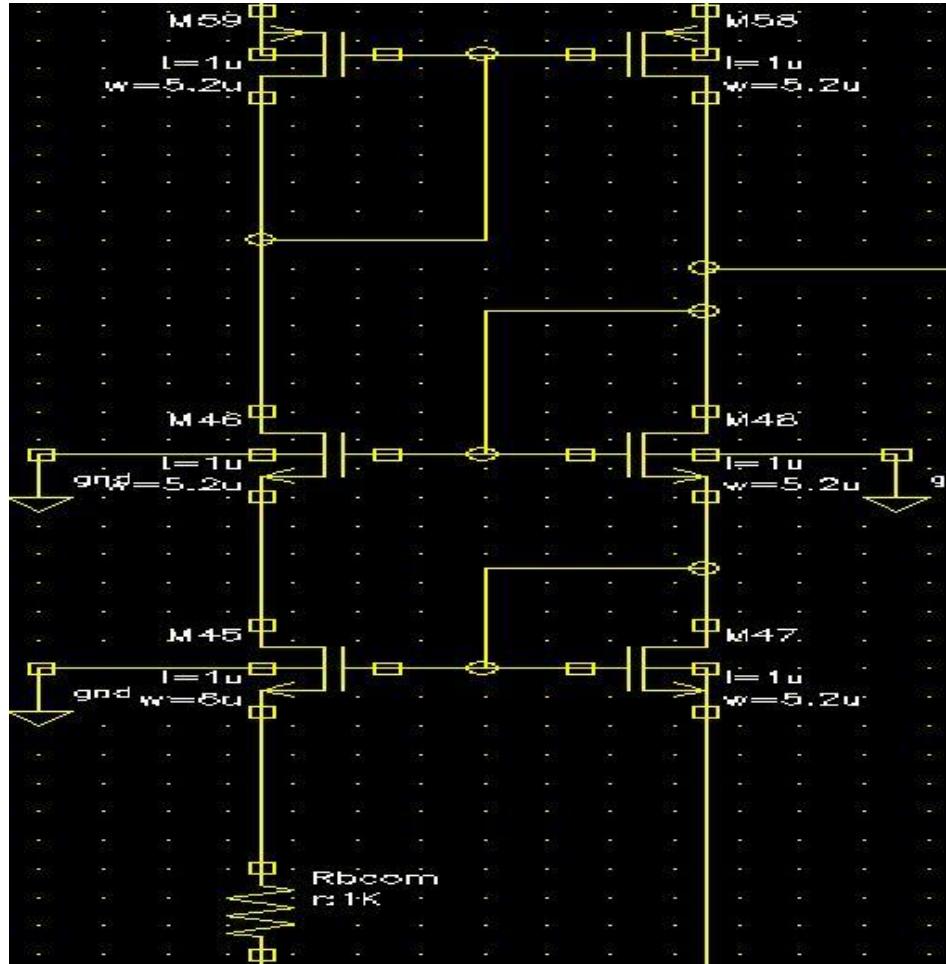


# Comparator-Bias-Layout

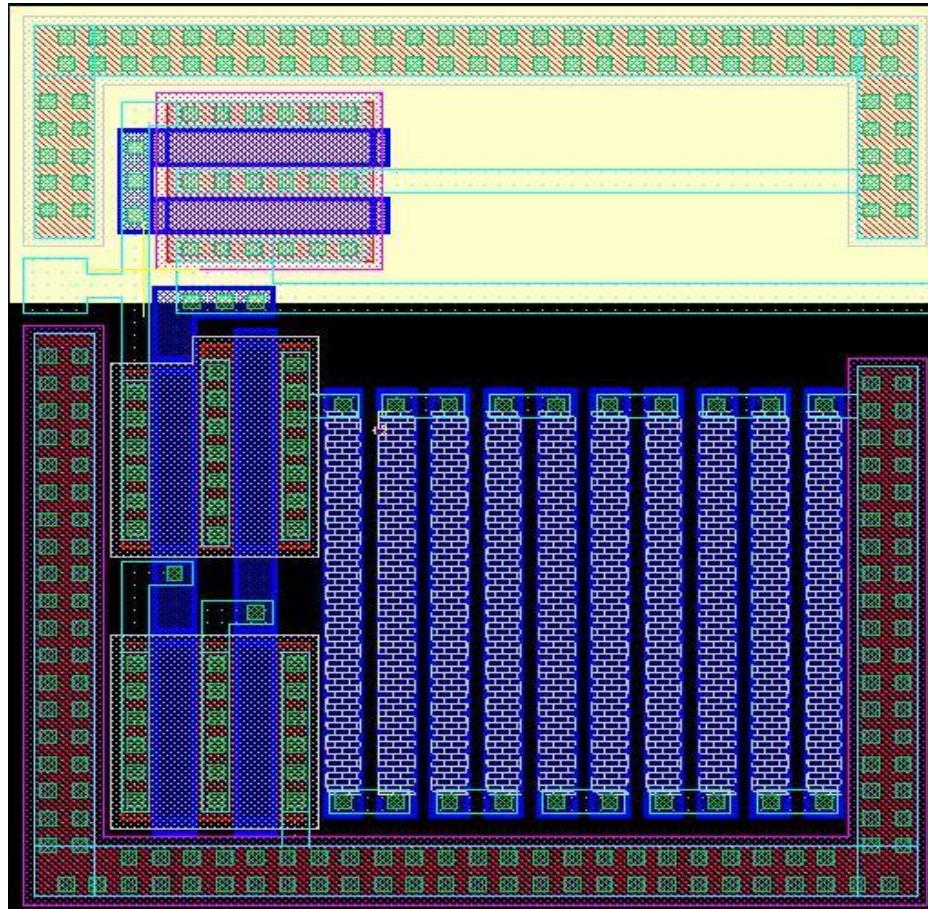


# Comparator-M44-Schematic

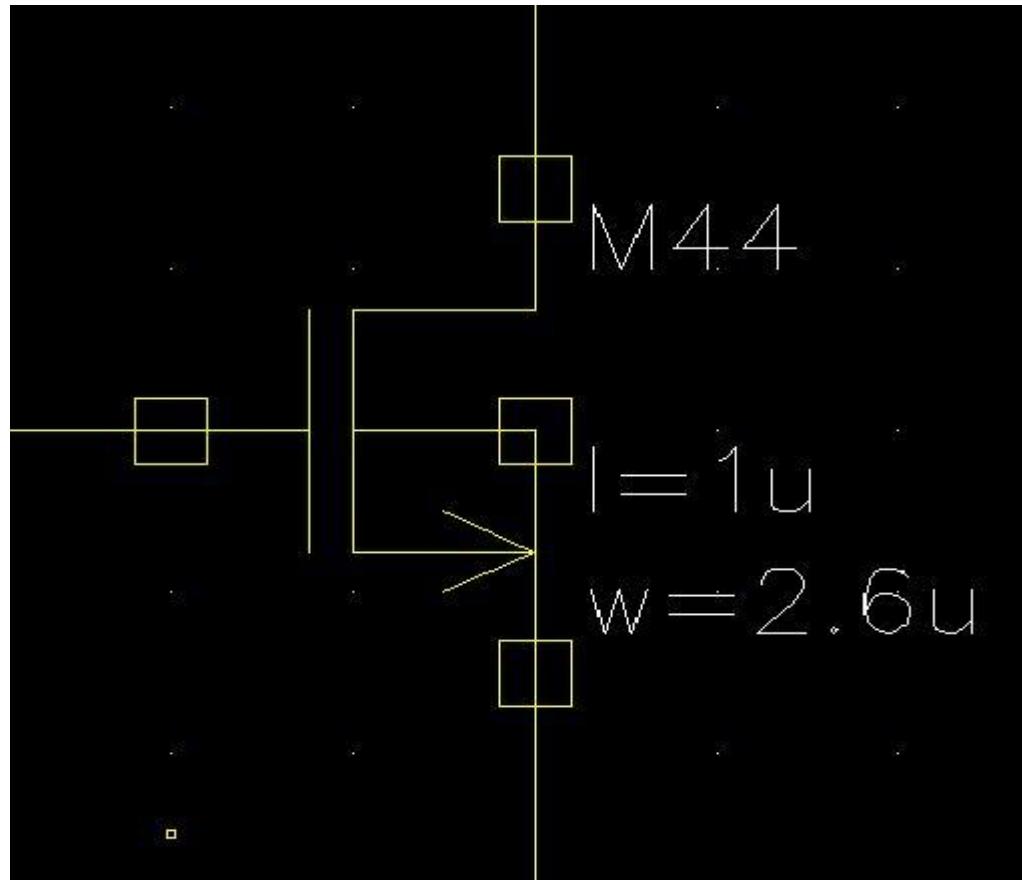


# Comparator-M44-Layout

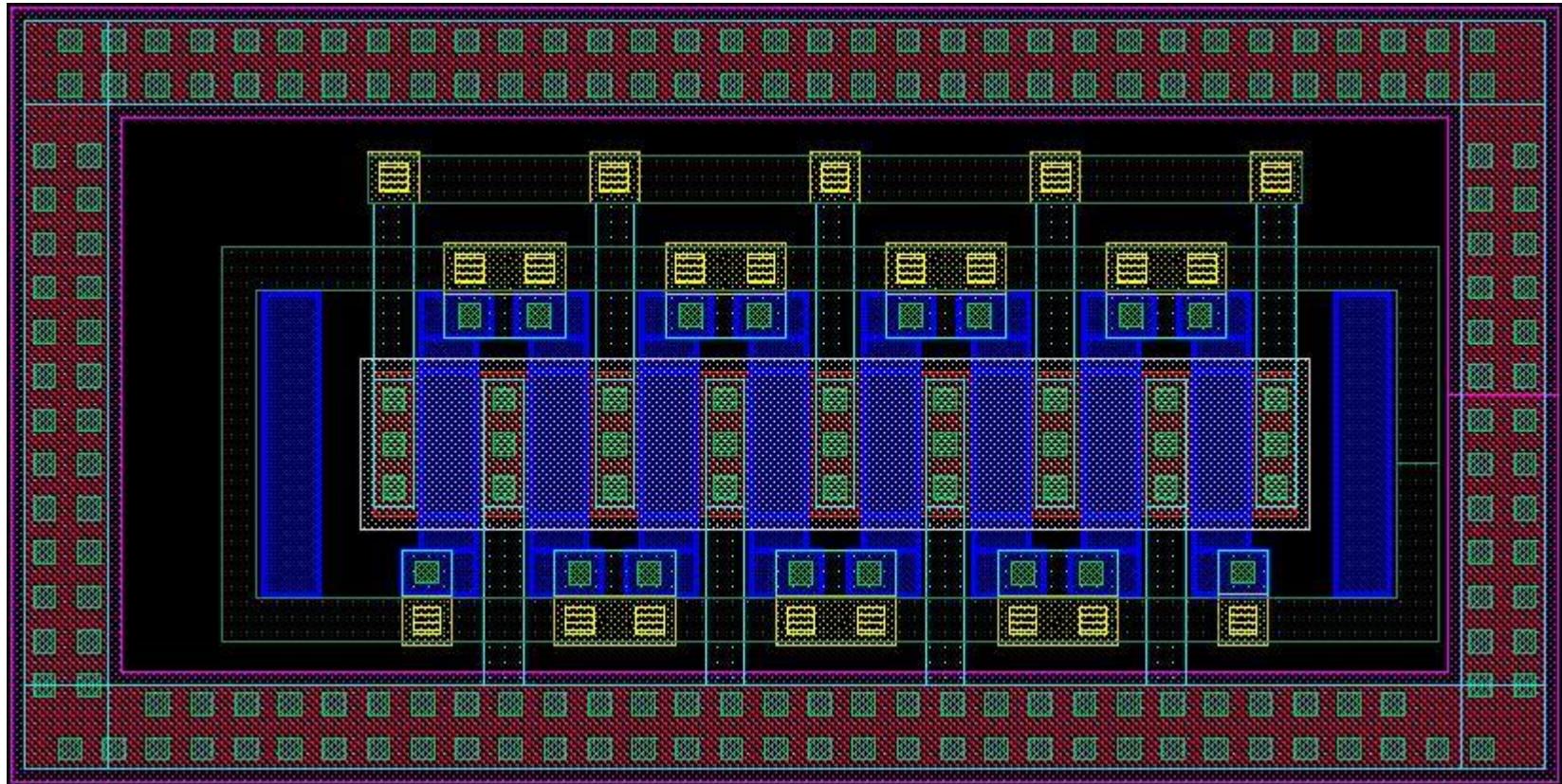


# Comparator-M49-Schematic

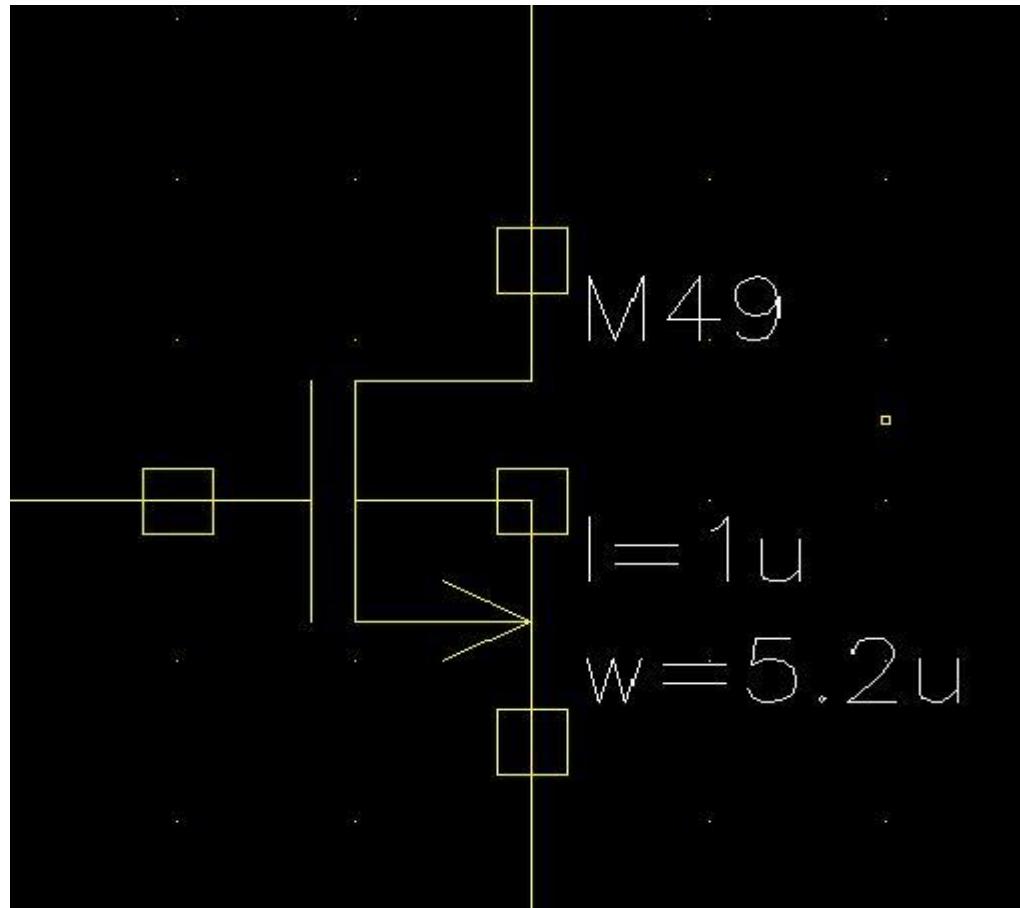


# Comparator-M49-Layout

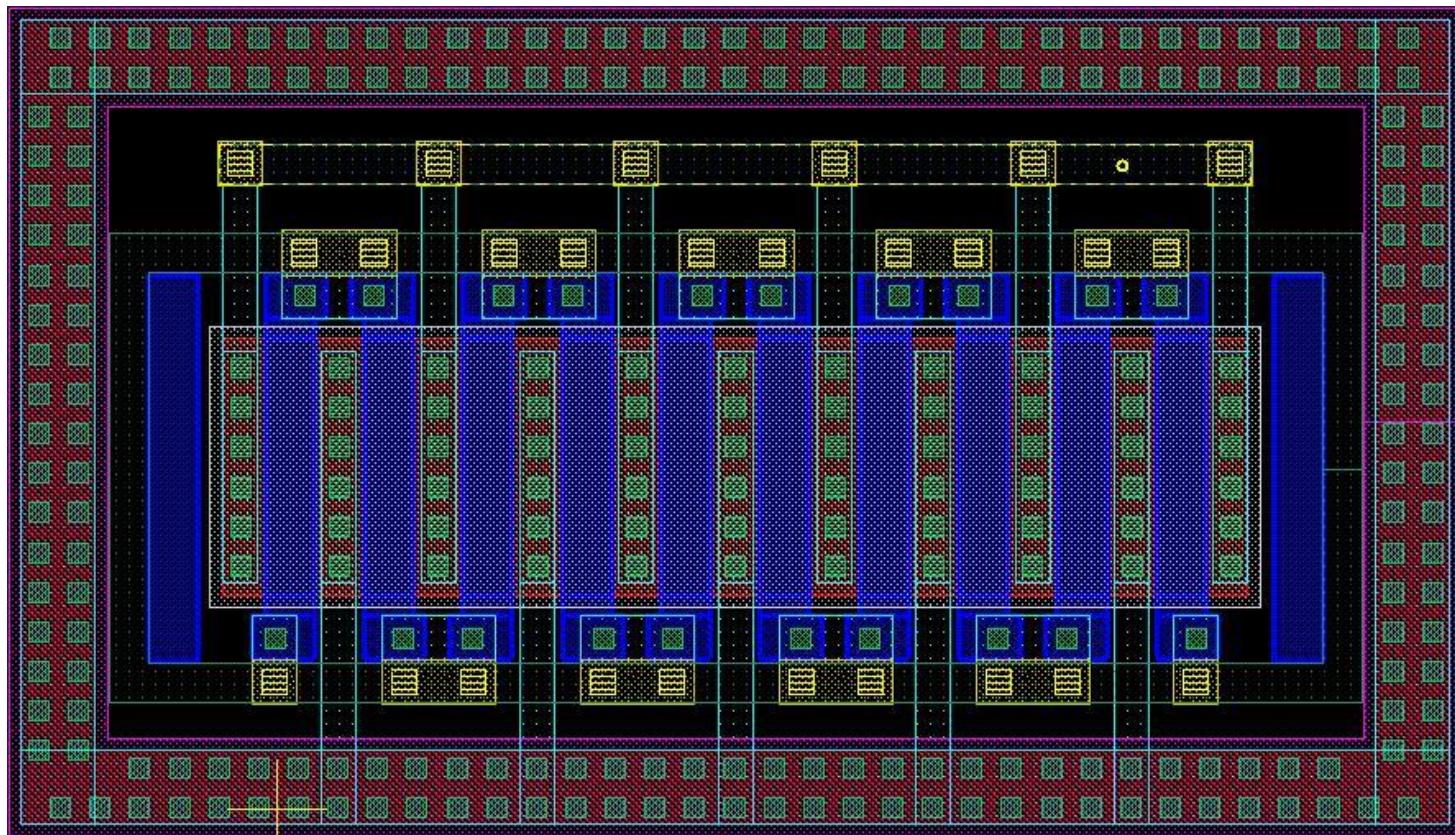


# Comparator-M50,55-Schematic

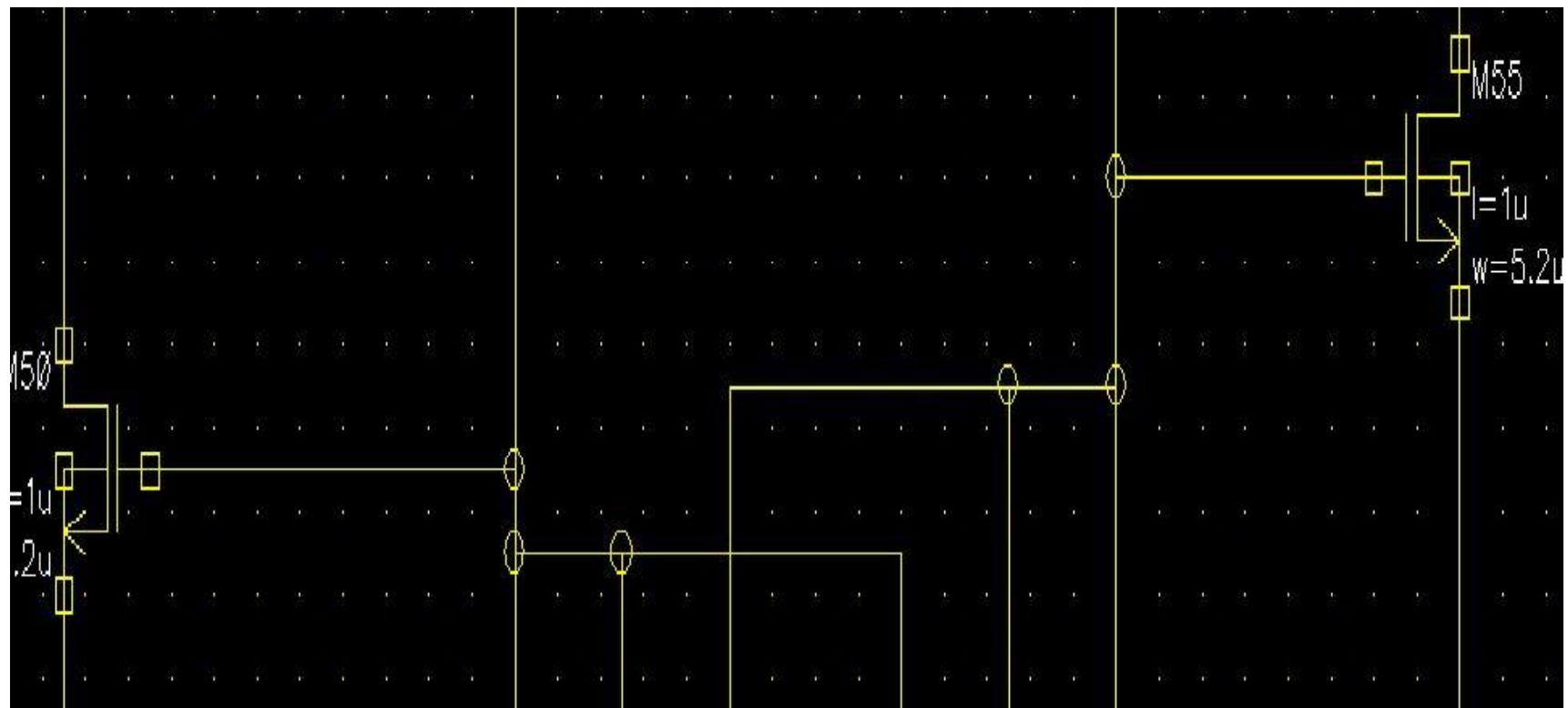


# Comparator-M50,55-Layout

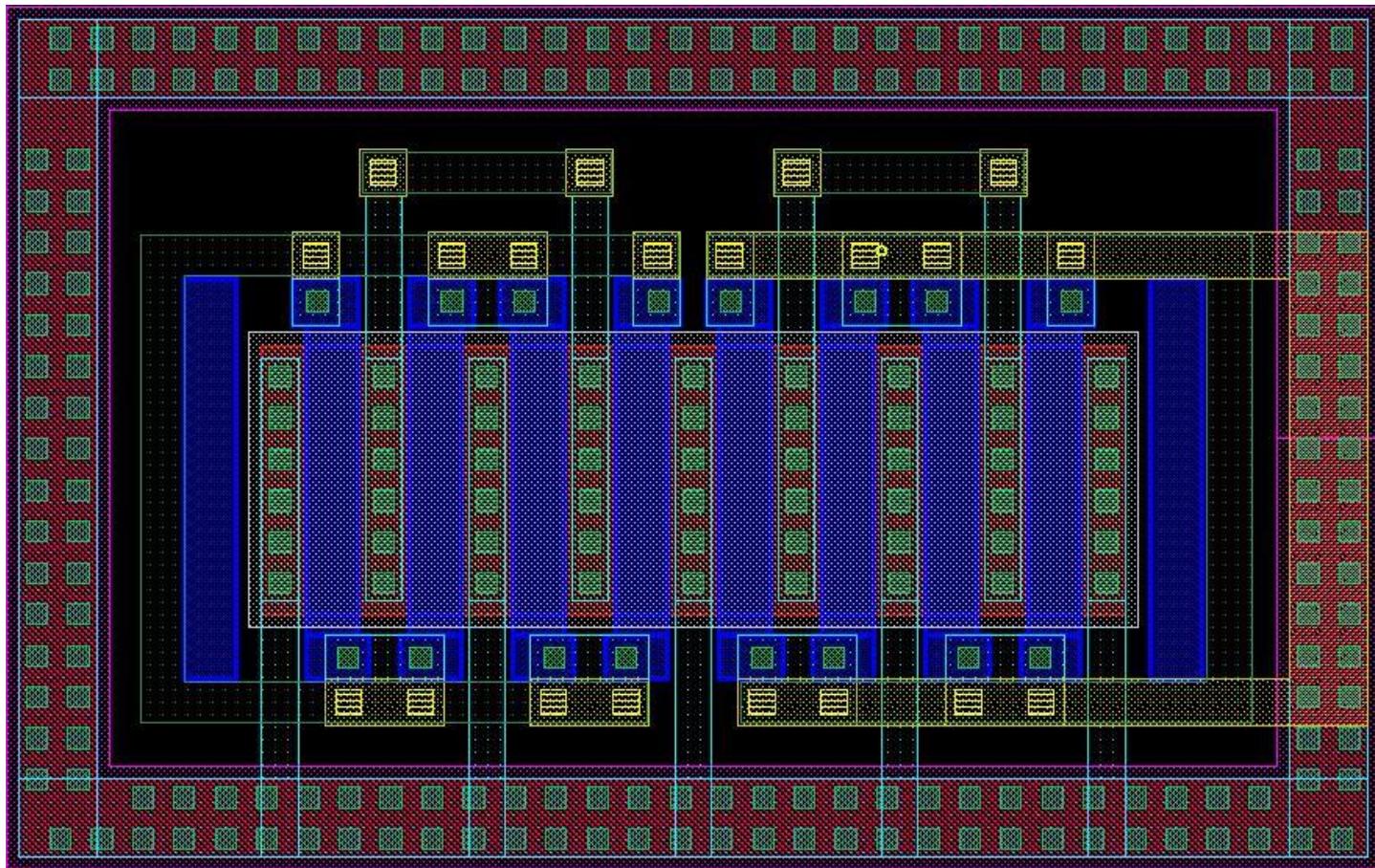


# Comparator-M51~54-Schematic

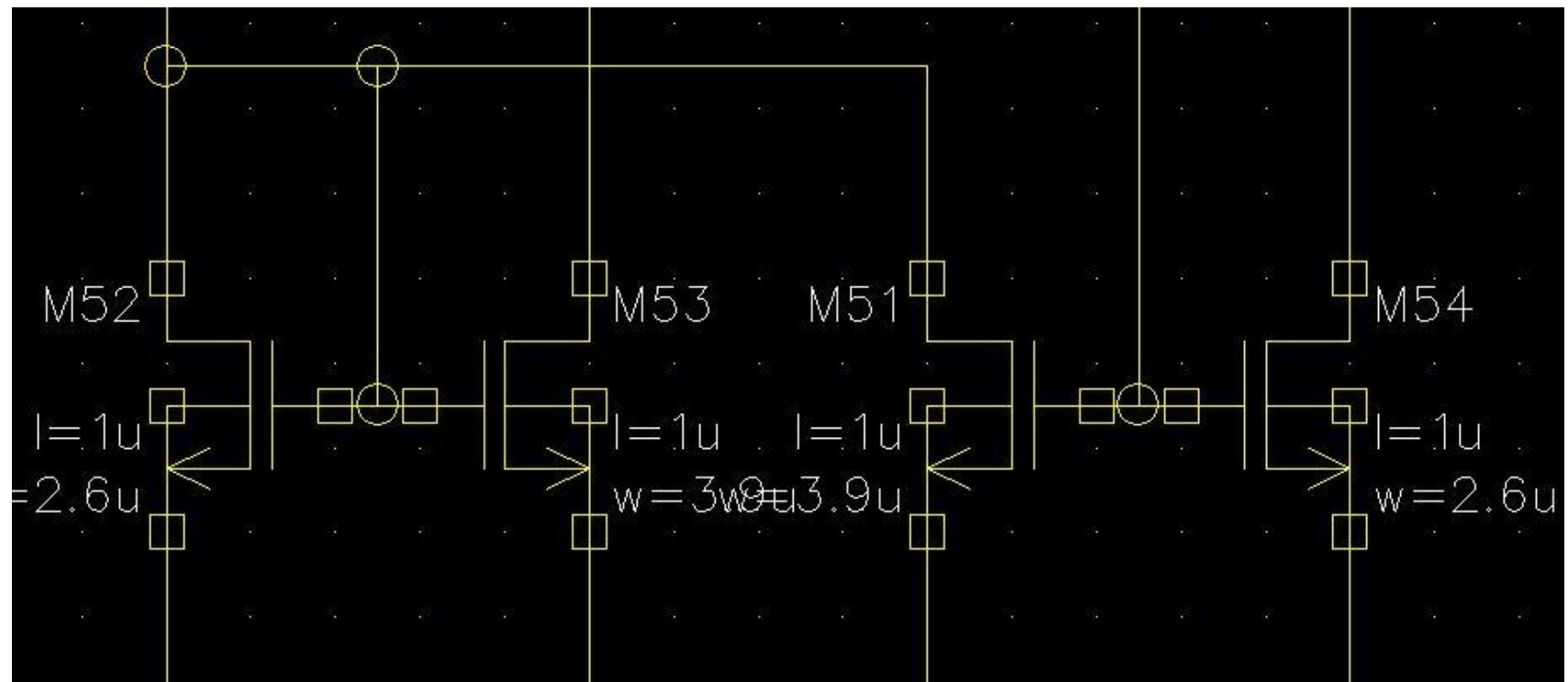


# Comparator-M51~54-Layout

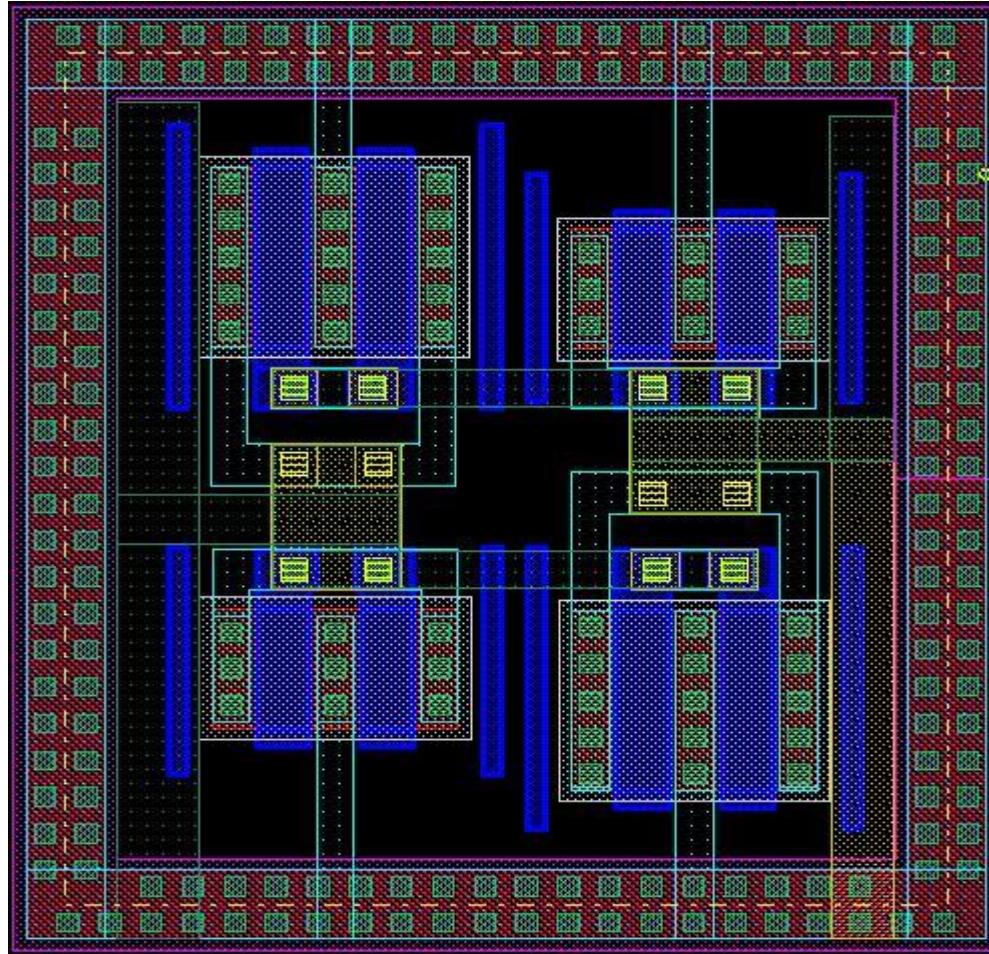


# Comparator-M56-Schematic

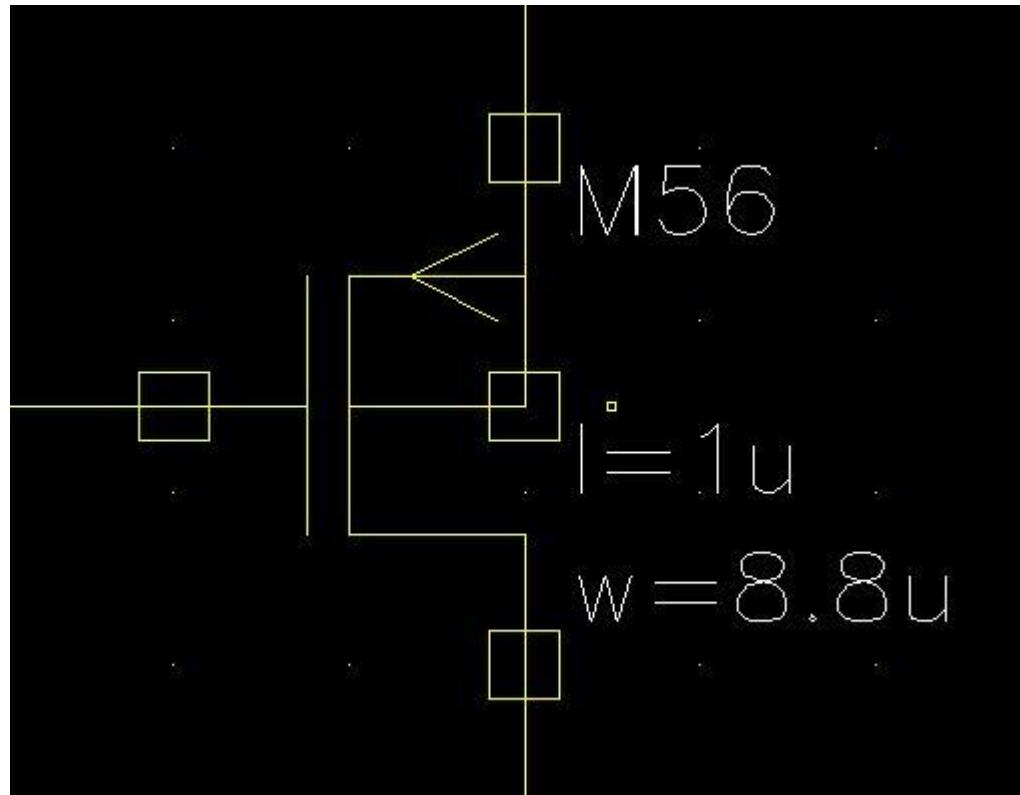


# Comparator-M56-Layout

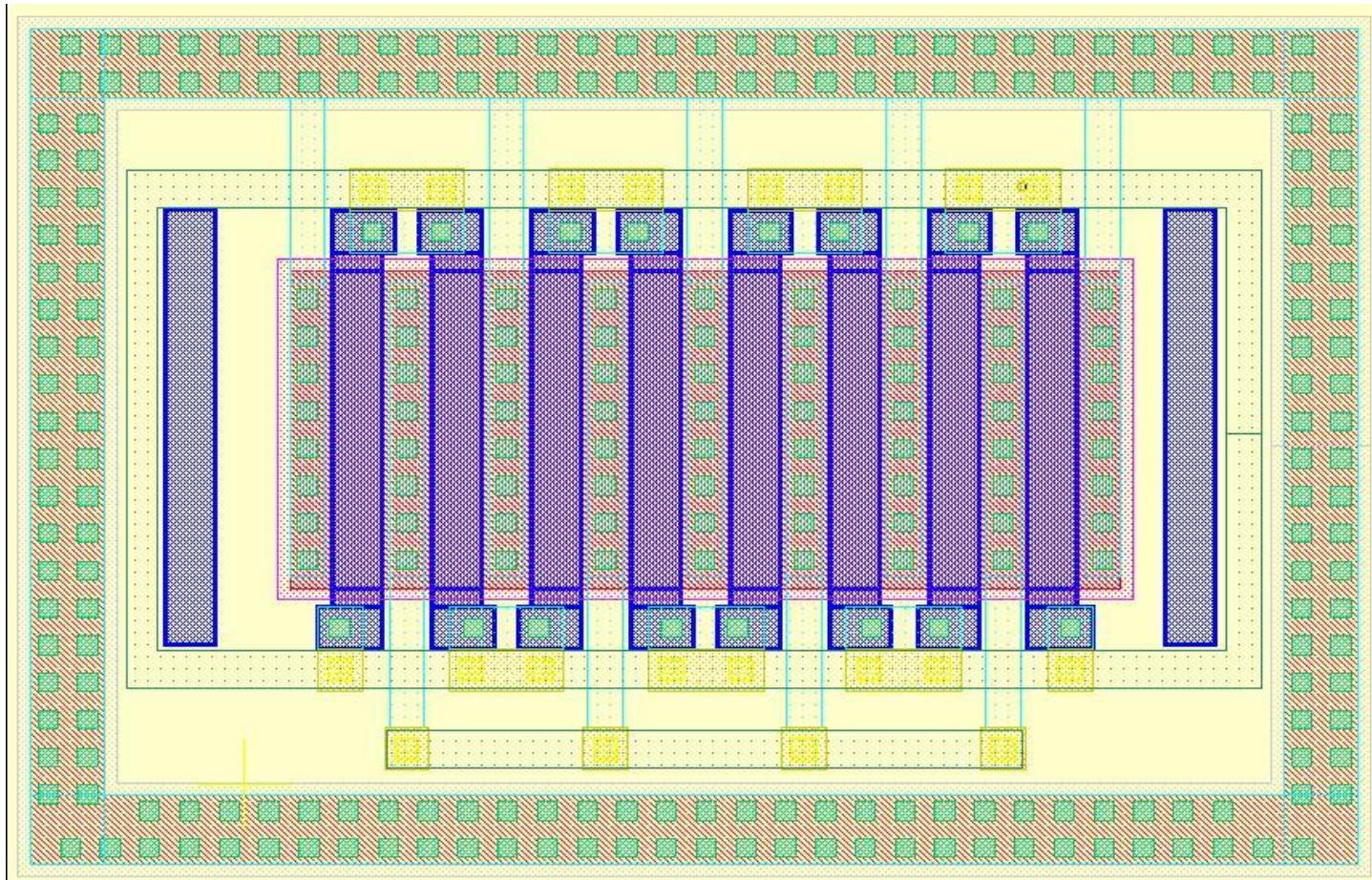


# Compatator-M57-Schematic

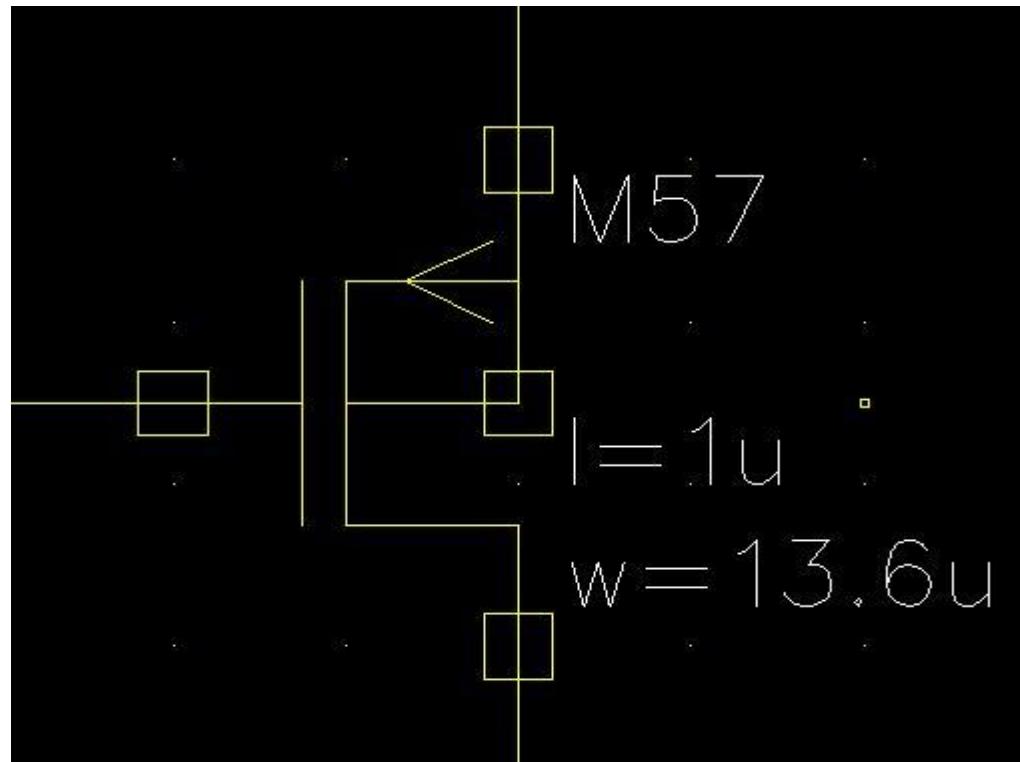


# Compatator-M57-Layout

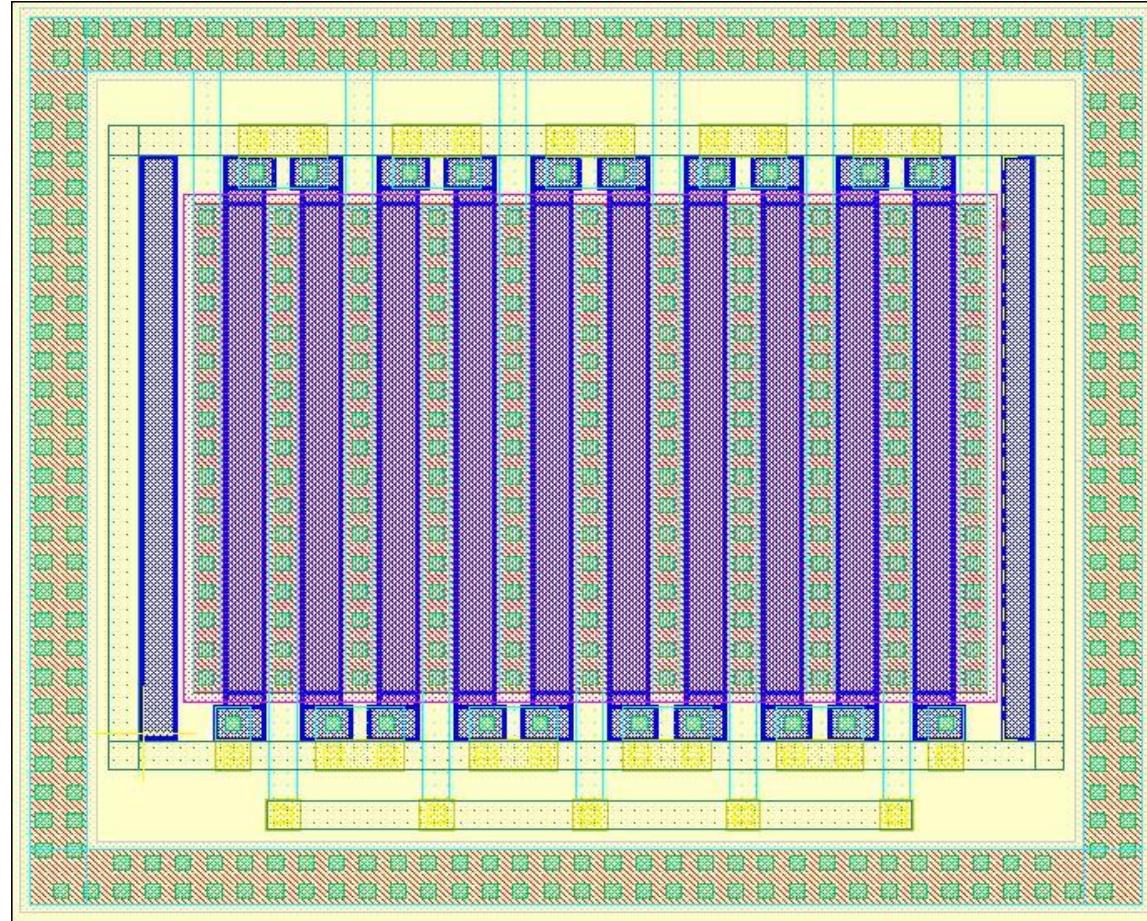


# Comparator-M60-Schematic

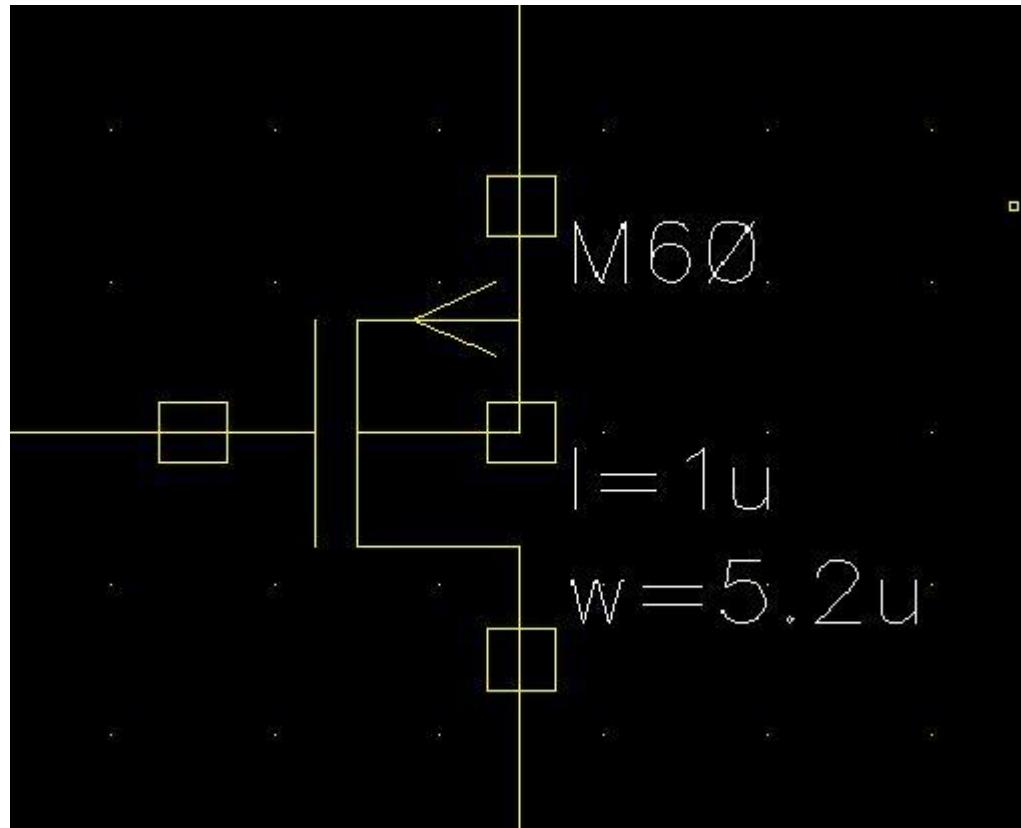


# Comparator-M60-Layout

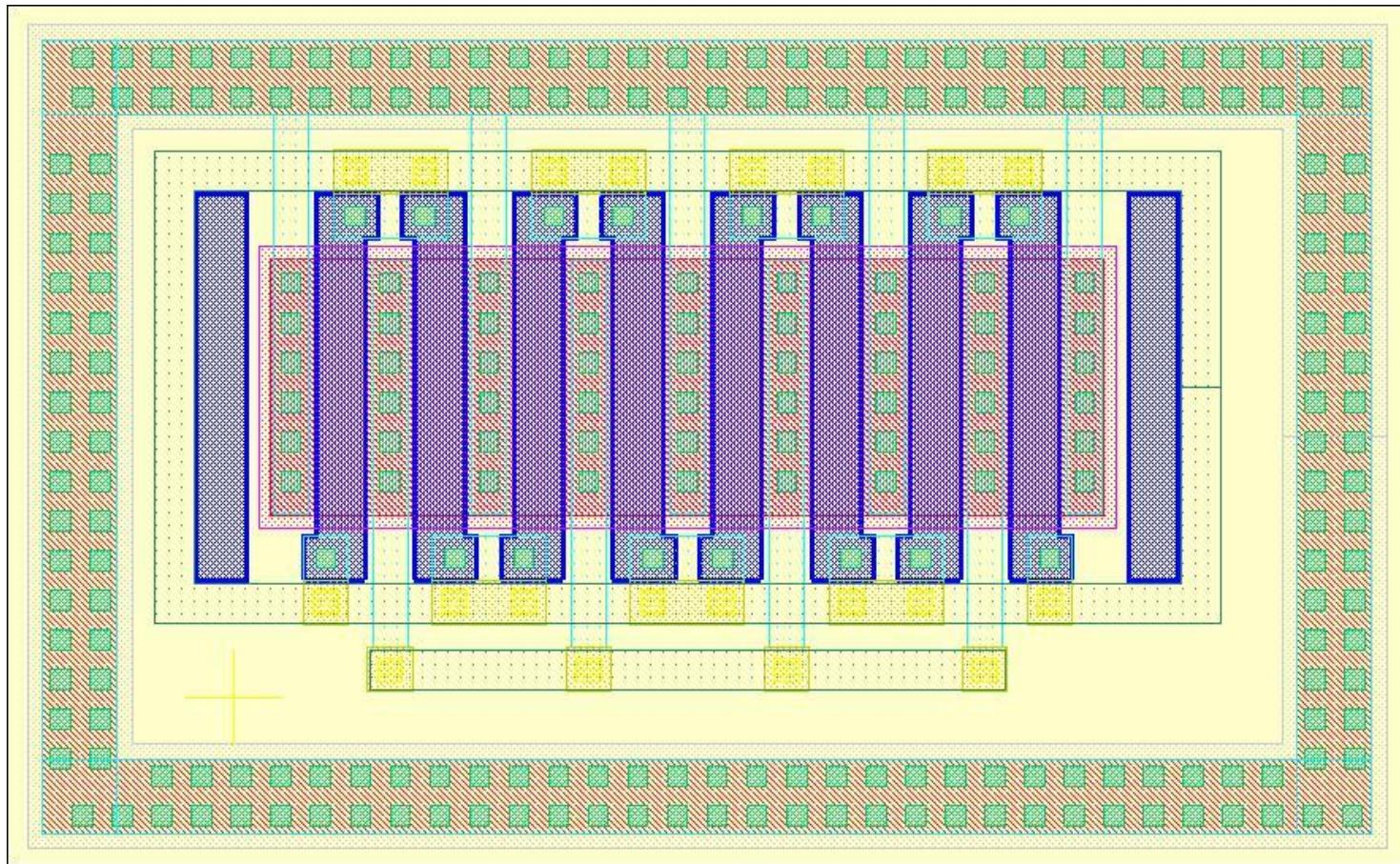


# Comparator-M61~62-Schematic

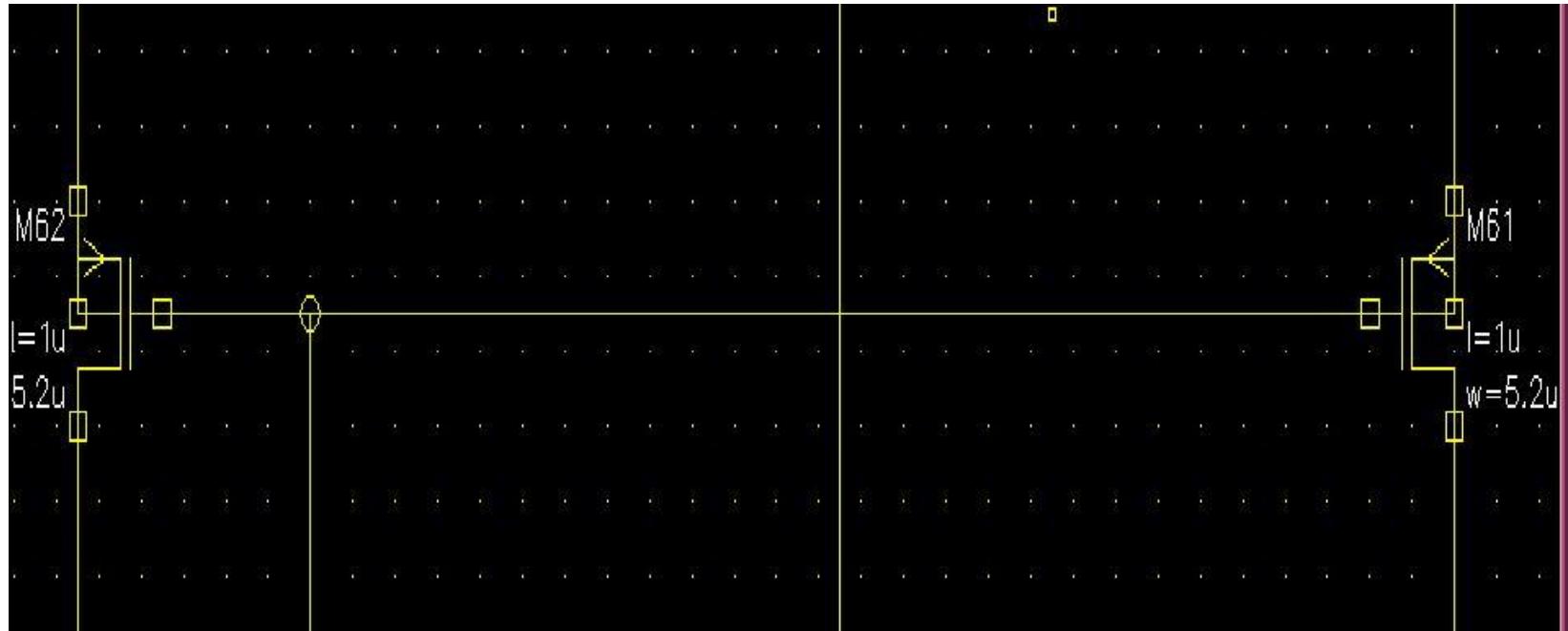


# Comparator-M61~62-Layout

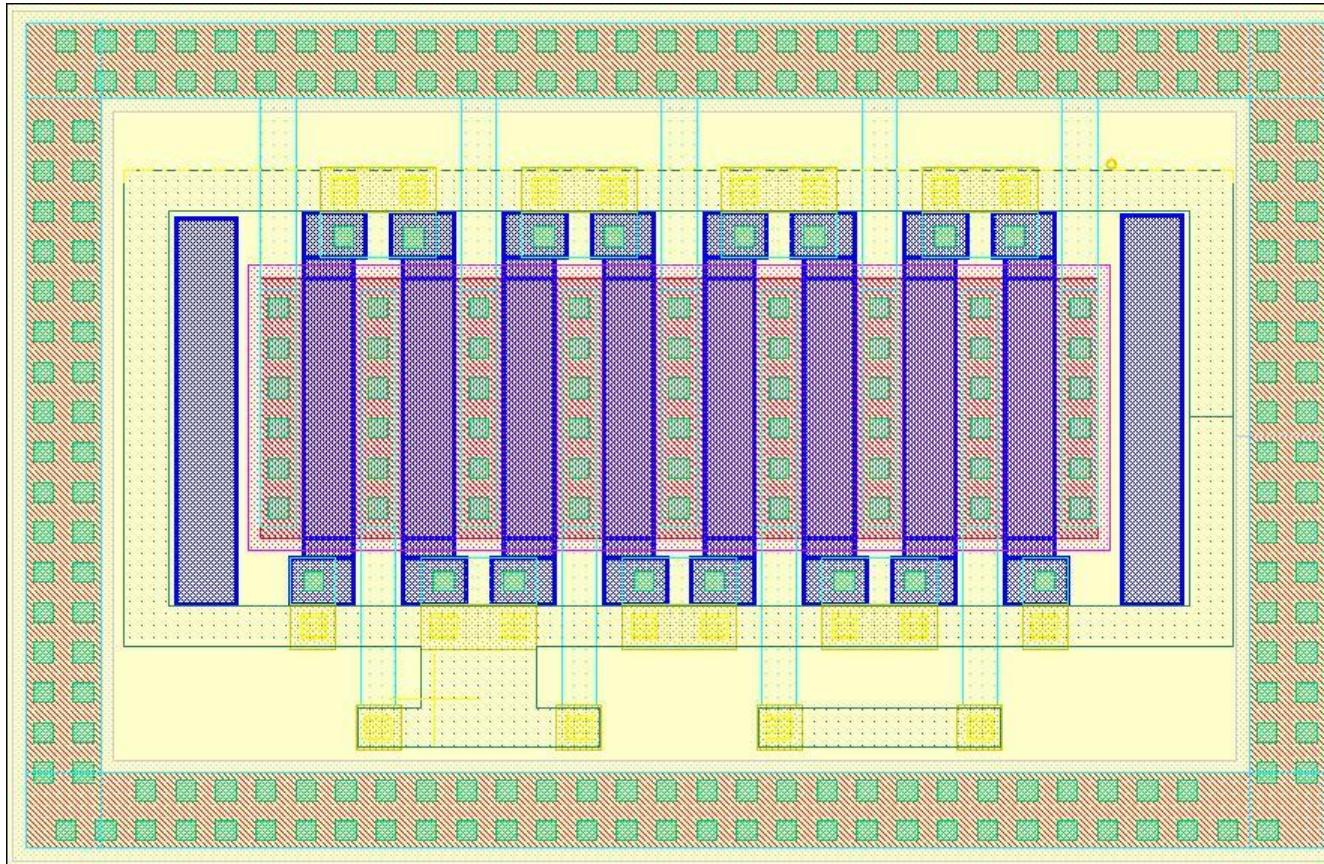


# Comparator-M63~64-Schematic

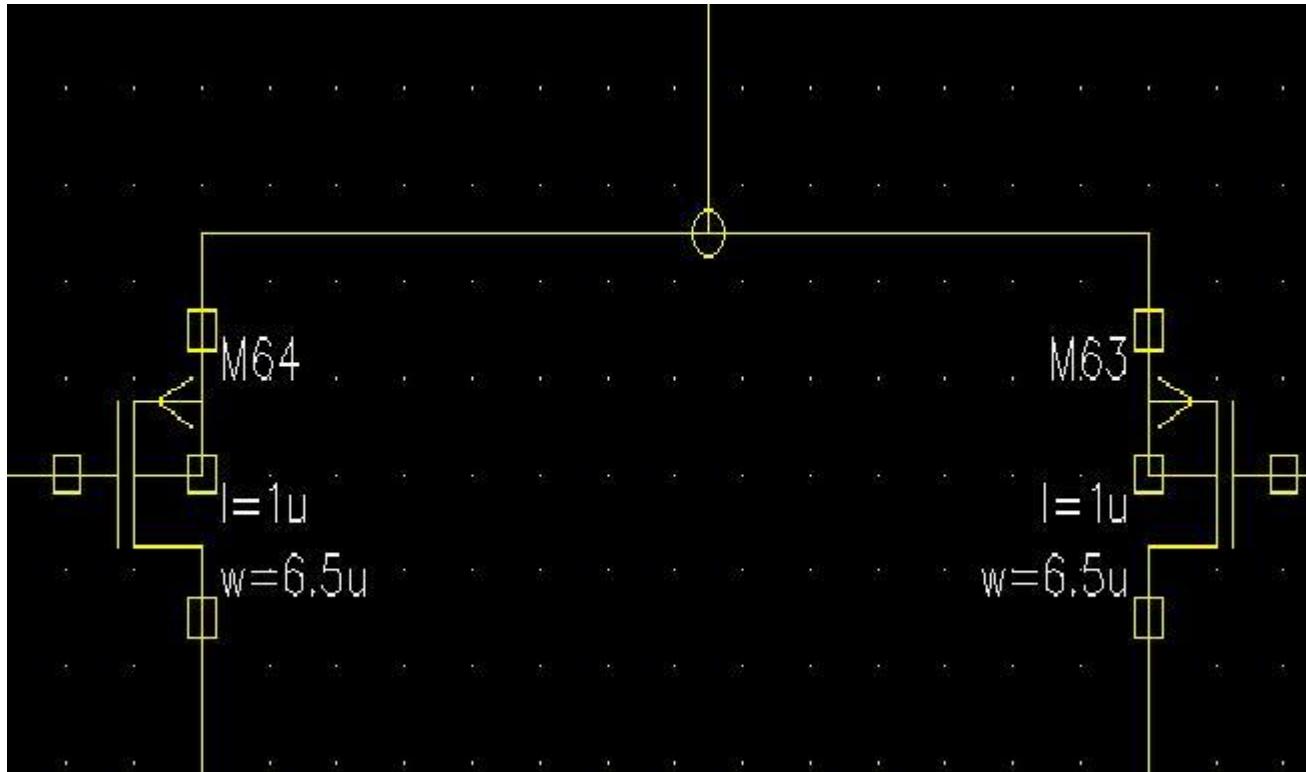


# Comparator-M63~64-Layout

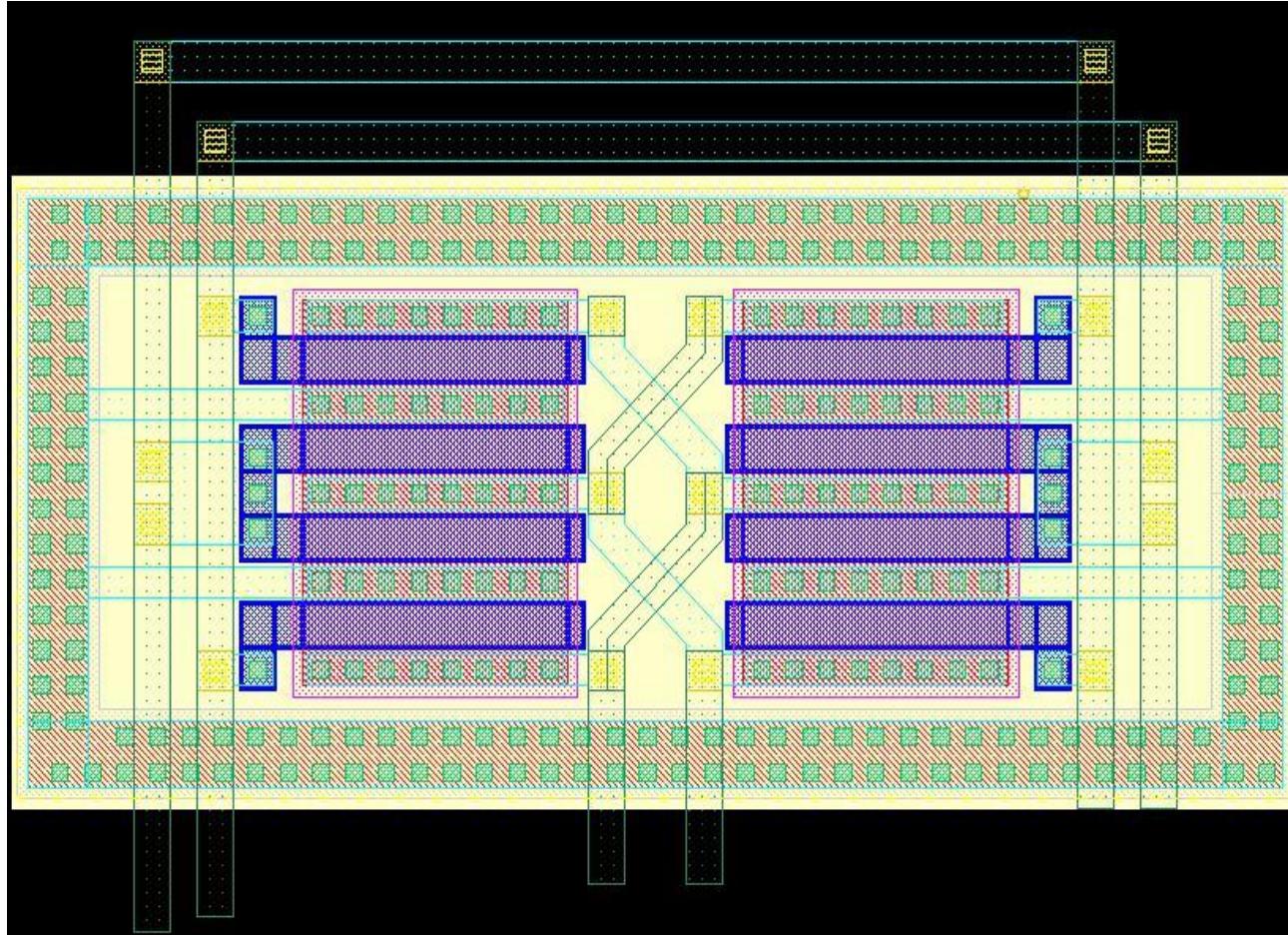


# Comparator-Layout

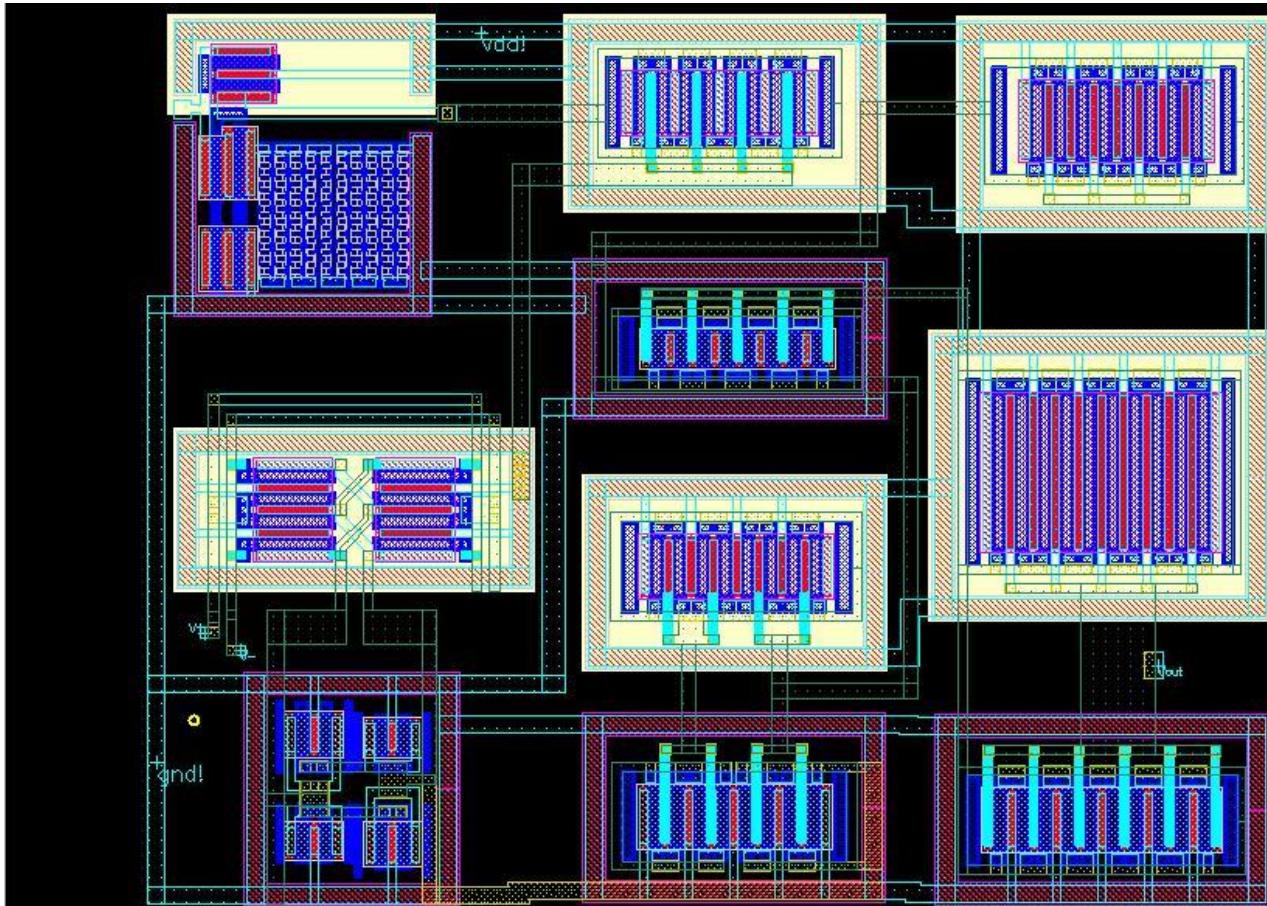

# Comparator-Lvs-OK

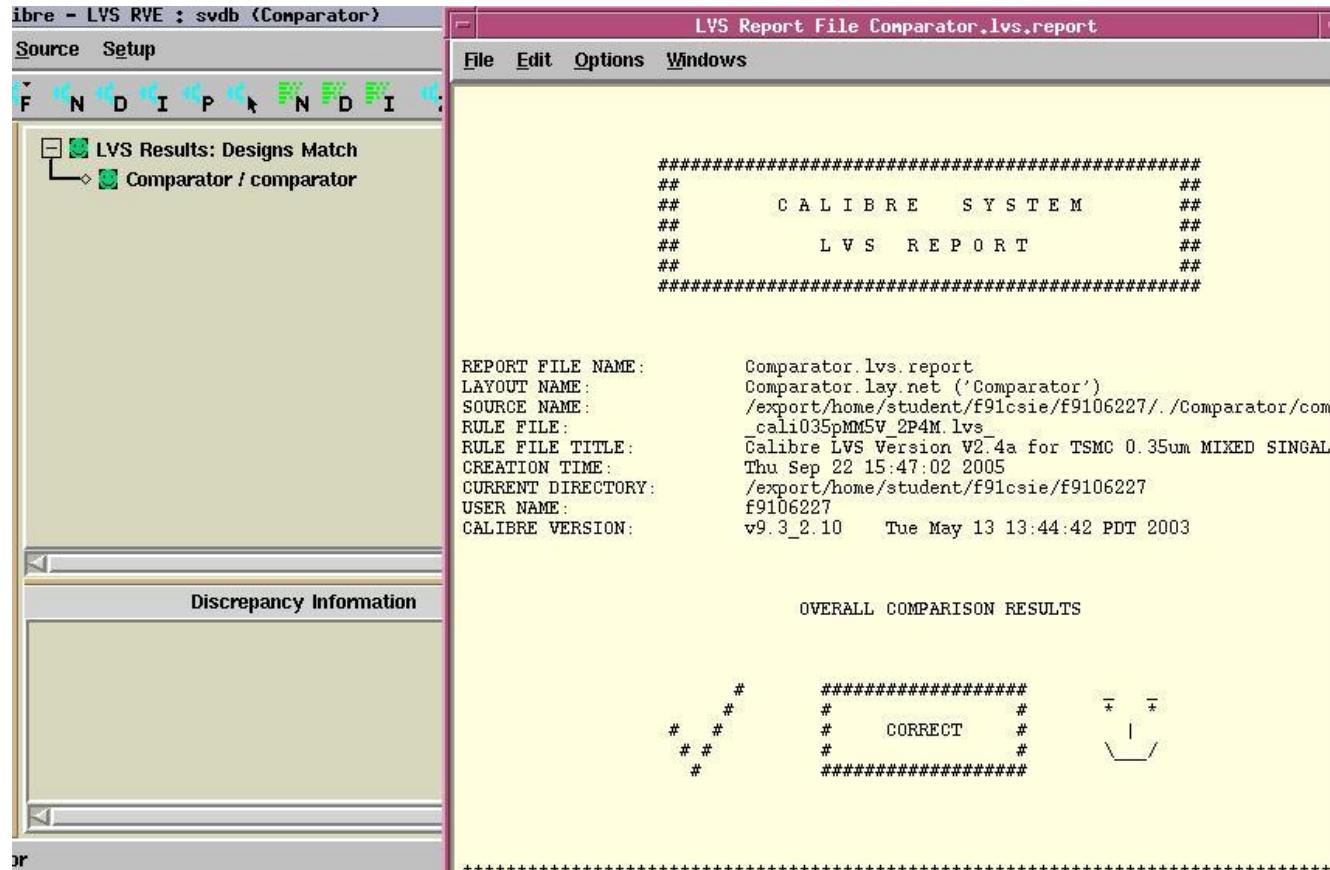

# Comparator-Run PEX

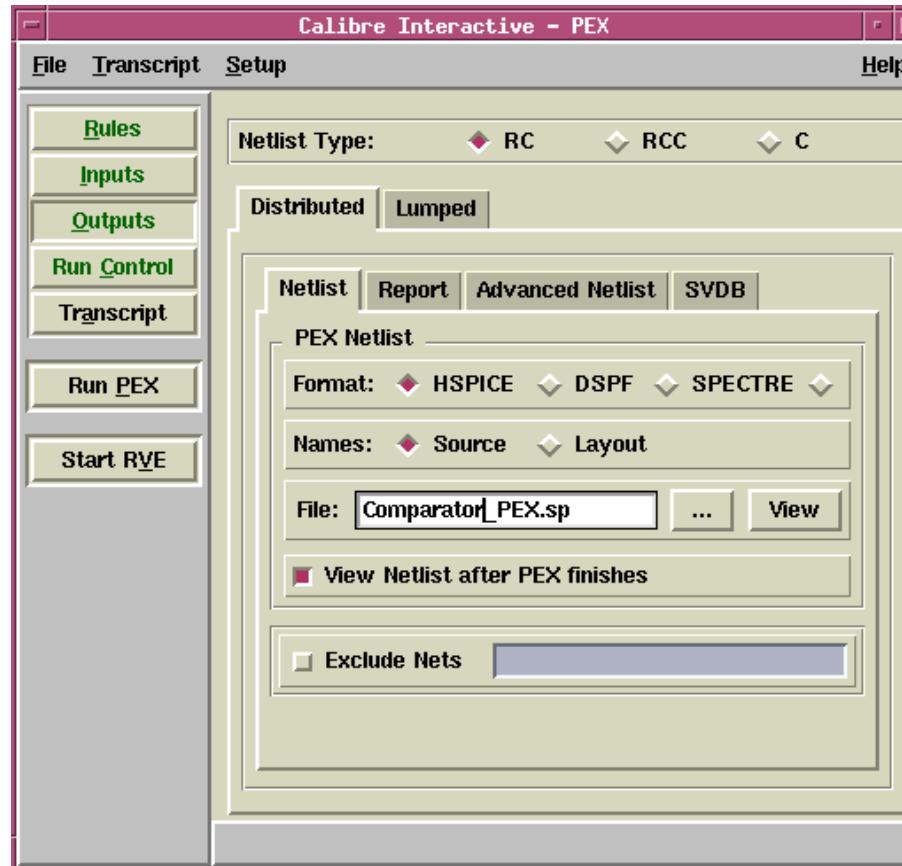


# Comparator-Run PEX-Result


The screenshot shows two windows from the Calibre Interactive - PEX software. The left window is titled "Calibre Interactive - PEX" and contains a "Transcript" tab which is currently selected. The transcript shows an error message: "ERROR: PEX BACKANNOTATION DISTRI". Below this, it lists various parameters and statistics related to the PEX run, such as reading layout netlist, outputting to source GDS, and processing parasitic models. The right window is titled "PEX Netlist File - Comparator\_PEX.sp" and displays the actual netlist code. The code includes header information like file creation date and version, and defines components like comparators with their connections to V+, VOUT, GND, and VDD. It also specifies net widths (W) and lengths (L) for various metal layers (MM48, MM46, MM45, MM51, MM53, MM50, MM44) across different nodes.

```
* File: Comparator_PEX.sp
* Created: Wed Oct 12 19:08:05 2005
* Program "Calibre xRC"
* Version "v9.3_2.10"
*
.included Comparator_PEX.sp.pex
.subckt comparator V+ V- VOUT GND! VDD!
*
* gnd! gnd!
* vdd! vdd!
* Vout Vout
* V- V-
* V+ V+
-----
mMM48 N_net32_MM48_d N_net32_MM48_g N_net24_MM47_d N_GND!_MM45_b NCH L=1e-06
+ W=5.2e-06
mMM46 N_net30_MM46_d N_net32_MM46_g net22_N_GND!_MM45_b NCH L=1e-06 W=5.2e-06
mMM47 N_net24_MM47_d N_net24_MM47_g N_GND!_MM47_s N_GND!_MM45_b NCH L=1e-06
+ W=5.2e-06
mMM45 net22_N_net24_MM45_g N_net5_MM45_s N_GND!_MM45_b NCH L=1e-06 W=6e-06
mMM51_1 N_net50_MM51_1_d N_net38_MM51_1_g N_GND!_MM51_2_s N_GND!_MM53_2_b
+ NCH L=1e-06 W=3.9e-06
mMM51_2 N_net52_MM51_2_d N_net38_MM51_2_g N_GND!_MM51_2_s N_GND!_MM53_2_b
+ NCH L=1e-06 W=3.9e-06
mMM53_1 N_net38_MM53_1_d N_net52_MM53_1_g N_GND!_MM53_2_s N_GND!_MM53_2_b
+ NCH L=1e-06 W=3.9e-06
mMM53_2 N_net38_MM53_2_d N_net52_MM53_2_g N_GND!_MM53_2_s N_GND!_MM53_2_b
+ NCH L=1e-06 W=3.9e-06
mMM50_1 N_net50_MM50_2_d N_net52_MM50_1_g N_GND!_MM50_1_s N_GND!_MM53_2_b
+ NCH L=1e-06 W=5.2e-06
mMM44_1 N_net10_MM44_1_d N_net14_MM44_1_g N_GND!_MM44_2_s N_GND!_MM53_2_b
+ NCH L=1e-06 W=2.6e-06
mMM50_2 N_net50_MM50_2_d N_net52_MM50_2_g N_GND!_MM50_3_s N_GND!_MM53_2_b
+ NCH L=1e-06 W=5.2e-06
mMM44_2 N_net10_MM44_3_d N_net14_MM44_2_g N_GND!_MM44_2_s N_GND!_MM53_2_b
+ NCH L=1e-06 W=2.6e-06
mMM50_3 N_net50_MM50_4_d N_net52_MM50_3_g N_GND!_MM50_3_s N_GND!_MM53_2_b
+ NCH L=1e-06 W=5.2e-06
mMM44_3 N_net10_MM44_3_d N_net14_MM44_3_g N_GND!_MM44_4_s N_GND!_MM53_2_b
+ NCH L=1e-06 W=2.6e-06
mMM50_4 N_net50_MM50_4_d N_net52_MM50_4_g N_GND!_MM55_1_s N_GND!_MM53_2_b
```


# VRG-M25-Schematic

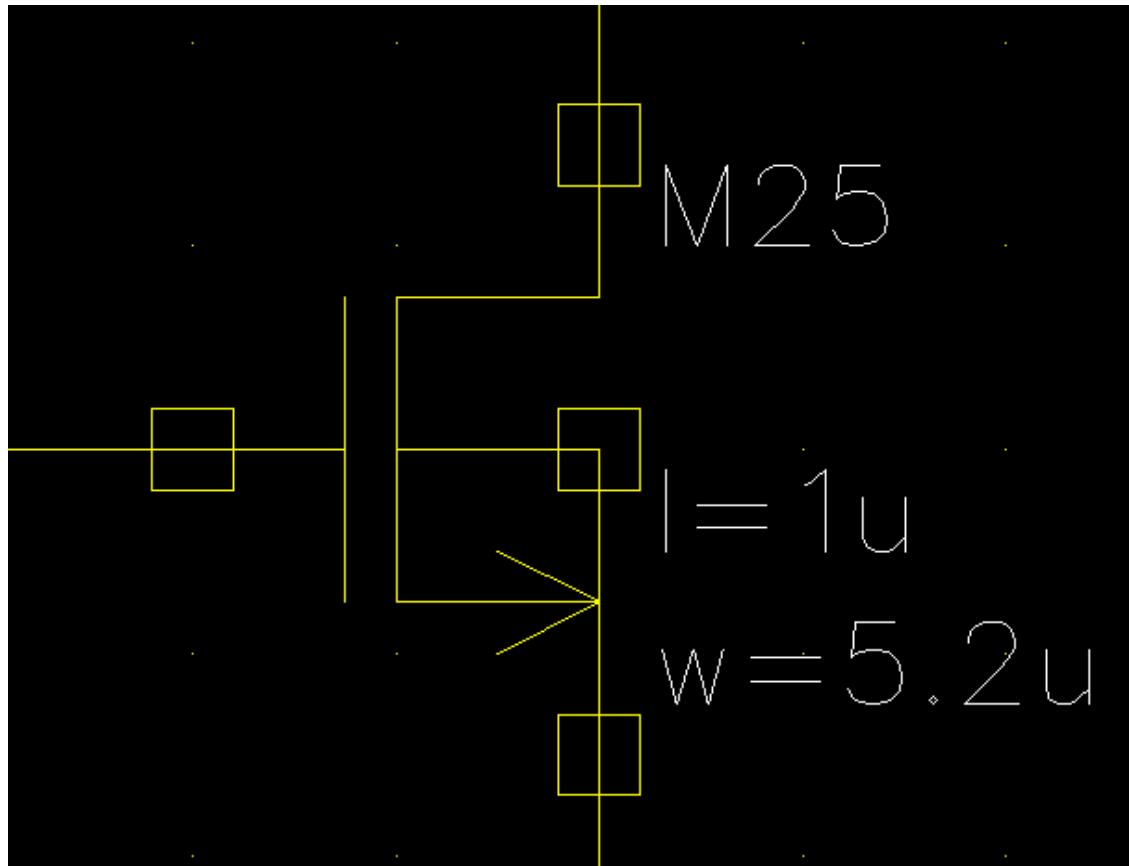


# VRG-M25-Layout

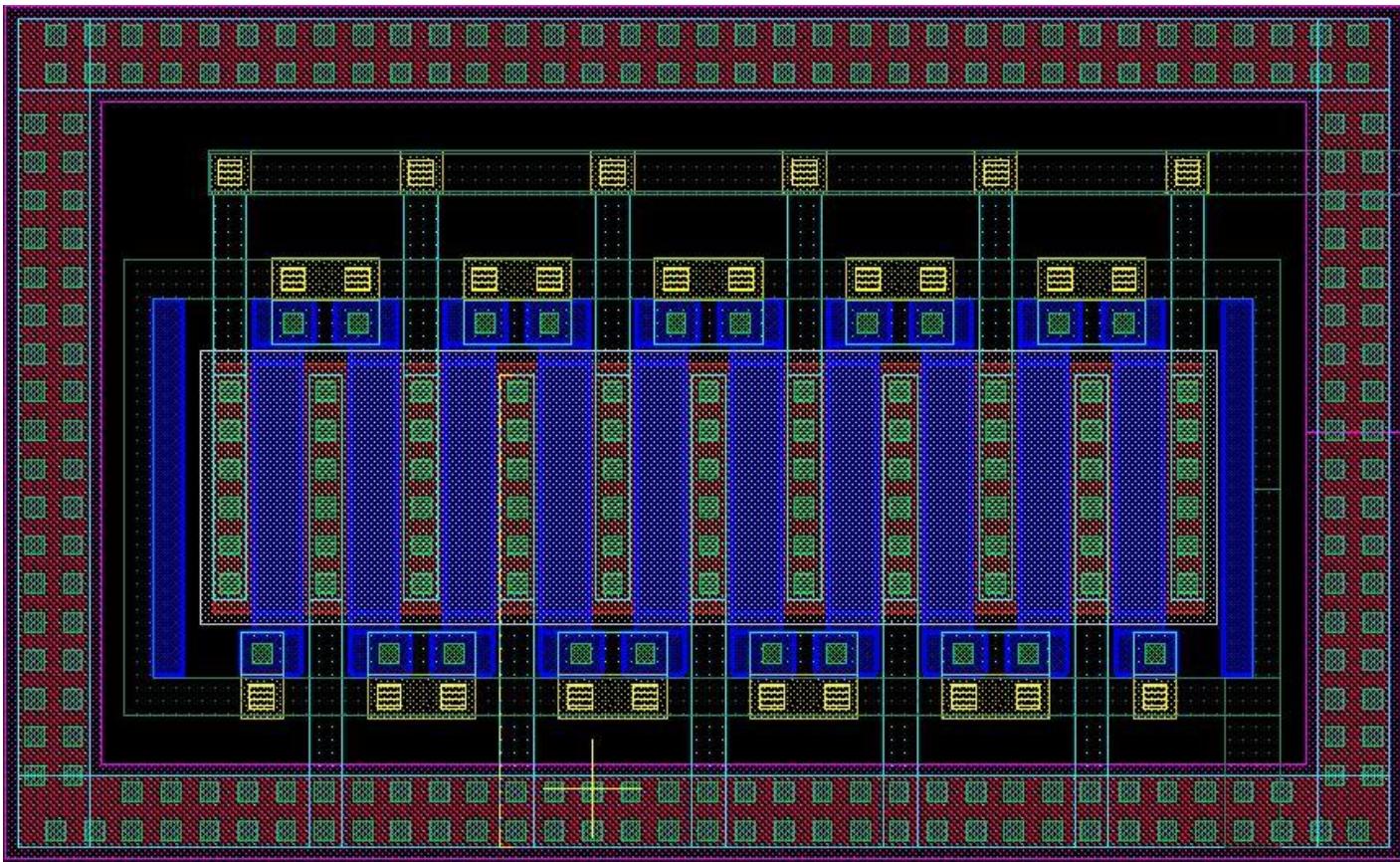


# VRG-M26-Schematic

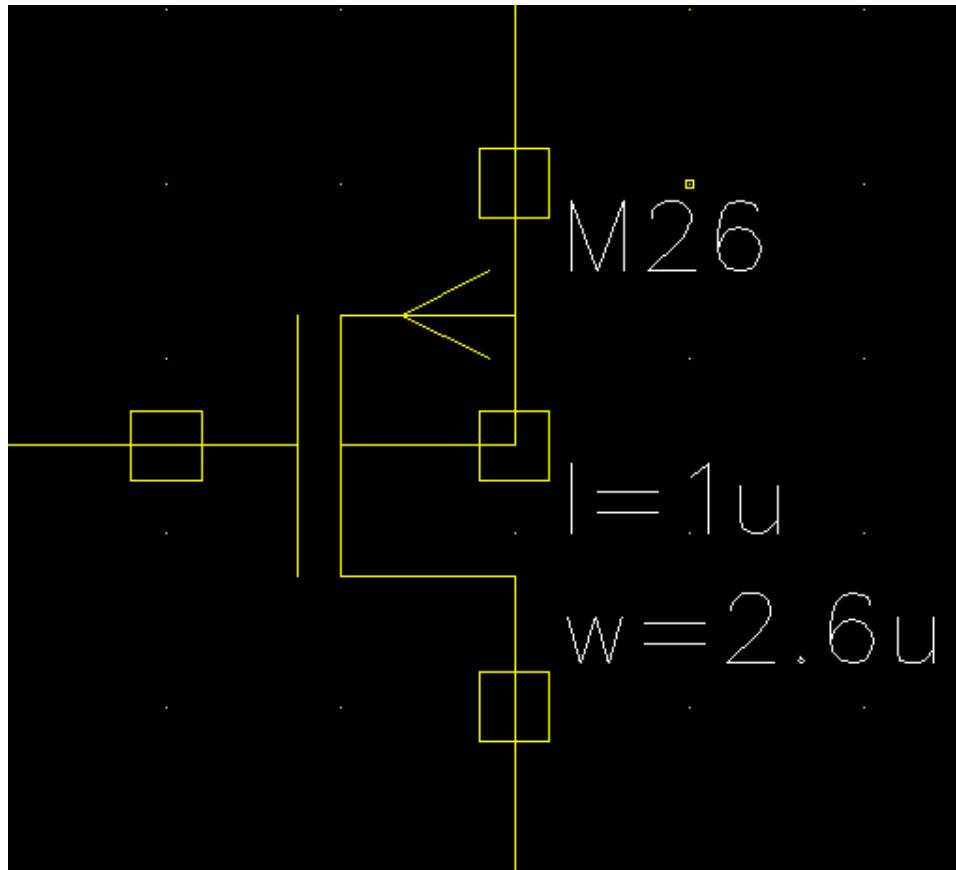


# VRG-M26-Layout

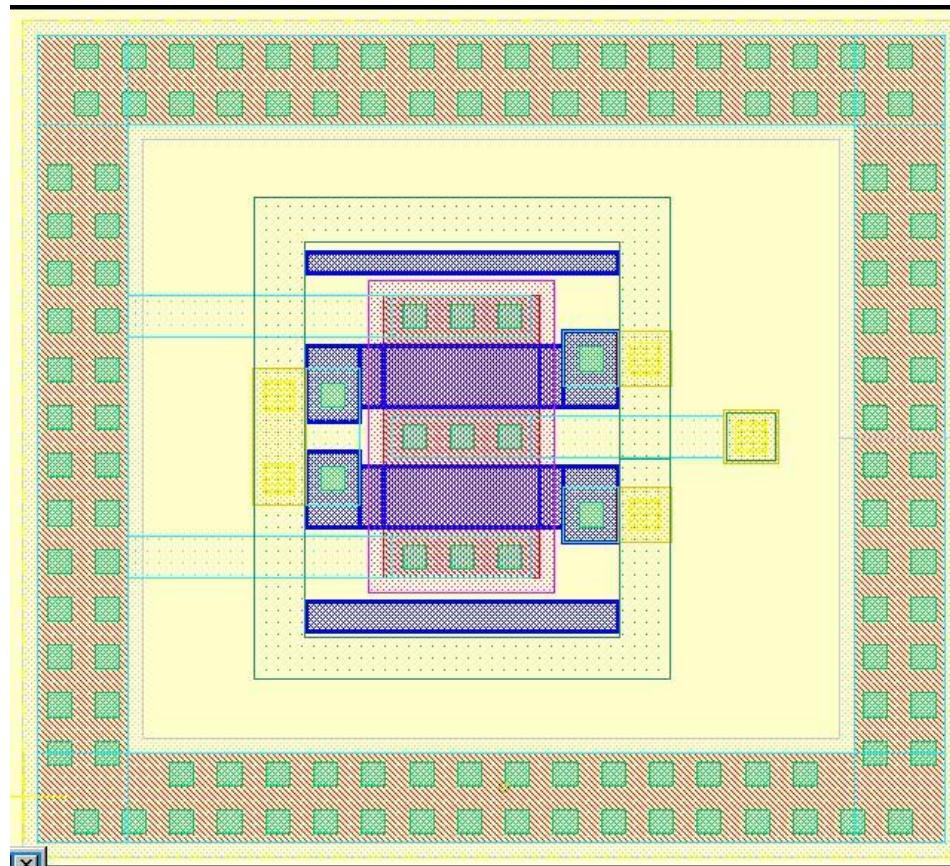


# VRG-M27-Schematic

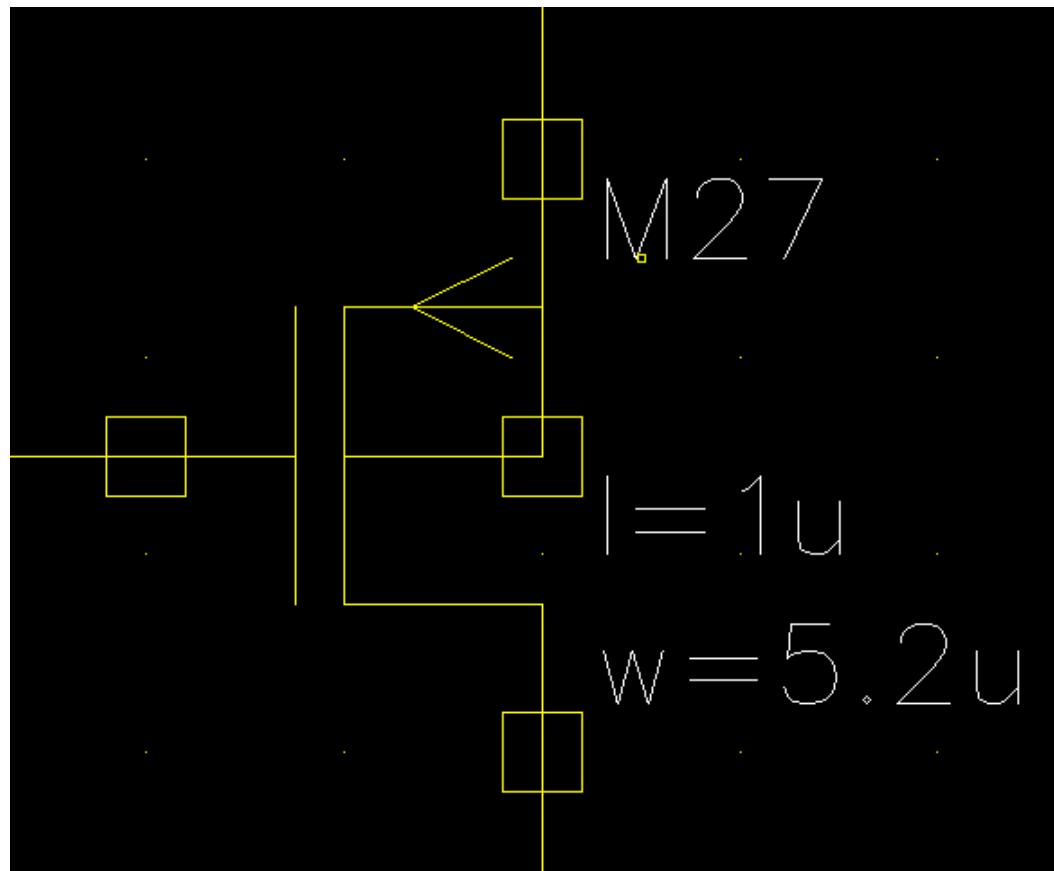


# VRG-M27-Layout

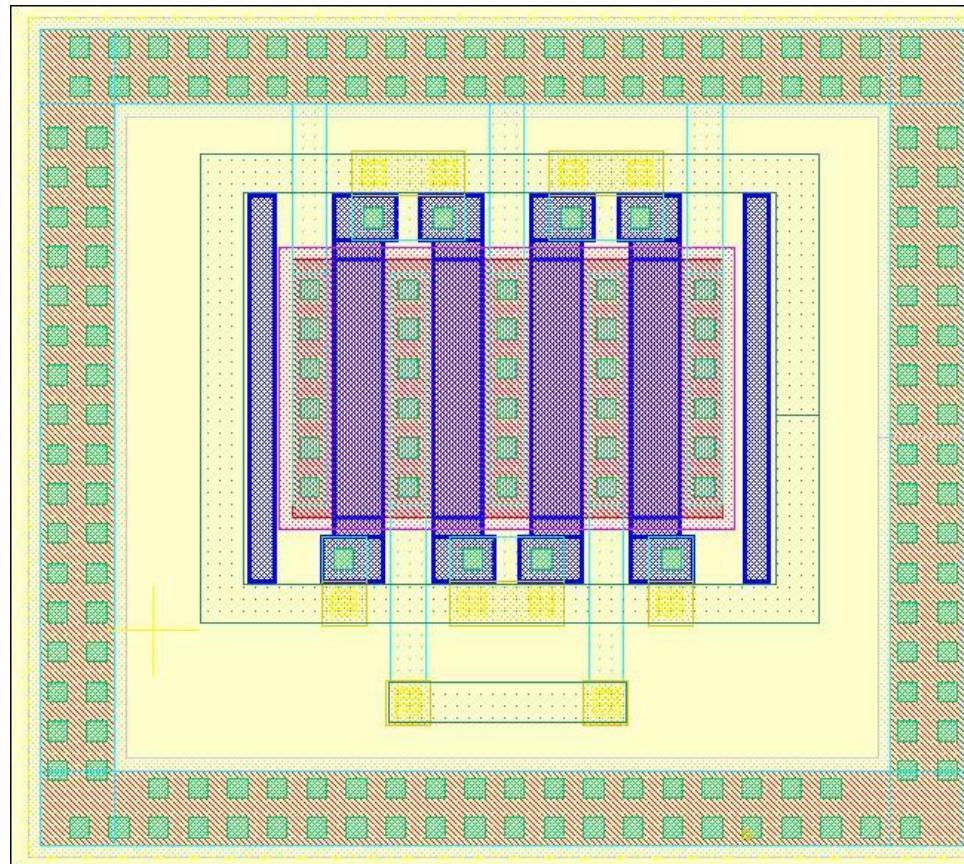


# VRG-M28-Schematic

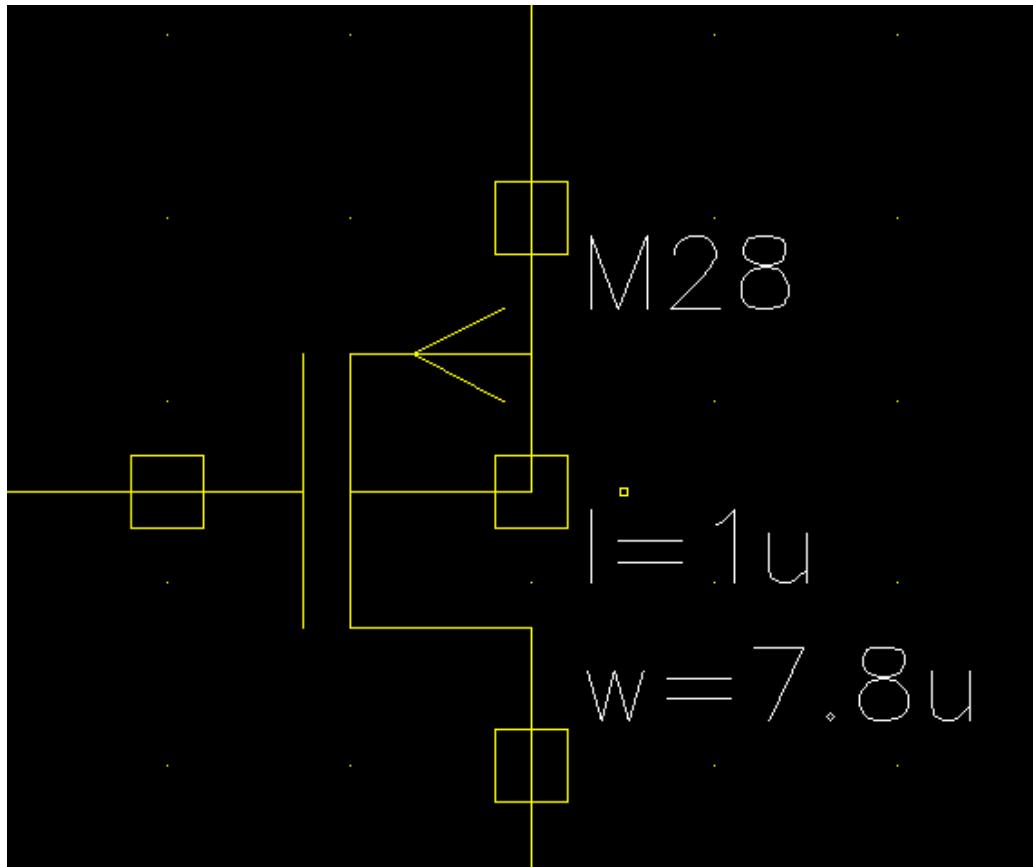


# VRG-M28-Layout

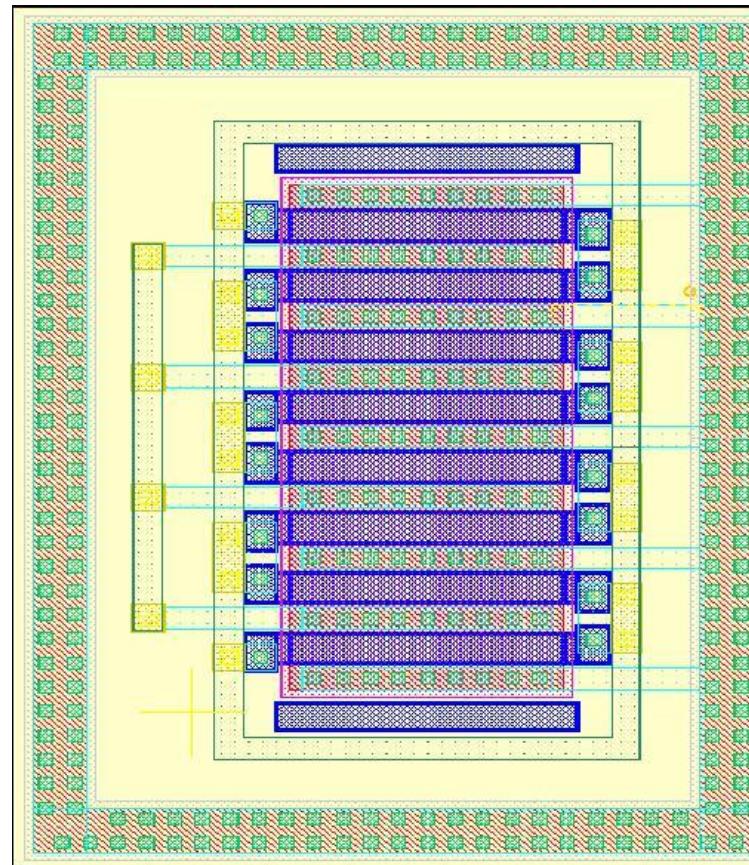


# VRG-M29-Schematic

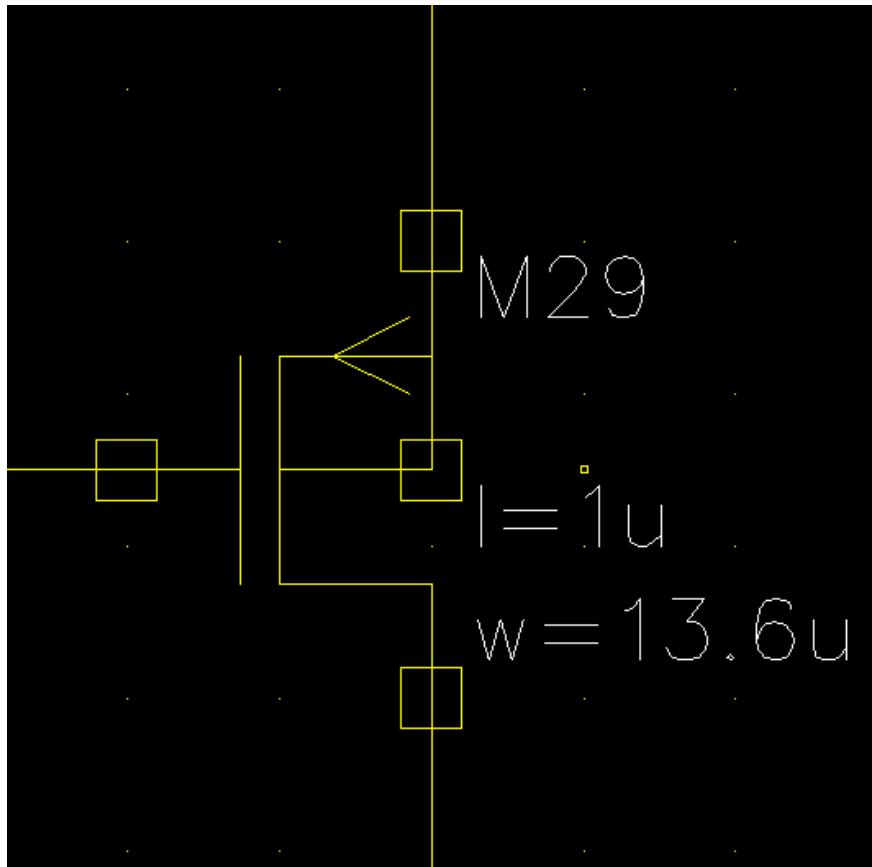


# VRG-M29-Layout

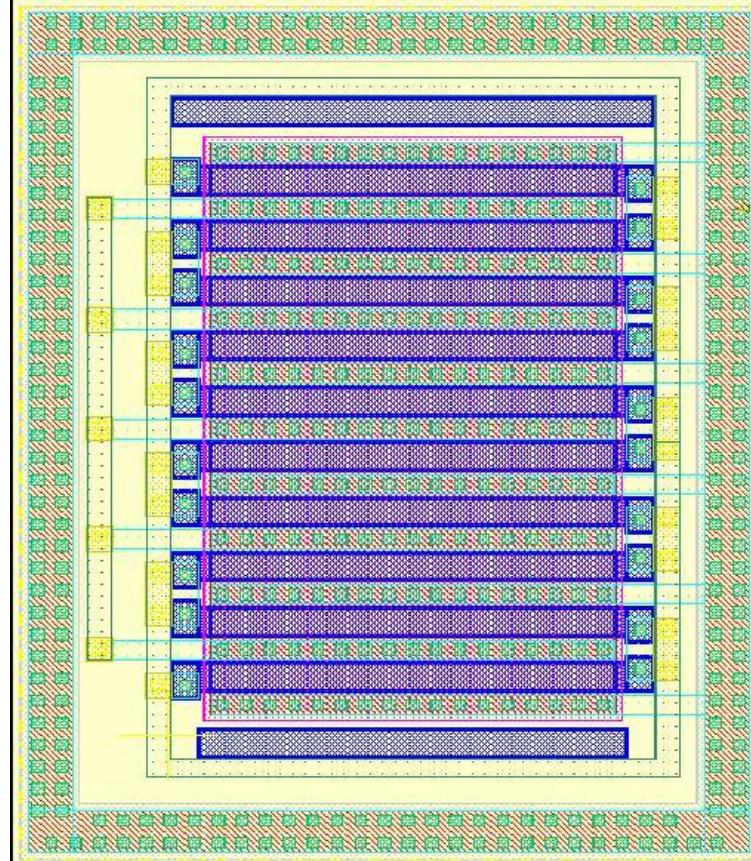


# VRG-M30-Schematic

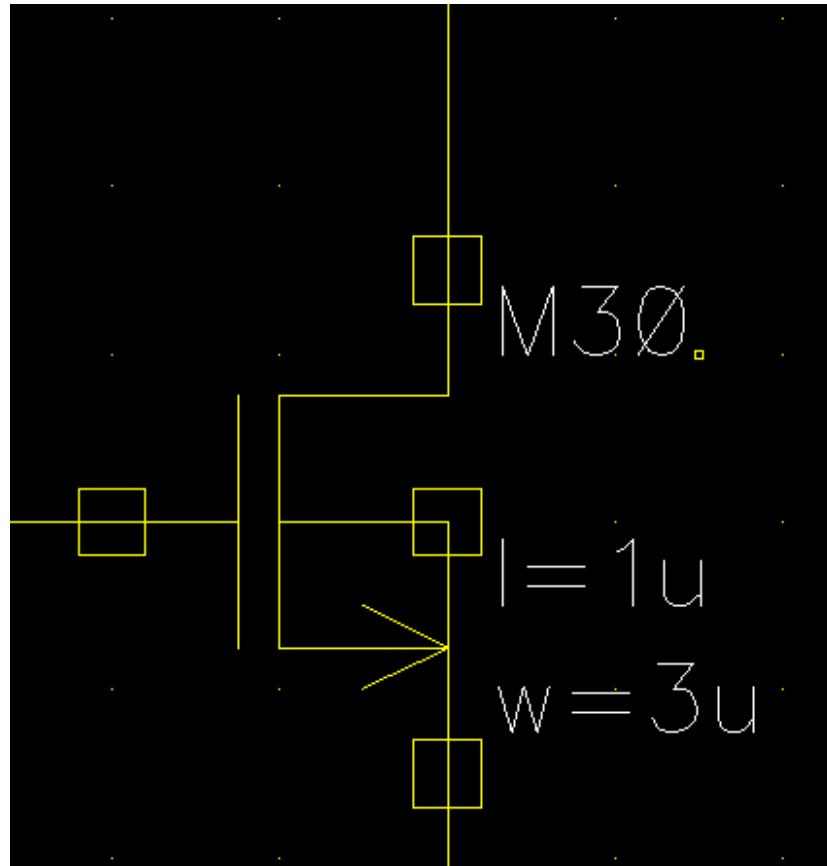


# VRG-M30-Layout

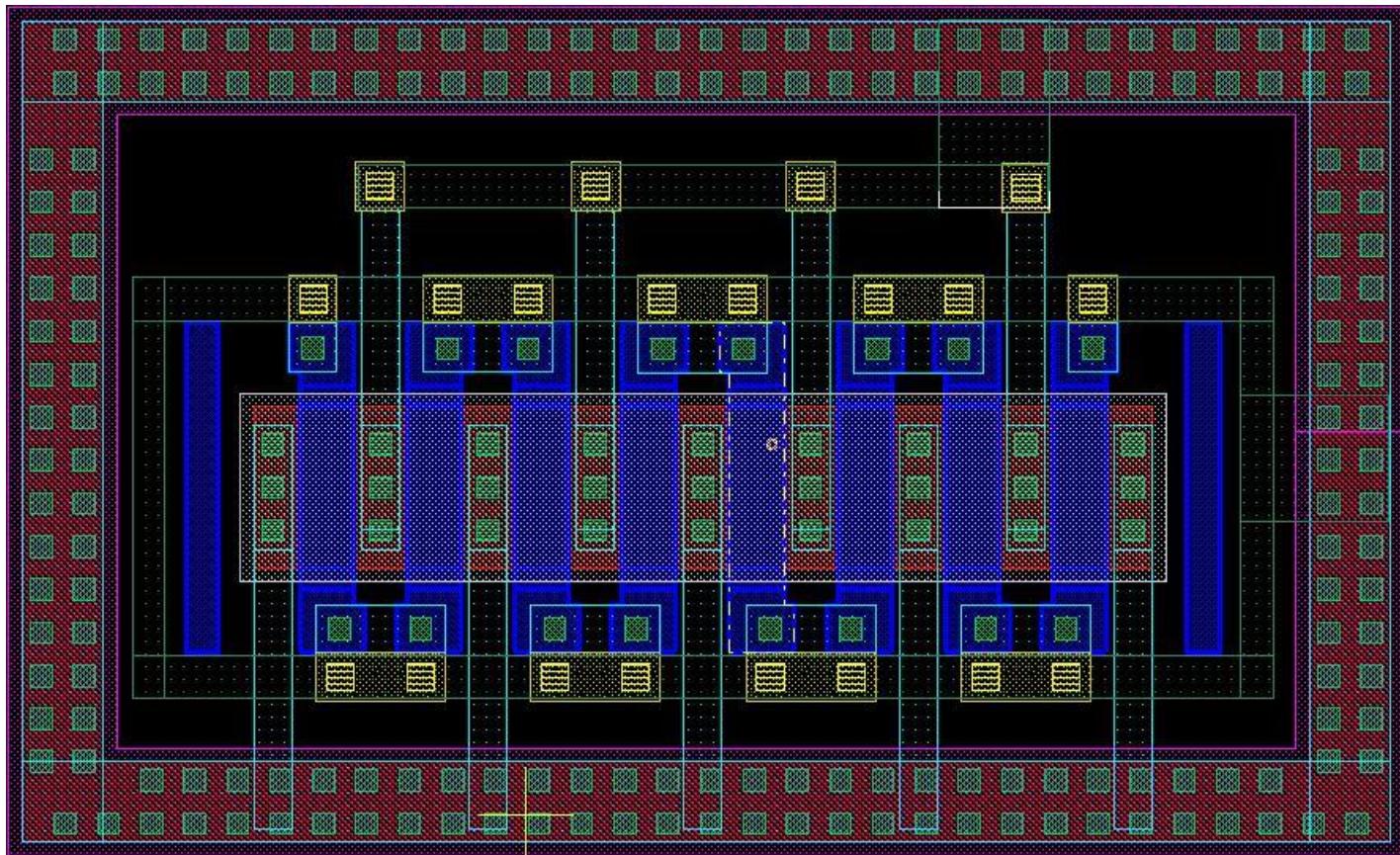


# VRG-M31-Schematic

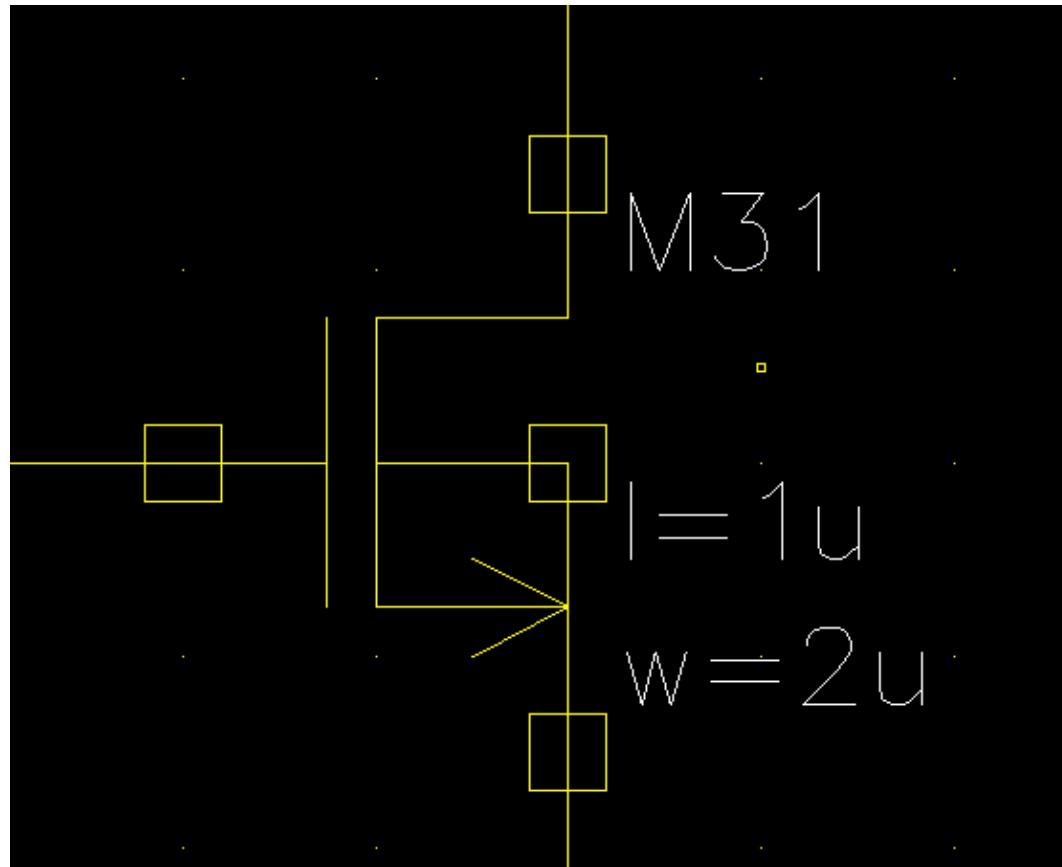


# VRG-M31-Layout

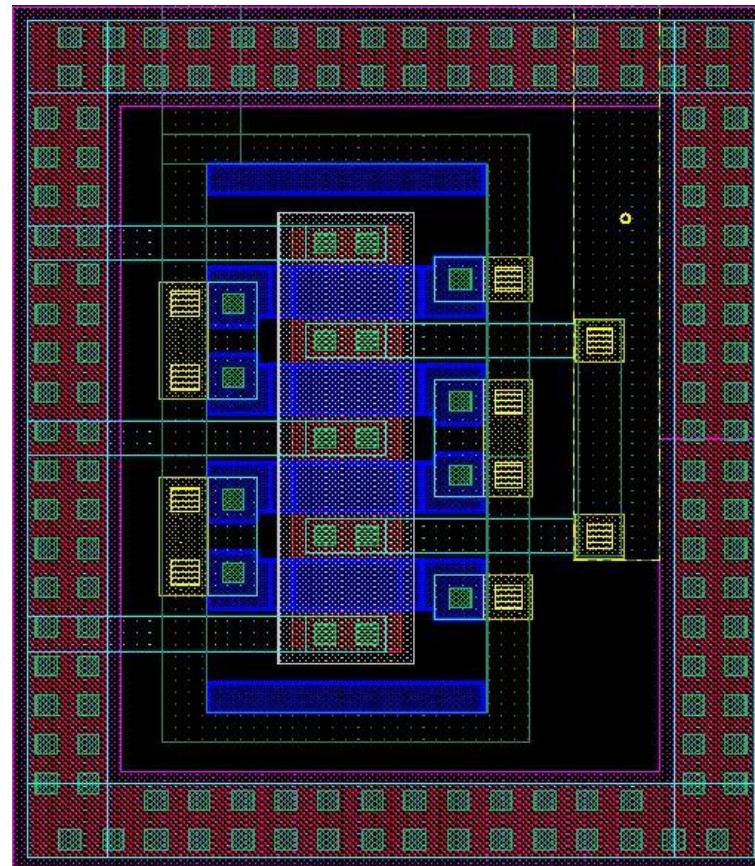


# VRG-M32-Schematic

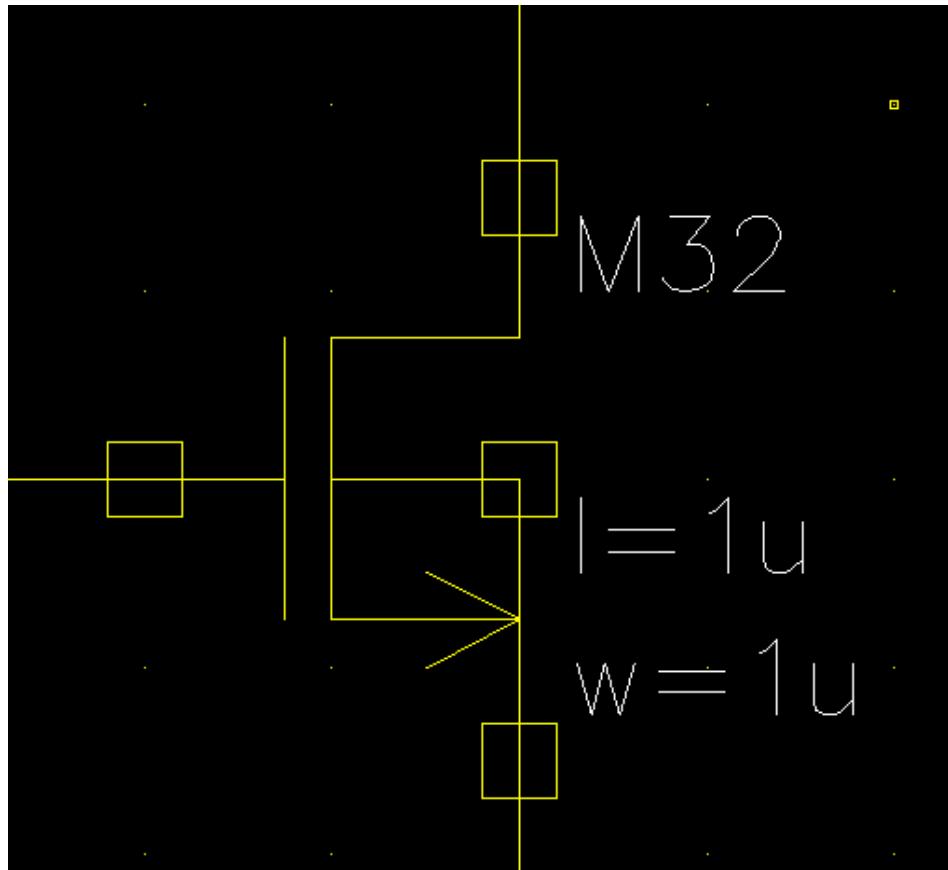


# VRG-M32-Layout

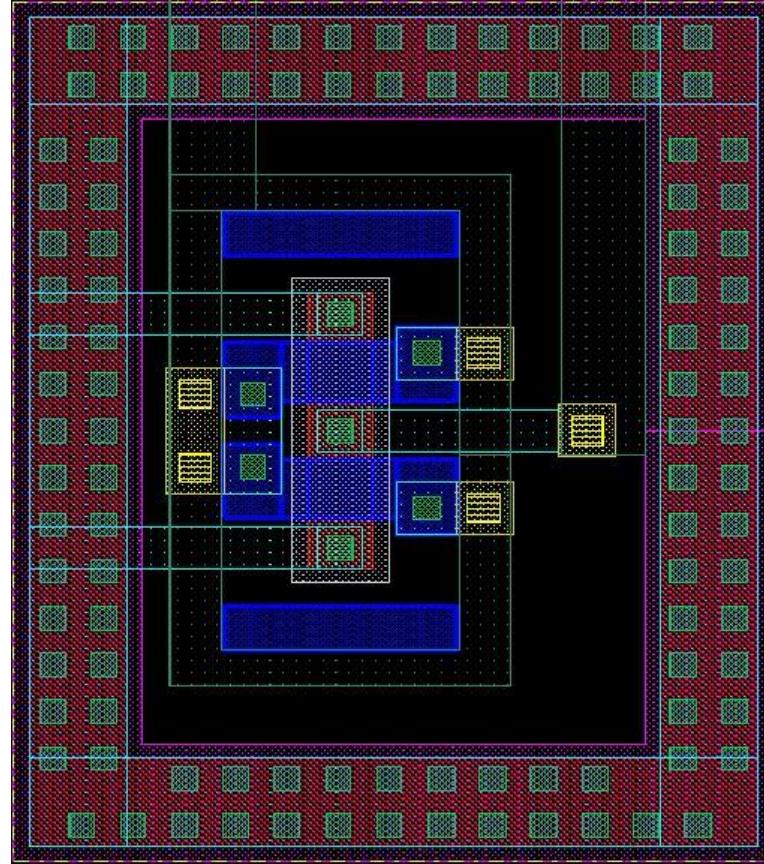


# VRG-Ccl-Schematic

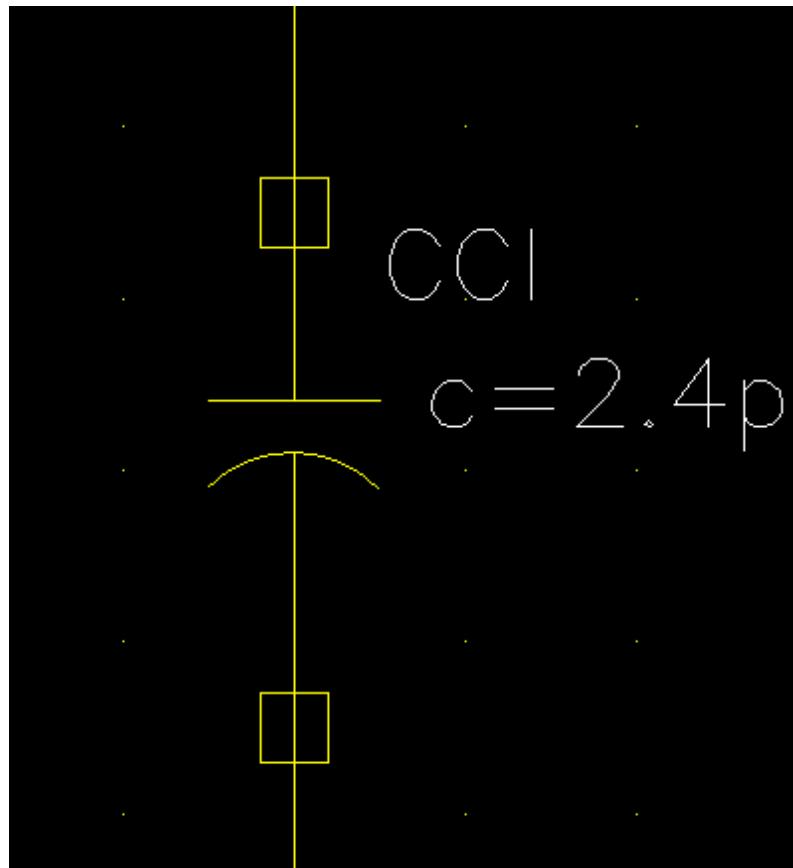

# VRG-Ccl-Layout

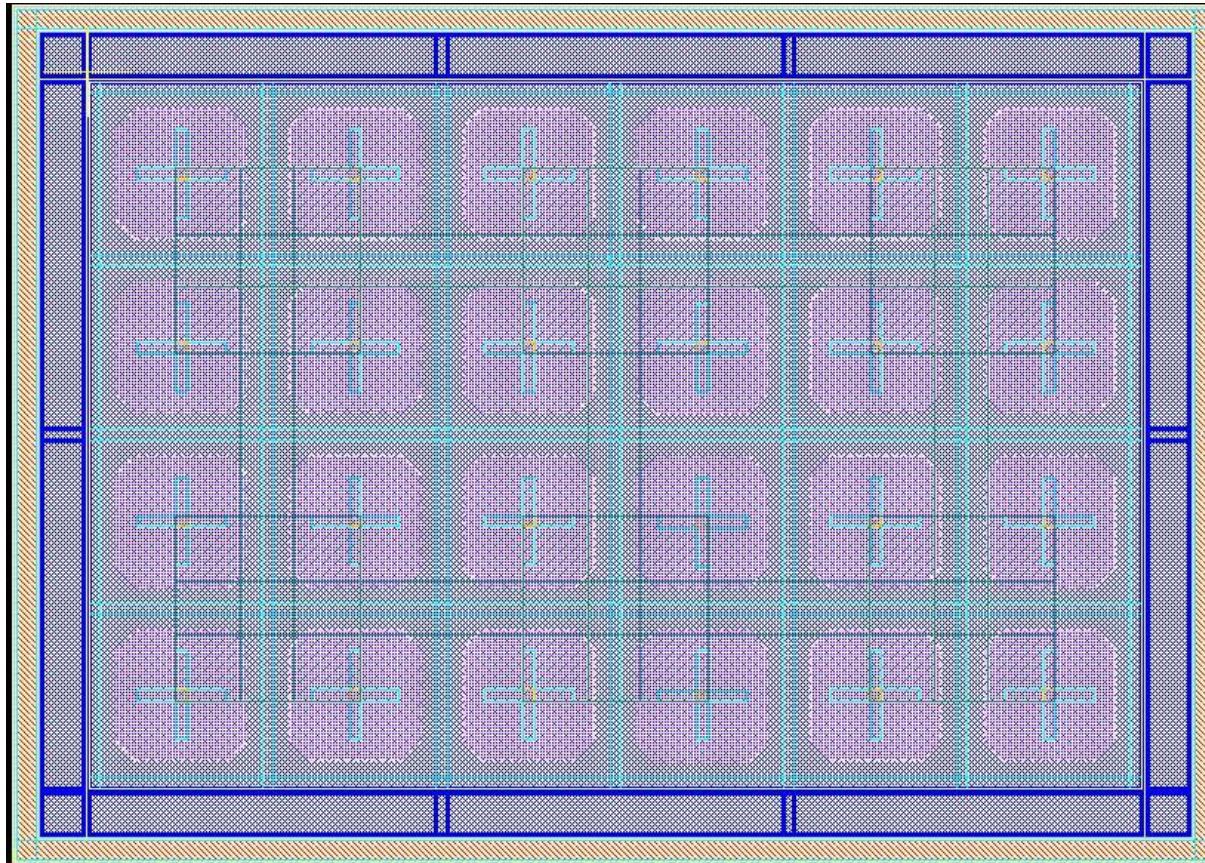

# VRG-Layout

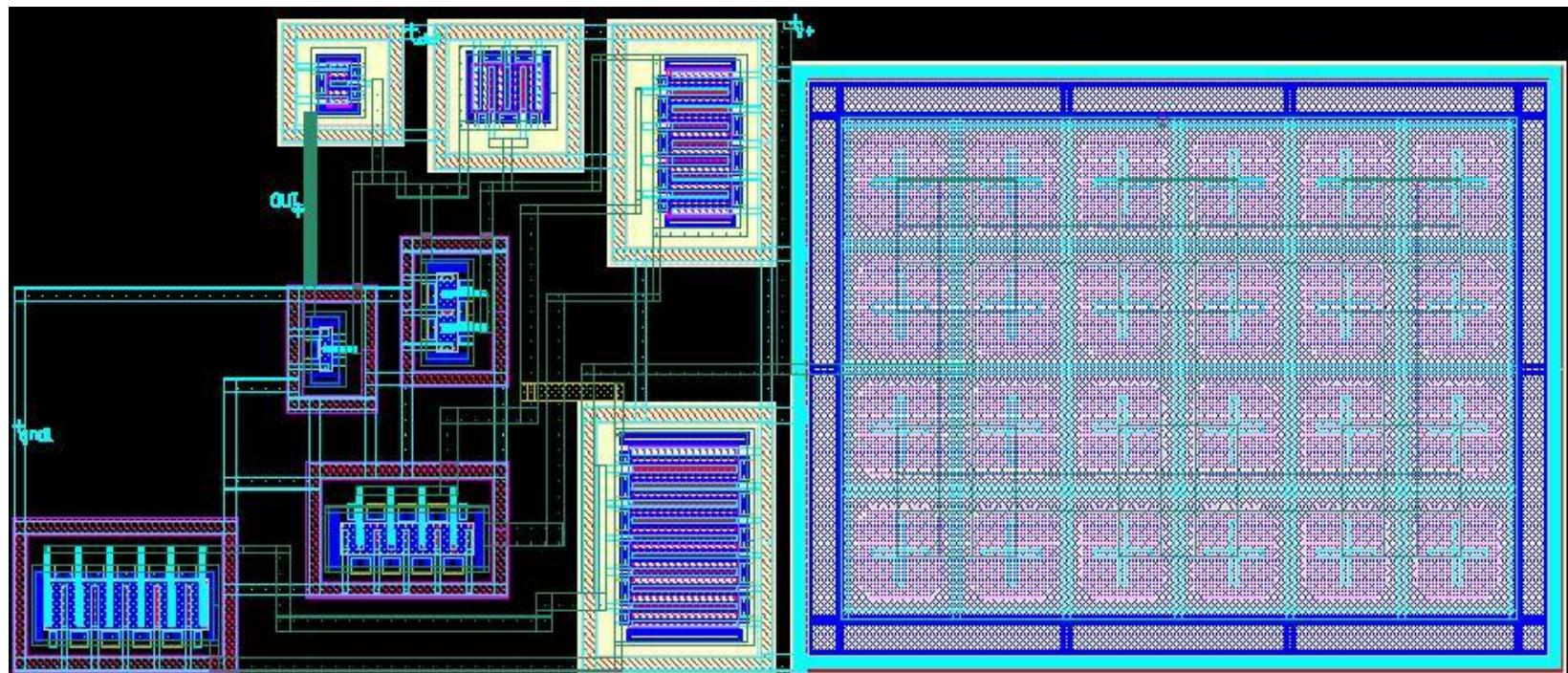

# VRG-LVS-OK


The screenshot shows a software interface for a Design Rule Check (DRC) or Layout vs. Schematic (LVS) comparison. On the left, a tree view displays a single node under 'LVS Results: Designs Match' labeled 'VRG1 / VRG'. The main window contains the LVS report output.

```
#####
##      C A L I B R E      S Y S T E M      ##
##      L V S      R E P O R T      ##
#####
NAME: VRG1.lvs.report
      VRG1.lay.net ('VRG1')
      /export/home/student/f91csie/f9106227/. ./VRG/VRG1.sp (
      _cali035pMM5V_2P4M.lvs
FILE: Calibre LVS Version V2.4a for TSMC 0.35um MIXED SINGAL
      Wed Sep 28 19:24:38 2005
STORY: /export/home/student/f91csie/f9106227
      f9106227
VERSION: v9.3_2.10      Tue May 13 13:44:42 PDT 2003

OVERALL COMPARISON RESULTS

#
#      #####      #
#      #      CORRECT      #
#      #      #####      #
#      #      #
#
***** CELL SUMMARY *****
```

# VRG-R/C Run PEX

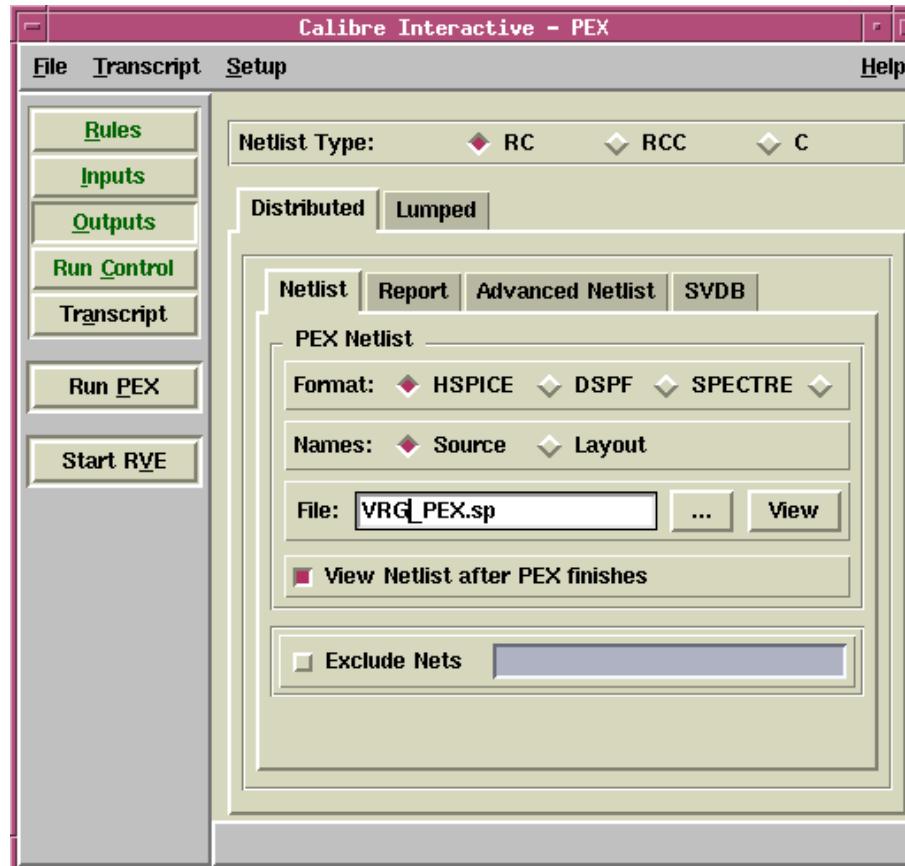


# VRG-R/C Run PEX Success


The image shows two windows from the Calibre Interactive software interface. The left window is titled "Calibre Interactive - PEX" and displays a transcript of the PEX process. It starts with an error message: "ERROR: PEX BACKANNOTATION DISTRIBUTION". Following this, it lists various layout and netlist reading steps, including "READING LAYOUT NETLIST VRG1", "READING LAYOUT TO SOURCE CRO", and "OUTPUT NETLIST FILE NAME VRG". It also shows the processing of parasitic models and the output of parasitic model instances. The right window is titled "PEX Netlist File - VRG\_PEX.sp" and displays the generated netlist script. The script includes header information like the file name, creation date, and program used, followed by detailed net definitions for components like MM25 and MM32, including their connections to N\_GND and VDD.

```
* File: VRG_PEX.sp
* Created: Wed Oct 12 19:05:17 2005
* Program "Calibre xRC"
* Version "v9.3_2.10"
*
.include VRG_PEX.sp.pex
.subckt VRG V+ OUT GND! VDD!
*
* gnd! gnd!
* vdd! vdd!
* V+ V+
* OUT OUT
mMM25_1 N_V+ MM25_1_d N_net9_MM25_1_g N_GND!_MM25_2_s N_GND!_MM25_10_b NCH
+ L=1e-06 W=5.2e-06
mMM25_2 N_V+ MM25_3_d N_net9_MM25_2_g N_GND!_MM25_2_s N_GND!_MM25_10_b NCH
+ L=1e-06 W=5.2e-06
mMM25_3 N_V+ MM25_3_d N_net9_MM25_3_g N_GND!_MM25_4_s N_GND!_MM25_10_b NCH
+ L=1e-06 W=5.2e-06
mMM25_4 N_V+ MM25_5_d N_net9_MM25_4_g N_GND!_MM25_4_s N_GND!_MM25_10_b NCH
+ L=1e-06 W=5.2e-06
mMM25_5 N_V+ MM25_5_d N_net9_MM25_5_g N_GND!_MM25_6_s N_GND!_MM25_10_b NCH
+ L=1e-06 W=5.2e-06
mMM25_6 N_V+ MM25_7_d N_net9_MM25_6_g N_GND!_MM25_6_s N_GND!_MM25_10_b NCH
+ L=1e-06 W=5.2e-06
mMM25_7 N_V+ MM25_7_d N_net9_MM25_7_g N_GND!_MM25_8_s N_GND!_MM25_10_b NCH
+ L=1e-06 W=5.2e-06
mMM25_8 N_V+ MM25_9_d N_net9_MM25_8_g N_GND!_MM25_8_s N_GND!_MM25_10_b NCH
+ L=1e-06 W=5.2e-06
mMM25_9 N_V+ MM25_9_d N_net9_MM25_9_g N_GND!_MM25_10_s N_GND!_MM25_10_b
+ NCH L=1e-06 W=5.2e-06
mMM25_10 N_V+ MM25_10_d N_net9_MM25_10_g N_GND!_MM25_10_s N_GND!_MM25_10_b
+ NCH L=1e-06 W=5.2e-06
mMM32_1 N_net17_MM32_2_d N_OUT_MM32_1_g N_GND!_MM32_1_s N_GND!_MM25_10_b
+ NCH L=1e-06 W=1e-06
mMM32_2 N_net17_MM32_2_d N_OUT_MM32_2_g N_GND!_MM32_2_s N_GND!_MM25_10_b
+ NCH L=1e-06 W=1e-06
mMM30_1 N_net9_MM30_2_d N_net13_MM30_1_g N_GND!_MM30_1_s N_GND!_MM25_10_b
+ NCH L=1e-06 W=3e-06
mMM30_2 N_net9_MM30_2_d N_net13_MM30_2_g N_GND!_MM30_3_s N_GND!_MM25_10_b
+ NCH L=1e-06 W=3e-06
```


# Oscillator-M33~43-Schematic

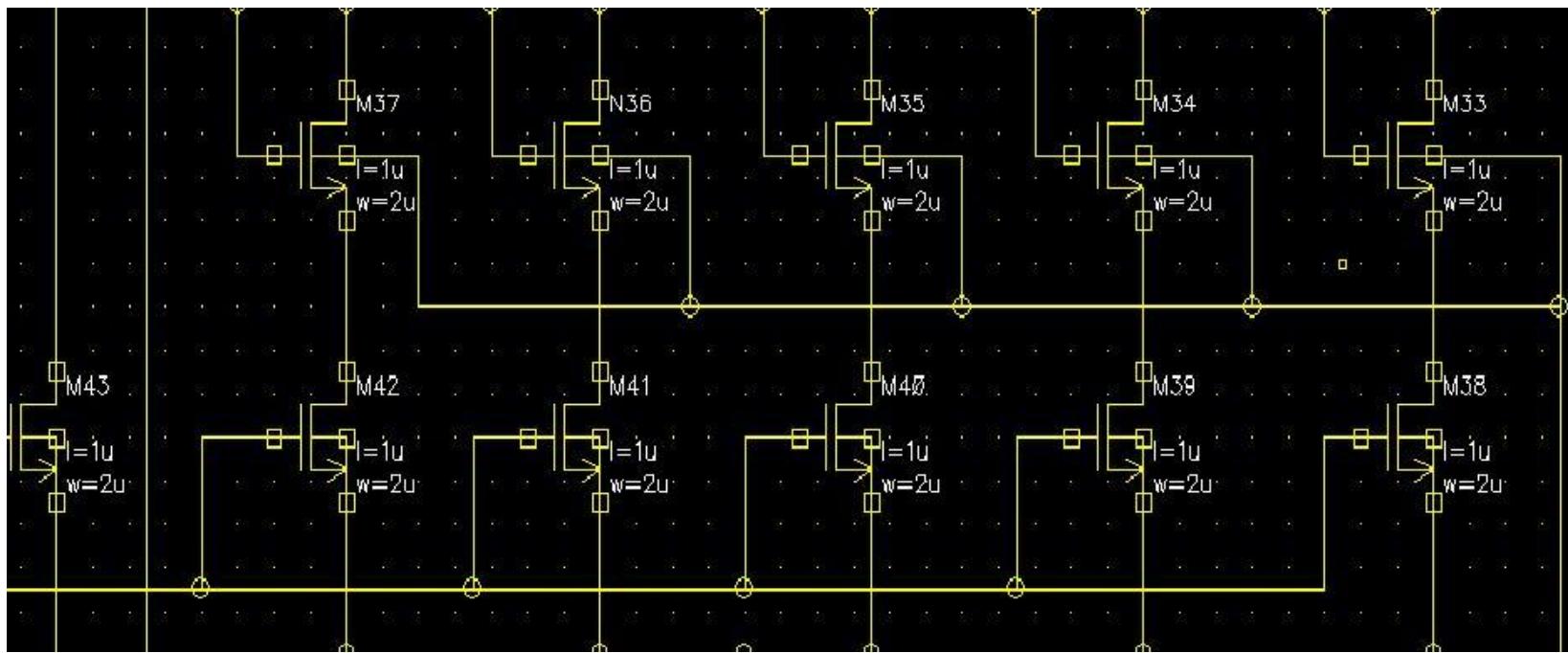


# Oscillator-M33~43-Layout

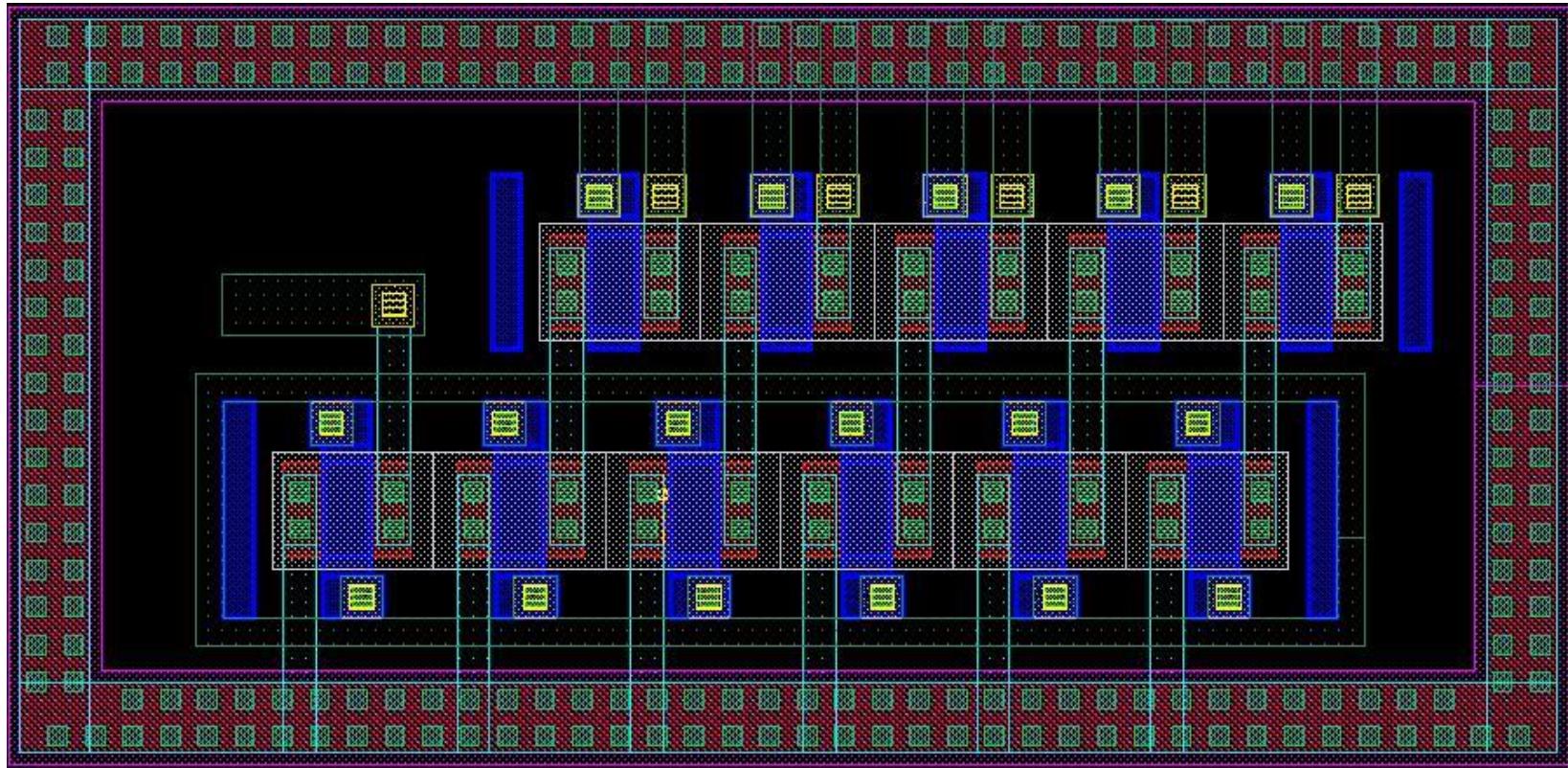


# Oscillator-M0,8,9,17~24-Schematic

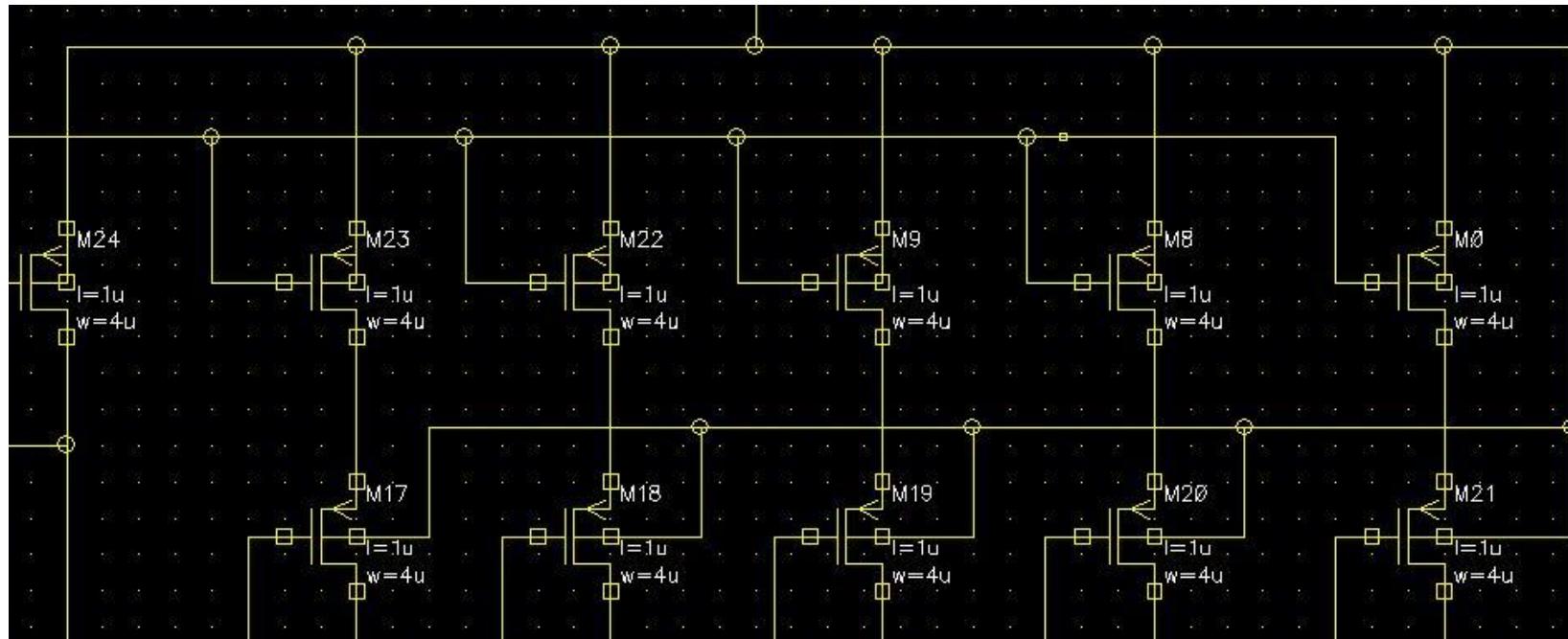


# Oscillator-M0,8,9,17~24-Layout

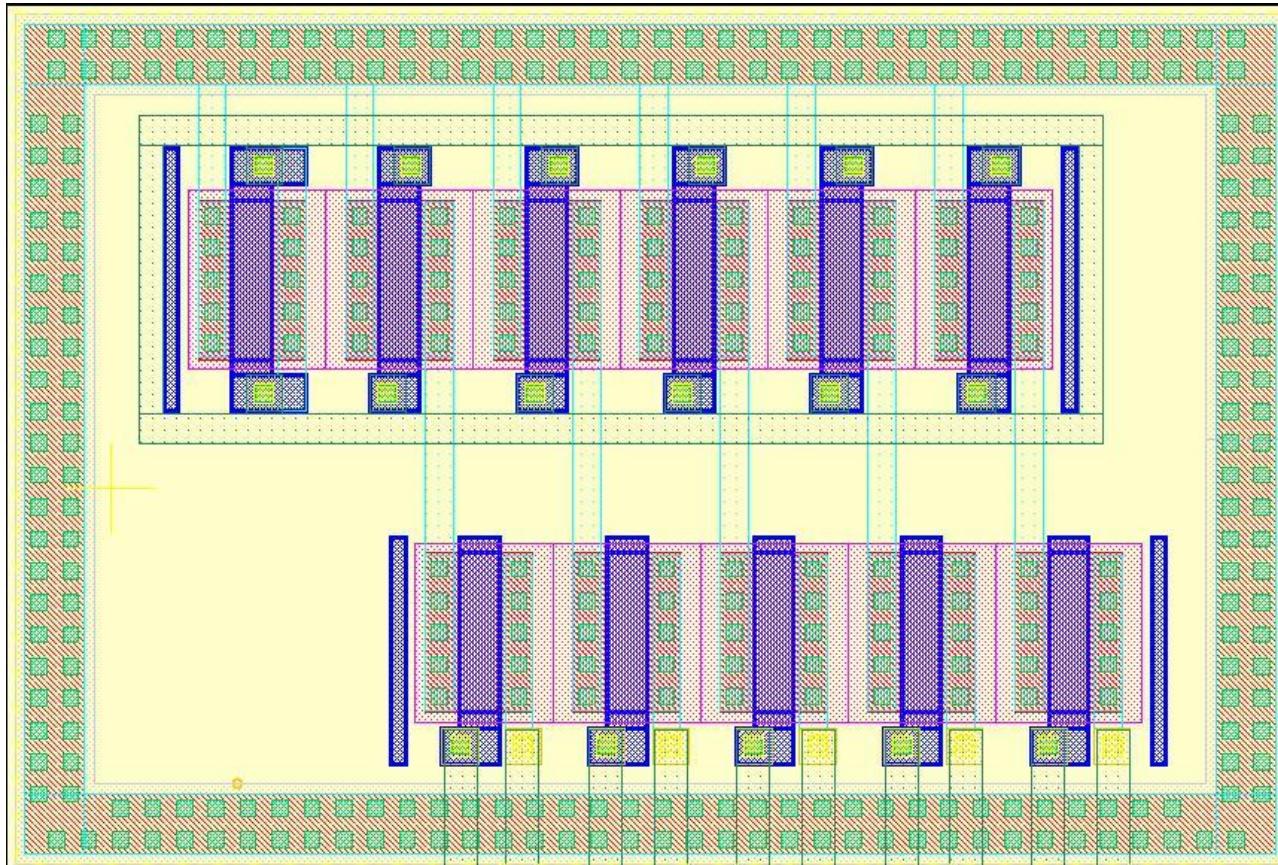


# Oscillator-Layout

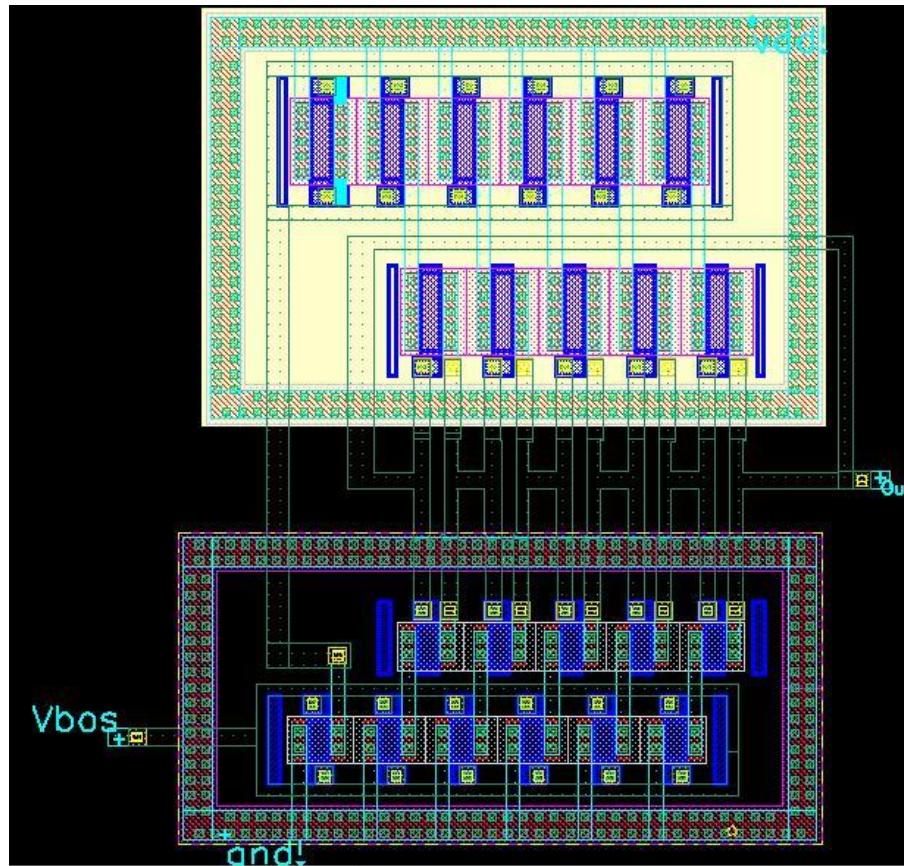

# Oscillator-Lvs OK

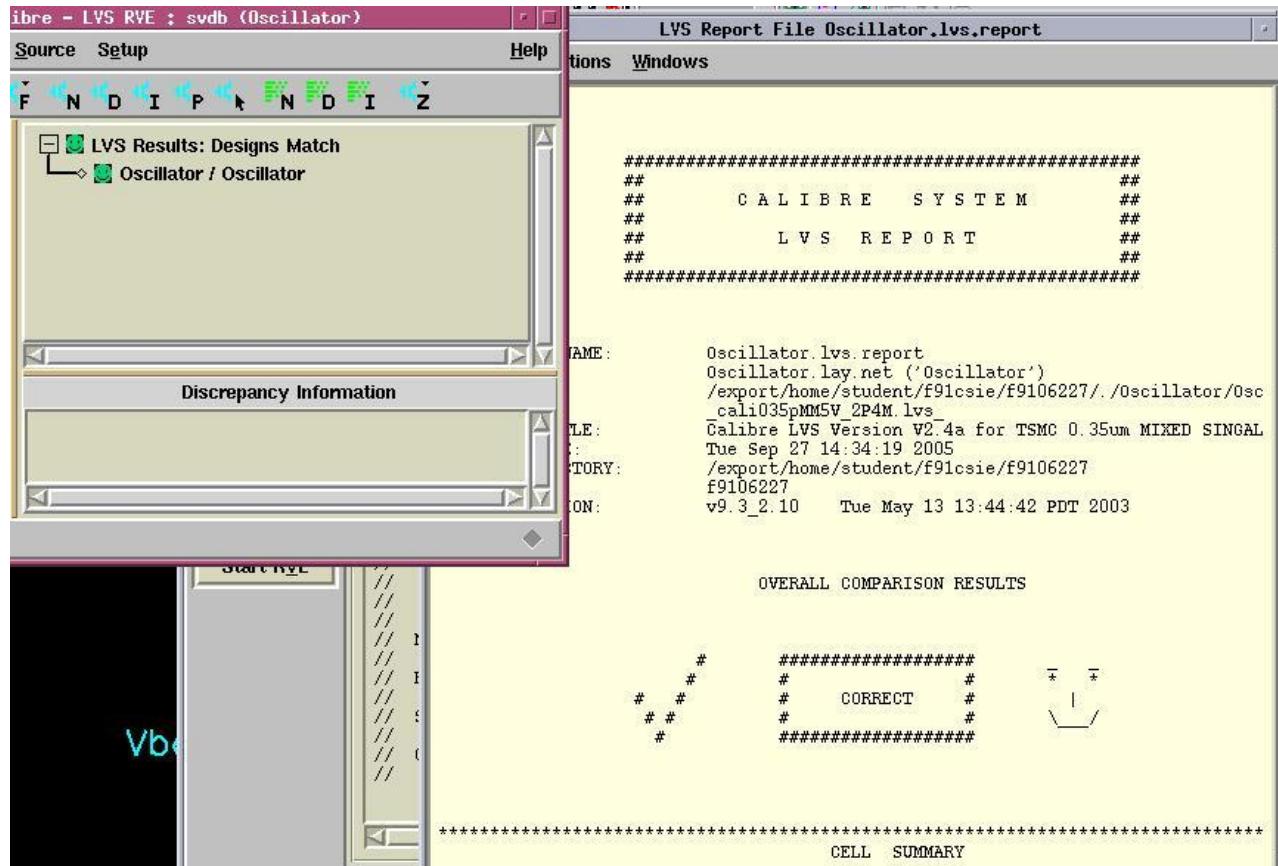

# Oscillator-R/C Run PEX

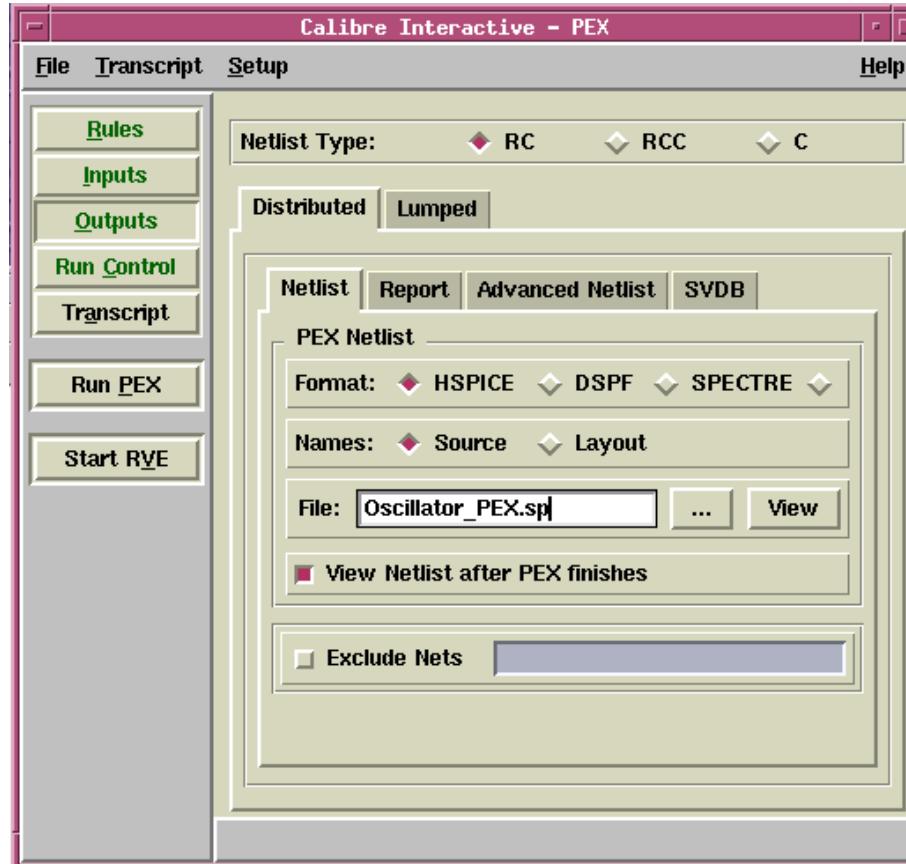


# Oscillator-R/C Run PEX Success


The screenshot shows two windows from the Calibre Interactive - PEX application. The left window is titled "Calibre Interactive - PEX" and has tabs for Transcript, Setup, Rules, Inputs, Outputs, Run Control, Transcript, Run PEX, and Start RVE. The "Transcript" tab is selected, displaying a log message: "ERROR: PEX BACKANNOTATION DISTRIBUTION". Below this, there is a detailed report of layout statistics and a summary of completed tasks. The right window is titled "PEX Netlist File - Oscillator\_PEX.sp" and displays a large block of Verilog-like netlist code. The code defines various nodes (e.g., MM34, MM38, MM43, MM24, MM42, MM41, MM23, MM22, MM9, MM8, MM37, MM17, MN36) and their connections, including power and ground pins (VDD!, VDD, GND!, GND). The code is annotated with comments indicating file creation date, program version, and specific node definitions.

```
* File: Oscillator_PEX.sp
* Created: Wed Oct 12 18:57:37 2005
* Program "Calibre xRC"
* Version "v9.3_2.10"
*
.include Oscillator_PEX.sp.pex
.subckt Oscillator -VBOS OUT GND! VDD!
*
* gnd! gnd!
* Out Out
* vdd! vdd!
* Vbos Vbos
mMM34 N_net31_MM34_d N_net35_MM34_g N_net7_MM34_s N_GND!_MM33_b NCH L=1e-06
+ W=2e-06
mMM38 N_net3_MM38_d N_VBOS_MM38_g N_GND!_MM38_s N_GND!_MM33_b NCH L=1e-06
+ W=2e-06
mMM33 N_OUT_MM33_d N_net31_MM33_g N_net3_MM33_s N_GND!_MM33_b NCH L=1e-06
+ W=2e-06
mMM0 N_net54_MM0_d N_net89_MM0_g N_VDD!_MM0_s N_VDD!_MM21_b PCH L=1e-06 W=4e-06
mMM43 N_net89_MM43_d N_VBOS_MM43_g N_GND!_MM43_s N_GND!_MM33_b NCH L=1e-06
+ W=2e-06
mMM24 N_net89_MM24_d N_net89_MM24_g N_VDD!_MM24_s N_VDD!_MM21_b PCH L=1e-06
+ W=4e-06
mMM42 N_net19_MM42_d N_VBOS_MM42_g N_GND!_MM42_s N_GND!_MM33_b NCH L=1e-06
+ W=2e-06
mMM41 N_net15_MM41_d N_VBOS_MM41_g N_GND!_MM41_s N_GND!_MM33_b NCH L=1e-06
+ W=2e-06
mMM23 N_net70_MM23_d N_net89_MM23_g N_VDD!_MM23_s N_VDD!_MM21_b PCH L=1e-06
+ W=4e-06
mMM22 N_net66_MM22_d N_net89_MM22_g N_VDD!_MM22_s N_VDD!_MM21_b PCH L=1e-06
+ W=4e-06
mMM9 N_net62_MM9_d N_net89_MM9_g N_VDD!_MM9_s N_VDD!_MM21_b PCH L=1e-06 W=4e-06
mMM8 N_net58_MM8_d N_net89_MM8_g N_VDD!_MM8_s N_VDD!_MM21_b PCH L=1e-06 W=4e-06
mMM37 N_net43_MM37_d N_OUT_MM37_g N_net19_MM37_s N_GND!_MM33_b NCH L=1e-06
+ W=2e-06
mMM17 N_net43_MM17_d N_OUT_MM17_g N_net70_MM17_s N_VDD!_MM21_b PCH L=1e-06
+ W=4e-06
mMN36 N_net39_MN36_d N_net43_MN36_g N_net15_MN36_s N_GND!_MM33_b NCH L=1e-06
+ W=2e-06
mMM35 N_net35_MM35_d N_net39_MM35_g N_net11_MM35_s N_GND!_MM33_b NCH L=1e-06
```

# PWM-Pre-Simulation

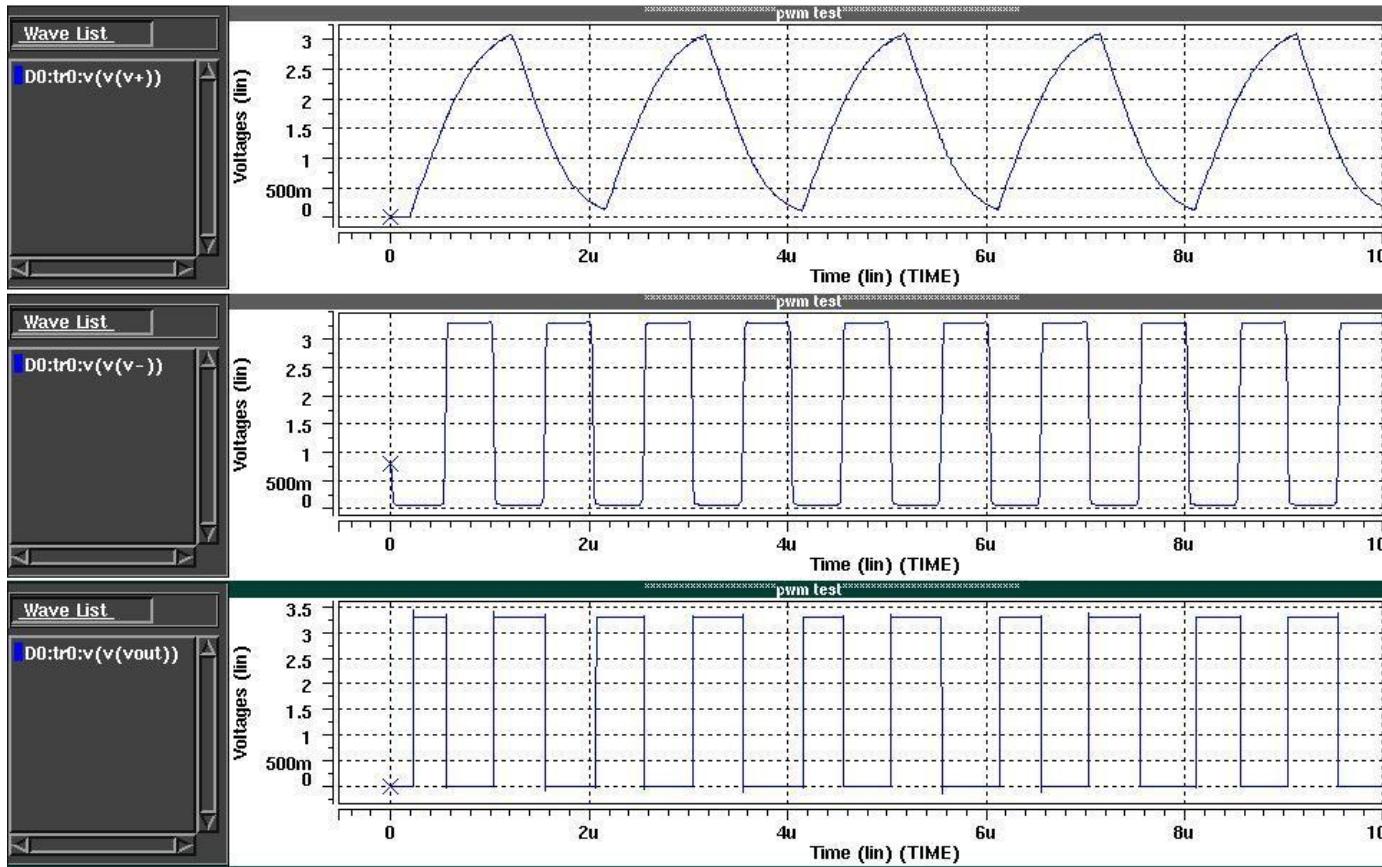

# PWM-Layout

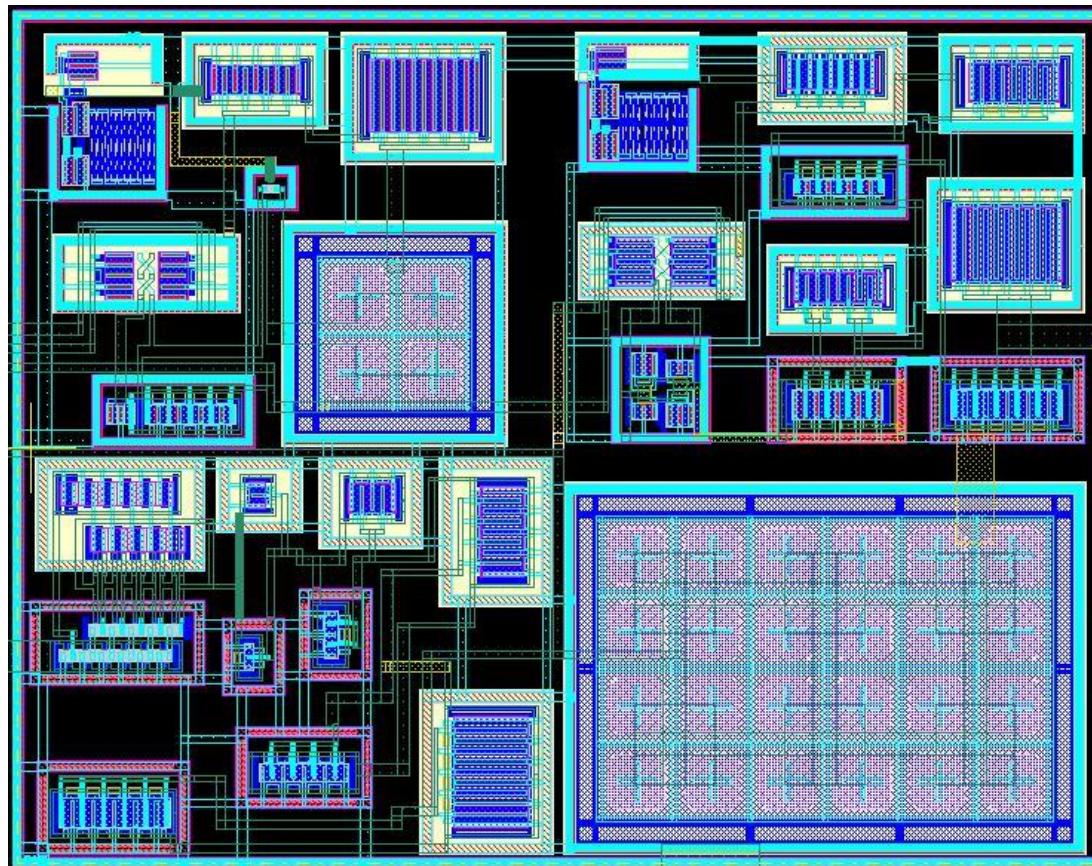

# PWM-Lvs OK


The screenshot shows the Calibre LVS interface. On the left, there's a tree view of files under 'Input Files' and 'Output Files'. Under 'Output Files', 'LVS Report' is expanded, showing a yellow warning icon next to 'Extraction R'. The main window title is 'LVS Results: Designs Match' with a green checkmark icon, and it also shows a green checkmark icon next to 'PWM / PWM'. The report content is as follows:

```
#####
##          C A L I B R E      S Y S T E M      ##
##          L V S      R E P O R T      ##
#####
REPORT FILE NAME: PWM.lvs.report
LAYOUT NAME: PWM.lay.net ('PWM')
SOURCE NAME: /export/home/student/f91csie/f9106227/. ./PWM/PWM.sj
RULE FILE: _cali035pMM5V_2P4M.lvs_
RULE FILE TITLE: Calibre LVS Version V2.4a for TSMC 0.35um MIXED S:
CREATION TIME: Fri Oct 7 13:32:20 2005
CURRENT DIRECTORY: /export/home/student/f91csie/f9106227
USER NAME: f9106227
CALIBRE VERSION: v9.3_2.10 Tue May 13 13:44:42 PDT 2003

OVERALL COMPARISON RESULTS

#
#          #####
#          #      CORRECT      #
#          #          #
#          #####
***** CELL SUMMARY *****
```

# PWM-R/C Run PEX

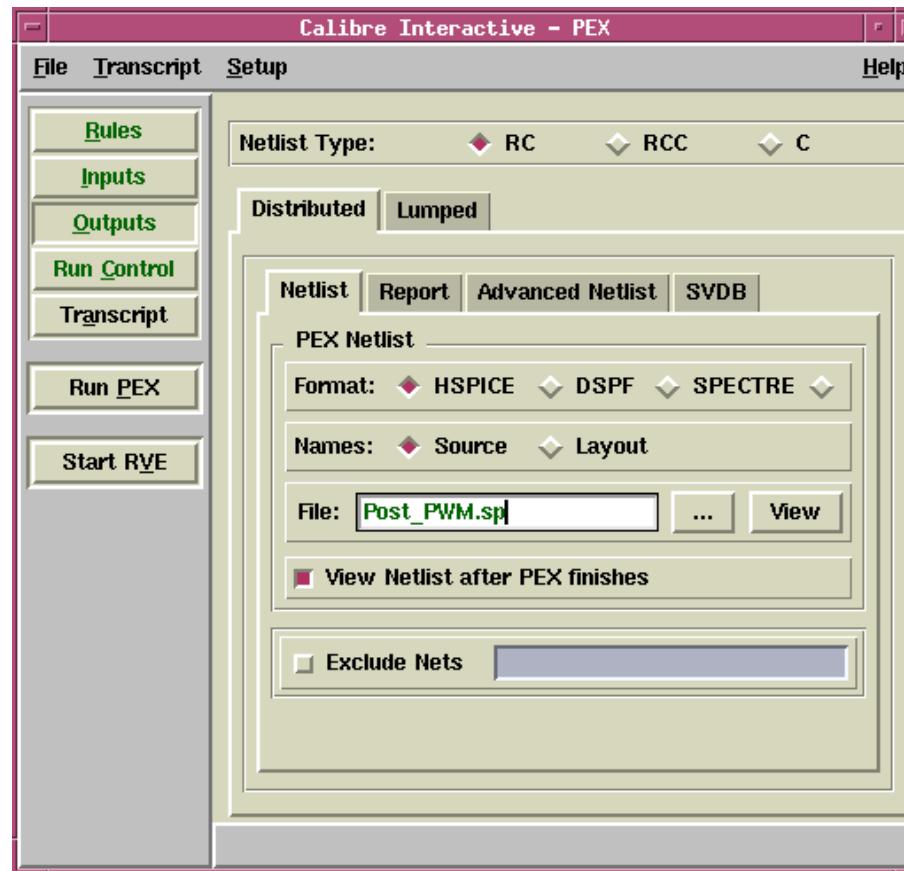

# PWM-R/C Run PEX Success


The screenshot shows two windows from the Calibre Interactive interface. The left window, titled 'Calibre Interactive - F', displays a transcript of the PEX process. It starts with 'ERROR: PEX BACKANNOTATION D' and then lists various layout-related steps like reading netlists, outputting parasitic models, and processing parasitic models. It also shows the pdbs file name, root cell name, total nets, top-level nets, non-top-level nets, degenerate nets, merged nets, and error nets. The transcript concludes with 'CALIBRE xRC::FORMATTER' and 'TOTAL CPU TIME = 0 REA'. The right window, titled 'PEX Netlist File - Post\_PWM.sp', shows the generated netlist script. The script includes header information (File: Post\_PWM.sp, Created: Wed Oct 12 20:06:23 2005, Program: "Calibre xRC", Version: "v9.3.2.10"), component definitions (e.g., MM25, MM33), and connection statements (e.g., V+, V-, Vin+, Vin-, Vb0s, Vb0s). The bottom of the netlist shows memory usage statistics: Edit Row 1 Col 1.

```
* File: Post_PWM.sp
* Created: Wed Oct 12 20:06:23 2005
* Program "Calibre xRC"
* Version "v9.3.2.10"
*
*.include Post_PWM.sp.pex
.subckt PWM VBOS VIN+ VIN- V- VDD! V+ VOUT GND!
*
* gnd! gnd!
* vdd! vdd!
* Vout Vout
* V+ V+
* V- V-
* Vin- Vin-
* Vin+ Vin+
* Vb0s Vb0s
mMM25_1 N_V+ MM25_1_d N_net177_MM25_1_g N_GND!_MM25_2_s N_GND!_MM33_b NCH
+ L=1e-06 W=5.2e-06
mMM25_2 N_V+ MM25_3_d N_net177_MM25_2_g N_GND!_MM25_2_s N_GND!_MM33_b NCH
+ L=1e-06 W=5.2e-06
mMM25_3 N_V+ MM25_3_d N_net177_MM25_3_g N_GND!_MM25_4_s N_GND!_MM33_b NCH
+ L=1e-06 W=5.2e-06
mMM25_4 N_V+ MM25_5_d N_net177_MM25_4_g N_GND!_MM25_4_s N_GND!_MM33_b NCH
+ L=1e-06 W=5.2e-06
mMM25_5 N_V+ MM25_5_d N_net177_MM25_5_g N_GND!_MM25_6_s N_GND!_MM33_b NCH
+ L=1e-06 W=5.2e-06
mMM25_6 N_V+ MM25_7_d N_net177_MM25_6_g N_GND!_MM25_6_s N_GND!_MM33_b NCH
+ L=1e-06 W=5.2e-06
mMM25_7 N_V+ MM25_7_d N_net177_MM25_7_g N_GND!_MM25_8_s N_GND!_MM33_b NCH
+ L=1e-06 W=5.2e-06
mMM25_8 N_V+ MM25_9_d N_net177_MM25_8_g N_GND!_MM25_8_s N_GND!_MM33_b NCH
+ L=1e-06 W=5.2e-06
mMM25_9 N_V+ MM25_9_d N_net177_MM25_9_g N_GND!_MM25_10_s N_GND!_MM33_b NCH
+ L=1e-06 W=5.2e-06
mMM34_N_net197_MM34_d N_net193_MM34_g N_net221_MM34_s N_GND!_MM33_b NCH L=1e-06
+ W=2e-06
mMM25_10 N_V+ MM25_10_d N_net177_MM25_10_g N_GND!_MM25_10_s N_GND!_MM33_b
+ NCH L=1e-06 W=5.2e-06
mMM38_N_net225_MM38_d N_VBOS_MM38_g N_GND!_MM38_s N_GND!_MM33_b NCH L=1e-06
+ W=2e-06
mMM33_N_net187_MM33_d N_net197_MM33_g N_net225_MM33_s N_GND!_MM33_b NCH L=1e-06
+ W=2e-06
mMM32_1 N_net169_MM32_2_d N_net187_MM32_1_g N_GND!_MM32_1_s N_GND!_MM33_b
+ NCH L=1e-06 W=1e-06
mMM32_2 N_net169_MM32_2_d N_net187_MM32_2_g N_GND!_MM32_2_s N_GND!_MM33_b
```

# Chapter 4. Final Project


高雄第一科大電子系 郭永超副教授

# PWM Design

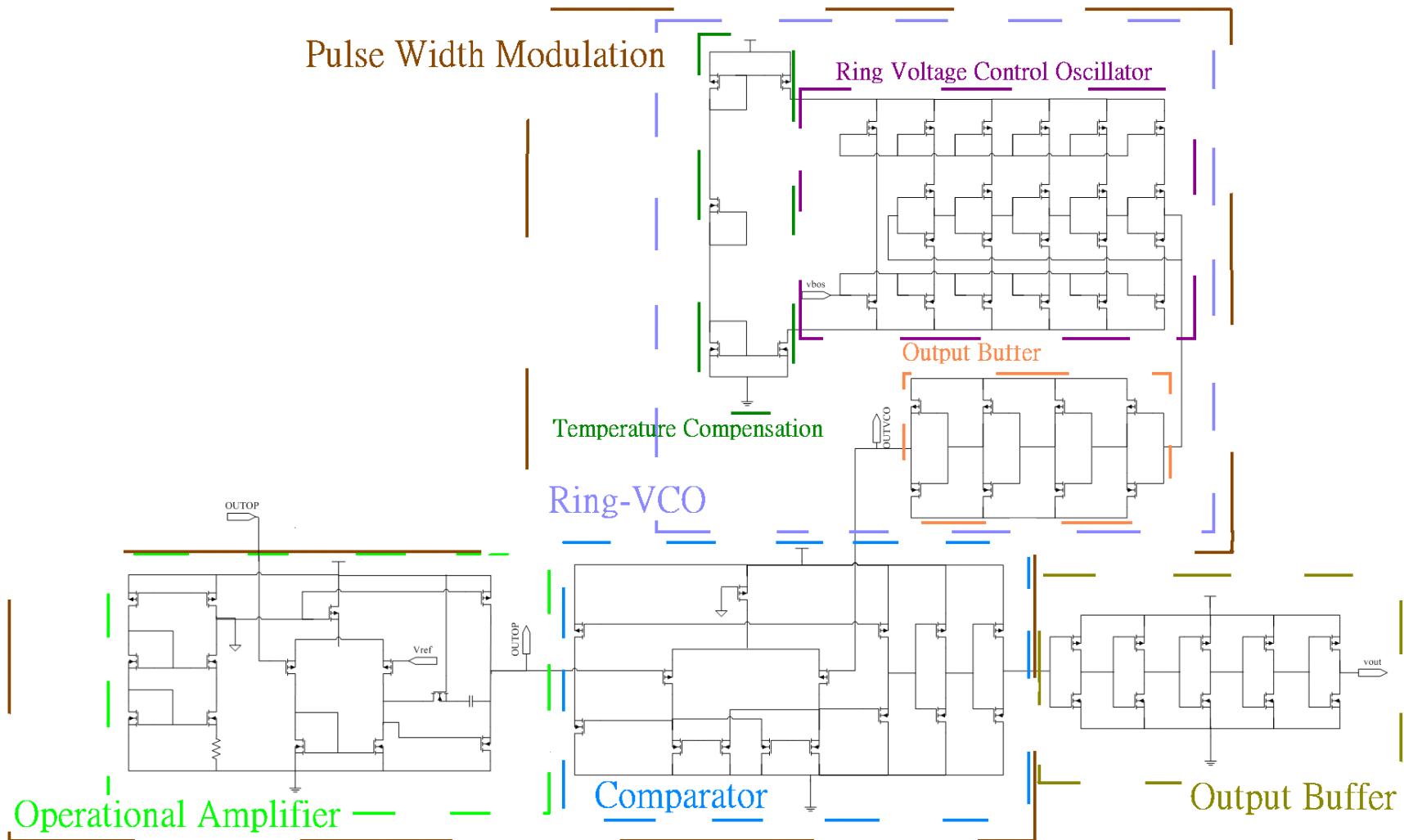

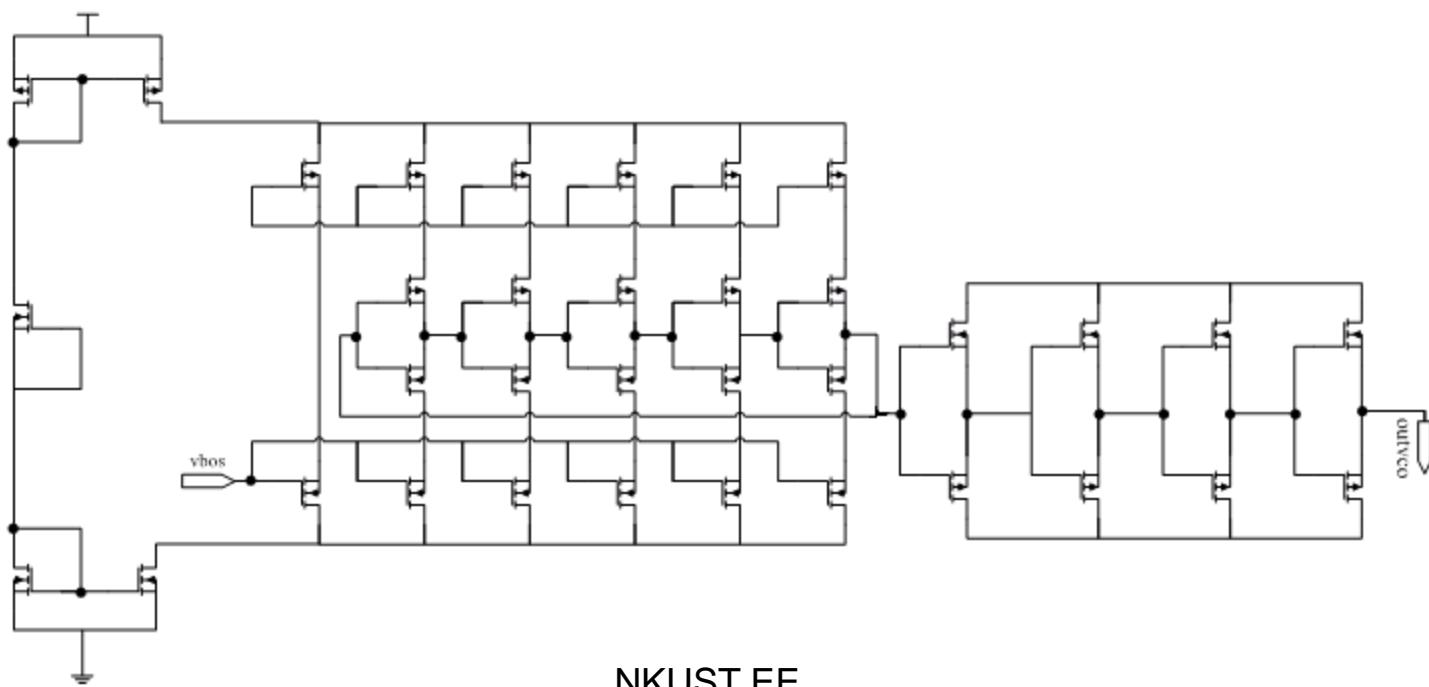
# VCO

- 環型震盪器是利用奇數反向器串接，達到在輸出端產生固定頻率之方波，並且可透過**vbos**外接電壓訊號控制頻率，**vbos**電壓愈高，頻率愈高；反之**vbos**電壓愈低，頻率愈低。利用溫度補償的概念，將環型震盪器加以改良，使環型震盪器不易受溫度影響它的準確度。



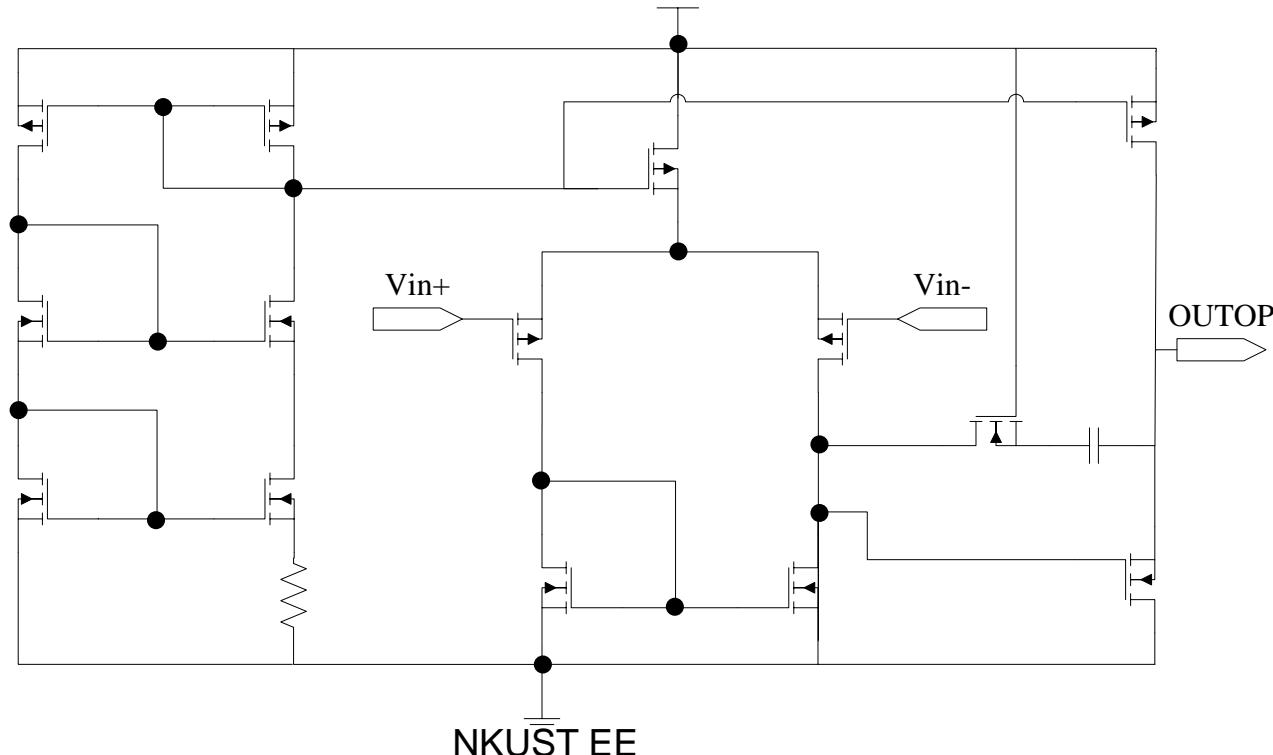
# OP

- 將Converter之Sensor輸出值與參考電壓V<sub>ref</sub>作比較，並將差值放大



# Comparator

- 以運算放大器輸出值與環狀電壓控制震盪器輸出值為輸入，比較兩者後輸出脈波訊號。

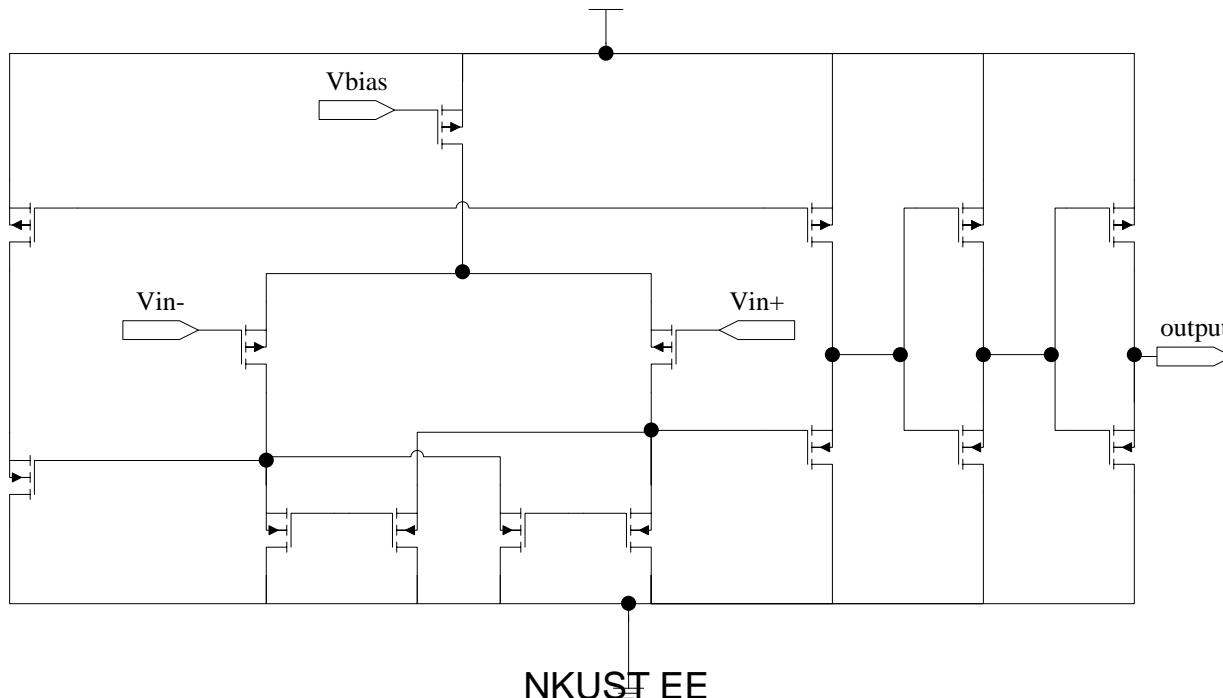

# OP Design-Spec.

	Specification	Pre-sim	Post-sim
Av	$A_o \geq 70 \text{ db}$	70 db	72 db
Phase margin	$\Phi M \geq 45^\circ$	$48^\circ$	$53^\circ$
Unit-gain frequency	$F_o \leq 200 \text{ MHz}$	97 MHz	71 MHz
Cc	$< 4 \text{ pf}$	0.4 pf	0.4 pf
Slew rate	$\leq 250 \text{ v}/\mu\text{s}$	75 v/ $\mu\text{s}$	72 v/ $\mu\text{s}$
Offset	0v	0.31v	0.26v
ICMR	0v – 5v	0.31v – 4.67v	0.26v – 4.68v
PSRR	$>60 \text{ db}$	73 db	76db
CMRR	$>60 \text{ db}$	47 db	54 db
Power Dissipation	$< 10 \text{ mV}$	5.4768 mV	4.06 mV

# OP Design (1/2)

$$\text{Let } SR = 250v/\mu 5 \text{ } Cc = 0.4pF$$

$$\mu_p C_{ox} = 50\mu \text{ and } \mu_n C_{ox} = 150\mu$$

$$250\mu = I_{D5}/0.4 \times 10^{-12}$$

$$I_{D5} = 100\mu 0$$

$$I_{D5} = 0.5 \times 50\mu \times (W/L)_5$$

$$(W/L)_5 = 16$$

$$(W/L)_6 = \frac{I_{D6}}{I_{D3}} \times (W/L)_3 = 27$$

$$(W/L)_7 = \frac{500 \times 10^{-6}}{0.5 \times 50\mu \times 0.25} = 80$$

$$I_{D3} = 0.5 \times 150\mu \times (W/L)_3$$


$$(W/L)_3 = (W/L)_4 = 2.7$$

$$f_0 = 200MHz, 2\pi \times f_0 = 1.256 \times 10^9$$

$$gmI = \omega_n C = 5.024 \times 10^{-4}$$

$$(gmI)^2 = 2 \times 50\mu \times (W/L)_I$$

$$(W/L)_I = (W/L)_2 = 50.5$$

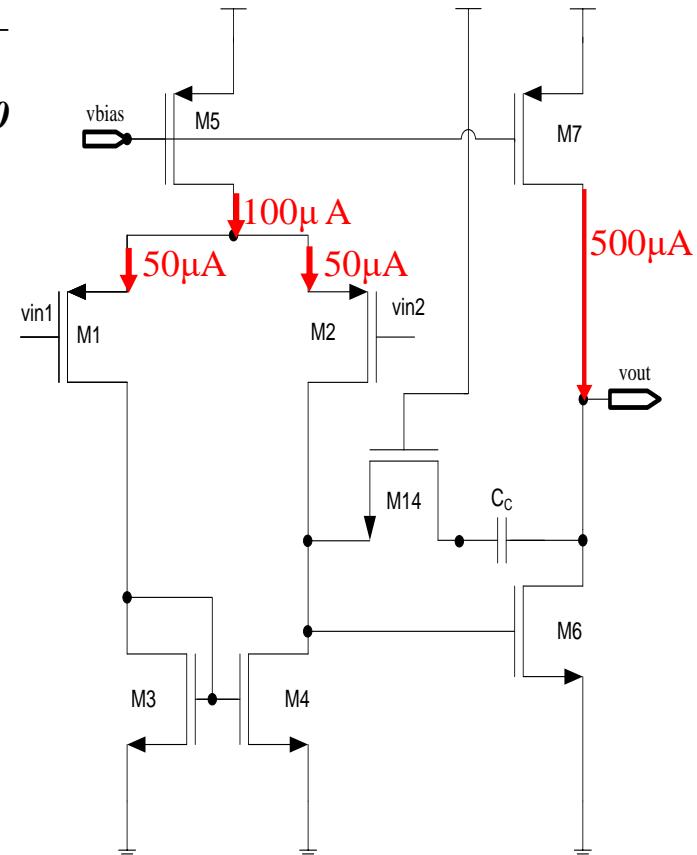

# OP Design (2/2)

\*Differential pair


```
M1  net2  vin-  net1  net1  PCH5  W=13u  L=1u  M=4
M2  net3  vin+  net1  net1  PCH5  W=13u  L=1u  M=4
M3  net2  net2  gnd!  gnd!  NCH5  W=4.5u      L=1u  M=1
M4  net3  net2  gnd!  gnd!  NCH5  W=4.5u      L=1u  M=1
M5  net1  net036 vdd!  vdd!  PCH5  W=4u       L=1u  M=4
```

\*Single-Stage Amplifier


```
M6  vout  net3  gnd!  gnd!  NCH5  W=6u      L=1u  M=8
M7  vout  net036 vdd!  vdd!  PCH5  W=11u     L=1u  M=7
```

\*Compensation

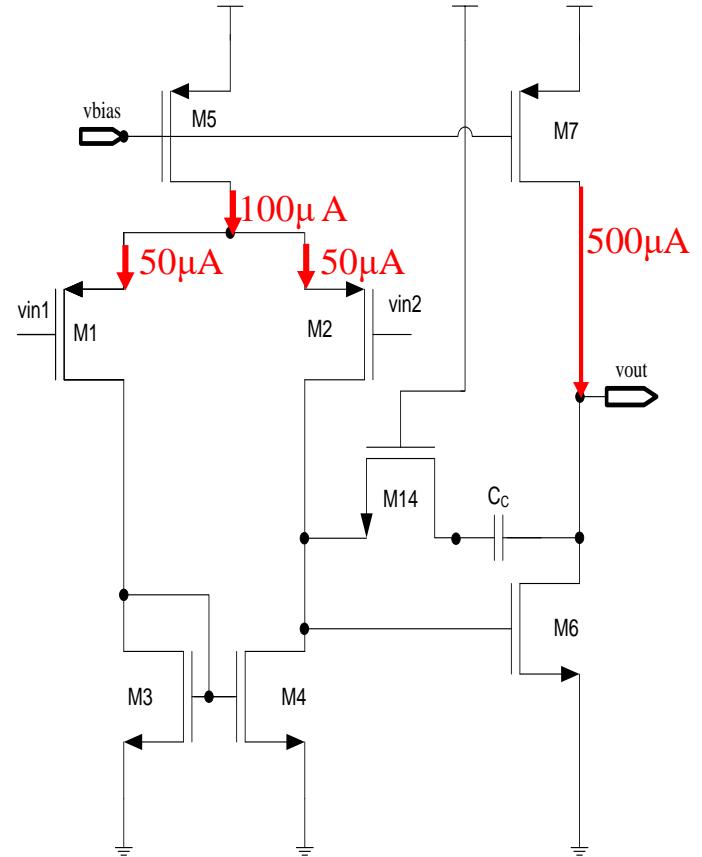
```
M14  net4  vdd!  net3  gnd!  NCH5  W=1.8u  L=1u  M=1
Ccc  net4  vout  0.4pF
```




# Simulation of OP (1/2)

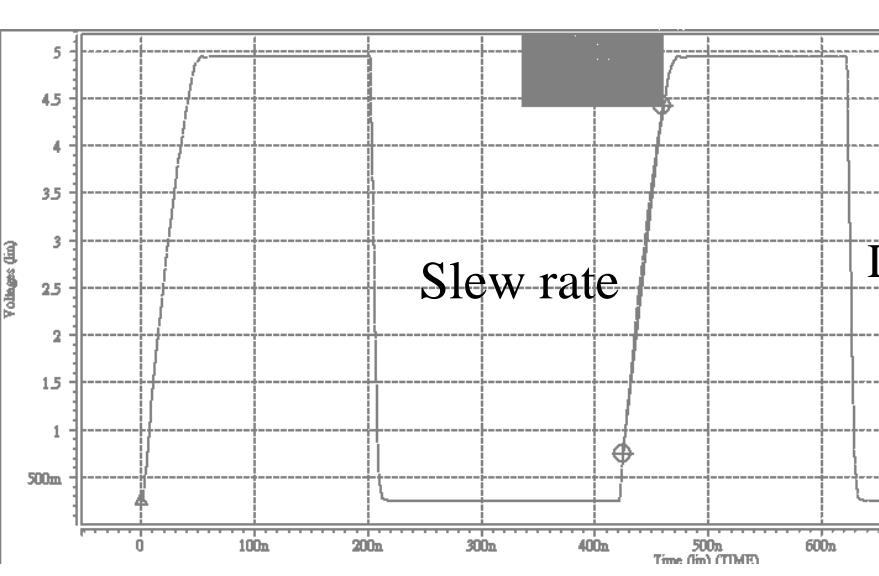


Slew rate

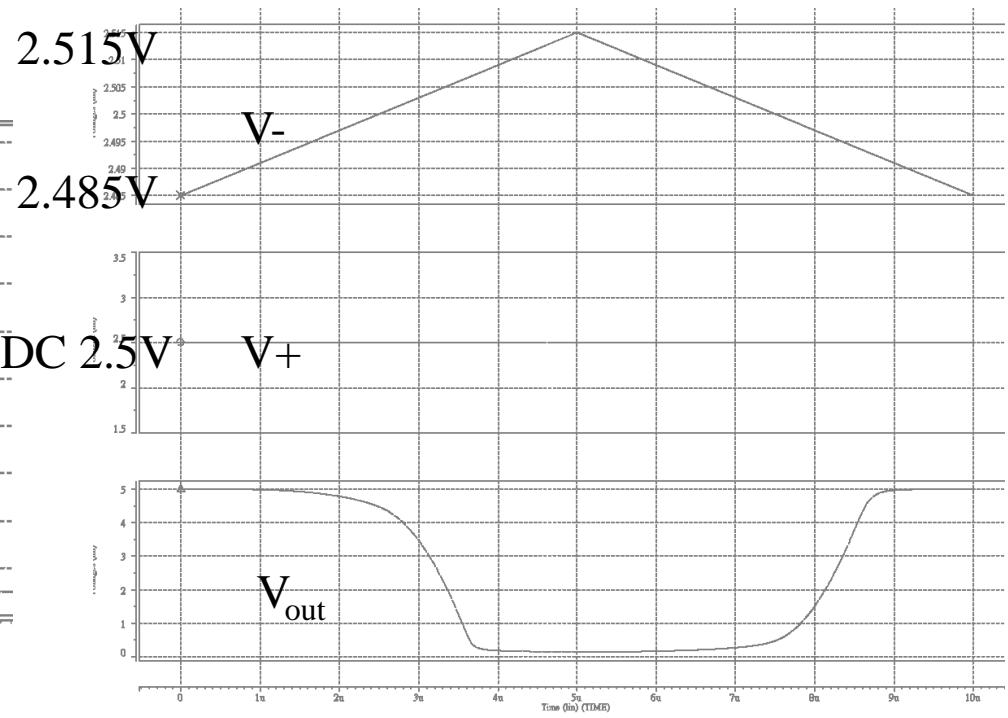


# Simulation of OP (2/2)

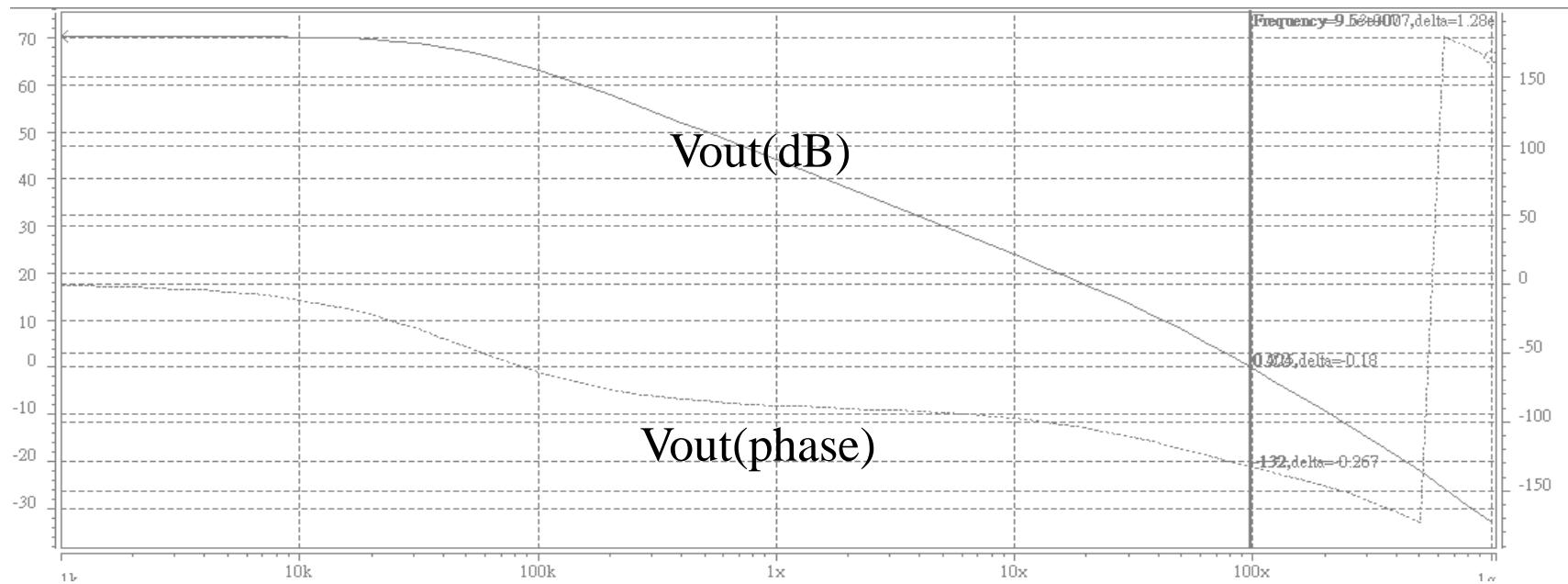

# Layout of PWM

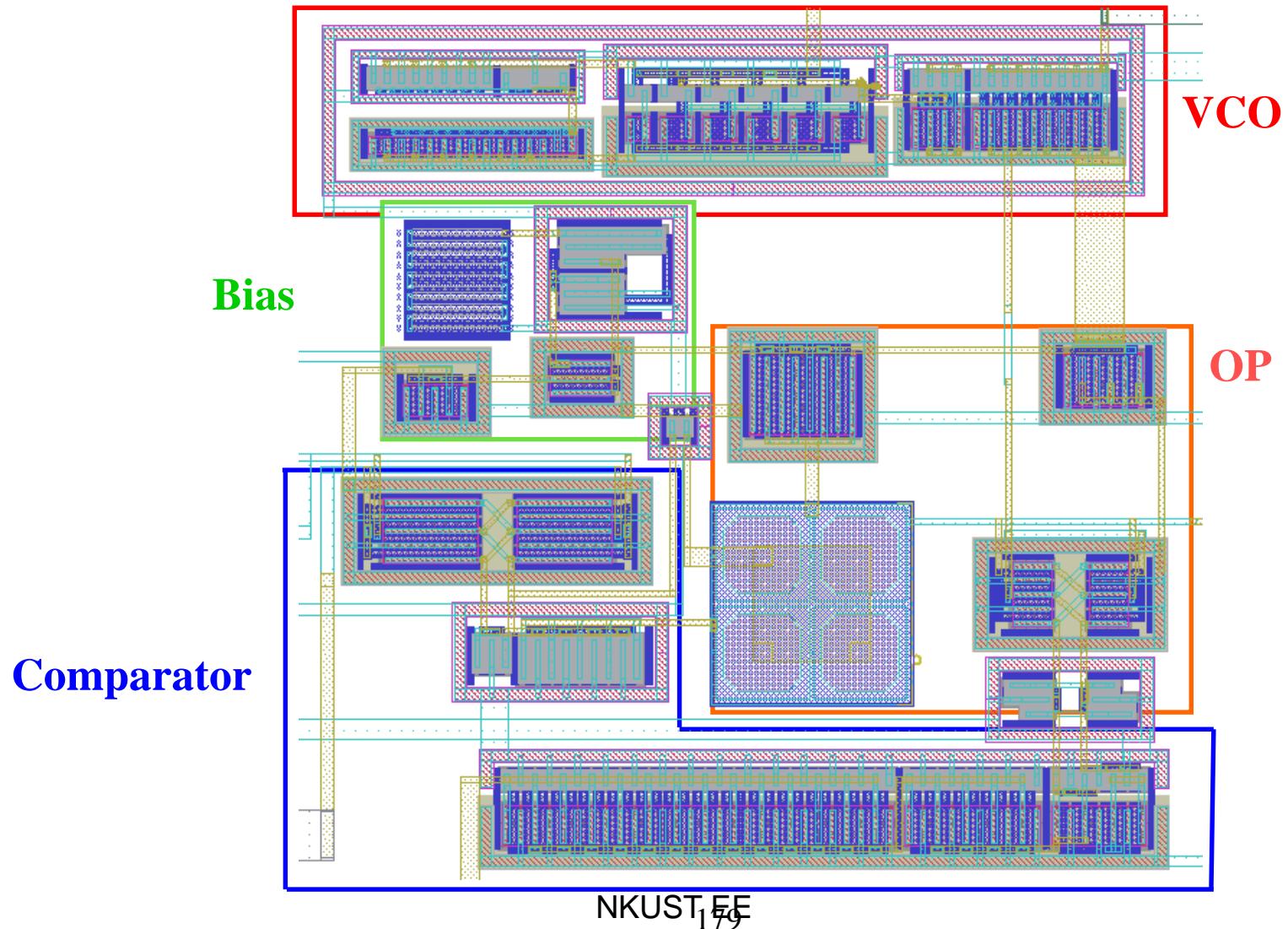


# Simulation of PWM

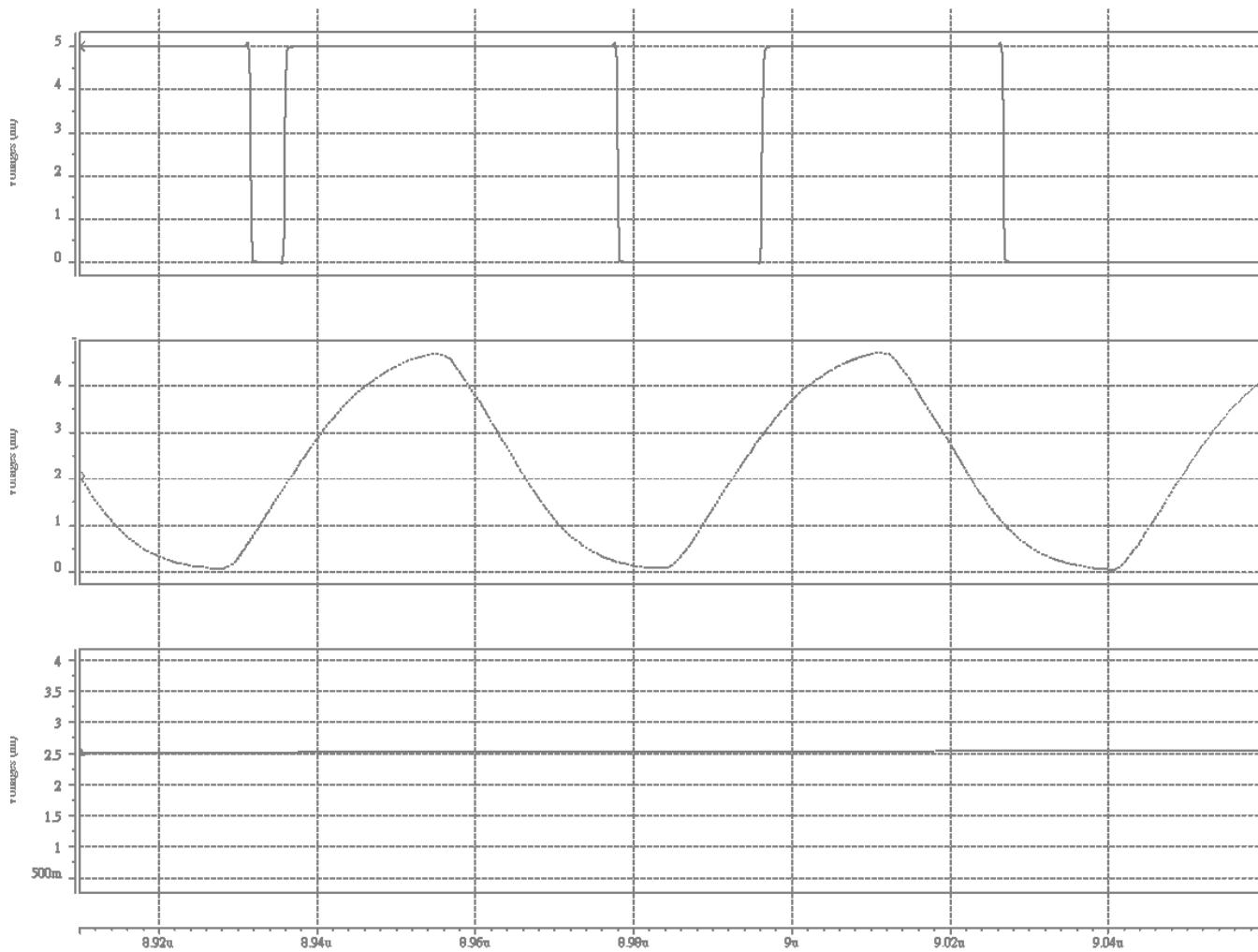


# Boost's Transfer Function in CCM Mode (1/3)


basic boost converter

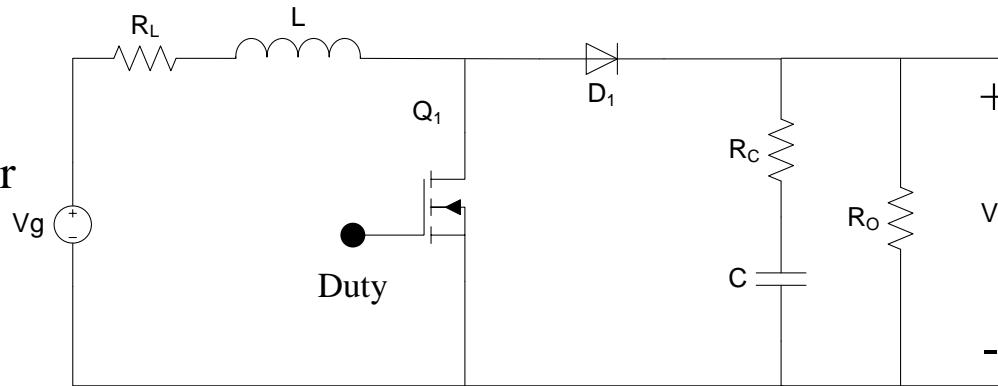

switch in position 1

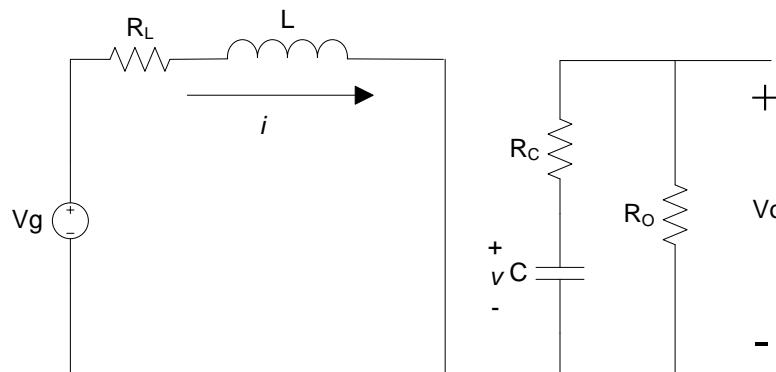

switch in position 2

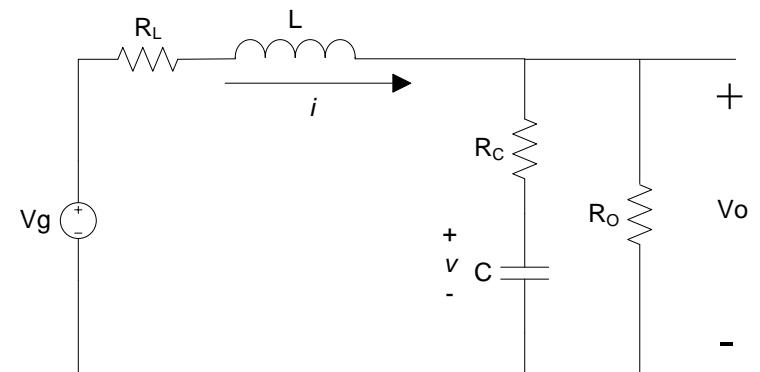

# Boost's Transfer Function in CCM Mode (2/3)

Analysis of boost converter in continuous-conduction mode (by KVL):


Subinterval 1: switch on

$$L \frac{di}{dt} = -(R_L)i + v_g$$

$$C \frac{dv}{dt} = \frac{v}{R_o + R_c}$$

$$V_o = \left( \frac{R_o}{R_o + R_c} \right) v$$

$$i_i = i$$

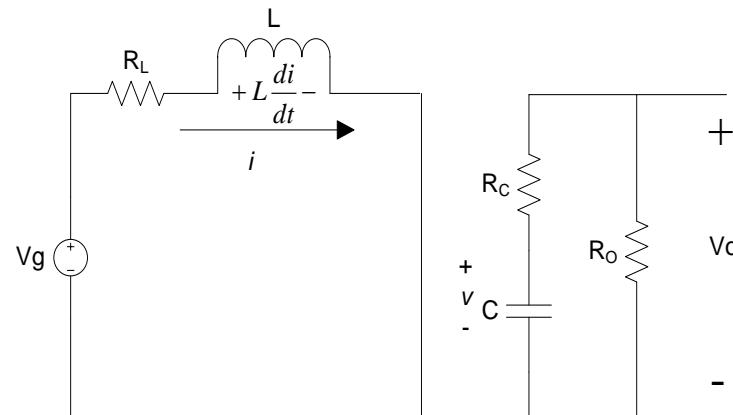


Subinterval 2: switch off

$$L \frac{di}{dt} = -\left( R_L + \frac{R_o R_c}{R_o + R_c} \right) i - \left( \frac{R_o}{R_o + R_c} \right) v + v_g$$

$$C \frac{dv}{dt} = \frac{R_o}{R_o + R_c} i - \frac{v}{R_o + R_c}$$

$$V_o = \left( \frac{R_o R_c}{R_o + R_c} \right) i + \left( \frac{R_o}{R_o + R_c} \right) v$$


$$i_i = i$$

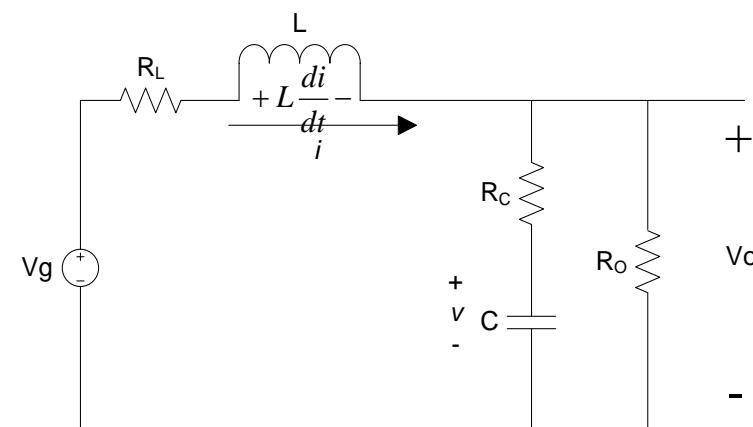
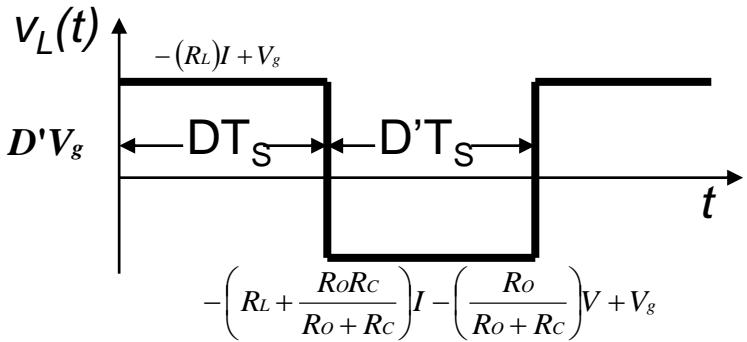
# Boost's Transfer Function in CCM Mode (3/3)


Volt-second balance

$$\begin{aligned}\langle v_L \rangle &= -D\mathbf{I}R_L + DV_i - D'\mathbf{I}R_L + D' \frac{RoRc}{Ro + Rc} I - D' \left( \frac{Ro}{Ro + Rc} \right) V + D'V_g \\ &= - \left( R_L + D' \frac{RoRc}{Ro + Rc} \right) I - \left( \frac{D'Ro}{Ro + Rc} \right) V + V_g \\ V_o &= D' \left( \frac{RoRc}{Ro + Rc} \right) I + \left( \frac{Ro}{Ro + Rc} \right) V\end{aligned}$$




Capacitor charge balance
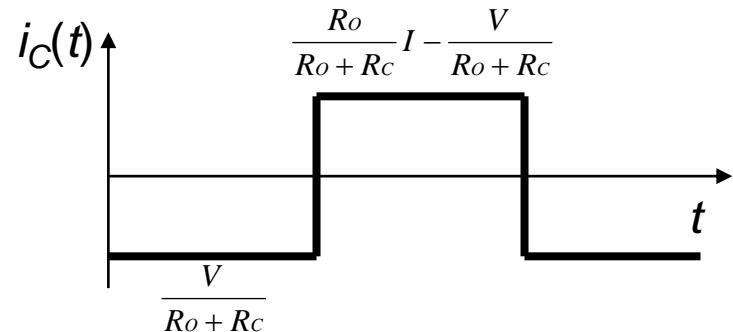
$$\begin{aligned}\langle i_c \rangle &= -\frac{DV}{Ro + Rc} + \frac{D'R_o}{Ro + Rc} I - \frac{D'V}{Ro + Rc} \\ &= \frac{D'R_o}{Ro + Rc} I - \frac{V}{Ro + Rc} \\ \mathbf{I}_i &= \mathbf{I}\end{aligned}$$



# Equivalent Circuits (1/2)

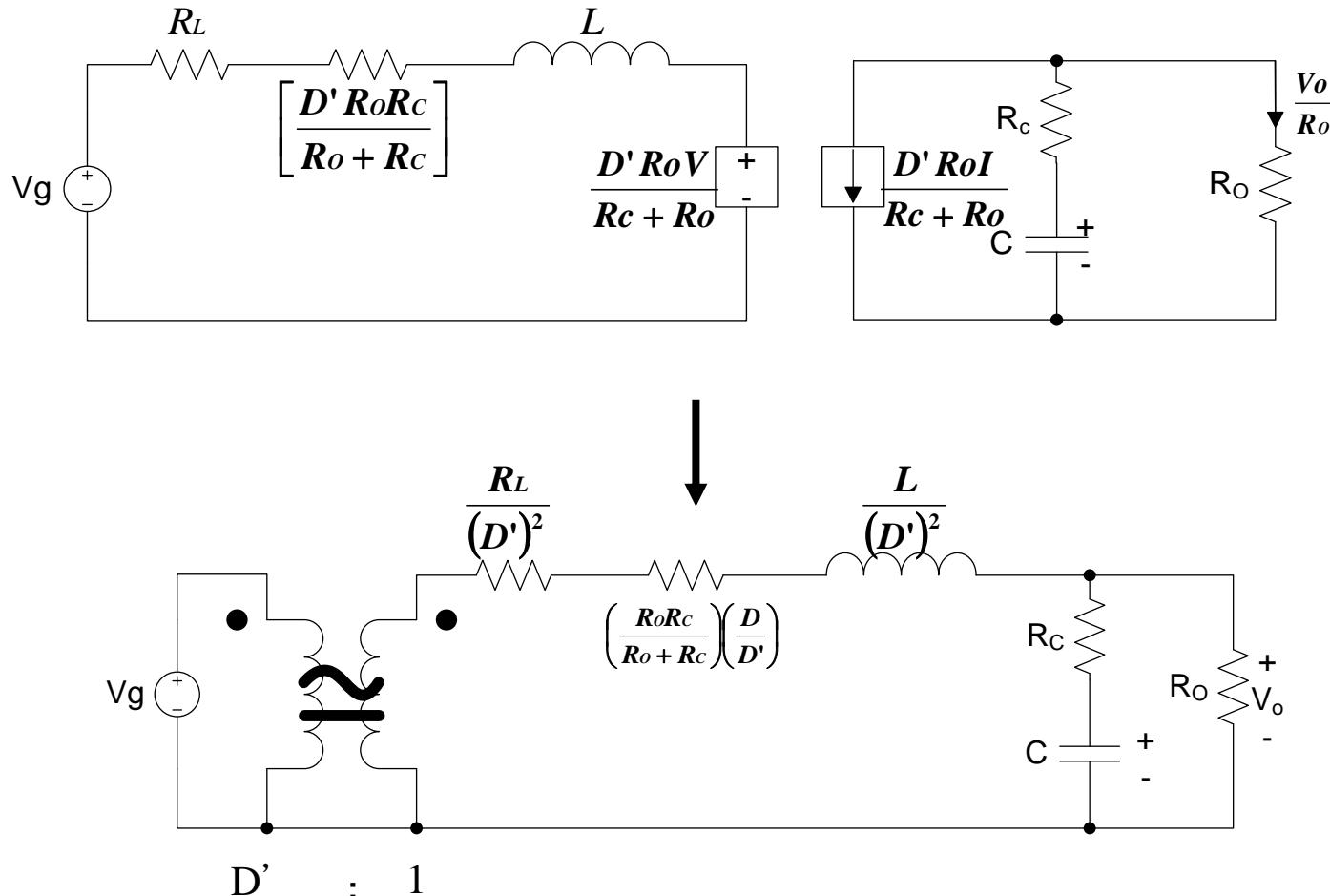

# Equivalent Circuits (2/2)

$$-\left(R_L + D' \frac{R_o R_c}{R_o + R_c}\right)I - \left(\frac{D' R_o}{R_o + R_c}\right)V + V_g = 0 \quad (1)$$

$$R_o D' I - V = 0; I = \frac{V}{R_o D'} \quad (2)$$

$$V_o = D' \left( \frac{R_o R_c}{R_o + R_c} \right) I + \left( \frac{R_o}{R_o + R_c} \right) V \quad (3)$$

$$I_i = I$$

$$V_o = V$$

$$V_g = \frac{R_L V}{R_o D'} + \frac{R_c V}{R_o + R_c} + \left( \frac{D' R_o}{R_o + R_c} \right) V \quad (2) \rightarrow (1)$$

$$V_g = V_o \left( \frac{R_L}{R_o D'} + \frac{R_c}{R_o + R_c} + \frac{D' R_o}{R_o + R_c} \right) \quad (2) \rightarrow (3)$$

$$\frac{V_o}{V_g} = \frac{1}{D'} \left[ \frac{1}{\frac{R_L}{R_o D'^2} + \frac{R_c}{(R_o + R_c) D'} + \frac{R_o}{R_o + R_c}} \right]$$

If  $R_o \gg R_c$ ;  $R_o \gg R_L$  then

$$\frac{V_o}{V_g} = \frac{1}{D'}$$

# Inductor and Capacitor

$$L \frac{\Delta I_L}{dt} = Vg$$

$$\Delta I_L = \frac{Vg}{L} DT_s$$

Solve for peak ripple

$$2\Delta I_L = \frac{Vg}{L} DT_s$$


The devices L calculated as follow :

$$L = \frac{VgDT_s}{2\Delta I_L}$$

$$\frac{dvc}{dt} = \frac{ic}{C} = \frac{-Vo}{RC} = \frac{I}{C} - \frac{V}{RC}$$

The devices C calculated as follow :

$$C = \frac{VDT_s}{2RAVo}$$

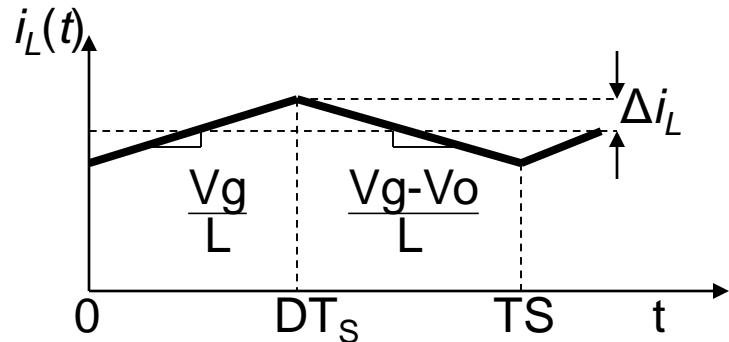

# Transient Steady

- Perturbation and linearization
- State-space averaging
- Simplified analysis of PWM converters using model of PWM switch

# Perturbation and Linearization

The averaged converterequations **(1/4)**

$$L \frac{di}{dt} = -\left( R_L + d' \frac{RoR_C}{Ro + R_C} \right) i - \left( \frac{d' Ro}{Ro + R_C} \right) v + v_g$$

$$C \frac{dv}{dt} = \frac{d' Ro}{Ro + R_C} i - \frac{v}{Ro + R_C}$$

$$v_o = d' \left( \frac{RoR_C}{Ro + R_C} \right) i + \left( \frac{Ro}{Ro + R_C} \right) v$$

$$i_i = i$$

Next step: perturbation and linearization.

$$\langle Vg(t) \rangle_{Ts} = Vg + \hat{v}_g$$

$$d(t) = D + \hat{d}$$

$$\langle i(t) \rangle_{Ts} = I + \hat{i}$$

$$\langle v(t) \rangle_{Ts} = V + \hat{v}$$

$$\langle i_i(t) \rangle_{Ts} = I_i + \hat{i}_i$$

$$d' = 1 - (D + \hat{d}) = D' - \hat{d}$$

Substitution to the averaged converterequations

# Perturbation and Linearization (2/4)

Perturbation of the averaged inductor equation

$$\begin{aligned}
 L \frac{d(I + \hat{i})}{dt} &= -\left( R_L + \left( D' - \hat{d} \left( \frac{RoRc}{Ro + Rc} \right) \right) (I + \hat{i}) - \left( \frac{(D' - \hat{d})Ro}{Ro + Rc} \right) (V + \hat{v}) + Vg + \hat{v}_g \right. \\
 &= -IR_L - \hat{i}R_L - D' \left( \frac{RoRc}{Ro + Rc} \right) I + \hat{d} \left( \frac{RoRc}{Ro + Rc} \right) I - D' \left( \frac{RoRc}{Ro + Rc} \right) \hat{i} + \hat{d} \left( \frac{RoRc}{Ro + Rc} \right) \hat{i} - \left( \frac{D'Ro}{Ro + Rc} \right) V + \left( \frac{\hat{d}(t)Ro}{Ro + Rc} \right) V - \left( \frac{D'Ro}{Ro + Rc} \right) \hat{v} + \left( \frac{\hat{d}Ro}{Ro + Rc} \right) \hat{v} + Vg + \hat{v}_g \\
 &= \underbrace{\left( Vg - IR_L - D' \left( \frac{RoRc}{Ro + Rc} \right) I - \left( \frac{D'Ro}{Ro + Rc} \right) V \right)}_{\text{Dc terms}} + \underbrace{\left( \hat{d} \left( \frac{RoRc}{Ro + Rc} \right) I - D' \left( \frac{RoRc}{Ro + Rc} \right) \hat{i} + \left( \frac{\hat{d}Ro}{Ro + Rc} \right) V - \left( \frac{D'Ro}{Ro + Rc} \right) \hat{v} + \hat{v}_g - \hat{i}R_L \right)}_{\text{1st order ac terms (linear)}} + \underbrace{\left( \hat{d} \left( \frac{RoRc}{Ro + Rc} \right) \hat{i} + \left( \frac{\hat{d}Ro}{Ro + Rc} \right) \hat{v} \right)}_{\text{2nd order ac terms (nonlinear)}}
 \end{aligned}$$

Upon discarding second-order terms, and removing dc terms (which add to zero), we are left with

$$\begin{aligned}
 L \frac{d\hat{i}}{dt} &= \left( \frac{\hat{d}RoRc}{Ro + Rc} \right) I + \left( \frac{\hat{d}Ro}{Ro + Rc} \right) V - \left( R_L + \frac{D'RoRc}{Ro + Rc} \right) \hat{i} - \left( \frac{D'Ro}{Ro + Rc} \right) \hat{v} + \hat{v}_g \\
 L \frac{d\hat{i}}{dt} &= - \left[ R_L + \frac{D'RoRc}{Ro + Rc} \right] \hat{i} - \left[ \frac{D'Ro}{Ro + Rc} \right] \hat{v} + \left[ \left( \frac{RoRc}{Ro + Rc} \right) I + \left( \frac{Ro}{Ro + Rc} \right) V \right] \hat{d} + \hat{v}_g
 \end{aligned}$$

# Perturbation and Linearization (3/4)

Perturbation of the averaged capacitor equation

$$\begin{aligned} C \frac{d(V + \hat{v})}{dt} &= \left( \frac{(D' - \hat{d})R_o}{R_o + R_c} \right) (I + \hat{i}) - \frac{(V + \hat{v})}{R_o + R_c} \\ &= \underbrace{\left( \frac{D'R_o}{R_o + R_c} I - \frac{V}{R_o + R_c} \right)}_{DC \text{ terms}} + \underbrace{\left( \frac{D'R_o}{R_o + R_c} \hat{i} - \frac{\hat{d}R_o}{R_o + R_c} I - \frac{\hat{v}}{R_o + R_c} \right)}_{\substack{1st \text{ order ac terms} \\ (linear)}} - \underbrace{\left( \frac{\hat{d}R_o}{R_o + R_c} \hat{i} \right)}_{\substack{2nd \text{ order ac terms} \\ (nonlinear)}} \end{aligned}$$

Upon discarding second-order terms, and removing dc terms (which add to zero), we are left with

$$C \frac{d\hat{v}}{dt} = \left( \frac{D'R_o}{R_o + R_c} \right) \hat{i} - \left( \frac{1}{R_o + R_c} \right) \hat{v} - \left( \frac{IR_o}{(R_o + R_c)} \right) \hat{d}$$

# Perturbation and Linearization (4/4)

Perturbation of the average input current and output voltage

$$\begin{aligned} V_O + \hat{v}_o &= \left( D' - \hat{d} \left( \frac{RoR_C}{Ro + R_C} \right) \right) (I + \hat{i}) + \left( \frac{Ro}{Ro + R_C} \right) (V + \hat{v}) \\ &= \underbrace{\left( \frac{D'(RoR_C)}{Ro + R_C} I + \frac{RoV}{Ro + R_C} \right)}_{DC \quad terms} + \underbrace{\frac{D'(RoR_C)}{Ro + R_C} \hat{i}}_{1nd \quad order} - \underbrace{\frac{\hat{d}(RoR_C)}{Ro + R_C} I}_{ac \quad terms} + \underbrace{\frac{Ro\hat{v}}{Ro + R_C}}_{2nd \quad order} - \underbrace{\left( \frac{\hat{d}(RoR_C)}{Ro + R_C} \hat{i} \right)}_{ac \quad terms \atop (nonlinear)} \end{aligned}$$

Upon discarding second-order terms, and removing dc terms (which add to zero), we are left with

$$\hat{v}_o = \left[ \frac{D'(RoR_C)}{Ro + R_C} \right] \hat{i} + \left[ \frac{Ro}{Ro + R_C} \right] \hat{v} - \left[ \frac{IRoR_C}{(Ro + R_C)} \right] \hat{d}$$

$$I_i + \hat{i}_i = I + \hat{i}$$

removing dc terms

$$\hat{i}_i = \hat{i}$$

# Small-Signal AC Equations


$$L \frac{d\hat{i}}{dt} = - \left[ R_L + \frac{D'RoR_C}{R_o + R_C} \right] \hat{i} - \left[ \frac{D'Ro}{R_o + R_C} \right] \hat{v} + \left[ \left( \frac{RoR_C}{R_o + R_C} \right) I + \left( \frac{Ro}{R_o + R_C} \right) V \right] \hat{d} + \hat{v}_g$$

$$C \frac{d\hat{v}}{dt} = \left[ \frac{D'Ro}{R_o + R_C} \right] \hat{i} - \left[ \frac{1}{R_o + R_C} \right] \hat{v} - \left[ \frac{IRo}{(R_o + R_C)} \right] \hat{d}$$

$$\hat{v}_o = \left[ \frac{D'(RoR_C)}{R_o + R_C} \right] \hat{i} + \left[ \frac{Ro}{R_o + R_C} \right] \hat{v} - \left[ \frac{IRoR_C}{(R_o + R_C)} \right] \hat{d}$$

$$\hat{i}_i = \hat{i}$$


# State-Space Averaging (1/13)

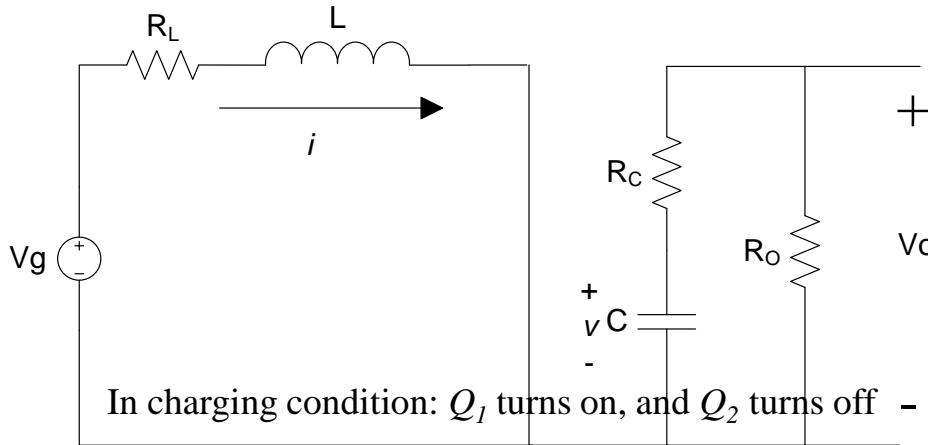

$$L \frac{di}{dt} = V_g - iR_L \quad \frac{di}{dt} = \frac{V_g}{L} - \frac{iR_L}{L} \quad (1)$$

$$C \frac{dv}{dt} = -\left( \frac{v}{R_c + R_o} \right) \quad \frac{dv}{dt} = -\left( \frac{v}{(R_c + R_o)C} \right) \quad (2)$$
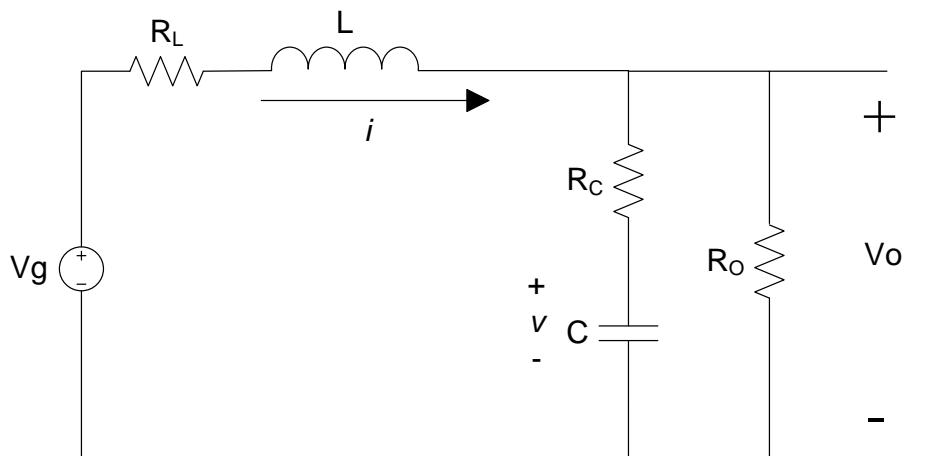
$$V_o = \left( \frac{R_o}{R_c + R_o} \right) v \quad (3)$$



$$L \frac{di}{dt} = \left( R_L + \frac{R_o R_c}{R_o + R_c} \right) i - \left( \frac{R_o}{R_o + R_c} \right) v + V_g$$

$$C \frac{dv}{dt} = \left( \frac{R_o}{R_o + R_c} \right) i - \frac{v}{R_o + R_c}$$

$$\frac{di}{dt} = \left( \frac{R_L + \frac{R_o R_c}{R_o + R_c}}{L} \right) i - \frac{1}{L} \left( \frac{R_o}{R_o + R_c} \right) v + \frac{V_g}{L} \quad (4)$$

$$\frac{dv}{dt} = \left[ \frac{R_o}{(R_o + R_c)C} \right] i - \frac{v}{(R_o + R_c)C} \quad (5)$$

$$V_o = \left( \frac{R_o R_c}{R_o + R_c} \right) i - \left( \frac{R_o}{R_o + R_c} \right) v \quad (6)$$

# State-Space Averaging (2/13)

We change equ.(1), (2) and (3) into state space functions:

$$\begin{aligned}\dot{x} &= A_1 x + B_1 u & \underline{x^T} &= \begin{bmatrix} i & v \end{bmatrix} & \underline{u^T} &= \begin{bmatrix} V_g \end{bmatrix} & \underline{y^T} &= \begin{bmatrix} V_o \end{bmatrix} \\ y &= C_1 x + E_1 u & \text{state vector} & \text{input vector} & \text{output vector} \\ & & A \longrightarrow \text{System Matrix} & B \longrightarrow \text{Input Matrix} \\ & & C \longrightarrow \text{Output Matrix} & E \longrightarrow \text{Feedforward Matrix}\end{aligned}$$

D is replace of E, so we don't confuse about duty and feedforward Matrix

The state equation is as follows

$$\begin{aligned}\dot{x} &= \begin{bmatrix} \dot{i} \\ \dot{v} \end{bmatrix} = \begin{bmatrix} -\frac{R_L}{L} & 0 \\ 0 & -\left[ \frac{1}{(R_C + R_O)C} \right] \end{bmatrix} \cdot \begin{bmatrix} i \\ v \end{bmatrix} + \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} \cdot \begin{bmatrix} V_g \end{bmatrix} = A_1 x + B_1 u \\ y &= \begin{bmatrix} V_o \end{bmatrix} = \begin{bmatrix} 0 & \frac{R_O}{R_C + R_O} \end{bmatrix} \cdot \begin{bmatrix} i \\ v \end{bmatrix} + [0] \cdot \begin{bmatrix} V_g \end{bmatrix} = C_1 x\end{aligned}$$

the constant vectors are

$$A_1 = \begin{bmatrix} -\frac{R_L}{L} & 0 \\ 0 & -\left[ \frac{1}{(R_C + R_O)C} \right] \end{bmatrix} \quad B_1 = \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} \quad C_1 = \begin{bmatrix} 0 & \frac{R_O}{R_C + R_O} \end{bmatrix}$$

# State-Space Averaging (3/13)

In the same way, We change equ.(4), (5) and (6) into state space functions:

$$\dot{x} = A_2 x + B_2 u$$

$$y = C_2 x$$

The state equation is as follows

$$\dot{x} = \begin{bmatrix} i \\ v \end{bmatrix} = \begin{bmatrix} -\frac{R_L + \frac{RoR_C}{R_C + Ro}}{L} & -\frac{Ro}{(R_C + Ro)L} \\ \frac{Ro}{(R_C + Ro)C} & -\left[ \frac{1}{(R_C + Ro)C} \right] \end{bmatrix} \cdot \begin{bmatrix} i \\ v \end{bmatrix} + \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} \cdot [V_g] = A_1 x + B_1 u$$

$$y = [V_o] = \begin{bmatrix} RoR_C \\ R_C + Ro \end{bmatrix} \cdot \begin{bmatrix} i \\ v \end{bmatrix} + [0] \cdot [V_g] = C_2 x$$

the constant vectors are

$$A_2 = \begin{bmatrix} -\frac{R_L + \frac{RoR_C}{R_C + Ro}}{L} & -\frac{Ro}{(R_C + Ro)L} \\ \frac{Ro}{(R_C + Ro)C} & -\left[ \frac{1}{(R_C + Ro)C} \right] \end{bmatrix} \quad B_2 = \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} \quad C_2 = \begin{bmatrix} RoR_C \\ R_C + Ro \end{bmatrix}$$

# State-Space Averaging (4/13)

Evaluate averaged matrices

$$A' = DA_1 + D'A_2$$

$$= D \cdot \begin{bmatrix} -\frac{R_L}{L} & 0 \\ 0 & -\left[ \frac{1}{(R_C + R_o)C} \right] \end{bmatrix} + D' \cdot \begin{bmatrix} \left( \frac{R_L + \frac{R_o R_C}{R_C + R_o}}{L} \right) & -\frac{R_o}{(R_C + R_o)L} \\ \frac{R_o}{(R_C + R_o)C} & -\left[ \frac{1}{(R_C + R_o)C} \right] \end{bmatrix}$$

$$= \begin{bmatrix} \left( \frac{R_L + D' \frac{R_o R_C}{R_C + R_o}}{L} \right) & -\left( \frac{R_o}{(R_C + R_o)L} \right) D' \\ \left( \frac{R_o}{(R_C + R_o)C} \right) D' & -\left[ \frac{1}{(R_C + R_o)C} \right] \end{bmatrix}$$

$$B' = DB_1 + D'B_2$$

$$= D \cdot \begin{bmatrix} \gamma_L \\ 0 \end{bmatrix} + D' \cdot \begin{bmatrix} \gamma_L \\ 0 \end{bmatrix} = \begin{bmatrix} \gamma_L \\ 0 \end{bmatrix}$$

$$C' = DC_1 + D'C_2$$

$$= D \begin{bmatrix} 0 & \frac{R_o}{R_C + R_o} \end{bmatrix} + D' \begin{bmatrix} \frac{R_o R_C}{R_C + R_o} & \frac{R_o}{R_C + R_o} \end{bmatrix}$$

$$= \begin{bmatrix} D' R_o R_C & R_o \\ R_C + R_o & R_C + R_o \end{bmatrix}$$

# State-Space Averaging (5/13)

The averaged (nonlinear) state equations :

$$\dot{\bar{x}} = \left( d(t) A_1 + d(t)' A_2 \right) \langle x(t) \rangle_{Ts} + \left( d(t) B_1 + d(t)' B_2 \right) \langle u(t) \rangle_{Ts}$$

$$\langle y(t) \rangle_{Ts} = \left( d(t) C_1 + d(t)' C_2 \right) \bar{x} + \left( d(t) E_1 + d(t)' E_2 \right) \langle u(t) \rangle_{Ts}$$

Let

$$\langle x(t) \rangle_{Ts} = \bar{X} + \hat{x}$$

$$\langle y(t) \rangle_{Ts} = \bar{Y} + \hat{y}$$

$$\langle u(t) \rangle_{Ts} = \bar{U} + \hat{u}$$

$$d(t) = D + \hat{d}$$

Dc terms drop out of equations. Second-order (nonlinear) terms are small when the small-signal assumption is satisfied. We are left with :

$$K \cdot \dot{\bar{x}} = A \cdot \bar{x} + B \cdot \bar{u} + [(A_1 - A_2)x + (B_1 - B_2)u] \hat{d}(t)$$

$$y = C \cdot \bar{x} + E \cdot \bar{u} + [(C_1 - C_2)x + (E_1 - E_2)u] \hat{d}(t)$$

This is the desired result.

# State-Space Averaging (6/13)

Evaluate matrices in small-signal model:

$$E = (A_1 - A_2)x + (B_1 - B_2)u$$

$$\begin{aligned}
 &= \begin{bmatrix} R_o R_C \\ -\frac{R_L}{L} + \frac{R_L + \frac{R_o R_C}{R_C + R_o}}{L} \\ 0 - \frac{R_o}{(R_C + R_o)C} \end{bmatrix} \begin{bmatrix} I \\ V \\ 0 \end{bmatrix} + \begin{bmatrix} \frac{1}{L} - \frac{1}{L} \\ 0 \end{bmatrix} V_g \\
 &= \begin{bmatrix} \frac{R_o R_C}{R_C + R_o} \\ \frac{R_o}{(R_C + R_o)L} \\ -\frac{R_o}{(R_C + R_o)C} \end{bmatrix} \begin{bmatrix} I \\ V \\ 0 \end{bmatrix} = \begin{bmatrix} \frac{(R_C + D' R_o)V}{D'(R_C + R_o)L} \\ \frac{V}{D'(R_C + R_o)C} \end{bmatrix} \quad (V = (D')R_O I)
 \end{aligned}$$

$$(C_1 - C_2)x + (E_1 - E_2)u$$

$$= \begin{bmatrix} 0 - \frac{R_o R_C}{R_C + R_o} & \frac{R_o}{R_C + R_o} - \frac{R_o}{R_C + R_o} \end{bmatrix} \begin{bmatrix} I \\ V \end{bmatrix}$$

$$= \left( -\frac{R_o R_C}{R_C + R_o} \right) I$$

# State-Space Averaging (7/13)

Small - signal ac state equations :

$$\begin{bmatrix} L & 0 \\ 0 & C \end{bmatrix} \begin{bmatrix} i \\ \dot{v} \end{bmatrix} = \begin{bmatrix} -\left( \frac{R_L + D' \frac{RoR_C}{R_C + Ro}}{L} \right) & \left( \frac{Ro}{(R_C + Ro)L} \right) D' \\ \left( \frac{Ro}{(R_C + Ro)C} \right) D' & -\left[ \frac{1}{(R_C + Ro)C} \right] \end{bmatrix} \begin{bmatrix} i \\ v \end{bmatrix} + \begin{bmatrix} \frac{V_g}{R_C} \\ 0 \end{bmatrix}$$

$$[V_o] = \begin{bmatrix} D'RoR_C & Ro \\ R_C + Ro & R_C + Ro \end{bmatrix} \begin{bmatrix} i \\ v \end{bmatrix}$$

Construction of ac equivalent circuit

Small - signal ac equations, in scalar form:

$$\frac{di}{dt} = -\left( \frac{R_L + D' \frac{RoR_C}{R_C + Ro}}{L} \right) i - \left( \frac{D'Ro}{(R_C + Ro)L} \right) v + \frac{1}{L} V_g + \left( \frac{(R_C + D'Ro)V}{D'(R_C + Ro)L} \right) d$$

$$\frac{dv}{dt} = \left[ \frac{D'Ro}{(R_C + Ro)C} \right] i - \left[ \frac{1}{(R_C + Ro)C} \right] v - \left[ \frac{IRo}{(R_C + Ro)C} \right] d$$

$$V_o = \left( \frac{D'RoR_C}{R_C + Ro} \right) i + \left( \frac{Ro}{R_C + Ro} \right) v - \left( \frac{IRoR_C}{R_C + Ro} \right) d$$

# State-Space Averaging (8/13)

Next, we transform the equivalent circuit small-signal ac equations into Laplace inductor equation

$$sL\hat{i}(s) = -\left(R_L + \frac{D'RoR_C}{R_C + R_O}\right)\hat{i}(s) - \left(\frac{D'Ro}{R_C + R_O}\right)\hat{v}(s) + \left(\frac{V(D'Ro + R_C)}{D'(R_C + R_O)}\right)\hat{d}(s) + v_g(s)$$
$$\left(sL + R_L + \frac{D'RoR_C}{R_C + R_O}\right)\hat{i}(s) + \left(\frac{D'Ro}{R_C + R_O}\right)\hat{v}(s) = \left(\frac{V(D'Ro + R_C)}{D'(R_C + R_O)}\right)\hat{d}(s) + v_g(s)$$

capacitor equation

$$sC\hat{v}(s) = \left(\frac{D'Ro}{R_C + R_O}\right)\hat{i}(s) - \frac{\hat{v}(s)}{R_C + R_O} - \left(\frac{IR_O}{R_C + R_O}\right)\hat{d}(s)$$

output equation

$$\hat{V}_O(s) = \left(\frac{D'RoR_C}{R_C + R_O}\right)\hat{i}(s) + \left(\frac{Ro}{R_C + R_O}\right)\hat{v}(s) - \left(\frac{IR_O R_C}{R_C + R_O}\right)\hat{d}(s)$$

# State-Space Averaging (9/13)

$$\begin{aligned}
 G_{vg}(s) &= \frac{\hat{V}_o(s)}{\hat{V}_g(s)} \Big|_{\substack{\hat{d}(s)=0 \\ \hat{i}_{load}=0}} = \frac{\hat{y}(s)}{\hat{u}(s)} \Big|_{\substack{\hat{d}(s)=0 \\ \hat{i}_{load}=0}} = C'(SI - A')^{-1}B' \\
 &= \begin{bmatrix} D'R_oR_c & R_o \\ R_c + R_o & R_c + R_o \end{bmatrix} \begin{bmatrix} S & 0 \\ 0 & S \end{bmatrix} - \begin{bmatrix} -\left(\frac{R_L}{L} + \frac{D'R_oR_c}{(R_c + R_o)L}\right) & -\left(\frac{R_o}{(R_c + R_o)L}\right)D' \\ \left(\frac{R_o}{(R_c + R_o)C}\right)D' & -\left[\frac{1}{(R_c + R_o)C}\right] \end{bmatrix}^{-1} \cdot \begin{bmatrix} \gamma_L \\ 0 \end{bmatrix} \\
 &= \begin{bmatrix} D'R_oR_c & R_o \\ R_c + R_o & R_c + R_o \end{bmatrix} \cdot \begin{bmatrix} S + \left(\frac{R_L}{L} + \frac{D'R_oR_c}{(R_c + R_o)L}\right) & \left(\frac{R_o}{(R_c + R_o)L}\right)D' \\ -\left(\frac{R_o}{(R_c + R_o)C}\right)D' & S + \left[\frac{1}{(R_c + R_o)C}\right] \end{bmatrix}^{-1} \cdot \begin{bmatrix} \gamma_L \\ 0 \end{bmatrix} \\
 \text{ps: } K &= \begin{bmatrix} a & b \\ c & d \end{bmatrix}, \quad K^{-1} = \frac{1}{ad - bc} \begin{bmatrix} d & -b \\ -c & a \end{bmatrix}
 \end{aligned}$$

# State-Space Averaging (10/13)

$$\begin{aligned}
G_{vg}(s) &= \frac{\hat{V}_o(s)}{\hat{V}_g(s)} \Big|_{\substack{\hat{d}(s)=0 \\ \hat{i}_{load}=0}} = \frac{\hat{y}(s)}{\hat{u}(s)} \Big|_{\substack{\hat{d}(s)=0 \\ \hat{i}_{load}=0}} = C'(SI - A')^{-1} B' \\
&= \frac{\frac{Ro}{Rc + Ro}}{S^2 + \frac{S \left[ \left( \frac{R_L}{Rc + Ro} + D' Ro R_C \right) C + L \right] + R_L + D' \frac{Ro R_C}{Rc + Ro} + \left( \frac{D' Ro}{Rc + Ro} \right)^2}{LC(Rc + Ro)}} \cdot [D' R_C \quad 1] \cdot \begin{bmatrix} S + \left[ \frac{1}{(Rc + Ro)C} \right] & \left( \frac{Ro}{(Rc + Ro)L} \right) D' \\ - \left( \frac{Ro}{(Rc + Ro)C} \right) D' & S + \left( \frac{R_L}{L} + \frac{D' Ro R_C}{(Rc + Ro)L} \right) \end{bmatrix} \cdot \begin{bmatrix} \gamma_L \\ 0 \end{bmatrix} \\
\text{Let } R' &= R_L + D' \frac{Ro R_C}{Rc + Ro} + \left( \frac{D'^2 Ro^2}{Rc + Ro} \right) \\
&= \frac{\frac{Ro}{Rc + Ro}}{S^2 + \frac{S \left[ \left( \frac{R_L}{Rc + Ro} + D' Ro R_C \right) C + L \right] + R'}{LC(Rc + Ro)}} \cdot \left[ \frac{D'}{C} \left( SR_C C + 1 \right) \quad \left( \frac{(D')^2 R_C R_O}{(R_C + R_O)L} \right) - S - \left( \frac{R_L}{L} + \frac{D' Ro R_C}{(Rc + Ro)L} \right) \right] \cdot \begin{bmatrix} \gamma_L \\ 0 \end{bmatrix} \\
&= \frac{\frac{Ro}{Rc + Ro} [D' (SR_C C + 1)] \frac{1}{L}}{S^2 + \frac{S \left[ \left( \frac{R_L}{Rc + Ro} + D' Ro R_C \right) C + L \right] + R'}{LC(Rc + Ro)}} = \frac{D' Ro [R_C S C + 1]}{(R_C + R_O) L C S^2 + S [(R_C + R_O) R_L + D' Ro R_C] C + L + R'}
\end{aligned}$$

# State-Space Averaging (11/13)

$$\begin{aligned}
G_{vd}(s) &= \frac{\hat{V}_o(s)}{\hat{d}(s)} \Bigg|_{\substack{\hat{V}_g(s)=0 \\ \hat{i}_{load}=0}} = \frac{\hat{y}(s)}{\hat{d}(s)} \Bigg|_{\substack{\hat{V}_g(s)=0 \\ \hat{i}_{load}=0}} = C'(SI - A')^{-1} E \\
&= \begin{bmatrix} D'RoRc & Ro \\ R_c + Ro & R_c + Ro \end{bmatrix} \begin{bmatrix} S & 0 \\ 0 & S \end{bmatrix} - \begin{bmatrix} -\left(\frac{R_L}{L} + \frac{D'RoRc}{(R_c + Ro)L}\right) & -\left(\frac{Ro}{(R_c + Ro)L}\right)D' \\ \left(\frac{Ro}{(R_c + Ro)C}\right)D' & -\left[\frac{1}{(R_c + Ro)C}\right] \end{bmatrix}^{-1} \cdot \begin{bmatrix} \left(\frac{(R_c + D'Ro)V}{D'(R_c + Ro)L}\right) \\ \left(-\frac{V}{D'(R_c + Ro)C}\right) \end{bmatrix} \\
&= \frac{LCRo}{LC(R_c + Ro)S^2 + S\left[\left(\frac{R_L}{R_c + Ro} + D'RoRc\right)C + L\right] + R'} \begin{bmatrix} \frac{D'}{C}(SRcC + 1) & \left(\frac{(D')^2 R_c Ro}{(R_c + Ro)L}\right) - S - \left(\frac{R_L}{L} + \frac{D'RoRc}{(R_c + Ro)L}\right) \\ \left(\frac{(R_c + D'Ro)V}{D'(R_c + Ro)L}\right) \\ \left(-\frac{V}{D'(R_c + Ro)C}\right) \end{bmatrix} \\
&= \frac{\left(\frac{V}{D'}\right)(SRcC + 1) \left[ \left(\frac{Ro}{R_c + Ro}\right) \left[ \left(\frac{D'RoRc + (D')^2}{R_c + Ro}\right) - \frac{D'RoRc - (D')^2 R_c Ro}{R_c + Ro} \right] - SL - R_L \right]}{LC(R_c + Ro)S^2 + S\left[\left(\frac{R_L}{R_c + Ro} + D'RoRc\right)C + L\right] + R'} \\
&= \frac{\left(\frac{V}{D'}\right) \left[ \left(\frac{(D')^2 Ro^2}{R_c + Ro} - R_L\right) (1 + SRcC) \left[ 1 - \frac{SL}{\left(\frac{(D')^2 Ro^2}{R_c + Ro} - R_L\right)} \right] \right]}{LC(R_c + Ro)S^2 + S\left[\left(\frac{R_L}{R_c + Ro} + D'RoRc\right)C + L\right] + R'}
\end{aligned}$$

# State-Space Averaging (12/13)

The output impedance  $Z_{out}(s)$  is

$$Z_{out}(s) = \frac{\hat{V}_{o1}(s)}{\hat{i}_{o1}(s)} = \frac{\hat{V}_{o1}(s)}{\hat{V}_g(s)} \Big/ \frac{\hat{i}_{o1}(s)}{\hat{V}_g(s)}$$

the output current is expressed

$$\hat{i}_o = \frac{i_L}{D'}$$

$$\hat{y}_1(s) = i_o(s) = \begin{bmatrix} 1 \\ D' & 0 \end{bmatrix} \begin{bmatrix} i_L(s) \\ V_C(s) \end{bmatrix} = C'' \hat{x}(s)$$

we substituted equ.(31) for the above equation,

$$\hat{y}_1(s) = C''^T (SI - A')^{-1} B' \hat{u}(s) + C''^T (SI - A')^{-1} E \hat{d}(s)$$

therefore,

$$Z_{out}(s) = \left. \frac{\hat{V}_i(s)}{\hat{i}_{load}(s)} \right|_{\substack{\hat{d}(s)=0 \\ \hat{V}_g=0}} = \left. \frac{\hat{y}_2(s)}{\hat{u}(s)} \right|_{\substack{\hat{d}(s)=0 \\ \hat{V}_g=0}}$$

# State-Space Averaging (13/13)

$$\frac{\hat{i}_{o1}(s)}{\hat{V}_g(s)} = \begin{bmatrix} \frac{1}{D'} & 0 \end{bmatrix} \begin{bmatrix} S & 0 \\ 0 & S \end{bmatrix} - \begin{bmatrix} -\left(\frac{R_L}{L} + \frac{D' R_o R_c}{(R_c + R_o)L}\right) & -\left(\frac{R_o}{(R_c + R_o)L}\right) D' \\ \left(\frac{R_o}{(R_c + R_o)C}\right) D' & -\left[\frac{1}{(R_c + R_o)C}\right] \end{bmatrix}^{-1} \cdot \begin{bmatrix} \cancel{\frac{1}{L}} \\ 0 \end{bmatrix}$$

$$= \frac{(SC(R_c + R_o) + 1) \cancel{\frac{1}{D'}}}{(R_c + R_o)LCS^2 + S[(Rc + Ro)R_L + D'R_oR_c)C + L] + R'}$$

$$Z_{out}(s) = \frac{\hat{V}_{o1}(s)}{\hat{i}_{o1}(s)} = \frac{\hat{V}_{o1}(s)}{\hat{V}_g(s)} \Big/ \frac{\hat{i}_{o1}(s)}{\hat{V}_g(s)}$$

$$= \frac{\frac{D'R_o[R_cSC + 1]}{(R_c + R_o)LCS^2 + S[(Rc + Ro)R_L + D'R_oR_c)C + L] + R'}}{\frac{(SC(R_c + R_o) + 1) \cancel{\frac{1}{D'}}}{(R_c + R_o)LCS^2 + S[(Rc + Ro)R_L + D'R_oR_c)C + L] + R'}}$$

$$= \frac{(D')^2 R_o [R_c SC + 1]}{SC(R_c + R_o) + 1}$$

# Equivalent Circuits

inductor equation



$$\left( sL + R_L + \frac{D'RoRc}{Rc + Ro} \right) \hat{i}(s) + \left( \frac{D'Ro}{Rc + Ro} \right) \hat{v}(s) \\ = \left( \frac{V(D'Ro + Rc)}{D'(Rc + Ro)} \right) \hat{d}(s) + v_g(s)$$




capacitor eqn


$$sC\hat{v}(s) = \left( \frac{D'Ro}{Rc + Ro} \right) \hat{i}(s) - \frac{\hat{v}(s)}{Rc + Ro} - \left( \frac{IRo}{Rc + Ro} \right) \hat{d}(s)$$

output eqn
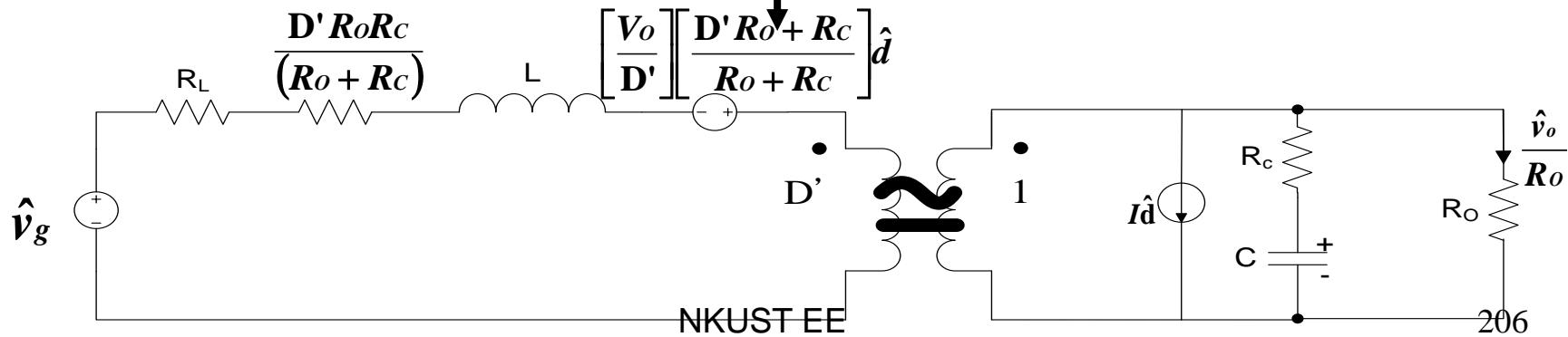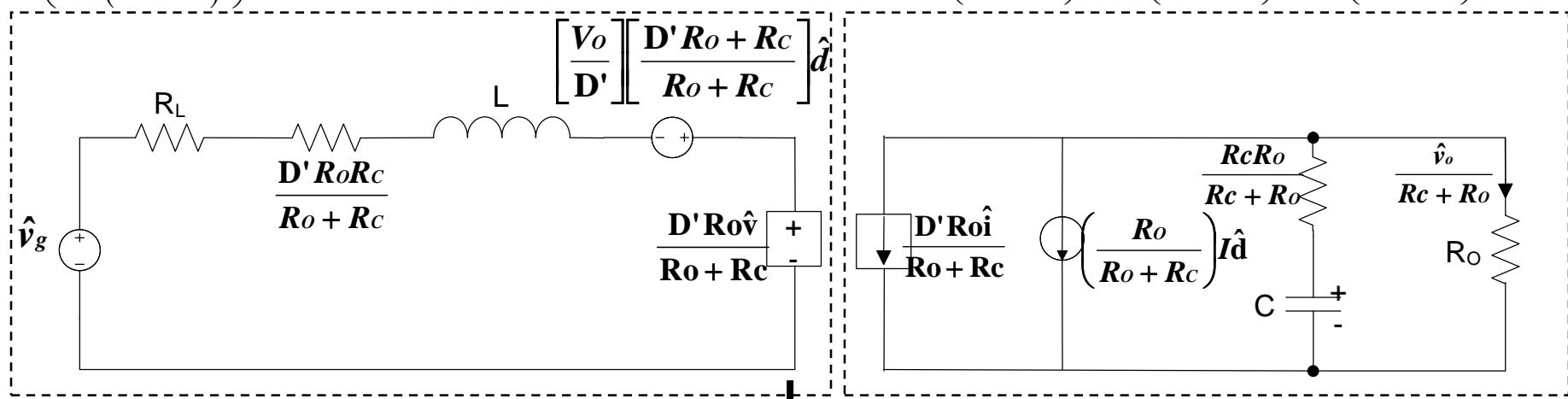
$$\hat{v}_o(s) = \left( \frac{D'RoRc}{Rc + Ro} \right) \hat{i}(s) + \left( \frac{Ro}{Rc + Ro} \right) \hat{v}(s) - \left( \frac{IRoRc}{Rc + Ro} \right) \hat{d}(s)$$



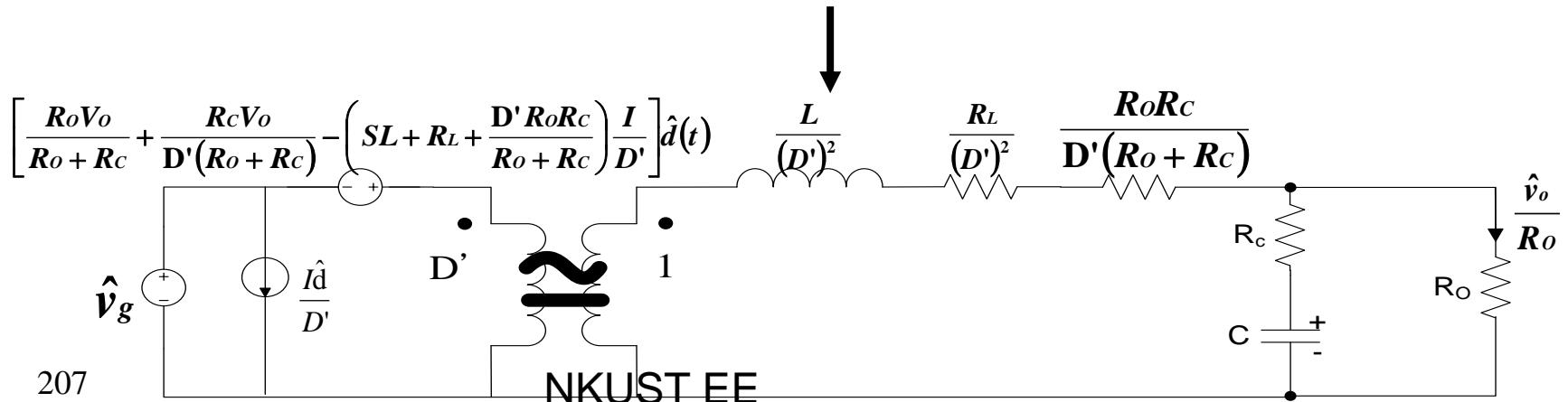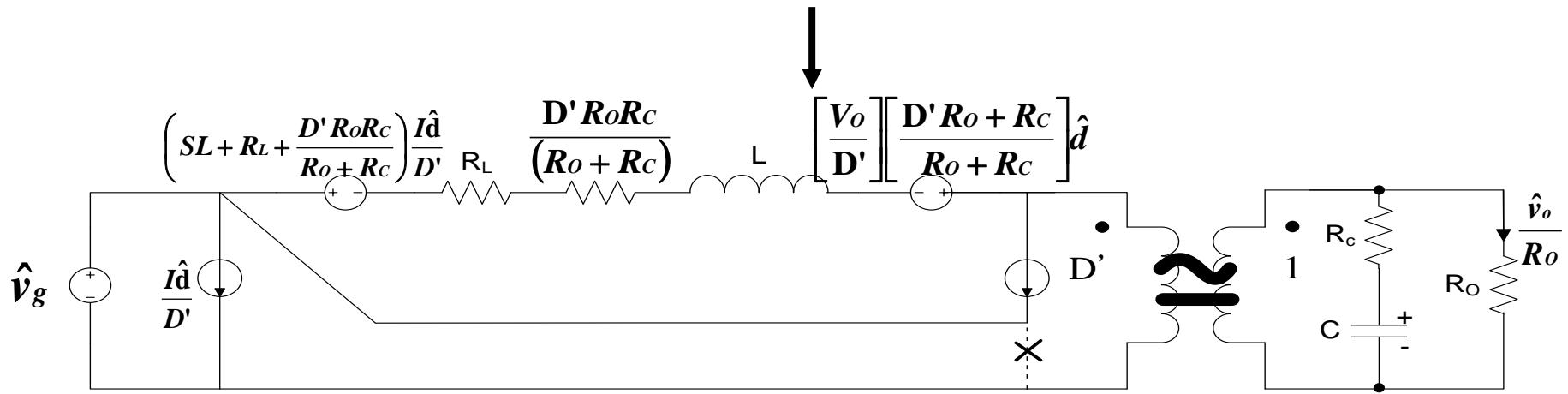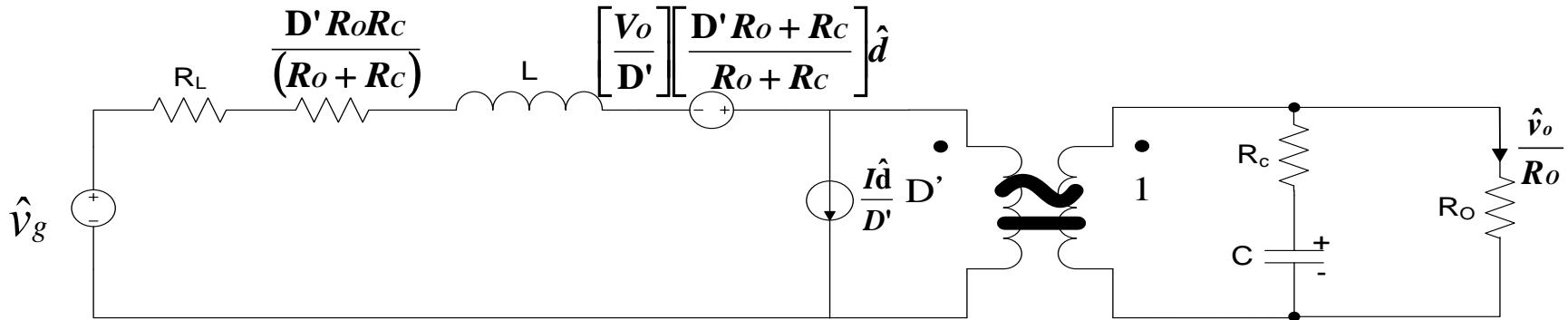

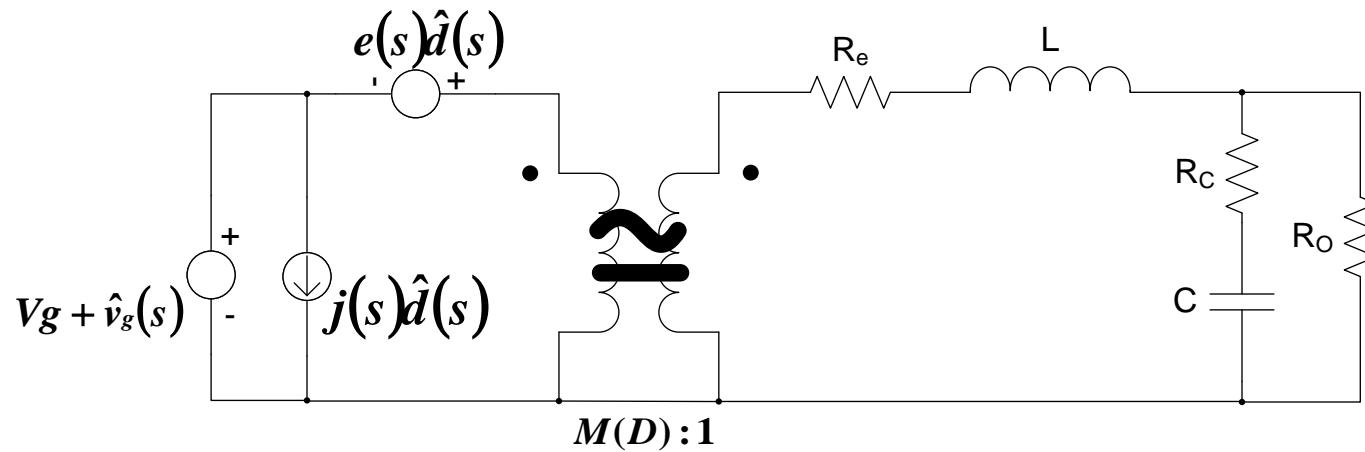

## Model parameters

$$e(s) = V_o \left[ \frac{R_o}{R_o + R_c} - \frac{R_L}{(D')^2 R_o} \right] \left[ 1 - \left( \frac{sL}{\frac{(D' R_o)^2}{R_o + R_c} - R_L} \right) \right]$$


$$j(s) = \frac{V_o}{(D')^2 R_o}$$

$$Le = \frac{L}{(D')^2}$$


$$R = \frac{R_L + (R_o // R_c) D D'}{(D')^2}$$

$$M(D) = D'$$


# PWM Modeling

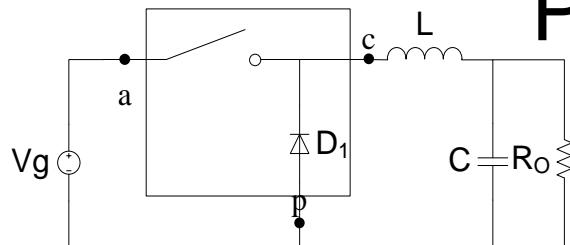


buck

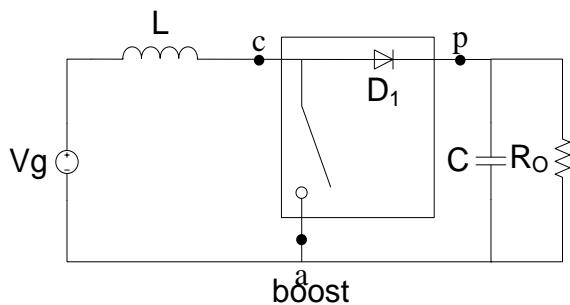


boost

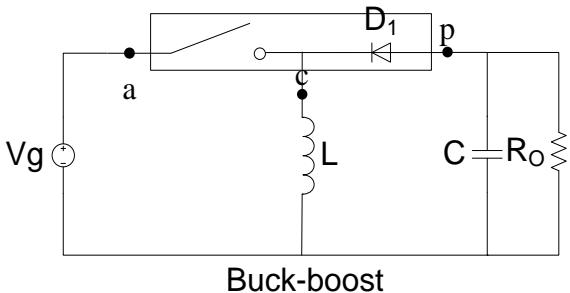

Buck-boost

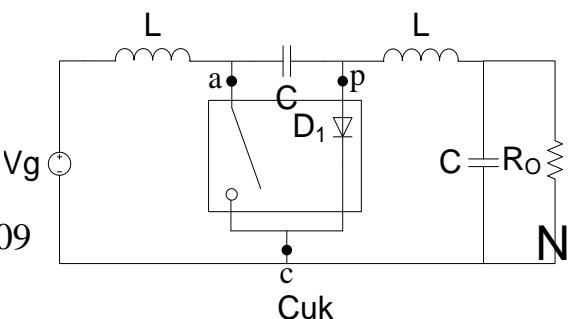


Cuk

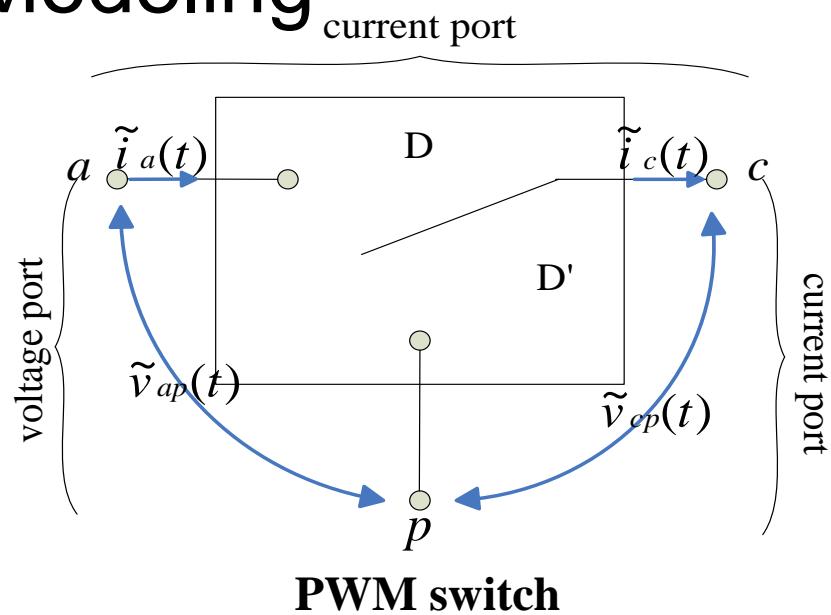

$$\tilde{i}_a = \begin{cases} \tilde{i}_c(t), & 0 \leq t \leq DT_s \\ 0, & DT_s \leq t \leq 2DT_s \end{cases}$$
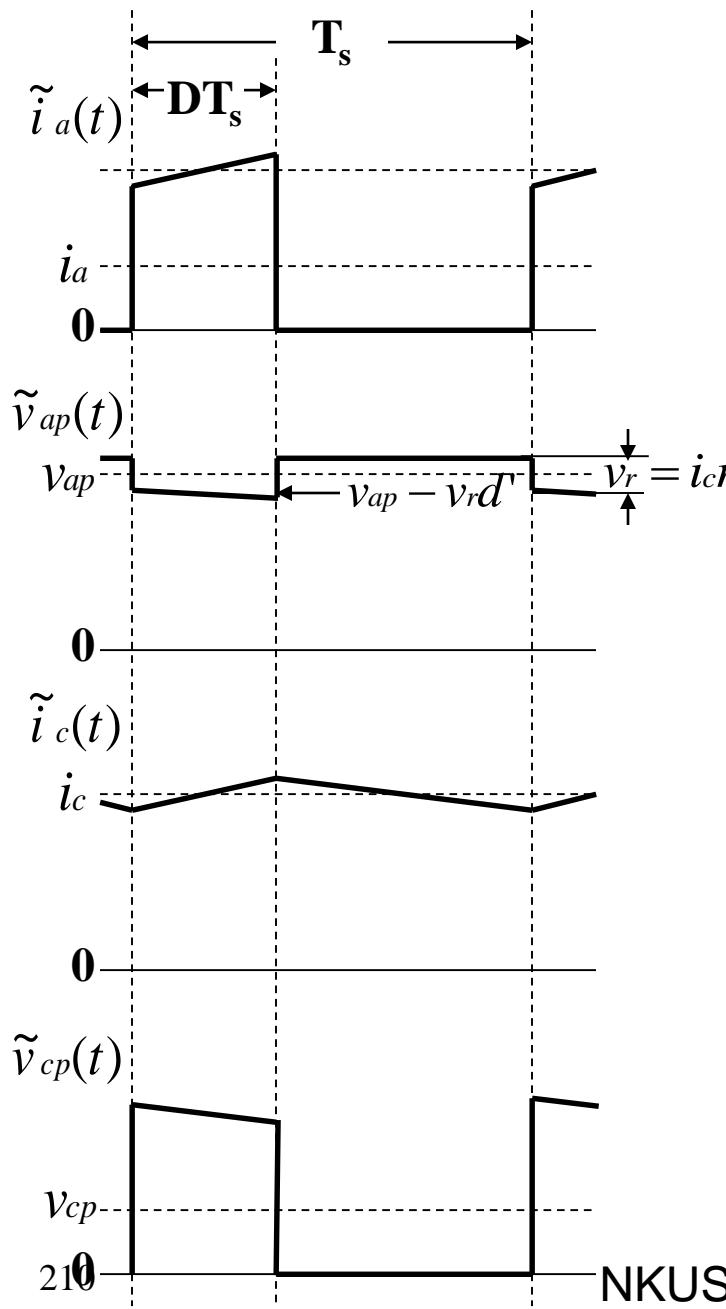
$$\tilde{v}_{cp} = \begin{cases} \tilde{v}_{ap}(t), & 0 \leq t \leq DT_s \\ 0, & DT_s \leq t \leq 2DT_s \end{cases}$$



$$v_r = i_c r_e$$

$$r_e = R_c \parallel R_o$$


$$r_e = R_c$$



(boost,buck - boost )

(Cuk )

$$i_a = di_c$$

$$v_{cp} = d(v_{ap} - i_c r_e d')$$

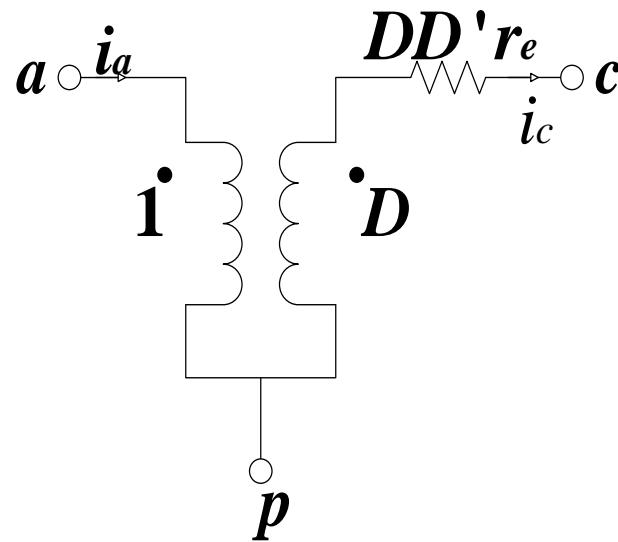

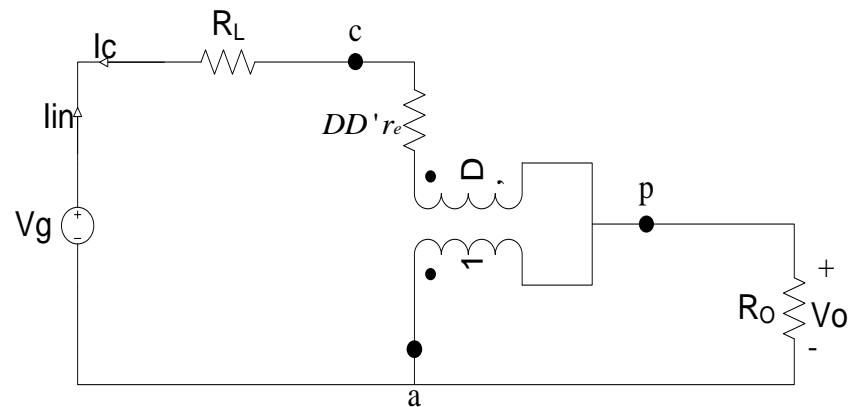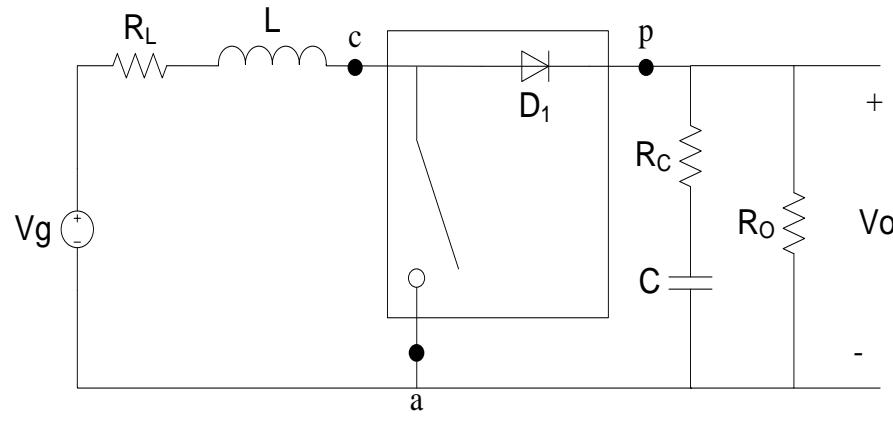

$$V_{ap} = -V_o$$

$$I_c = -I_{in} = -\frac{I_o}{D'}$$

$$M = \frac{V_o}{V_g}$$

$$= \frac{-V_{ap}}{-\frac{I_o}{D'}(R_L + r_e D D' + (D')^2 R_o)}$$

$$= \frac{I_o R_o}{\frac{I_o}{D'}(R_L + r_e D D' + (D')^2 R_o)}$$

$$= \frac{D' R_o}{(R_L + r_e D D' + (D')^2 R_o)}$$

$$= \frac{1}{D'} \frac{1}{1 + \frac{R_L}{(D')^2 R} + \frac{r_e D}{R D'}}$$

$$r_e = R_c \parallel R_o$$

$$i_a = d i_c$$

$$v_{cp} = d(v_{ap} - i_c r_e d')$$

*Perturbation and linearization*

$$\hat{i}_a = D \hat{i}_c + I_c \hat{d}$$


$$\hat{v}_{cp} = D(\hat{v}_{ap} + I_c r_e d' - \hat{i}_c r_e D') + \hat{d}(V_{ap} - I_c r_e D')$$

*which can be rearranged as*

$$\hat{v}_{ap} = \frac{\hat{v}_{cp}}{D} + \hat{i}_c r_e D' - [V_{ap} + I_c(D - D')r_e] \frac{\hat{d}}{D}$$

$$\text{let } V_D = V_{ap} + I_c(D - D')r_e$$
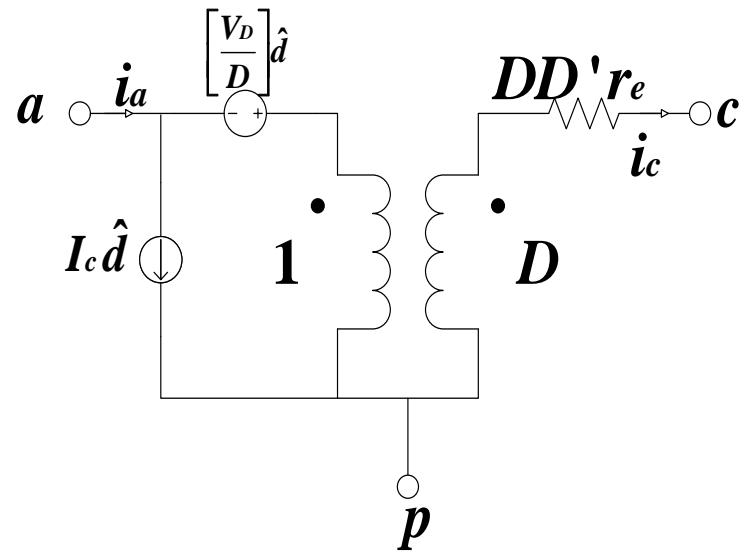
$$\hat{v}_{ap} = \frac{\hat{v}_{cp}}{D} + \hat{i}_c r_e D' - V_D \frac{\hat{d}}{D}$$



# Line Regulation


$$\frac{v_o(s)}{v_g(s)} = \frac{1}{D'} \frac{Ro \parallel \left( R_c + \frac{1}{sC} \right)}{\frac{(D')^2}{(D')^2} + sL + Ro \parallel \left( R_c + \frac{1}{sC} \right)}$$

$$= M \frac{(1 + s / s_{z1})}{1 + s / \omega_0 Q + s^2 / \omega_0^2}$$

$$s_{z1} = \frac{1}{R_c C}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \sqrt{\frac{R_L + r_e D' + (D')^2 Ro}{R_c + Ro}}$$
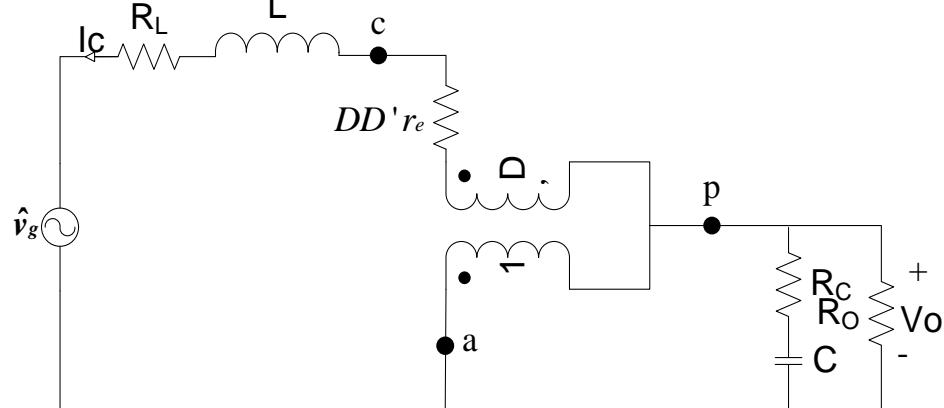
$$Q = \frac{\omega_0}{\frac{R_L + r_e D'}{L} + \frac{1}{C(R_c + Ro)}}$$




$$\frac{\hat{v}_o(s)}{\hat{d}(s)} = \frac{V_D}{D} \frac{Ro \parallel \left(Rc + \frac{1}{sC}\right)}{\frac{R_L + r_e DD'}{(D')^2} + sL + Ro \parallel \left(Rc + \frac{1}{sC}\right)} + I_c \left[ \left( \frac{R_L + r_e DD'}{(D')^2} + sL \right) \parallel Ro \parallel \left(Rc + \frac{1}{sC}\right) \right]$$

$$= K_d \frac{(1 + s / s_{z1})(1 + s / s_{z2})}{1 + s / \omega_0 Q + s^2 / \omega_0^2}$$

$$K_d = \frac{dV_o}{dD} = Vi \frac{dM}{dD} \cong \frac{Vi}{(D')^2}$$

$$s_{z2} = \frac{1}{L} \left( D' \frac{V_D}{I_c} - R_L - r_e DD' \right)$$
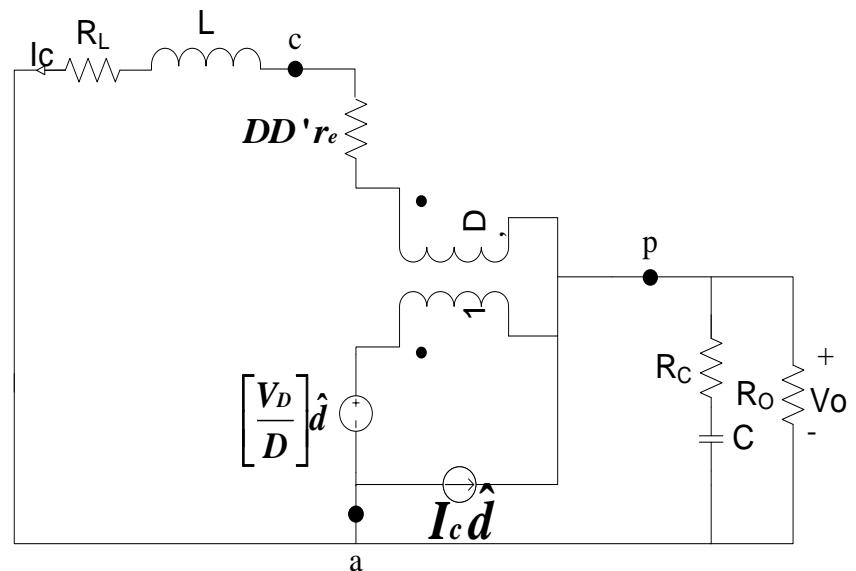
$$= \frac{(D')^2}{L} (Ro - Ro \parallel Rc) - \frac{R_L}{L}$$




# Load Regulation

$$\begin{aligned}
 Z_{out} &= \left( \frac{R_L + r_e DD'}{(D')^2} + \frac{sL}{D'} \right) \parallel \left( R_C + \frac{1}{sC} \right) \parallel R_o \\
 &= R' \frac{(1 + s/s_{z1})(1 + s/s_{z0})}{1 + s/\omega_0 Q + s^2/\omega_0^2}
 \end{aligned}$$

$$R' = R_o \parallel \frac{R_L + r_e DD'}{(D')^2}$$

$$s_{z0} = \frac{R_L + r_e DD'}{L}$$

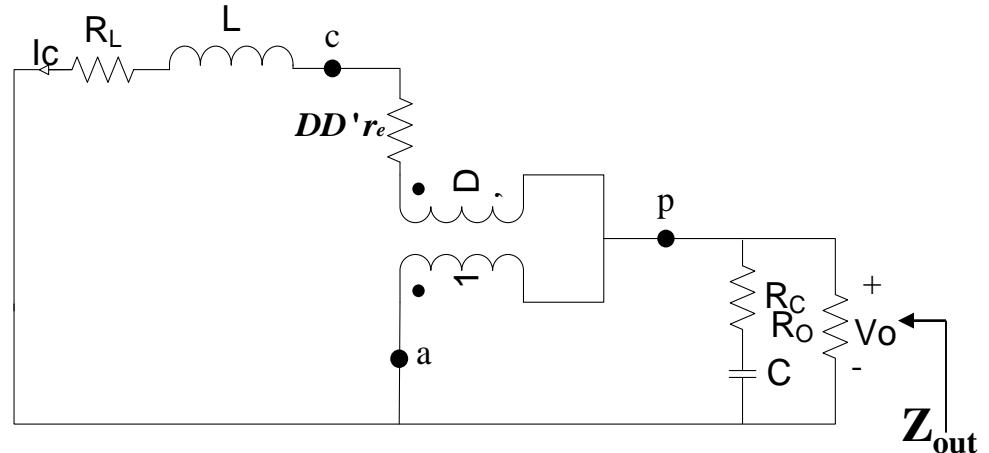

# Model parameters


$$e(s) = V_o \left[ \frac{R_o}{R_o + R_c} - \frac{R_L}{(D')^2 R_o} \right] \left[ 1 - \left( \frac{sL}{\frac{(D' R_o)^2}{R_o + R_c} - R_L} \right) \right]$$

$$j(s) = \frac{V_o}{(D')^2 R_o}$$

$$Le = \frac{L}{(D')^2}$$

$$R = \frac{R_L + (R_o // R_c) D D'}{(D')^2}$$


$$M(D) = D'$$

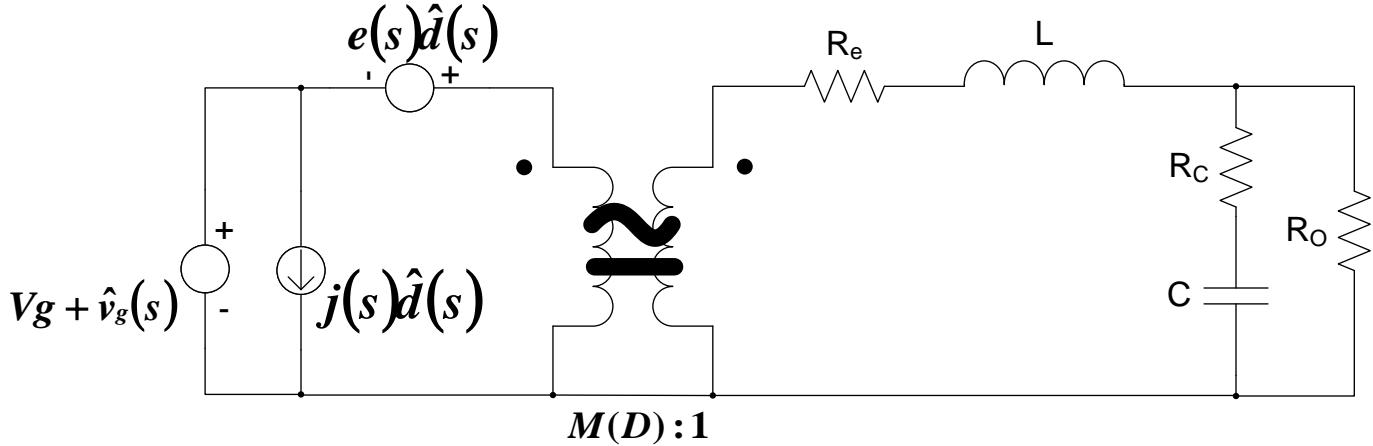

$$\hat{v}_{ap} = \frac{\hat{v}_{cp}}{D} + \hat{i}_c r_e D' - [V_{ap} + I_c(D - D')r_e] \frac{\hat{d}}{D}$$

$$\text{let } V_D = V_{ap} + I_c(D - D')r_e$$
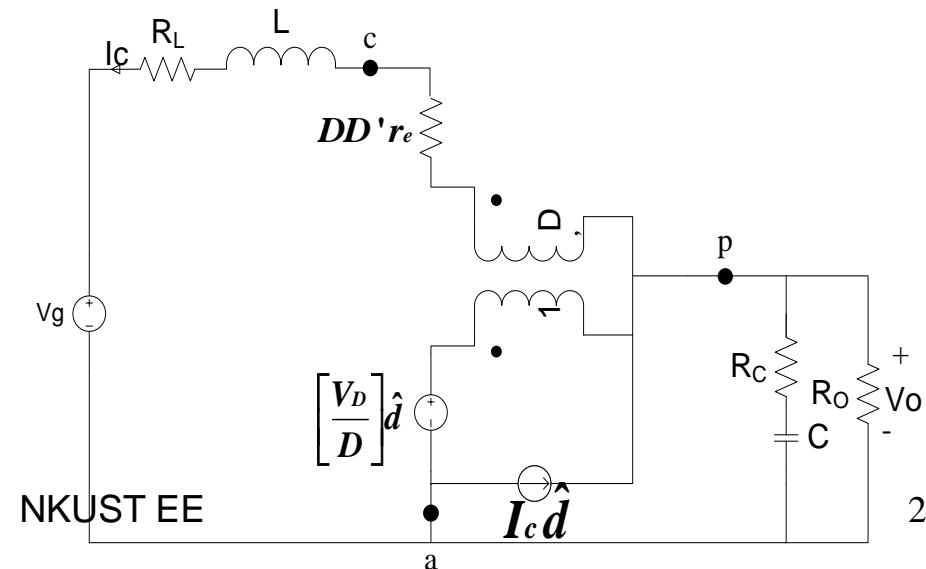
$$\hat{v}_{ap} = \frac{\hat{v}_{cp}}{D} + \hat{i}_c r_e D' - V_D \frac{\hat{d}}{D}$$



NKUST EE

216

# Perturbation and Linearization

1. The averaged converter equations
2. perturbation and linearization
3. Small-signal ac equations
4. Small-signal ac equivalent circuits
5. Calculate converter transfer function

Complex calculation

Easy understand

# State-Space Averaging

1. The averaged converter equations
2. Change equation into state space functions and set up varied
3. Evaluate averaged matrices
4. Calculate converter transfer function

Matrices calculate easily

It is not necessary to build equivalent circuits


# Simplified Analysis of PWM Converters

## Using Model of PWM Switch

1. Model of PWM switch
2. Substitution converter
3. Calculate converter transfer function

Fast modeling

# Lead (PD) Compensator

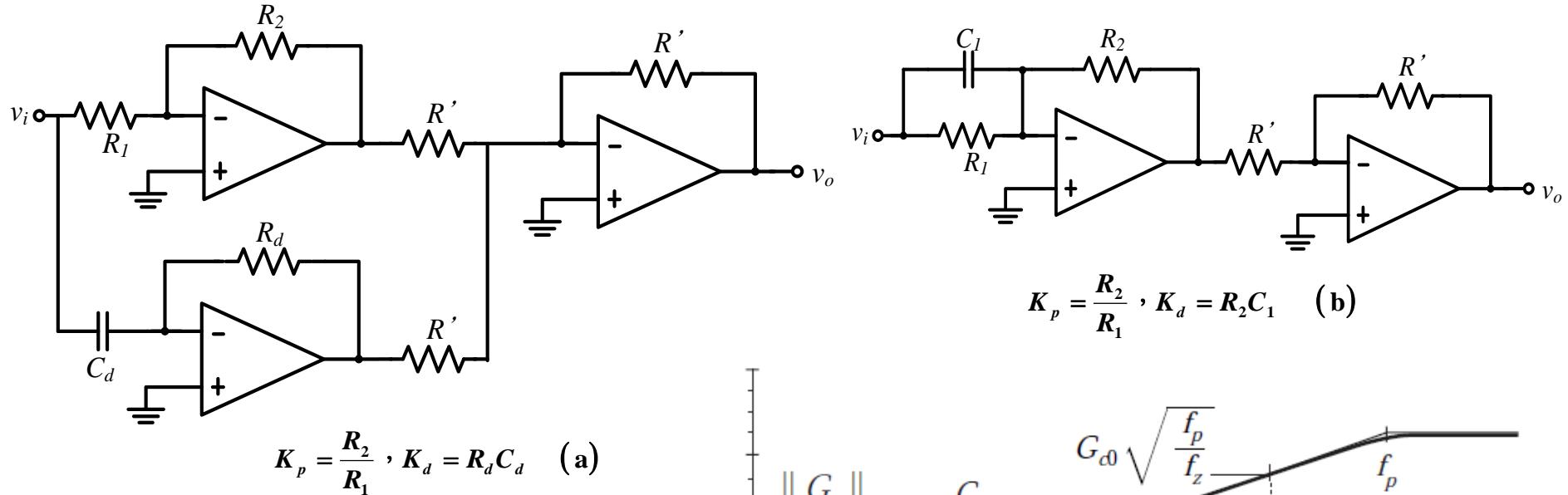


$$G_c = \frac{v_o(s)}{v_i(s)} = K_p + K_d s$$


$$= G_{c0} \frac{(1 + s/\omega_z)}{(1 + s/\omega_p)}$$

$$\qquad \qquad \qquad f_z/10 \qquad \qquad \qquad f_p/10$$
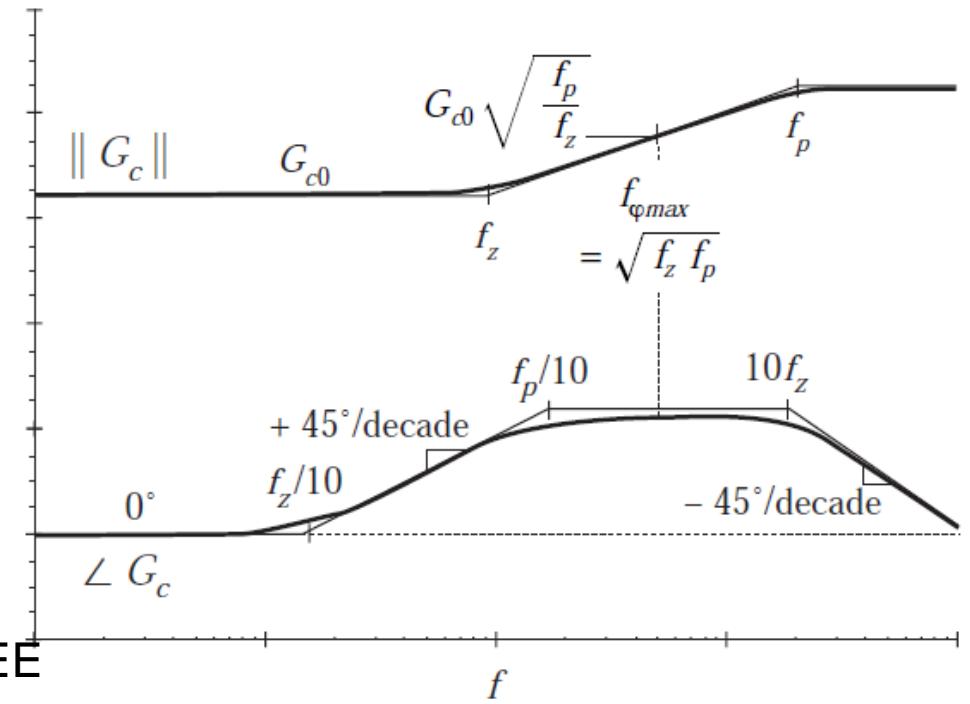
$$\qquad \qquad \qquad + 45^\circ/\text{decade} \qquad \qquad \qquad - 45^\circ/\text{decade}$$




# Lead-Lag Compensator

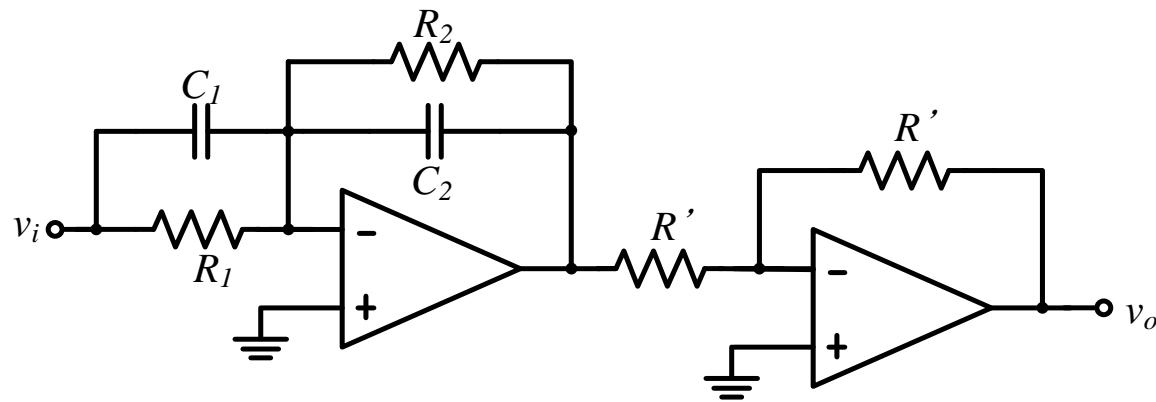


$$G_c = \frac{v_o(s)}{v_i(s)} = K_c \frac{(s + z_L)}{(s + p_L)}$$

# Lag (PI) Compensator

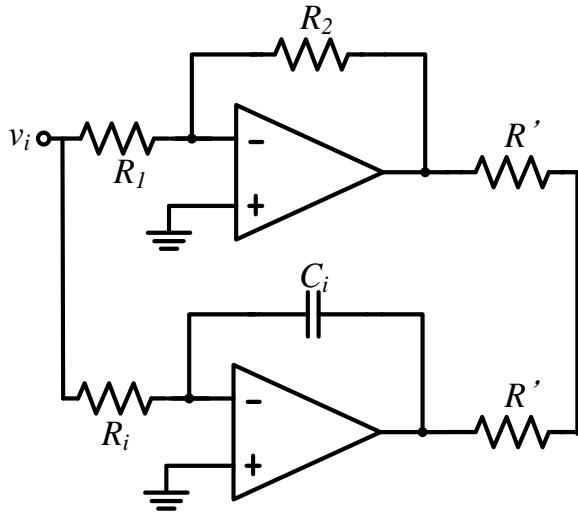


$$K_p = \frac{R_2}{R_1}, K_i = \frac{1}{R_i C_i} \quad (\text{a})$$

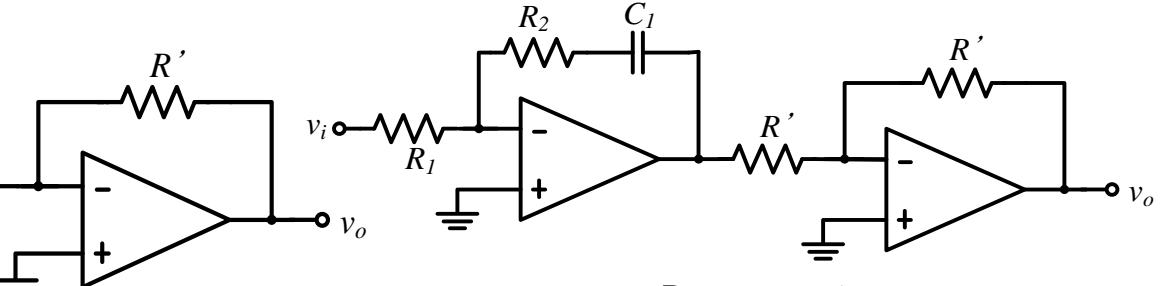
$$\begin{aligned} G_c &= \frac{v_o(s)}{v_i(s)} = K_p + K_i/s \\ &= G_{c\infty} (1 + \omega_l / s) \end{aligned}$$


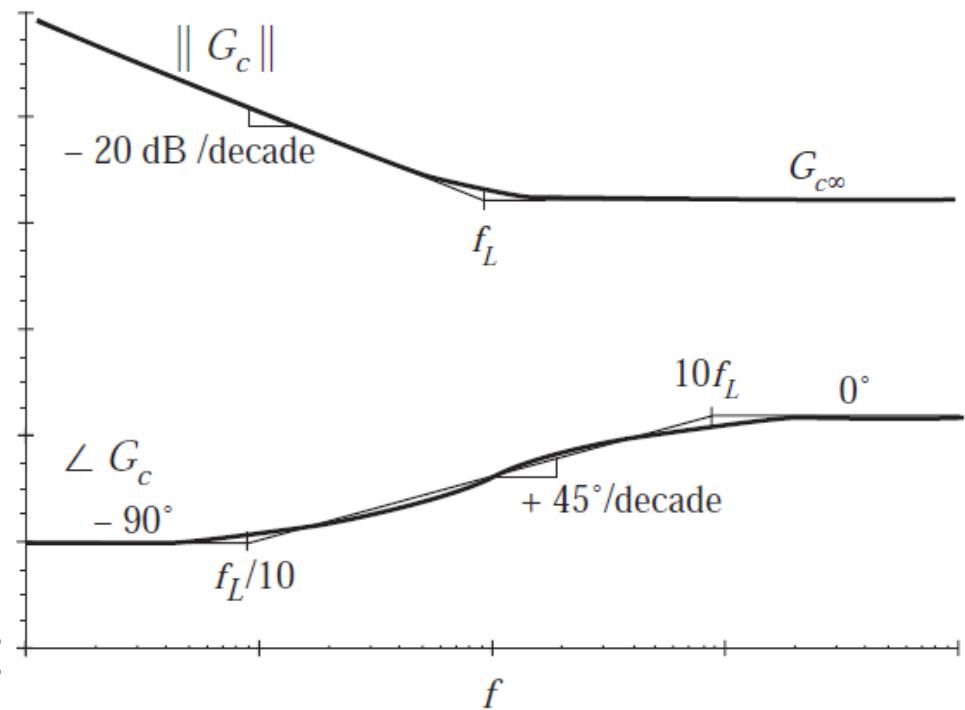
$$K_p = \frac{R_2}{R_1}, K_i = \frac{1}{R_1 C_1} \quad (\text{b})$$




# Combined (PID) Compensator

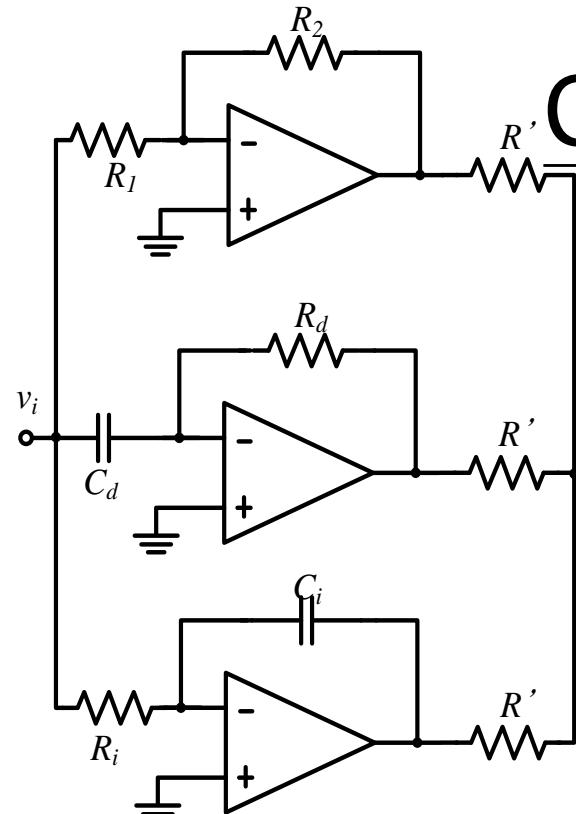


$$K_p = \frac{R_2}{R_1}, K_i = \frac{1}{R_i C_i} \quad (\text{a})$$

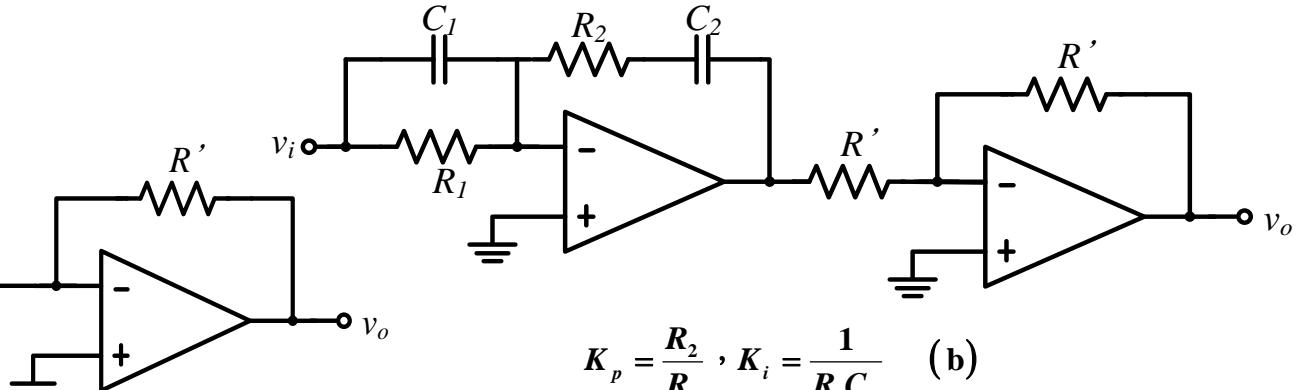
$$\begin{aligned} G_c &= \frac{v_o(s)}{v_i(s)} = K_p + K_d s + K_i / s \\ &= G_{cm} \frac{(1 + s/\omega_L)(1 + s/\omega_z)}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})} \end{aligned}$$



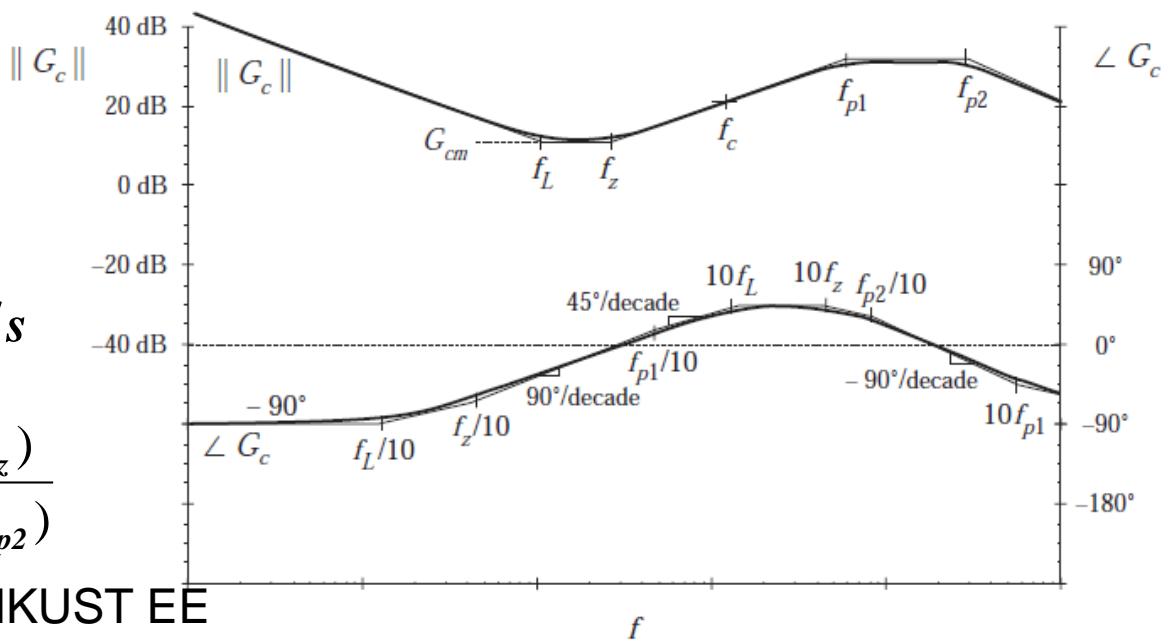
$$K_p = \frac{R_2}{R_1}, K_i = \frac{1}{R_1 C_1} \quad (\text{b})$$




# Type I

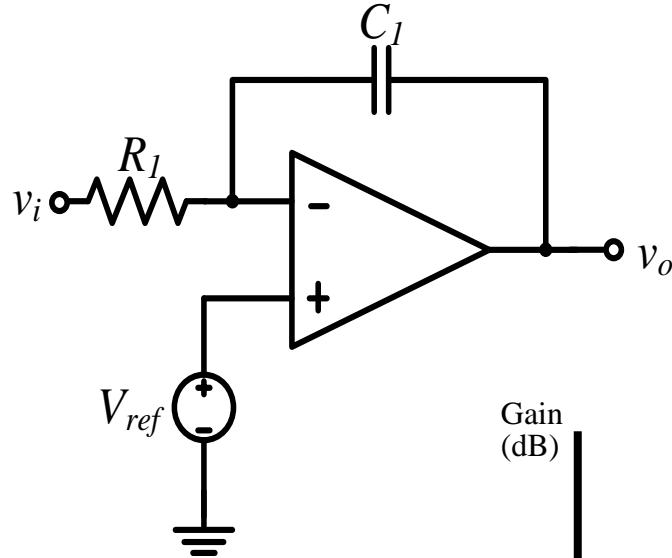
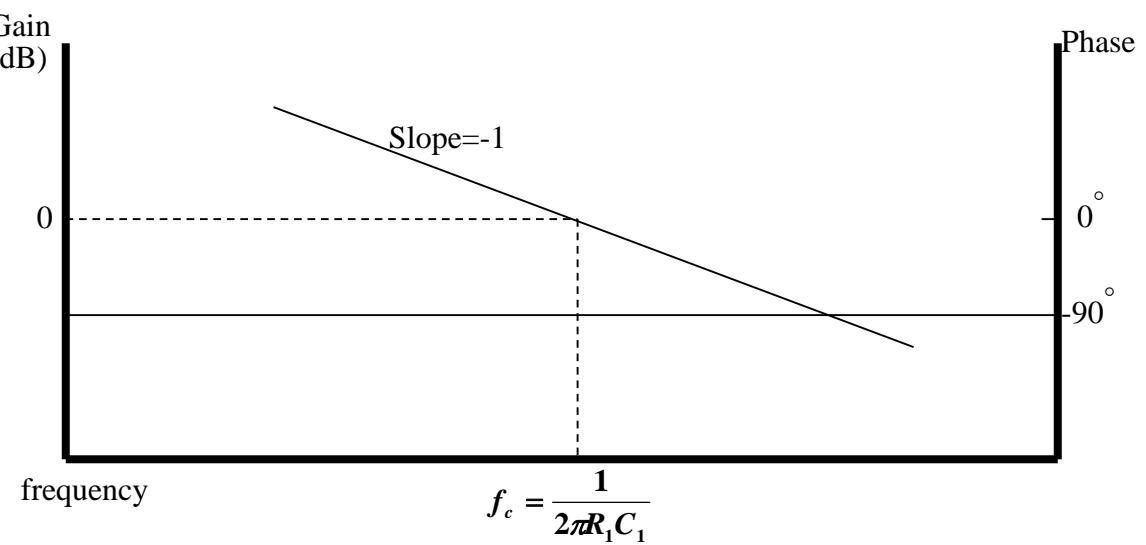
$$\frac{v_o(s)}{v_i(s)} = \frac{1}{R_1 C_1 s}$$




## Type II

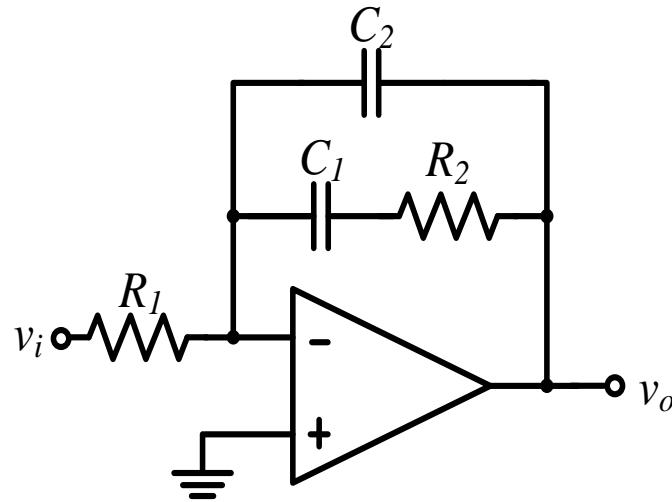


$$\frac{v_o(s)}{v_i(s)} = \frac{1 + sR_2C_1}{sR_1(C_1 + C_2) \left[ 1 + \frac{R_2C_1C_2}{(C_1 + C_2)} s \right]}$$

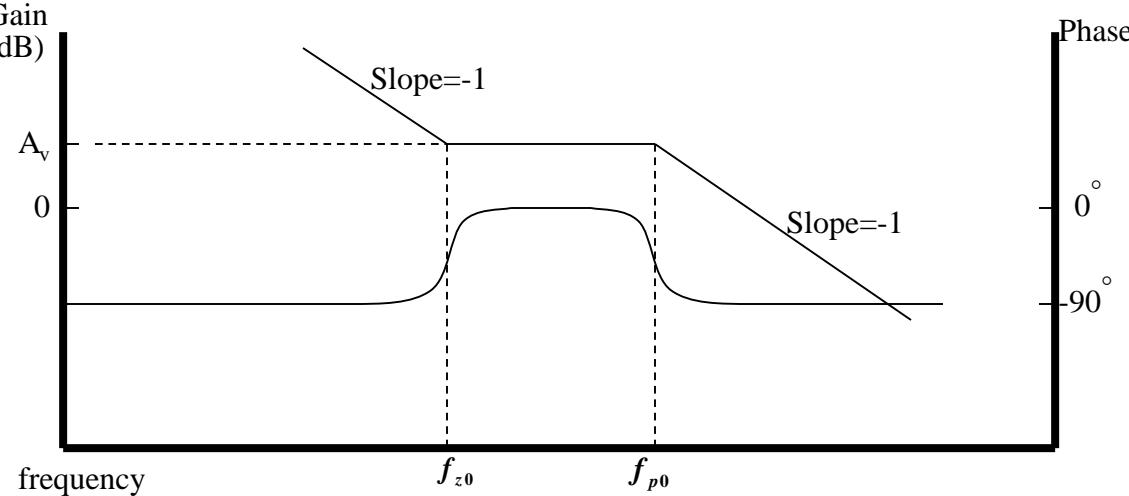
$$\approx \frac{1 + sR_2C_1}{sR_1C_1(1 + sR_2C_2)}$$



# Type III

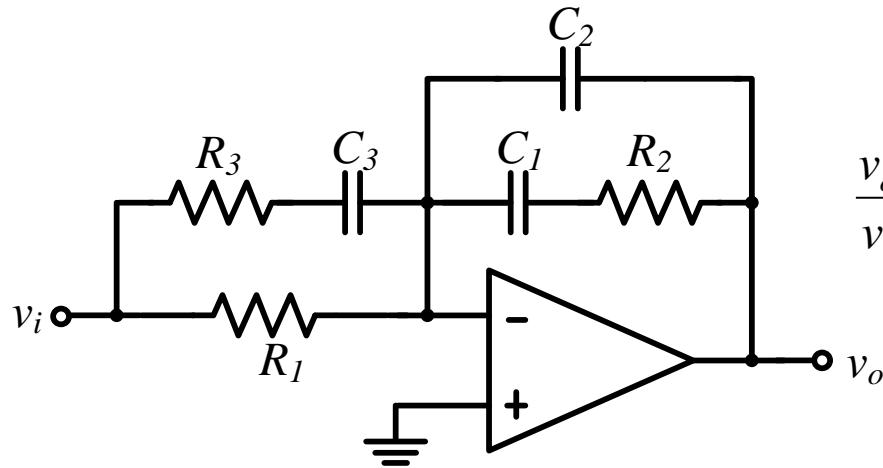
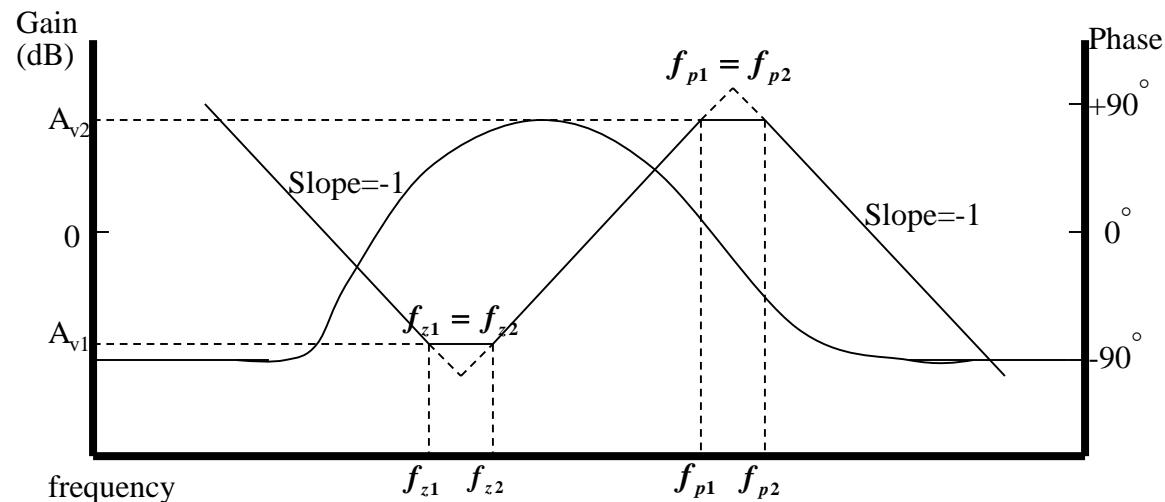
$$\begin{aligned} \frac{v_o(s)}{v_i(s)} &= \frac{(1+sR_2C_1)[1+s(R_1+R_3)C_3]}{sR_1(C_1+C_2)(1+sR_3C_3)\left[1+\frac{R_2C_1C_2}{(C_1+C_2)}s\right]} \\ &\approx \frac{(1+sR_2C_1)(1+sR_1C_3)}{sR_1C_1(1+sR_2C_2)(1+sR_3C_3)} \end{aligned}$$



# K-factor

	Type I	Type II	Type III
Enhance phase	$0^\circ$	$0^\circ < P < 90^\circ$	$0^\circ < P < 180^\circ$
$v_o(s)/v_i(s)$	$1/sR_1C_1$	$\frac{1+sR_2C_1}{sR_1C_1(1+sR_2C_2)}$	$\frac{(1+sR_2C_1)(1+sR_1C_3)}{sR_1C_1(1+sR_2C_2)(1+sR_3C_3)}$
$K=f_c/f_z=f_p/f_c$	1	$\text{Tan}[(P/2)+45]$	$\text{Tan}[(P/4)+45]$
Specifications	$C=1/2\pi f_c G$	$R_2=K/2\pi f_c C_1$ $C_1=C_2(K^2-1)$ $C_2=1/2\pi f_c GKR_1$	$R_2=K/2\pi f_c C_1$ $C_1=C_2(K^2-1)$ $C_2=1/2\pi f_c GR_1$ $R_3=R_1/(K^2-1)$ $C_3=1/2\pi f_c GKR_3$
	$R_1$ is based on actual need to select		

# Simulation of Boost

Result:



$$Av = -0.8\text{dB}$$

$$Q = 8.05\text{dB}$$

$$f_{p0} = 1.35\text{kHz}$$

$$\text{PM} = 42^\circ$$

$$f_{z0} = 4\text{kHz}$$

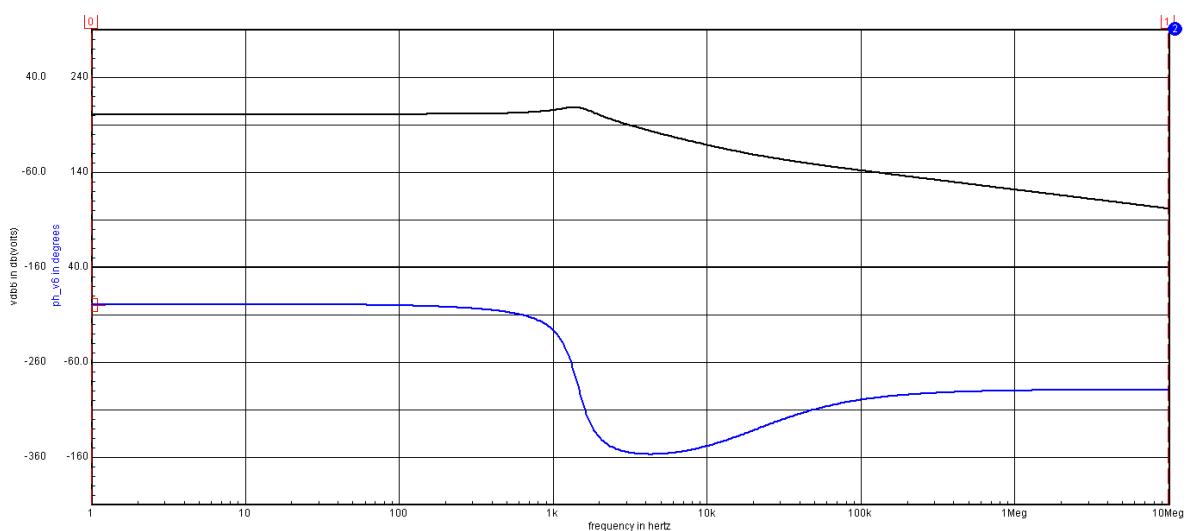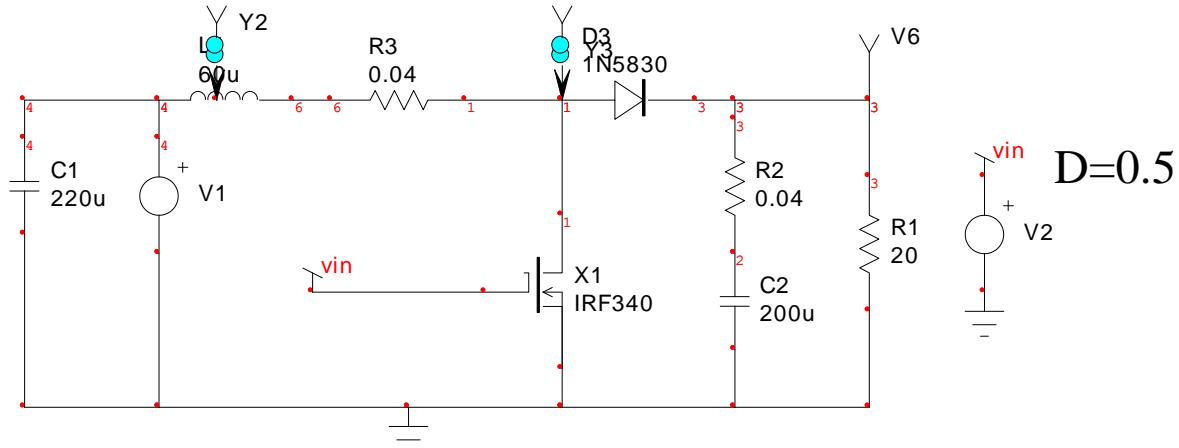

# Design Example

## Wireless Energy Harvesting IC and System Design for Smart Home

Advisor : Yeong-Chau Kuo (郭永超 副教授)


Graduate Student : Yi-Ming Huang (黃羿

銘)

# Outline

- Smart Home
- Battery Model and Charging Method
- Micro-grid
- Wireless Charger
- Controller Architecture
- Synthesis Software
- Measurement
- Conclusion

# Smart Home

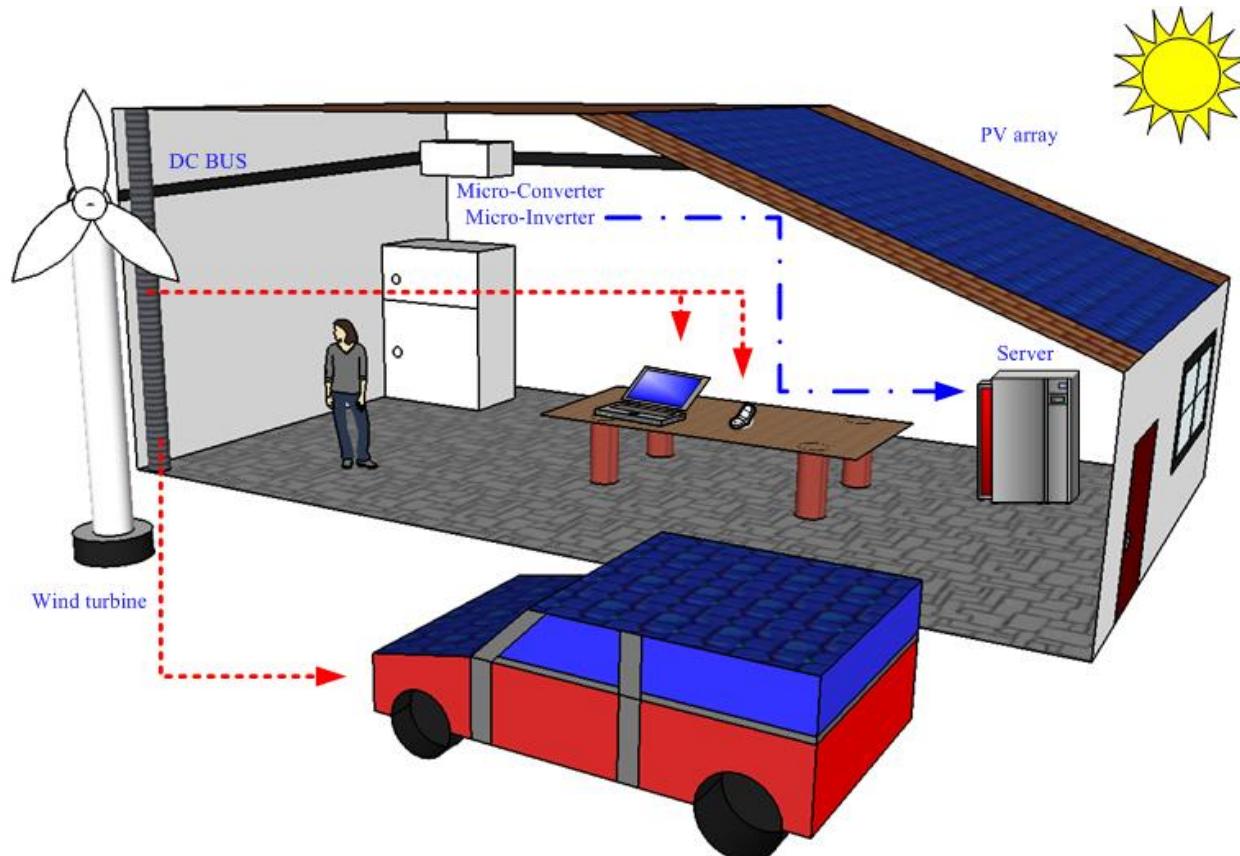


# Outline

- Smart Home
- **Battery Model and Charging Method**
- Micro-grid
- Wireless Charger
- Controller Architecture
- Synthesis Software
- Measurement
- Conclusion


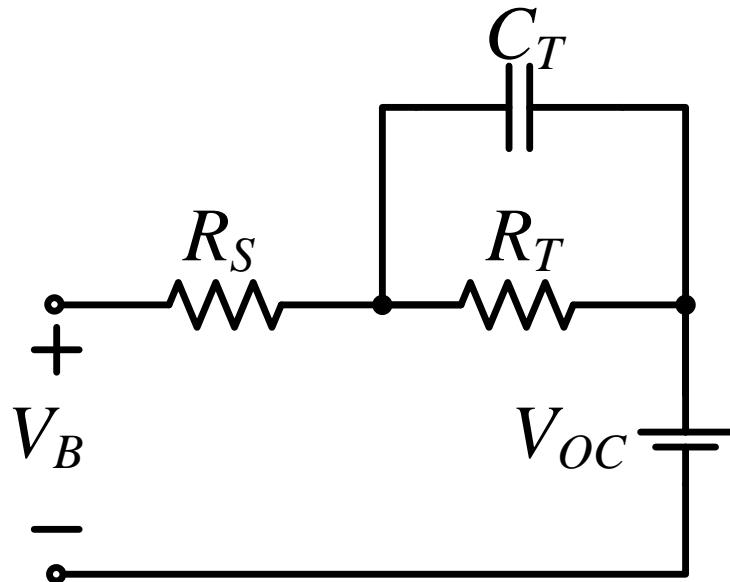
# Battery Model and Charging Method (1/2)

- 戴維寧模型
  - 串聯電阻( $R_S$ )
  - 自放電電阻( $R_{Self-discharge}$ )
  - 暫態響應的並聯電阻( $R_T$ )與電容( $C_T$ )
  - 開路電壓( $V_{OC}$ )


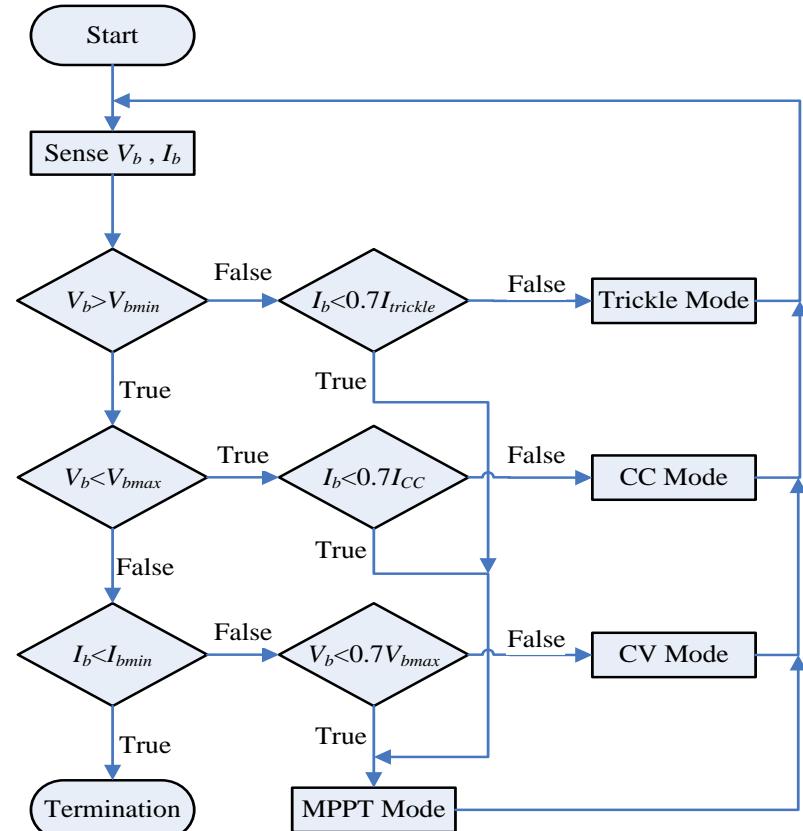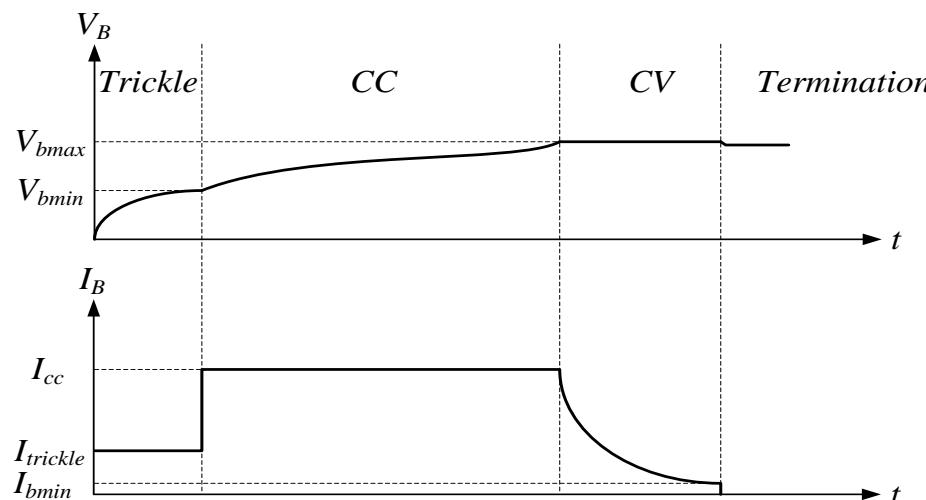
# Battery Model and Charging Method (2/2)

- 充電策略影響了電池的充電效率與壽命。
- 改良型三階段充電法
  - 最大功率追蹤(MPPT)演算法
  - 涓流充電(Trickle Mode)
  - 定電流(CC Mode)
  - 定電壓(CV Mode)




# Outline

- Smart Home
- Battery Model and Charging Method
- **Micro-grid**
- Wireless Charger
- Controller Architecture
- Synthesis Software
- Measurement
- Conclusion



# Micro-grid (1/5)

- **Micro-Converter**

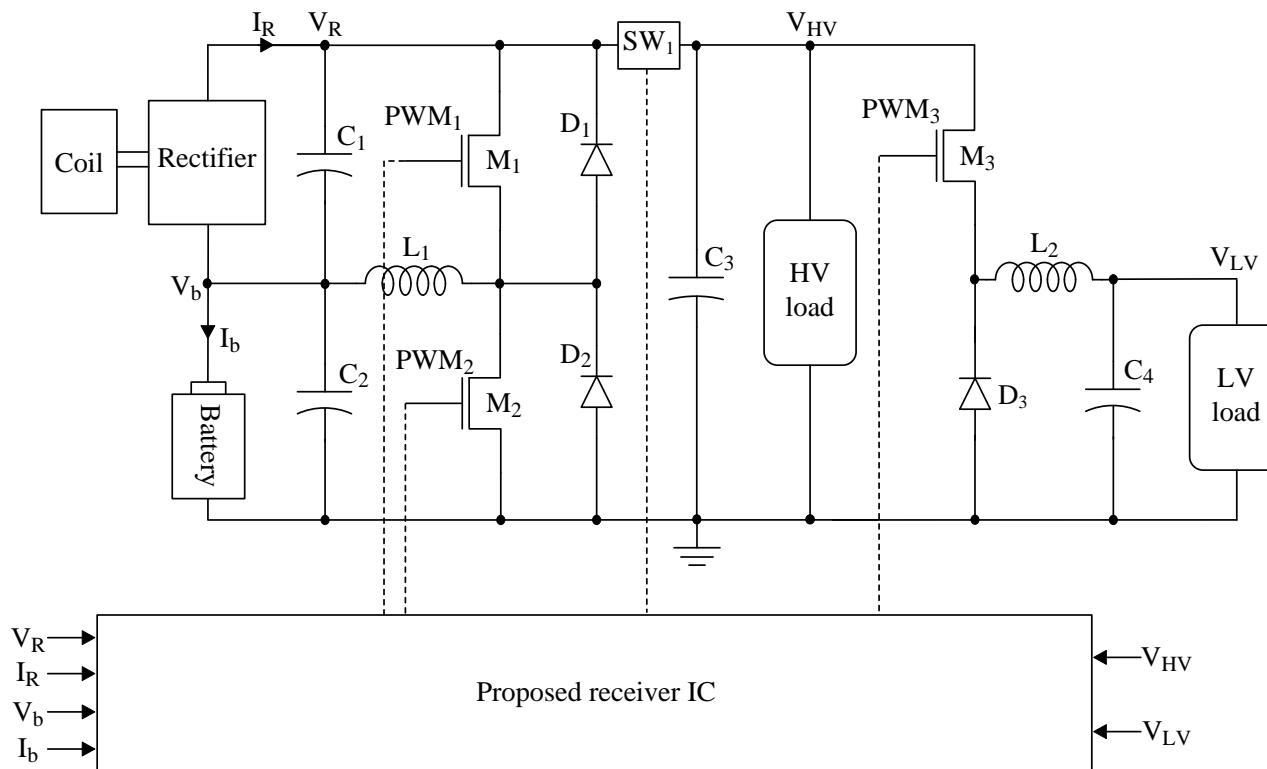


# Micro-grid (2/5)

- 動作原理

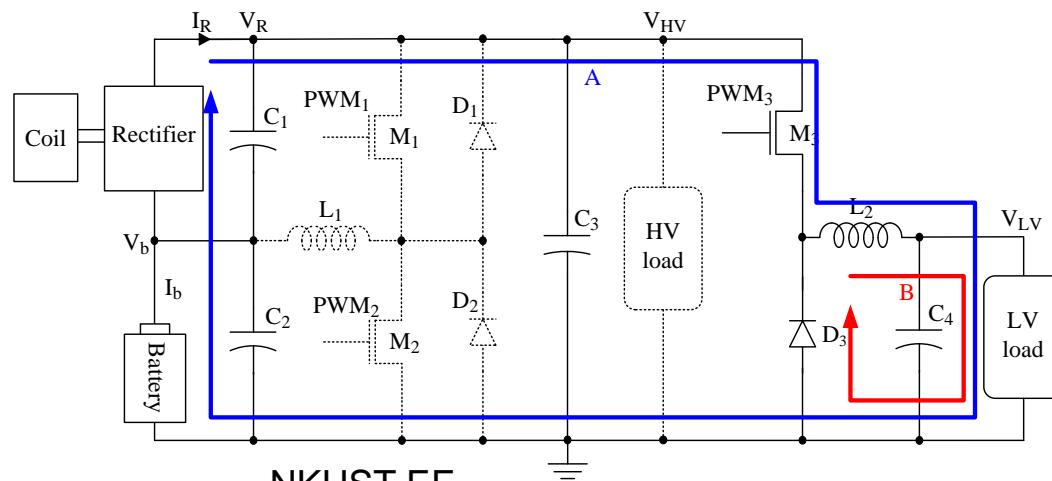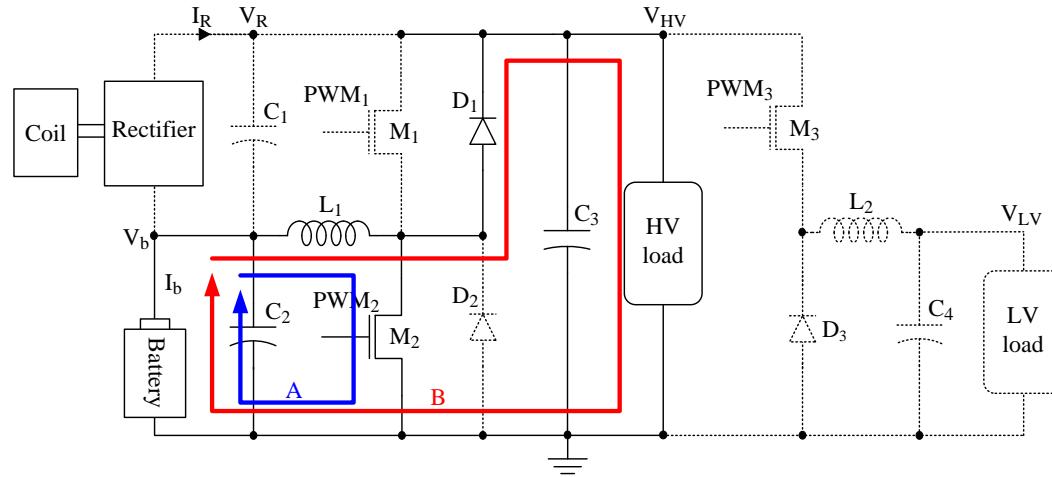


# Micro-grid (3/5)

- **Micro-Inverter**

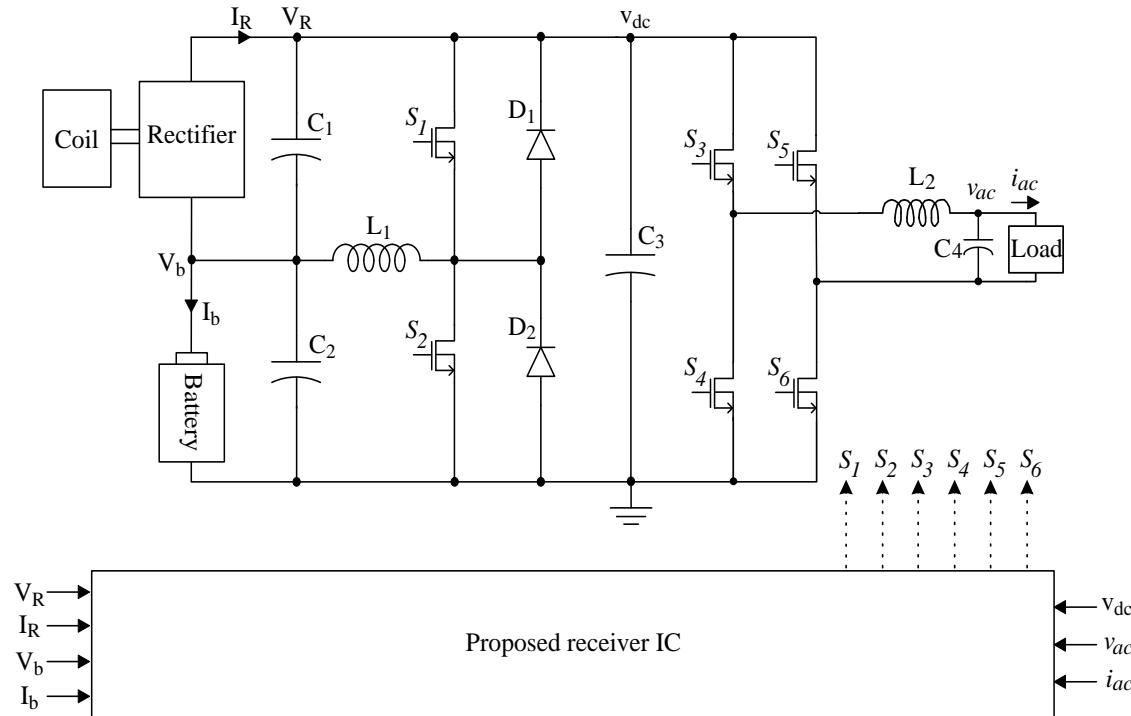


# Micro-grid (4/5)

- 動作原理

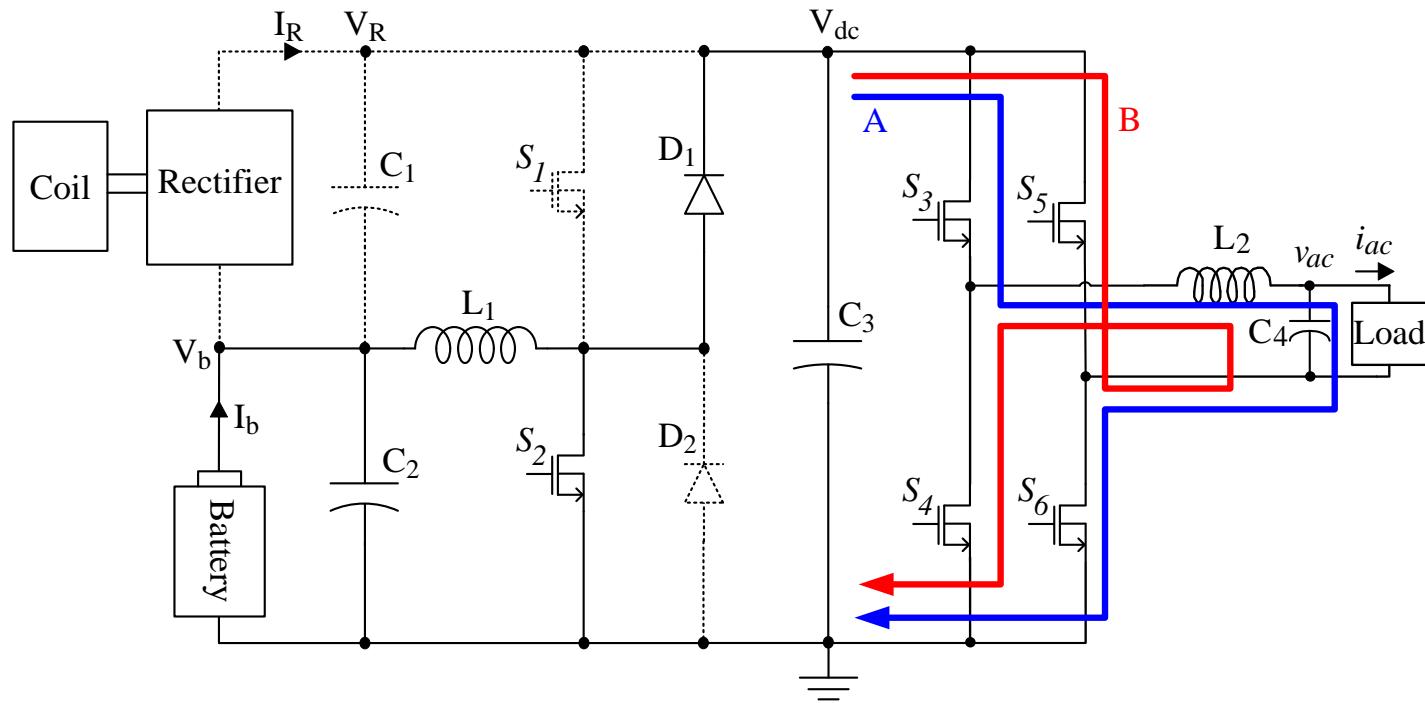

# Micro-grid (5/5)

- Smart meter


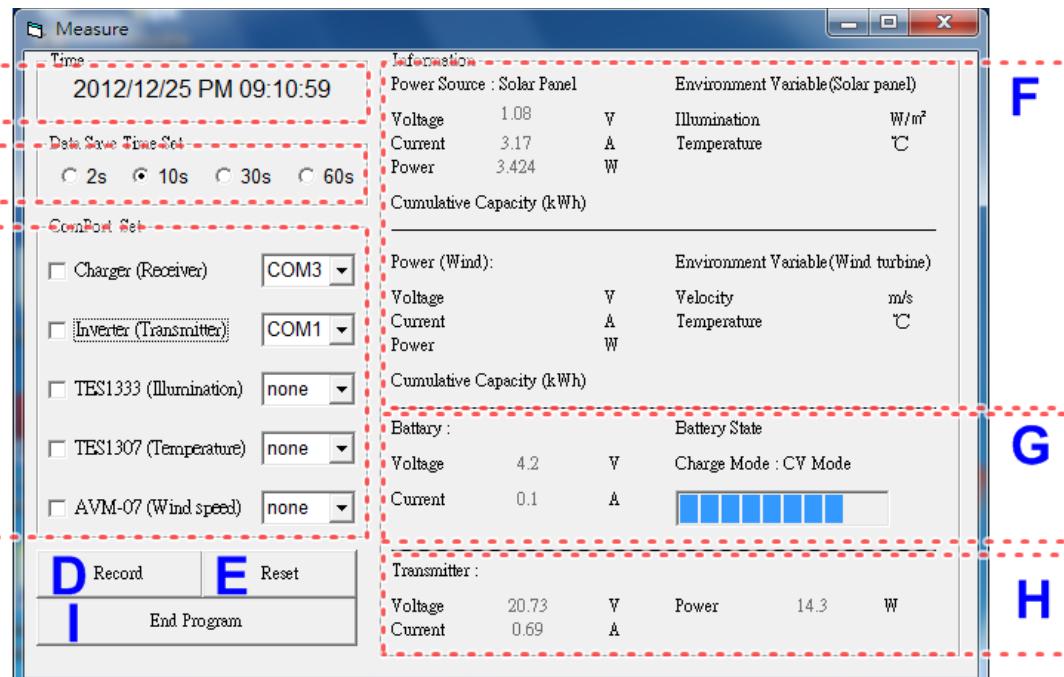


介面說明	
A	目前時間
B	資料記錄時間間隔
C	充電器的COMPORT選擇
D	開啟紀錄
E	重新設定
F	再生能源資訊端
G	無線充電接收端充電資訊
H	無線充電傳送端發電資訊
I	離開

# Outline

- Smart Home
- Battery Model and Charging Method
- Micro-grid
- **Wireless Charger**
- Controller Architecture
- Synthesis Software
- Measurement
- Conclusion

# Wireless Charger (1/10)

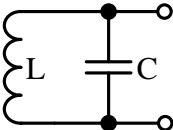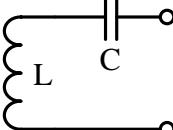
架構			
	磁感應	磁共振(並聯型)	磁共振(串聯型)
有效距離	短	長	中
效率	差	高	高
調整匹配	不用	容易	精密
充電系統	不適用	低功率	高功率

# Wireless Charger (2/10)

頻率	125K Hz	13M Hz	1G Hz
產品	有 (Palm , Sanyo)	無，發表 (MIT , Qualcomm)	有 (Powercast)
功率	5W	60W	0.1W
距離	5公厘	1公尺	數公尺
EMC	通過	未通過	未知
成本	低	高	高

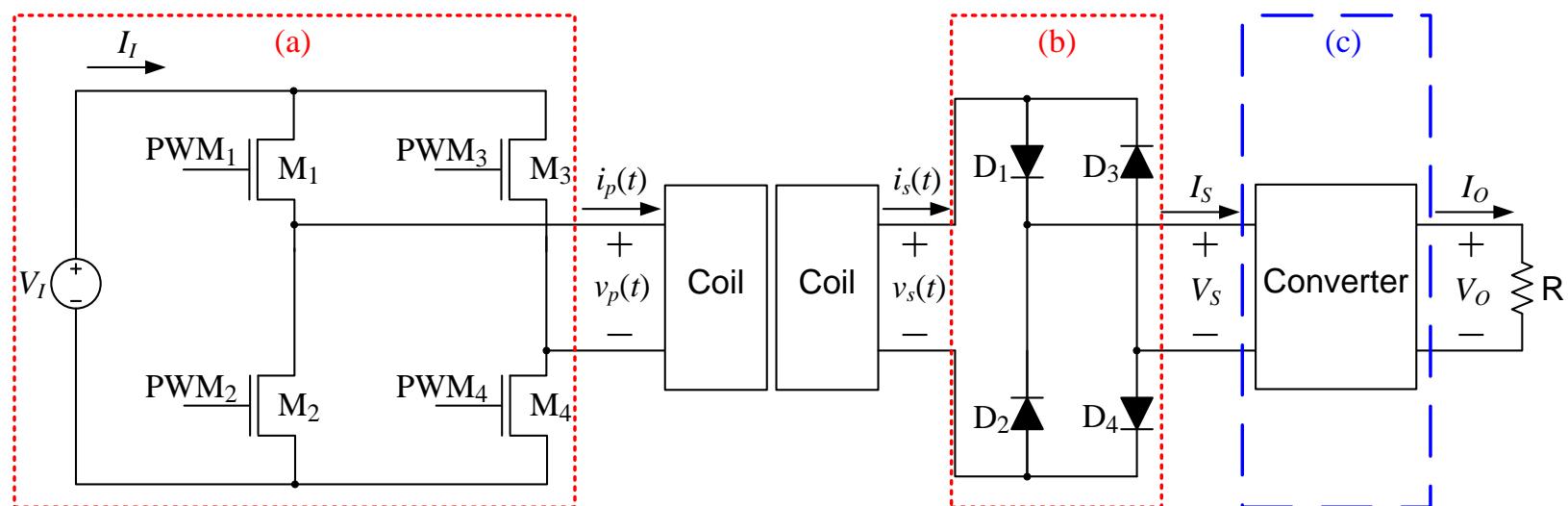
# Wireless Charger (3/10)

- 系統架構
  - a. DC/AC
  - b. AC/DC
  - c. DC/DC



# Wireless Charger (4/10)


- 線圈模型

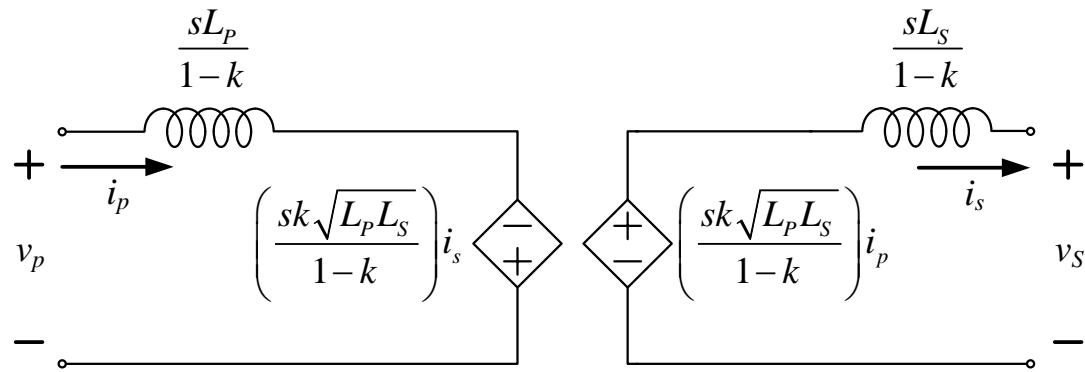

- 線圈補償架構
  - ZPA (Zero Phase Angle)
  - SS , SP , PS , PP
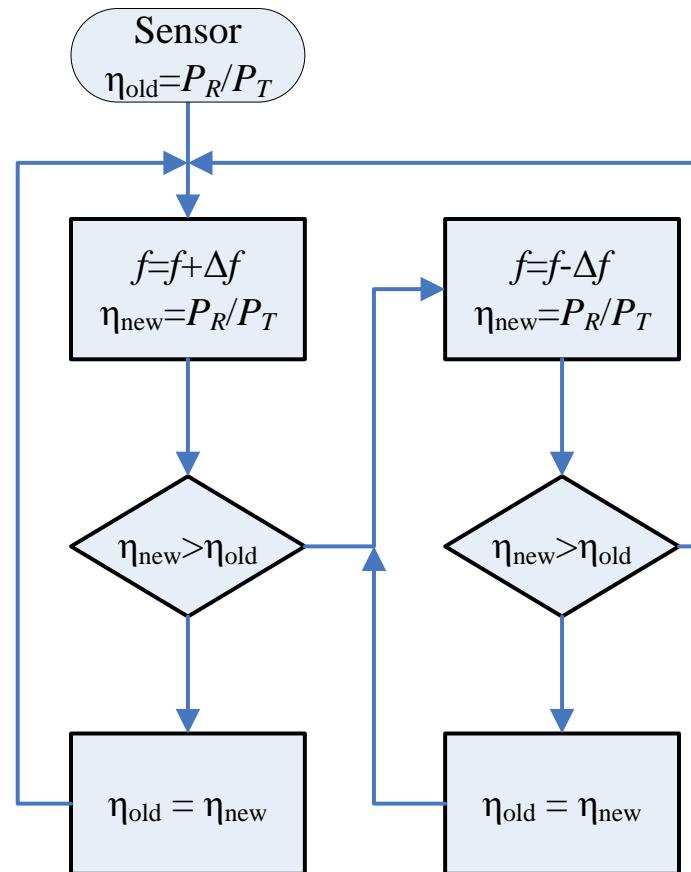
# Wireless Charger (5/10)

- 變頻追蹤演算法
  - $P_T$ : 傳送端功率
  - $P_R$ : 接收端功率
  - $\eta$ : 傳送效率




# Wireless Charger (6/10)

- 轉換器設計

	直流轉換率	電感值	電容值
Buck	$\frac{V_o}{V_I} = D$	$L \geq \frac{V_o T_s (1-D)}{2\Delta i_L}$	$C \geq \frac{V_o T_s^2 (1-D)}{16L\Delta v_o}$
Boost	$\frac{V_o}{V_I} = \frac{1}{D'}$	$L \geq \frac{DV_I T_s}{2\Delta i_L}$	$C \geq \frac{DI_o T_s}{2\Delta v_o}$
Buck-Boost	$\frac{V_o}{V_I} = -\frac{D}{D'}$	$L \geq \frac{V_o T_s (1-D)^2}{2\Delta i_L}$	$C \geq \frac{DI_o T_s}{2\Delta v_o}$

# Wireless Charger (7/10)


- Buck

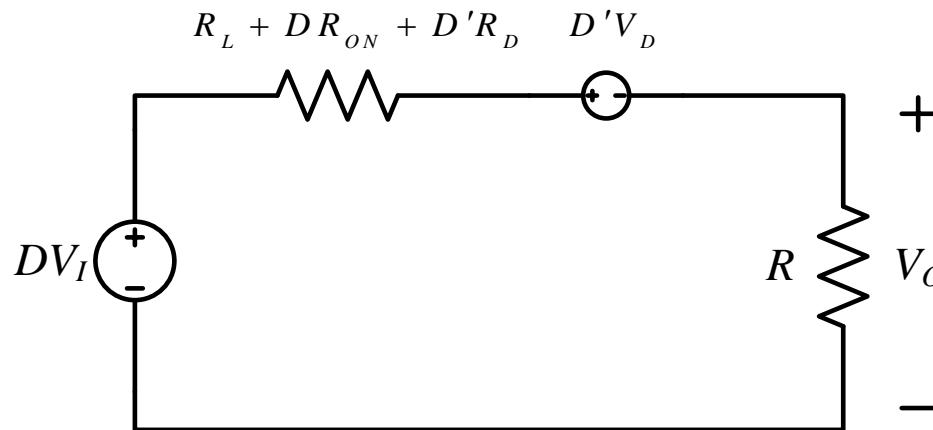

$$\eta = \frac{V_O I_O}{DV_I I_I} = \frac{\left(1 - \frac{D'V_D}{DV_S}\right)R}{R_L + DR_{ON} + D'R_D + R}$$

# Wireless Charger(8/10)


- Boost

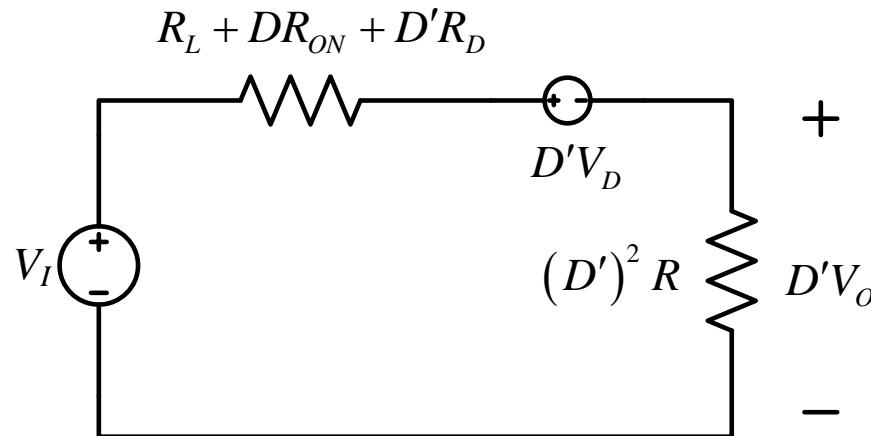

$$\eta = \frac{D'V_o I_o}{V_I I_I} = \frac{\left(1 - D' \frac{V_D}{V_I}\right) (D')^2 R}{R_L + DR_{ON} + D'R_D + (D')^2 R}$$

# Wireless Charger (9/10)


- Buck-Boost

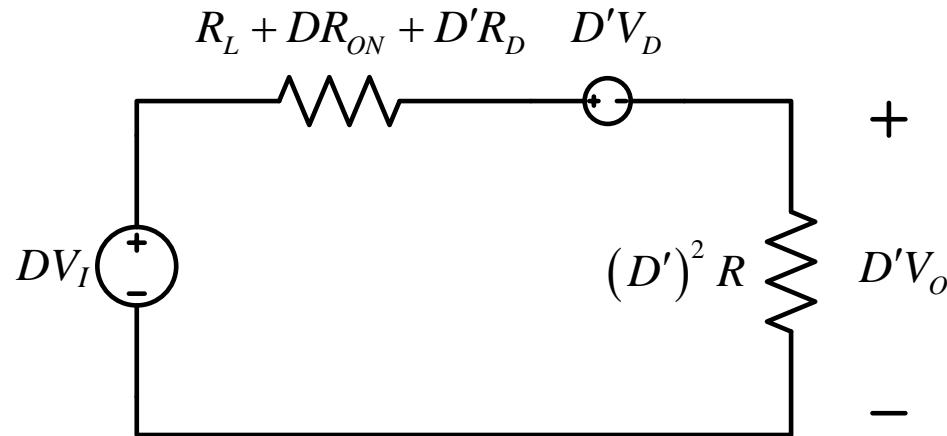

$$\eta = \frac{D'V_o I_o}{DV_I I_I} = \frac{\left(1 - \frac{D'V_D}{DV_I}\right)(D')^2 R}{R_L + DR_{ON} + D'R_D + (D')^2 R}$$

# Wireless Charger (10/10)


- 暫態分析
- 補償器設計
  - K factor

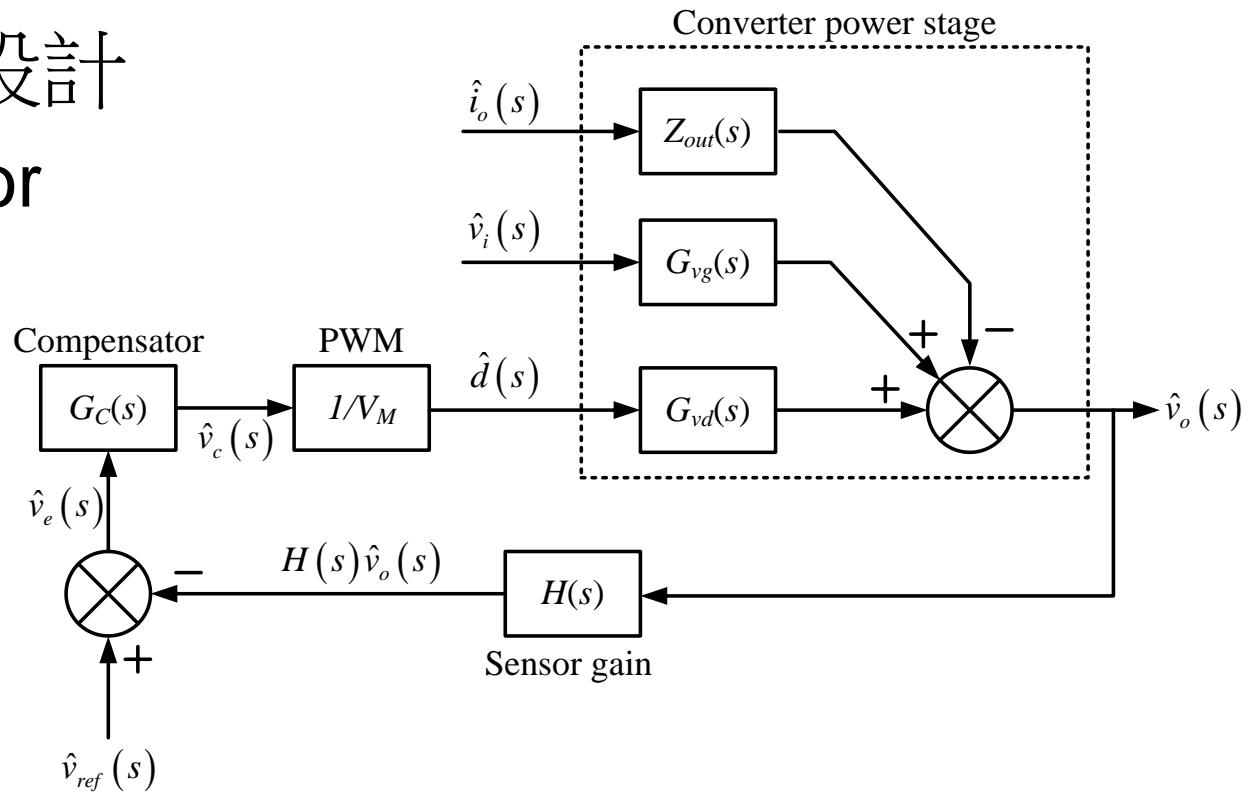

# Outline

- Smart Home
- Battery Model and Charging Method
- Micro-grid
- Wireless Charger
- **Controller Architecture**
- Synthesis Software
- Measurement
- Conclusion


# Controller Architecture (1/3)

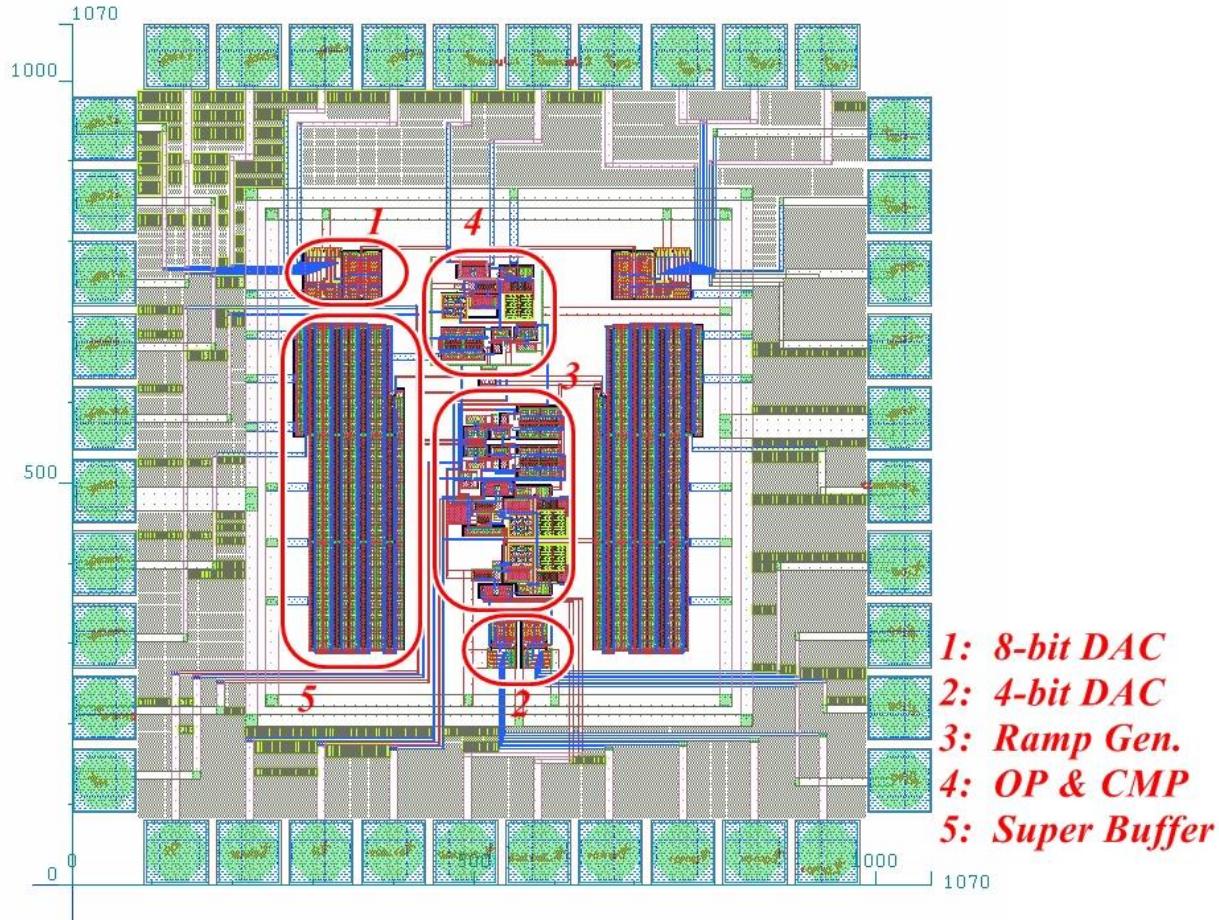

# Controller Architecture (2/3)




# Controller Architecture(3/3)

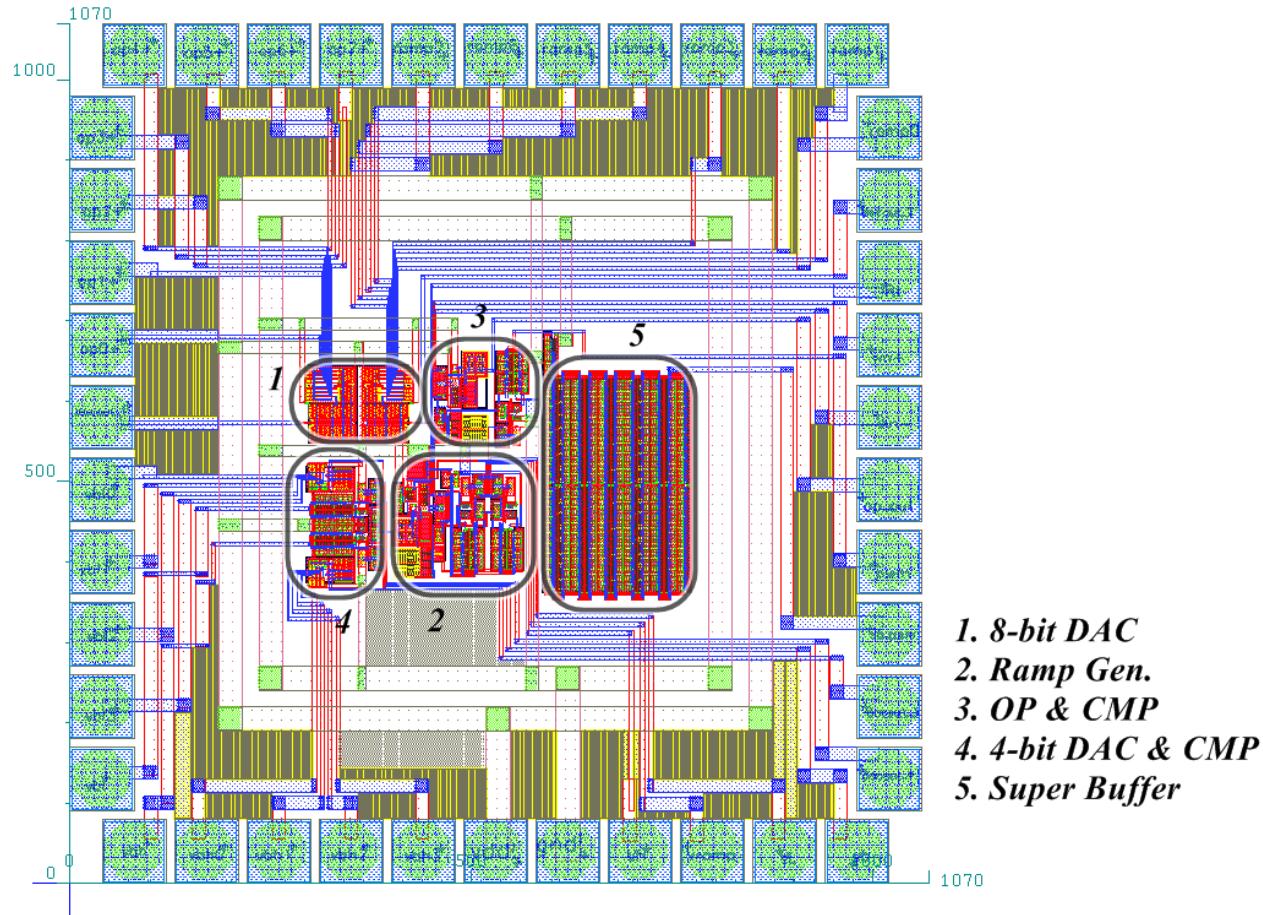

# Outline

- Smart Home
- Battery Model and Charging Method
- Micro-grid
- Wireless Charger
- Controller Architecture
- **Synthesis Software**
- Measurement

# Synthesis Software (1/3)

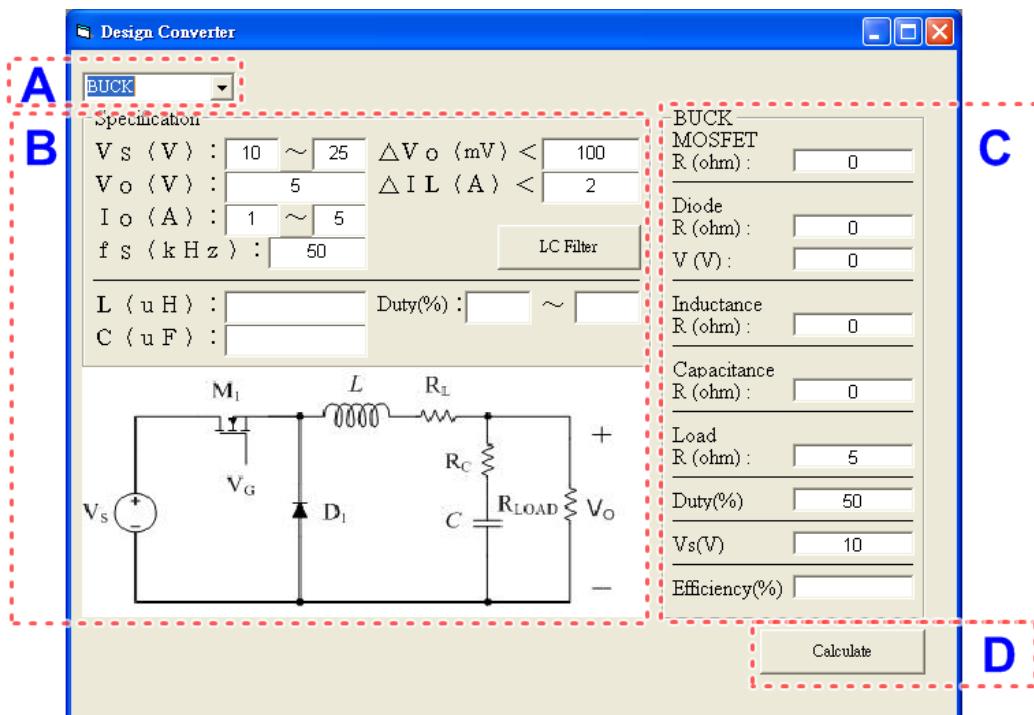


## 轉換器合成系統

- |   |                                    |
|---|------------------------------------|
| A | 選擇轉換器<br>(BUCK, BOOST, BUCK-BOOST) |
| B | 規格設定                               |
| C | 效率估算                               |
| D | 計算各參數值                             |


# Synthesis Software (2/3)

- 太陽能診斷系統

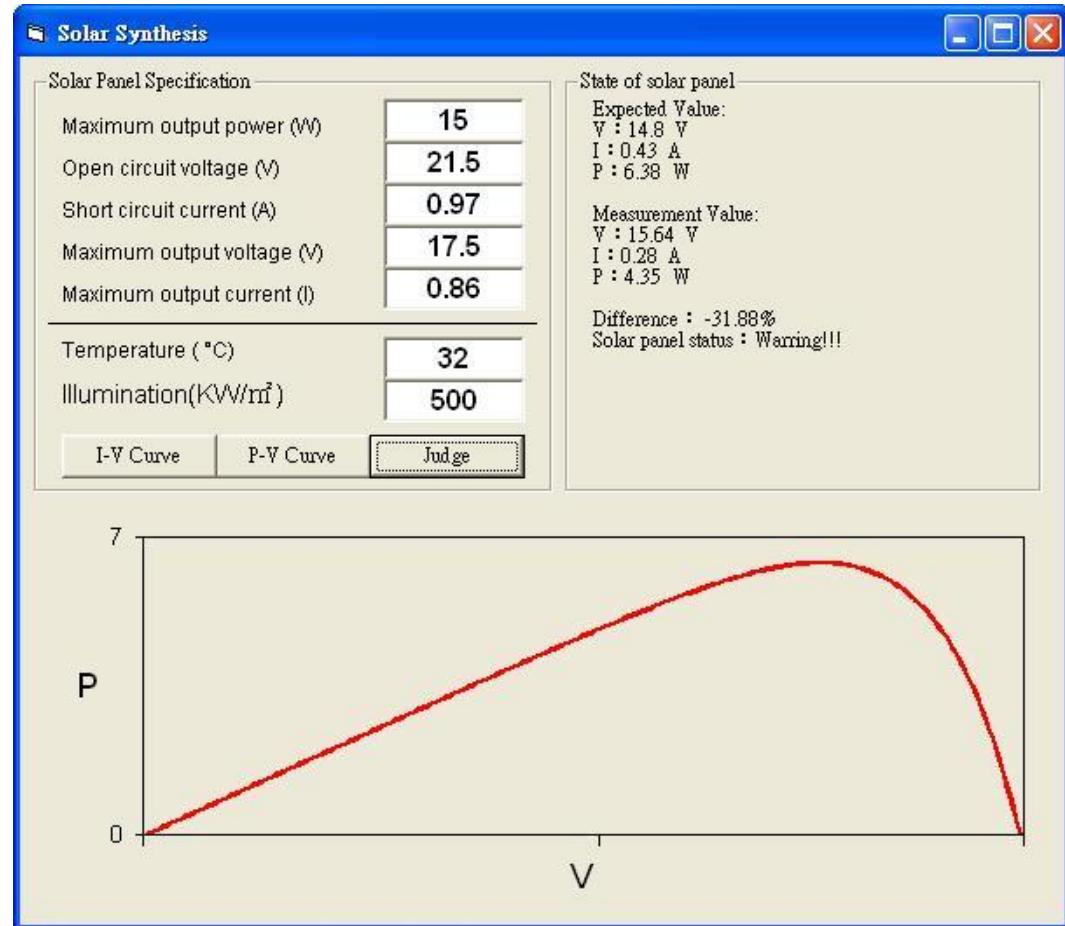

# Synthesis Software (3/3)

- 風能診斷系統

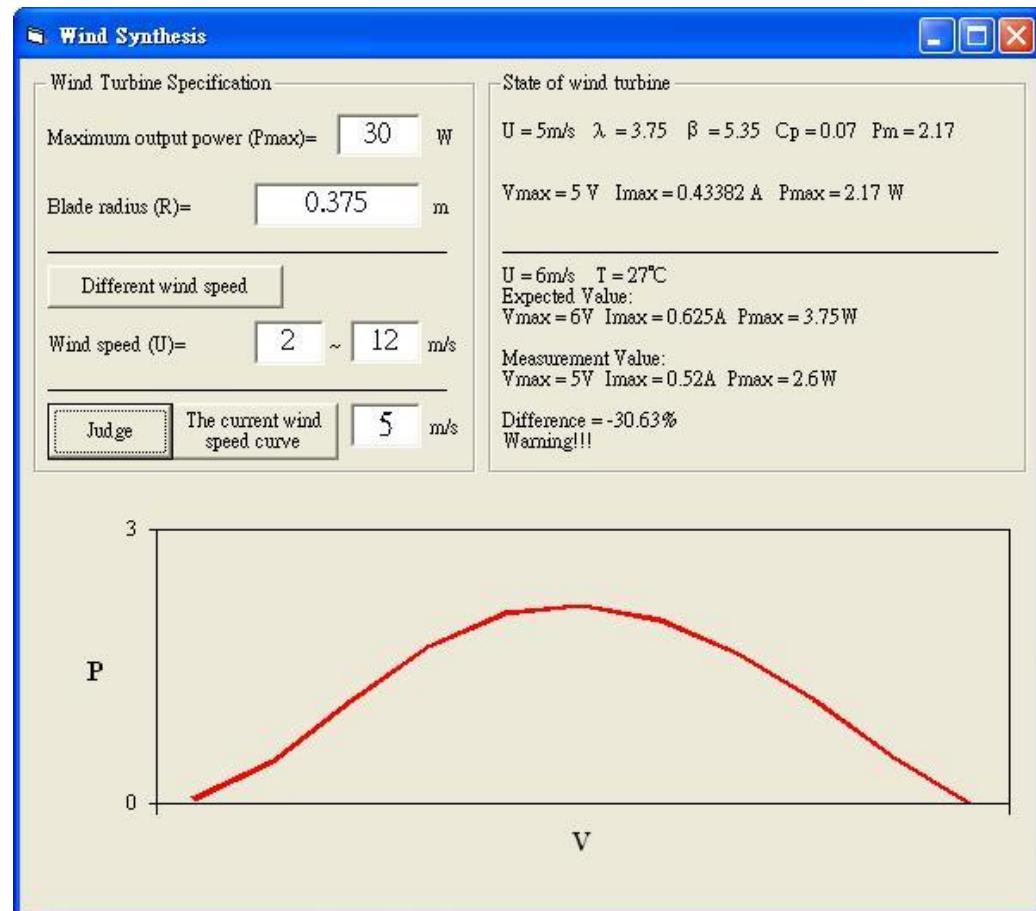


# Outline

- Smart Home
- Battery Model and Charging Method
- Micro-grid
- Wireless Charger
- Controller Architecture
- Synthesis Software
- **Measurement**
- Conclusion


# Measurement (1/4)

- 無線充電成品

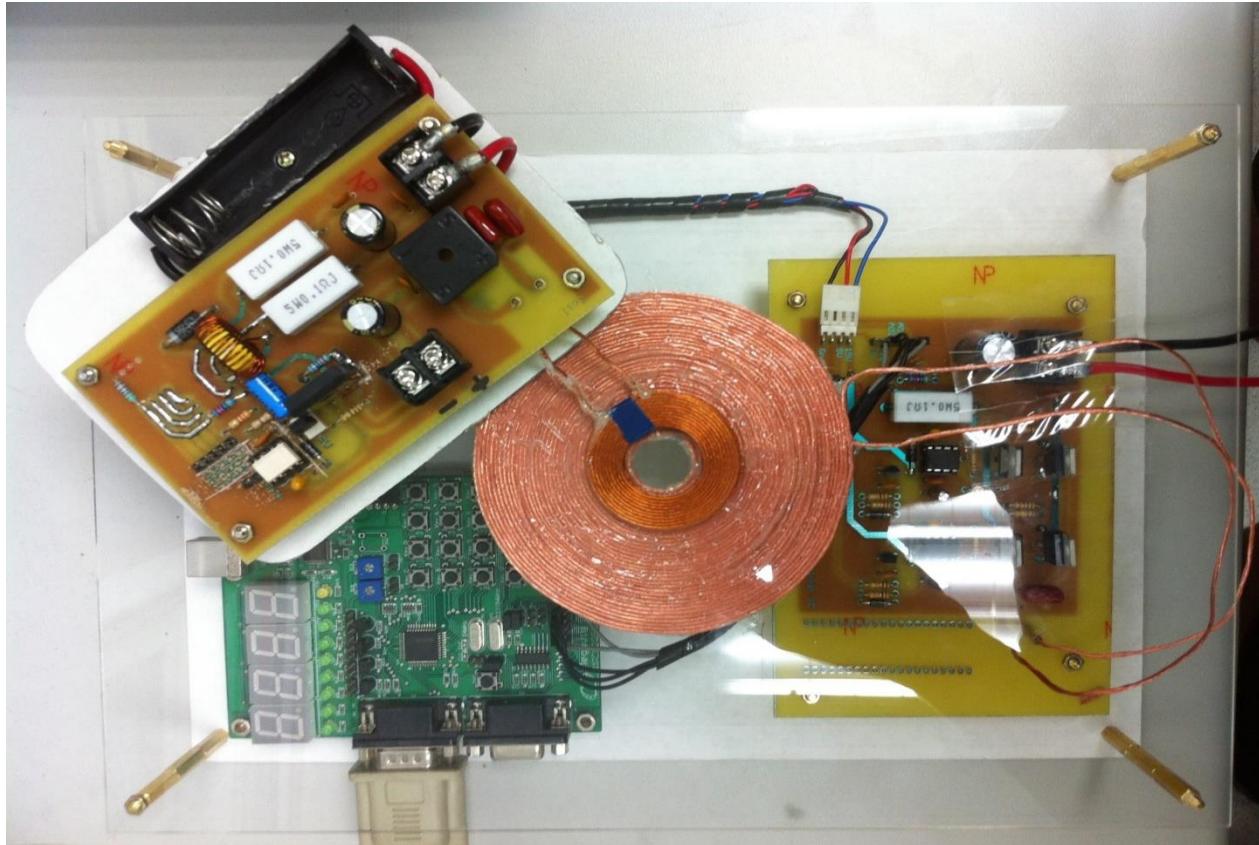


# Measurement (2/4)

- 無線充電系統

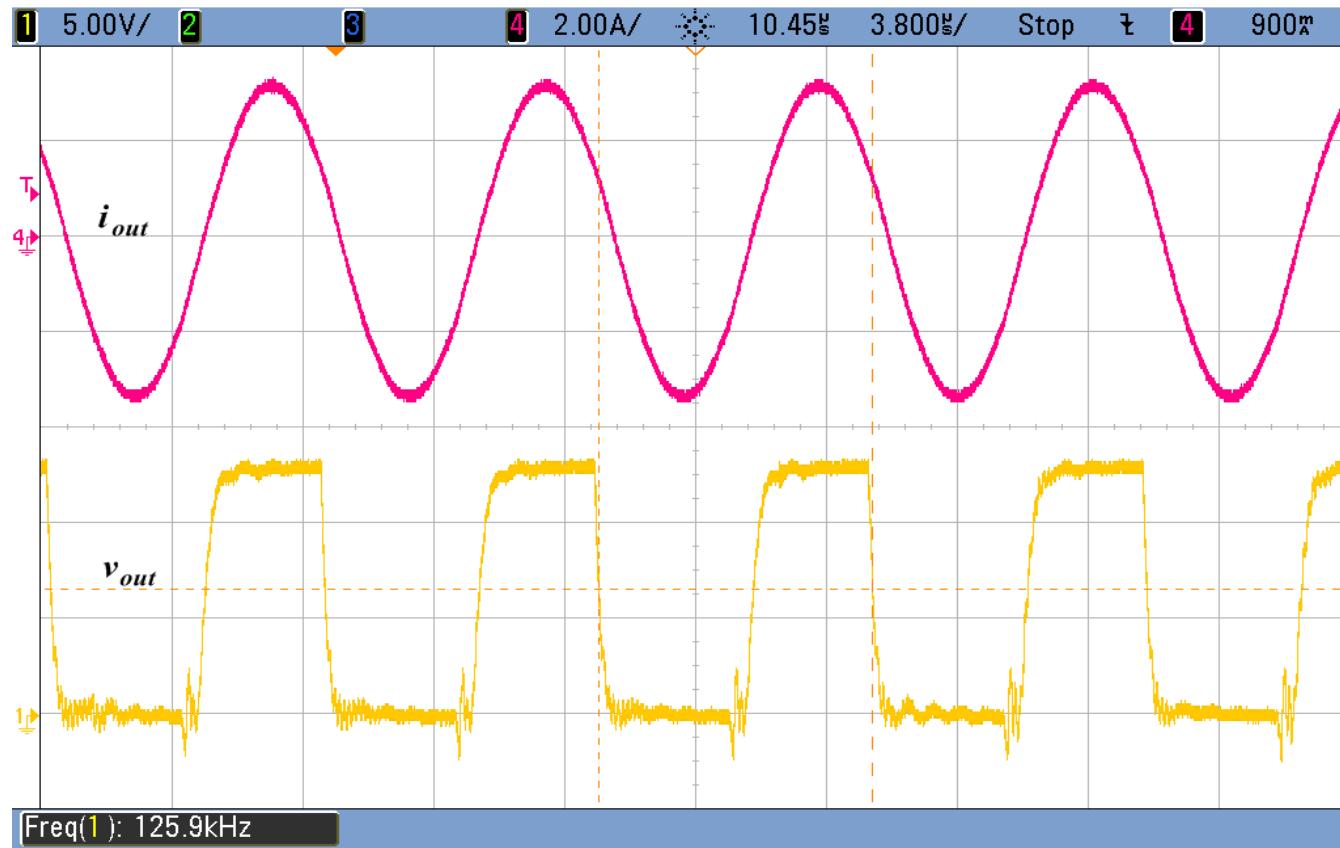


# Measurement (3/4)

- Micro-Inverter

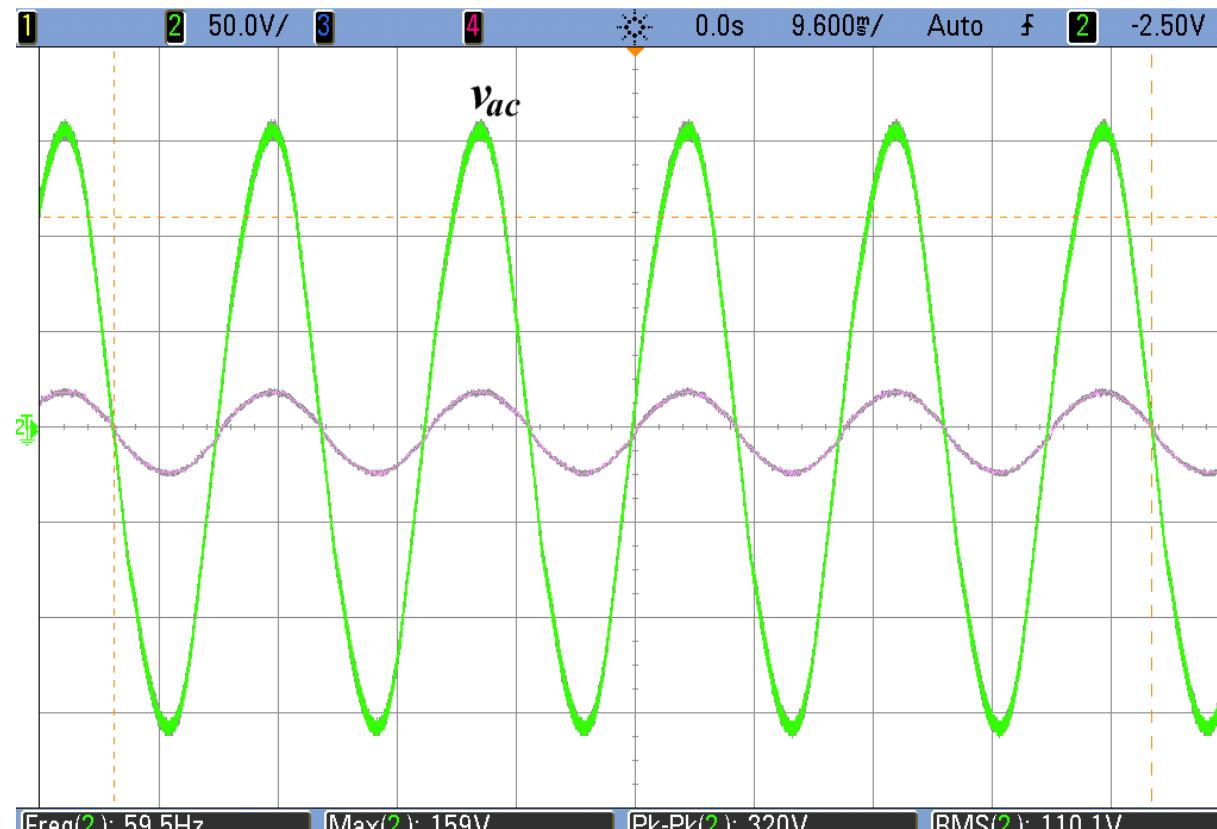
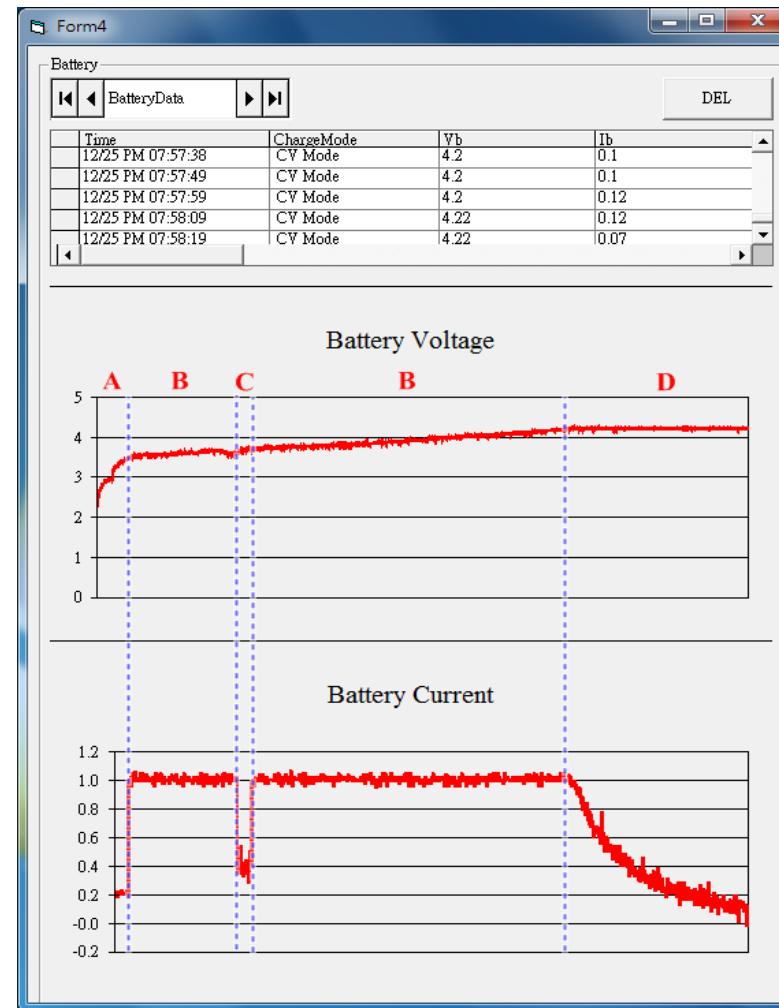
# Measurement (4/4)

- 充電結果
  - A. Trickle Mode
  - B. CC Mode
  - C. MPPT Mode
  - D. CV Mode



# Outline

- Smart Home
- Battery Model and Charging Method
- Micro-grid
- Wireless Charger
- Controller Architecture
- Synthesis Software
- Measurement
- Conclusion

# Conclusion

- 無線充電系統藉由各種模型的分析設計，提高其穩定度與可靠度，利用自行撰寫的電表系統，可管理各再生能源的用電情況與診斷分析系統運作情況，建立了未來智慧型家庭的雛型系統。
- 未來採用32位元的微控制器系統，將會使系統有更精確的控制，達到更佳的效率與穩定度，結合所開發的傳送器與接收器積體電路，可更縮小系統的體積與成本。

# Reference

- [1] P. E. Allen and D. R. Holberg, *CMOS Analog Circuit Design*, New York: Oxford, 2002.
- [2] B. Razavi, *Design of Analog CMOS Integrated Circuits*, New York: Wiley, 2001.
- [3] R. W. Erickson and D. Maksimovic, *Fundamentals of Power Electronics*, Kluwer Academic Publishers, 2th edition, 2001.
- [4] V. Vorperian, “Simplified analysis of PWM converters using model of PWM switch” *IEEE Trans. Aerospace Electron. Syst.*, vol. 26, pp. 490-496, May 1990.
- [5] H. D. Venable, “The  $\Delta$  factor: a new mathematical tool for stability analysis and synthesis,” *Proceedings of Powercon*. Mar., 1983.

負責編輯同學：  
劉俊宏、羅永杰、黃羿銘、  
童韋翔、吳宗翰、陳冠凱等  
(排名依照畢業順序)

Thanks for your attention!!